

CSE 390B, 2024 Winter

Building Academic Success Through Bottom-Up Computing

# Growth Mindset & Sequential Logic

Growth vs. Fixed Mindset, Introduction to Sequential Logic,  
Representing Time in Hardware, The Data Flip-Flop (DFF)

# Lecture Outline

## ❖ Growth vs. Fixed Mindset

- Setting SMART Goals

## ❖ Introduction to Sequential Logic

- The Problem of Combinational Logic
- Autopilot Control Circuit Example

## ❖ Representing Time in Hardware

- Clock Signals and Units of Time in Hardware

## ❖ The Data Flip-Flop (DFF)

- Implementation and Examples

# Growth vs. Fixed Mindset



FIXED



GROWTH

MINDSETS

# Setting SMART Goals

- ❖ **S** – Be specific, simple and significant.
- ❖ **M** – Make sure your goals are measurable. How many times within a week, month, the quarter do you want to do x goal?
- ❖ **A** – Make sure your goals are achievable. Is your goal within your scope of control?
- ❖ **R** – Be realistic and reasonable.
- ❖ **T** – Be time-bound. When will you accomplish your goal?

# SMART Goals Group Discussion

## WINTER QUARTER GOALS

What are skills, practices  
or habits that are not  
strengths YET?

## SPHERE OF CONTROL

Getting a 4.0 in a course

vs.

Attending course  
office hours

## SMART GOAL FRAMEWORK

**S** — Specific

**M** — Measurable

**A** — Achievable

**R** — Realistic

**T** — Timebound

Attending CSE 390B  
office hours at least  
5x this quarter  
(or once every other week)

# Lecture Outline

- ❖ Growth vs. Fixed Mindset
  - Setting SMART Goals
- ❖ Introduction to Sequential Logic
  - The Problem of Combinational Logic
  - Autopilot Control Circuit Example
- ❖ Representing Time in Hardware
  - Clock Signals and Units of Time in Hardware
- ❖ The Data Flip-Flop (DFF)
  - Implementation and Examples


# Why Consider Time Now?

## ❖ Needed for our **abstraction**

- We need to talk about hardware maintaining state for memory
- We need vocabulary to talk about time

 
## ❖ Needed for our **implementation**

- Physical implementations of chips cannot be instantaneous
- We need to account for physical delays in signal propagation



# The Problem with Combinational Logic

- ❖ Consider the following circuit:

 


- ❖ Let's assume that  $a=0$ ,  $b=1$ , and  $c=0$ 
  - The output should be 1
- ❖ What's the result if we change  $b=0$  and  $c=1$ ?
  - The result should still be 1
  - However, `out` is briefly 0 if we change  $c$  first



 
# Autopilot Control Circuit Example

- ❖ Consider this autopilot control circuit:
- Either the pilot or copilot is flying at any time
  - The pilot and copilot can separately request autopilot
  - Only the person flying can request autopilot



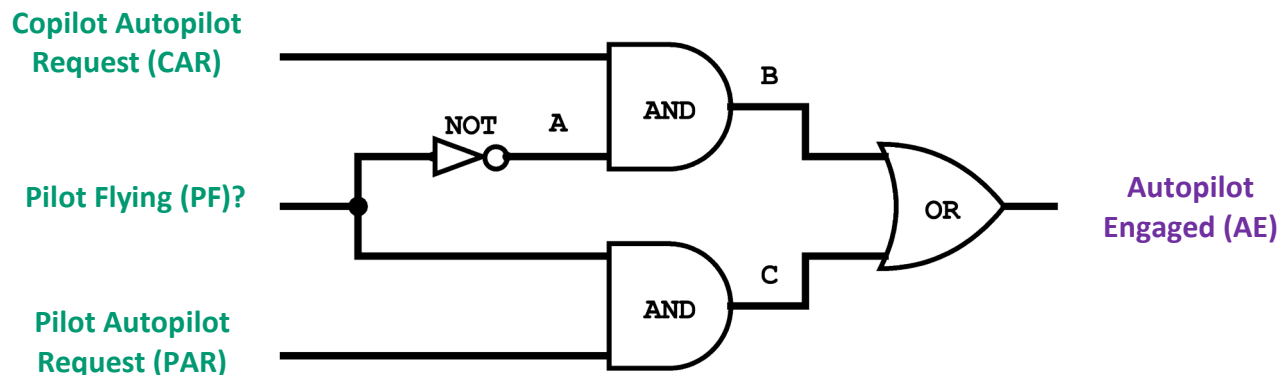
# Autopilot Control Circuit Example

- ❖ Consider this autopilot control circuit:
  - Either the pilot or copilot is flying at any time
  - The pilot and copilot can separately request autopilot
  - Only the person flying can request autopilot




- ❖ Let's assume every logic gate takes  $1\text{ms}$  to compute
  - For example, if an input changes at  $t=4\text{ms}$ , the gate will only output the new result at  $t=5\text{ms}$


# Autopilot Control Circuit Example

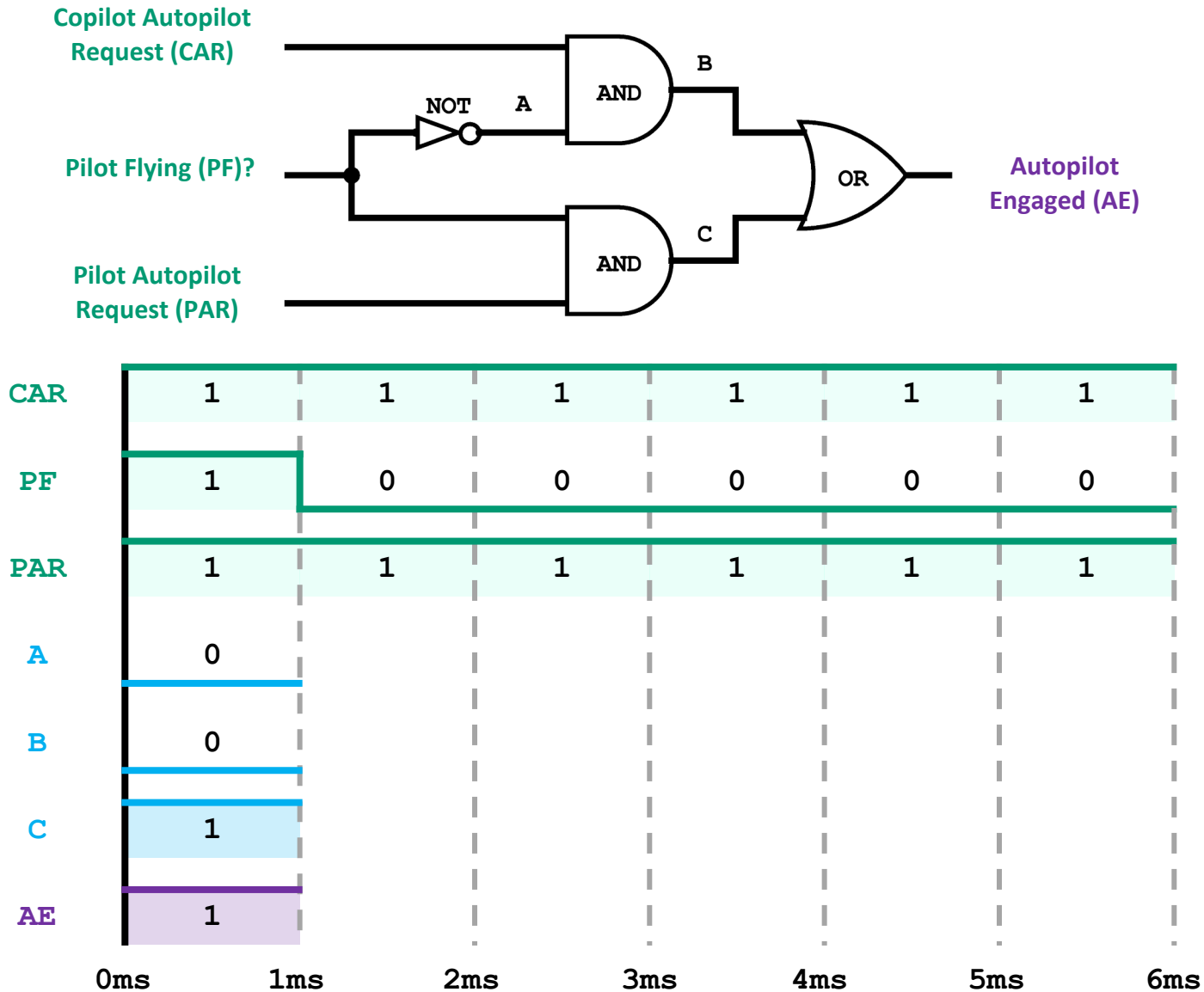


# Autopilot Control Circuit Example

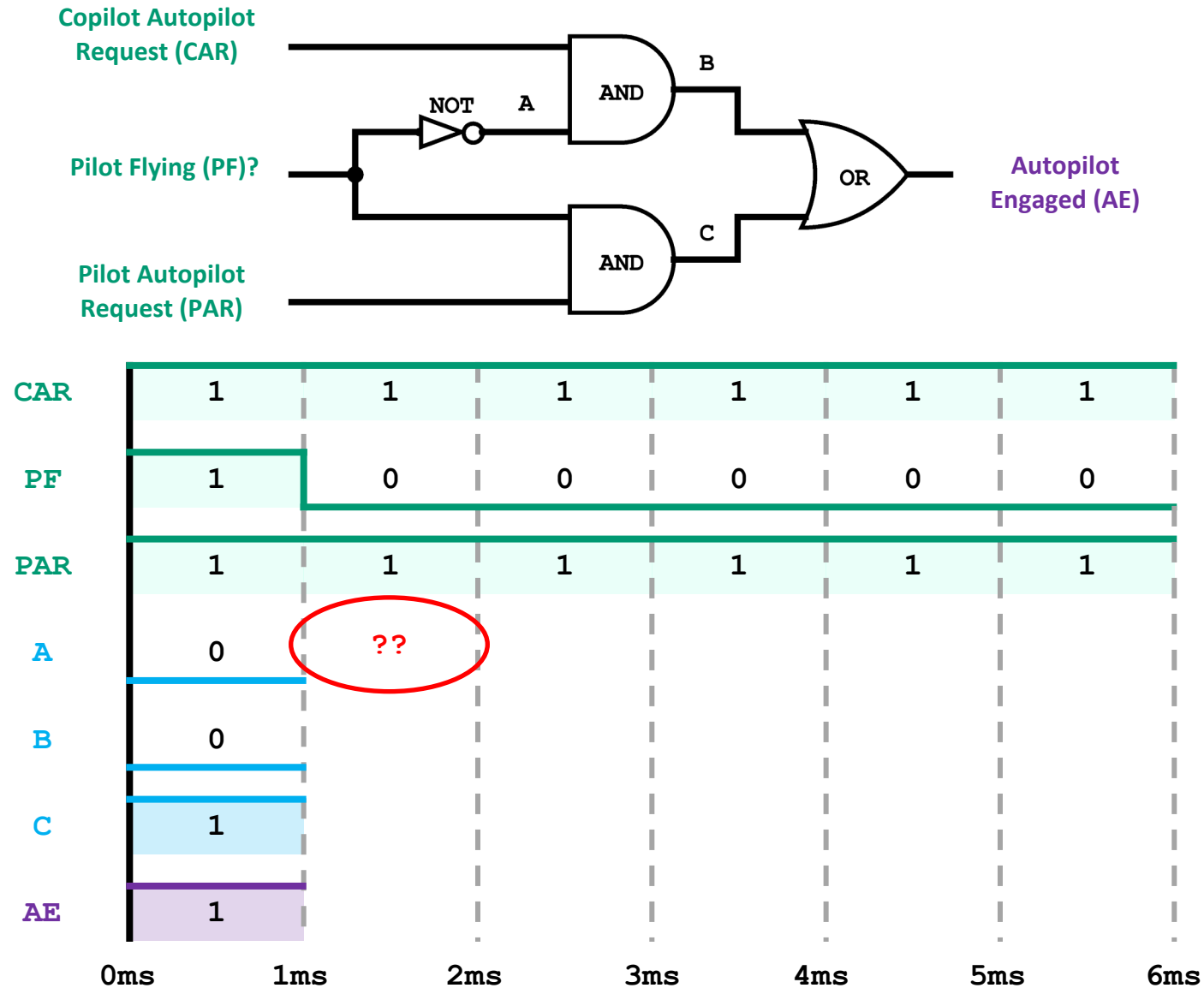


# Autopilot Control Circuit Example

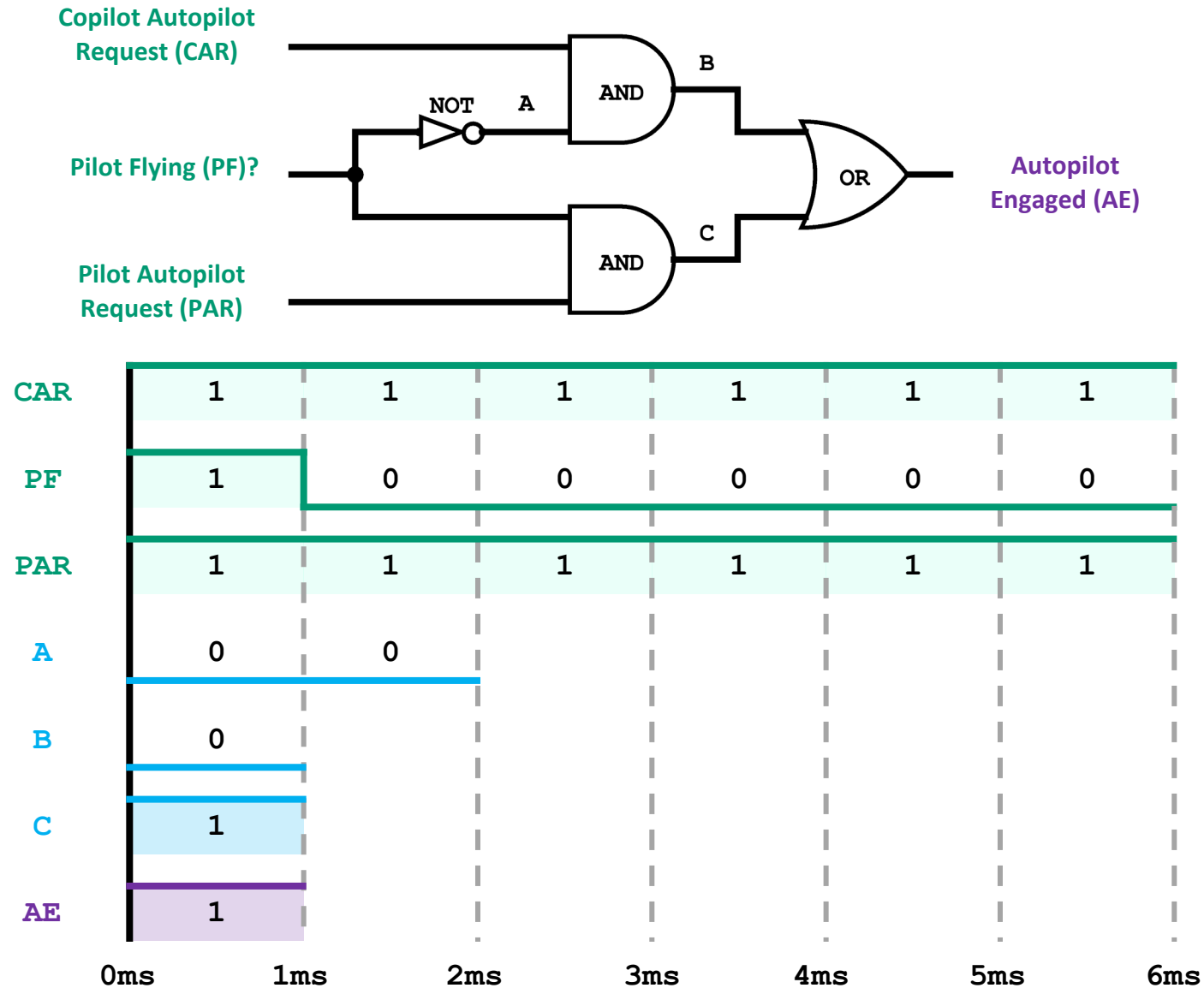

# Autopilot Control Circuit Example

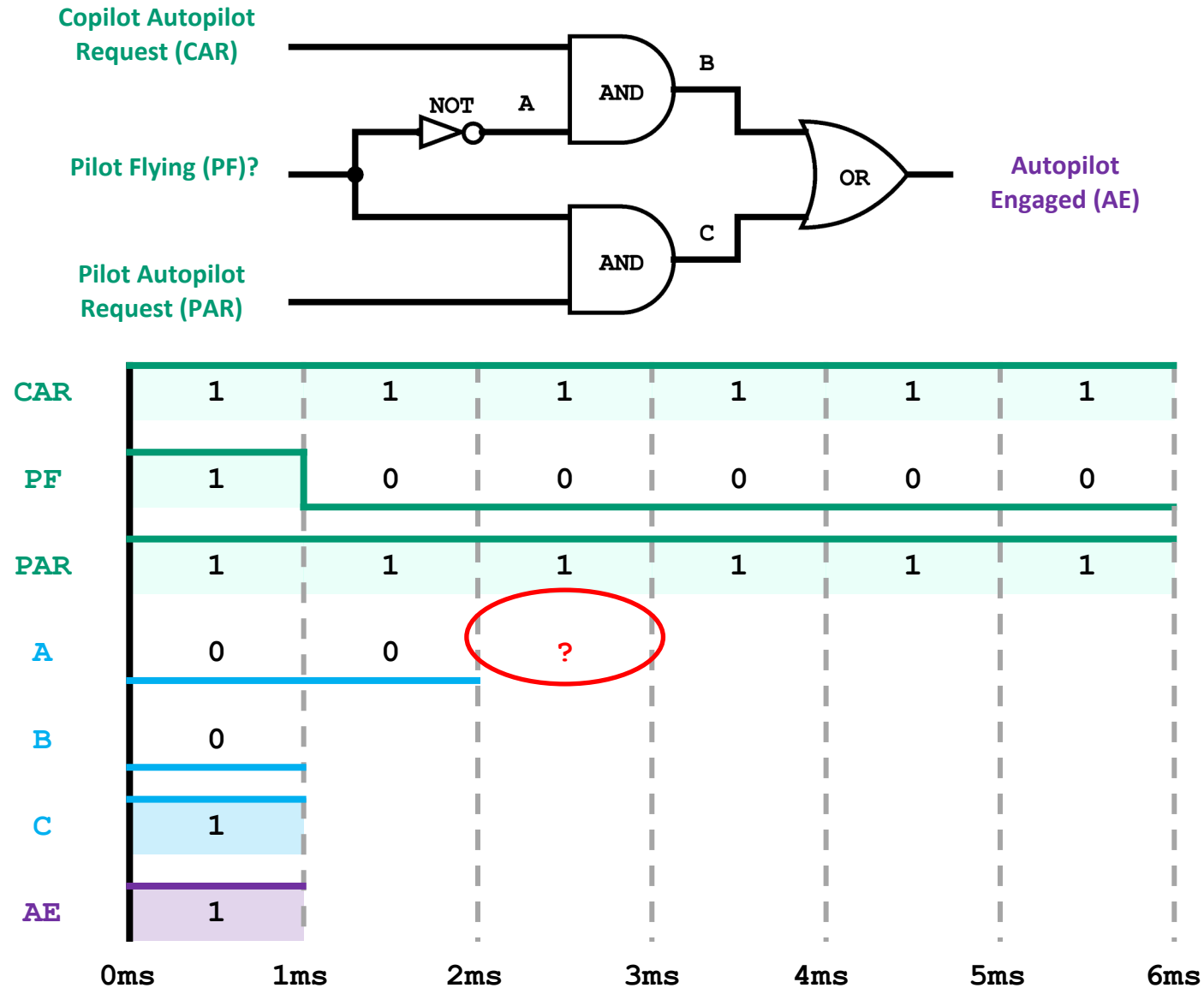

# Autopilot Control Circuit Example

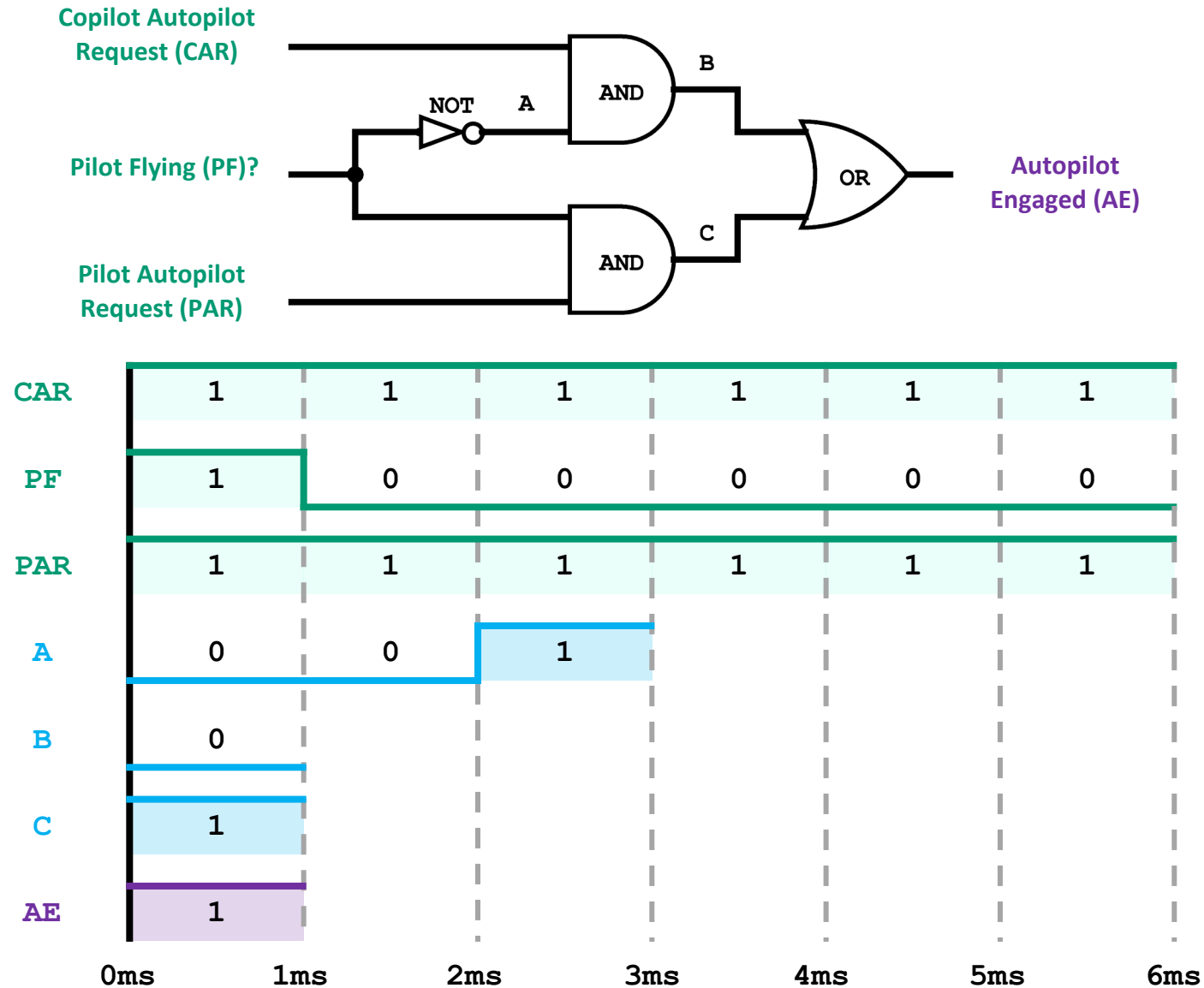

## < Lecture 5: Growth Mindset & Sequential Logic



When poll is active  
respond at

**PollEv.com**  
**/cse390b**

Send **cse390b** and your message  
to **22333**

**Describe the behavior of the Autopilot  
Engaged (AE) output between 1ms to  
6ms.**

Loading...




**POLLEV.COM/CSE390B**

Join by Text





# Autopilot Control Circuit Example

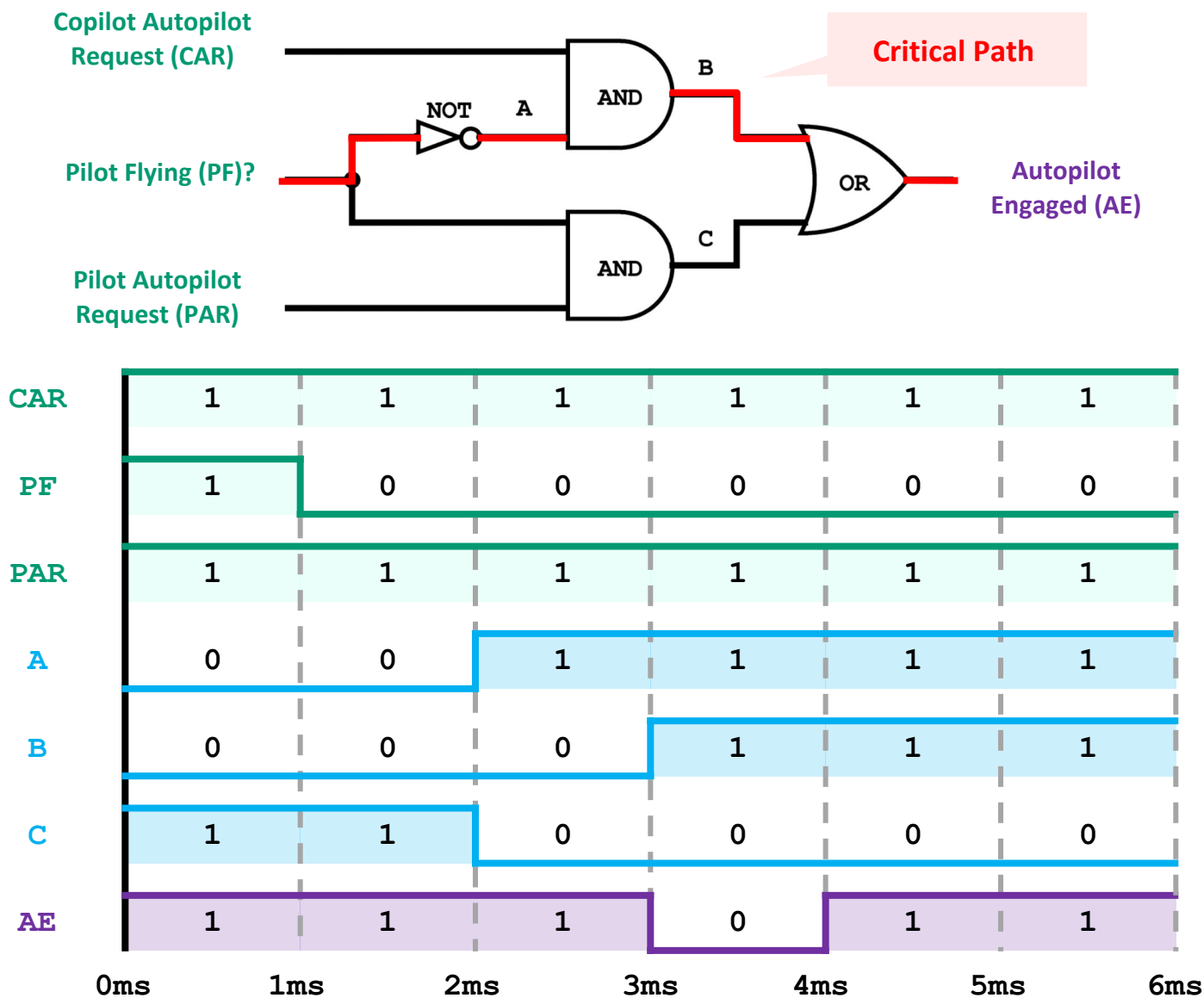


# Combinational vs. Sequential Logic

- ❖ So far, we have ignored “time” in our circuits
- ❖ Our chips used **combinational logic**
  - When given inputs, the chip computes its output instantaneously
  - The output is a function of the current inputs, with no memory of previous events
- ❖ Today, we'll start exploring what happens when we consider time, ultimately building to **sequential logic**


# What is Sequential Logic?

- ❖ Sequential logic incorporates time in hardware
- ❖ Output depends on present value of its input signals *and* a sequence of past inputs
- ❖ Sequential logic resolves the problem introduced with combinational logic
  - Does so by adding a **delay** for the entire circuit before evaluating the result
  - All the circuits will be evaluated between one **clock cycle** and the output will be evaluated at the end of the clock cycle

 
# Combinational vs. Sequential Abstraction



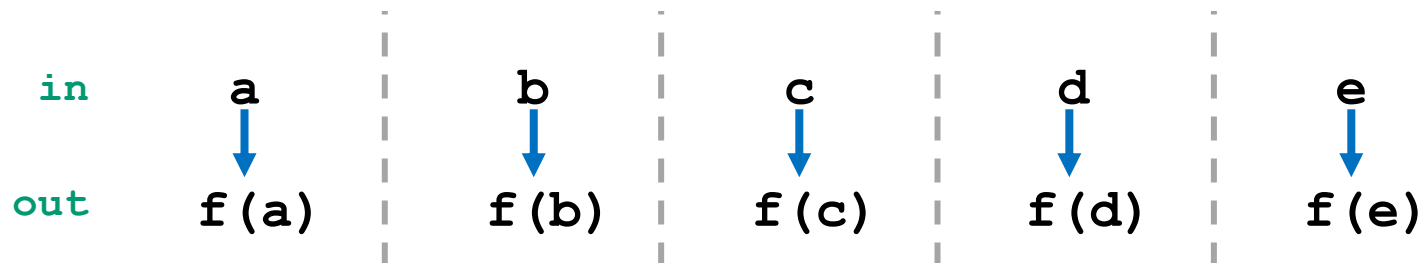**Combinational:** a function of the current inputs



 **Sequential:** a function of previous inputs (has “memory”)




# Lecture Outline

- ❖ Growth vs. Fixed Mindset
  - Setting SMART Goals
  
- ❖ Introduction to Sequential Logic
  - The Problem of Combinational Logic
  - Autopilot Control Circuit Example
  
- ❖ **Representing Time in Hardware**
  - **Clock Signals and Units of Time in Hardware**
  
- ❖ The Data Flip-Flop (DFF)
  - Implementation and Examples
 
# Representing Time: Clock Signals

- ❖ We physically represent time in hardware with a **clock signal**
  - A clock signal changes its frequency at a set time rate
  - Alternates between a low signal and a high signal of equal length
- ❖ A **cycle** is a period of time between a low and high signal
  - Represents one unit of time in hardware
  - We can change how long a unit of time is by alternating the length of the low and high signals



# Physical Timekeeping

- ❖ Hardware keeps track of time using an alternating signal
  - Creates the idea of **discrete time**: state changes only occur in discrete intervals, right when signal alternates

Physical  
Time




Clock  
Signal

1  
0



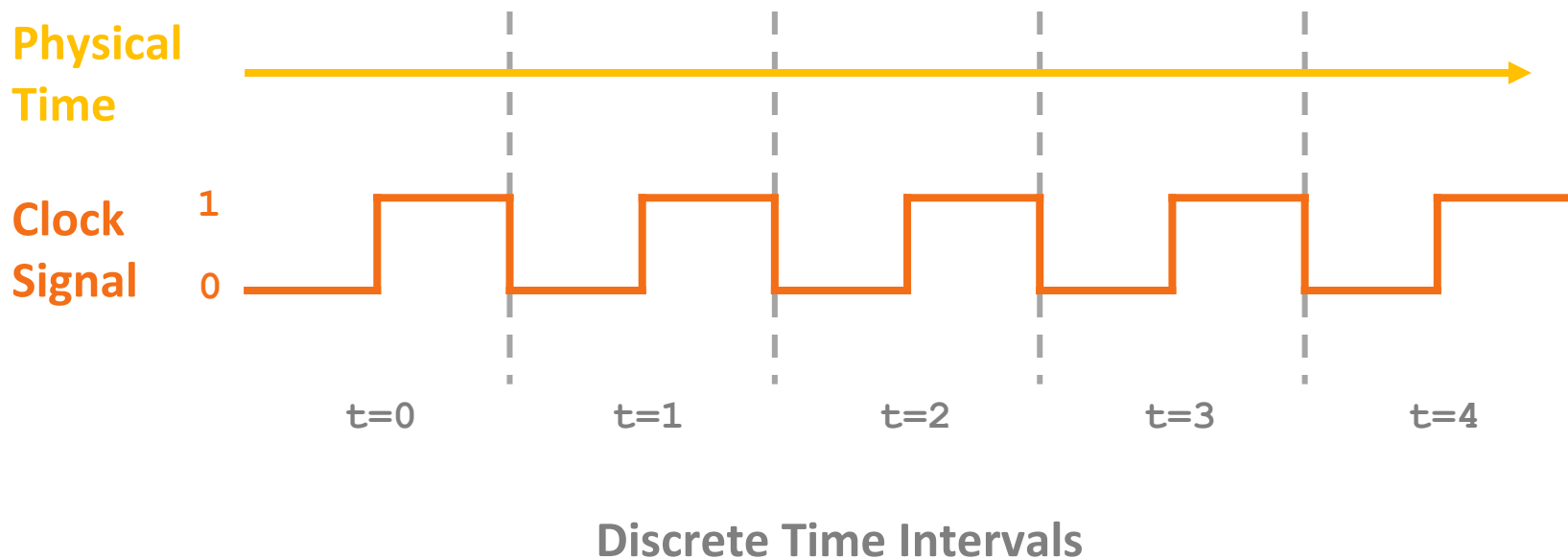
# Physical Timekeeping

- ❖ Hardware keeps track of time using an alternating signal
  - Creates the idea of **discrete time**: state changes only occur in discrete intervals, right when signal alternates






# Adding a Clock: Ideal

 


 - ❖ We want this behavior from a simple, combinational Not gate:



 
# Adding a Clock: Reality

- ❖ Combinational logic may be incorrect for a period immediately after inputs change
  - **Computation delays** (logic gates) and **propagation delays** (wires)



 
# Adding a Clock: Clock Cycles

- ❖ Choose a clock cycle length slightly longer than the delays


 
# Adding a Clock: Abstraction

- ❖ If we use a long enough clock cycle, we can *pretend* that combinational chips (like Not) work instantly



## < Lecture 5: Growth Mindset & Sequential Logic



When poll is active  
respond at

**PollEv.com**  
**/cse390b**

Send **cse390b** to  
**22333**



Which of the following statements about  
sequential logic is FALSE?



We're lost...

Current responses




# Lecture Outline

- ❖ Growth vs. Fixed Mindset
  - Setting SMART Goals
- ❖ Introduction to Sequential Logic
  - The Problem of Combinational Logic
  - Autopilot Control Circuit Example
- ❖ Representing Time in Hardware
  - Clock Signals and Units of Time in Hardware
- ❖ **The Data Flip-Flop (DFF)**
  - **Implementation and Examples**
 
# The Data Flip-Flop Gate

- ❖ Simplest state-keeping component
  - 1-bit input, 1-bit output
  - Wired to the clock signal
  - Always outputs its previous input:  $\text{out}(t) = \text{in}(t-1)$
- ❖ Implementation: a gate that can flip between two stable states (remembering 0 vs. remembering 1)
  - Gates with this behavior are “Data Flip Flops” (DFFs)





# Aside: Treating the DFF as a Primitive

- ❖ Disclaimer: DFFs can be made from Nand gates exclusively
  - But requires wiring them together in a “messy” loop that the hardware simulator can’t simulate and isn’t very educational
  
- ❖ For simplicity, we will treat the DFF as a primitive in the projects
  - Just like Nand, you can use the built-in implementation



# Data Flip-Flop (DFF) Behavior

  


# Sequential Chips

- ❖ A category of chips that utilize the clock signal, in addition to any combinational logic
  
- ❖ Capable of:
  - Maintaining state
  - Optionally, acting on that state and the current inputs
    - Can incorporate combinational logic as well
  
- ❖ Constructed from:
  - DFFs
  - Combinational logic (which is entirely constructed from Nand)

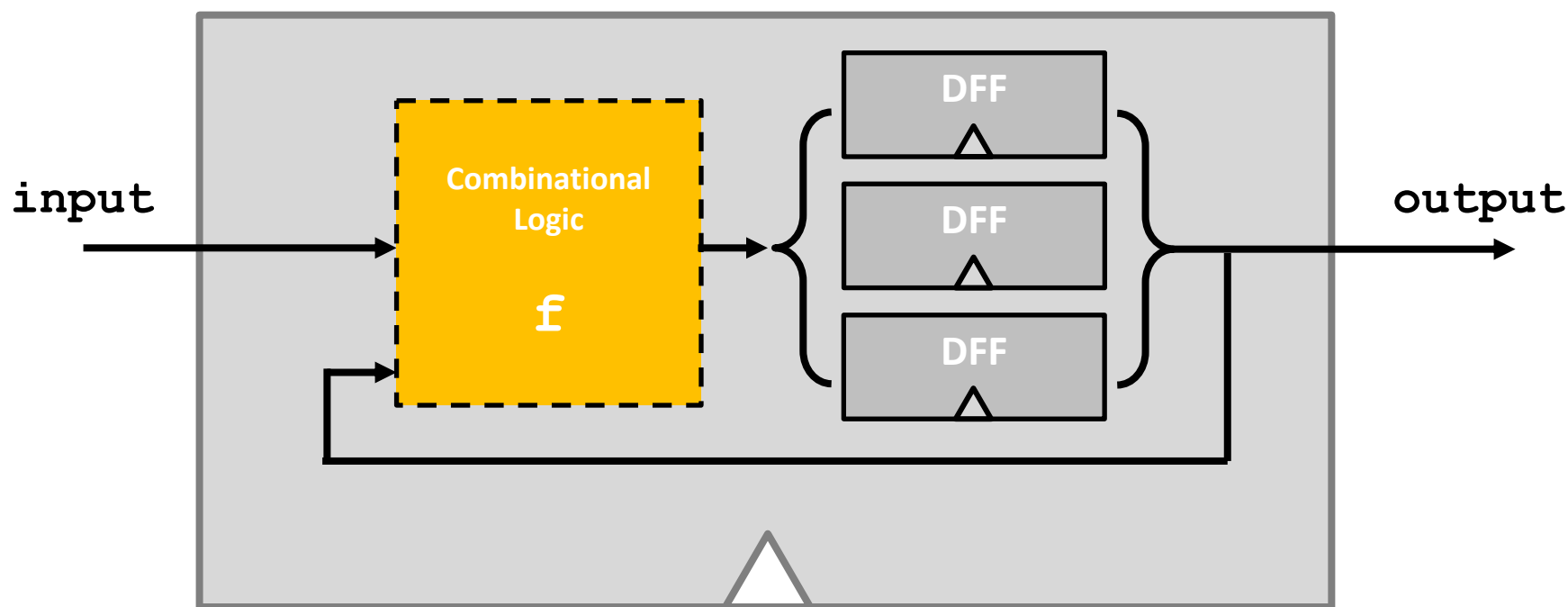
# Sequential Chips

$$\text{output}(t) = f(\text{state}(t-1), \text{input}(t))$$



# D Flip-Flop: Time Series

## ❖ DFF Specification:

 

$$\text{out}(t) = \text{in}(t-1)$$

<b>in</b>	0	0	1	1	0	1	0	...
<b>out</b>	0	0	0	1	1	0	1	...
<b>time</b>	<b>t=0</b>	<b>t=1</b>	<b>t=2</b>	<b>t=3</b>	<b>t=4</b>	<b>t=5</b>	<b>t=6</b>	...

Example:  $\text{out}(t=3) = \text{in}(t=2)$

# DFF Example 1: Specification

- ❖ Example specification:

$$\text{out}(t) = \text{Xor}(a(t-1), b(t-1))$$

- ❖ Takes two inputs,  $a$  and  $b$ , and outputs the  $\text{Xor}$  of them
  - Note that  $\text{out}$  at time  $t$  is determined by  $a$  and  $b$  at time  $t-1$
  - We will need to use a DFF
- ❖ Exercise: Draw out the corresponding circuit diagram and HDL implementation

# DFF Example 1: Time Series

❖ Example specification:

$$\text{out}(t) = \text{Xor}(a(t-1), b(t-1))$$

<b>a</b>	0	0	1	1	1	0	0	...
<b>b</b>	0	1	0	1	1	1	0	...
<b>out</b>	0	0	1	1	0	0	1	...
<b>time</b>	t=0	t=1	t=2	t=3	t=4	t=5	t=6	...

❖ Example:  $\text{out}(t=3) = \text{Xor}(a(t=2), b(t=2))$

# DFF Example 1: Circuit Diagram & HDL

- ❖ Example specification:

$$\text{out}(t) = \text{Xor}(a(t-1), b(t-1))$$

- ❖ Circuit diagram:


- ❖ HDL:

# DFF Example 1: Circuit Diagram & HDL

- ❖ Example specification:

$$\text{out}(t) = \text{Xor}(a(t-1), b(t-1))$$

- ❖ Circuit diagram:

 

- ❖ HDL:

```
CHIP Example1 {  
    IN a, b;  
    OUT out;  
  
    PARTS:  
    Xor(a=a, b=b, out=xorout);  
    DFF(in=xorout, out=out);  
}
```



# DFF Example 2: Specification

- ❖ Example specification:

$$\text{out}(t) = \text{Xor}(\text{out}(t-1), \text{in}(t-1))$$

- ❖ Notice how the specification uses  $\text{out}(t-1)$  as an input for  $\text{out}(t)$ 
  - Implies the necessity of circular wiring, separated by a DFF
- ❖ Exercise: Draw out the corresponding circuit diagram and HDL implementation

# DFF Example 2: Time Series

❖ Example specification:

$$\text{out}(t) = \text{Xor}(\text{out}(t-1), \text{in}(t-1))$$

<b>in</b>	0	0	1	1	1	0	0	...
<b>out</b>	0	0	0	1	0	1	1	...
<b>time</b>	t=0	t=1	t=2	t=3	t=4	t=5	t=6	...

❖ Example:  $\text{out}(t=1) = \text{Xor}(\text{in}(t=0), \text{out}(t=0))$

# DFF Example 2: Circuit Diagram & HDL

- ❖ Example specification:

$$\text{out}(t) = \text{Xor}(\text{out}(t-1), \text{in}(t-1))$$

- ❖ Circuit diagram:


- ❖ HDL:

# DFF Example 2: Circuit Diagram & HDL

- ❖ Example specification:

$$\text{out}(t) = \text{Xor}(\text{out}(t-1), \text{in}(t-1))$$

- ❖ Circuit diagram:

 

- ❖ HDL:

```
CHIP Example2 {
```

```
  IN in;
```

```
  OUT out;
```

```
  PARTS:
```

```
    Xor(a=in, b=prevout, out=xorout);
```

```
    DFF(in=xorout, out=prevout, out=out);
```

```
}
```

# DFF Example 3: Specification

- ❖ Example specification:

**$\text{out}(t) = \text{And}(\text{Not}(\text{out}(t-1)), \text{in}(t-1))$**

- ❖ Exercise: Draw out the corresponding circuit diagram and HDL implementation

# DFF Example 3: Time Series

❖ Example specification:

$$\text{out}(t) = \text{And}(\text{Not}(\text{out}(t-1)), \text{in}(t-1))$$

<b>in</b>	1	1	0	1	1	0	0	...
<b>out</b>	0	1	0	0	1	0	0	...
<b>time</b>	t=0	t=1	t=2	t=3	t=4	t=5	t=6	...

❖ Example:

$$\text{out}(t=1) = \text{And}(\text{Not}(\text{out}(t=0)), \text{in}(t=0))$$

# DFF Example 3: Circuit Diagram & HDL

- ❖ Example specification:

$$\text{out}(t) = \text{And}(\text{Not}(\text{out}(t-1)), \text{in}(t-1))$$

- ❖ Circuit diagram:


- ❖ HDL:

# DFF Example 3: Circuit Diagram & HDL

- ❖ Example specification:

$$\text{out}(t) = \text{And}(\text{Not}(\text{out}(t-1)), \text{in}(t-1))$$

- ❖ Circuit diagram:

 

- ❖ HDL:

```
CHIP Example3 {
```

```
  IN in;
```

```
  OUT out;
```

```
  PARTS:
```

```
    Not(in=prevout, out=notprevout);
```

```
    And(a=in, b=notprevout, out=andout);
```

```
    DFF(in=andout, out=prevout, out=out);
```

```
}
```



# Lecture 5 Reminders

- ❖ **Project 3 due this Friday (1/19) at 11:59pm**
- ❖ Amy has office hours tomorrow at 1:30pm in CSE2 151
  - Feel free to post your questions on the Ed board as well
- ❖ Eric will be out of town during Week 10
  - We will still have class together, more details to come