



Sequential logic

- State assignment (encoding state) in state machines
 - Sequential
 - One-hot
 - Output-oriented
- Communicating finite-state machines
 - Registers
 - Shift-registers
 - Counters

Can any sequential system be represented with a state diagram?

■ Shift register

  - input value shown on transition arcs
- output values shown within state node





Shift register in Verilog

```
module shift_register (clk, in, out);  
  
    input  clk;  
    input  in;  
    output [0:3] out;  
  
    reg [0:3] out;  
  
    initial begin  
        out = 0; // out[0:3] = {0, 0, 0, 0};  
    end  
  
    always @(posedge clk) begin  
        out = {in, out [0:2]};  
    end  
  
endmodule
```

Binary counter

  - Counter
 - ❑ 3 flip-flops to hold state
 - ❑ Logic to compute next state
 - ❑ Much simpler state diagram -> more complex logic
- Is there a relationship between state diagram and logic needed?




Binary counter in Verilog

```
module binary_counter (clk, c8, c4, c2, c1);  
    input      clk;  
    output     c8, c4, c2, c1;  
  
    reg [3:0] count;  
  
    initial begin count = 0; end  
  
    always @(posedge clk) begin  
        count = count + 4'b0001;  
    end  
  
    assign c8 = count[3];  
    assign c4 = count[2];  
    assign c2 = count[1];  
    assign c1 = count[0];  
  
endmodule
```

State machine for Lab 5

- Only 4 states
 - Output = state

 

SW[1]	SW[0]	Meaning	Pattern (LEDR[2:0])
0	0	Calm	1 0 1 0 1 0
0	1	Right to Left	0 0 1 0 1 0 1 0 0
1	0	Left to Right	1 0 0 0 1 0 0 0 1


State assignment in Lab 5

- 8 states
- Sequential state assignments
 - ❑ Number states 0 to 7 – 3 bits
 - ❑ Need logic to translate state number to outputs
- One-hot
 - ❑ 8 bits, one is true for each state
 - ❑ Need logic to translate state number to outputs
- Output-oriented
 - ❑ Exploit outputs as part of state
 - ❑ Easy translation to output
 - ❑ See previous slide

SW[1]	SW[0]	Meaning	Pattern (LEDR[2:0])
0	0	Calm	1 0 1 0 1 0
0	1	Right to Left	0 0 1 0 1 0 1 0 0
1	0	Left to Right	1 0 0 0 1 0 0 0 1


ALM: adaptive logic module

- The following types of functions can be realized in a single ALM:
 - ❑ Two independent 4-input functions
 - ❑ An independent 5-input function and an independent 3-input function
 - ❑ A 5-input function and a 4-input function, if they share one input
 - ❑ Two 5-input functions, if they share two inputs
 - ❑ An independent 6-input function
 - ❑ Two 6-input functions, if they share four inputs and share function
 - ❑ Some 7-input functions
- An ALM also has 4 bits of memory
 - ❑ We'll discuss later when we talk about sequential logic

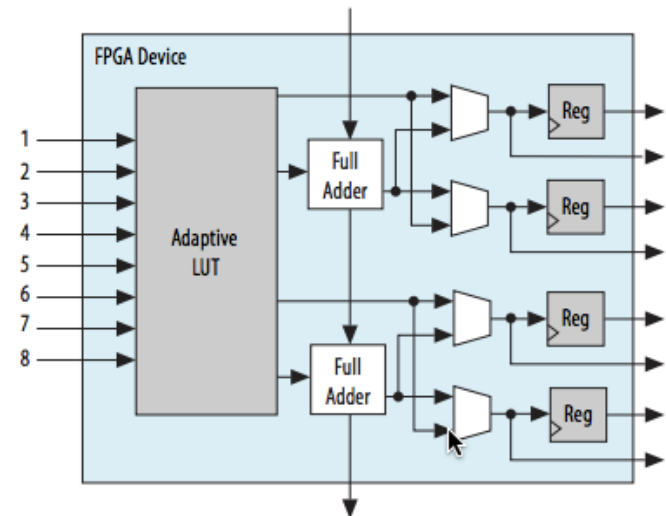


Registers

 - Collections of flip-flops with similar controls and logic
 - ❑ stored values somehow related (for example, form binary value)
 - ❑ share clock, reset, and set lines
 - ❑ similar logic at each stage
- Examples
 - ❑ shift registers
 - ❑ counters




Shift register

 - Holds samples of input
 - store last 4 input values in sequence
 - 4-bit shift register:



Universal shift register

 - Holds 4 values
 - ❑ serial or parallel inputs
 - ❑ serial or parallel outputs
 - ❑ permits shift left or right
 - ❑ shift in new values from left or right



clear sets the register contents and output to 0


s1 and s0 determine the shift function

s0	s1	function
0	0	hold state
0	1	shift right
1	0	shift left
1	1	load new input

Design of universal shift register


- Consider one of the 4 flip-flops
 - new value at next clock cycle:

clear	s0	s1	new value
1	—	—	0
0	0	0	output
0	0	1	output value of FF to left (shift right)
0	1	0	output value of FF to right (shift left)
0	1	1	input

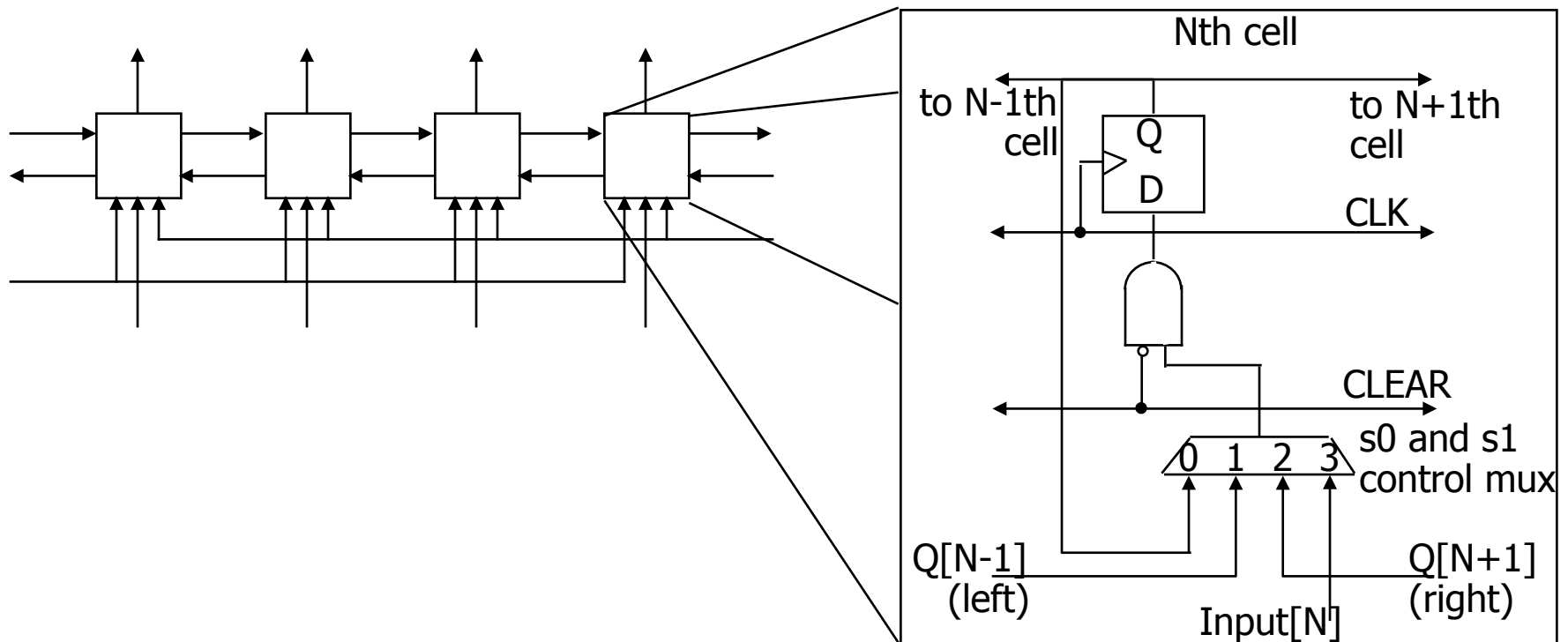


Shift register application

 - Parallel-to-serial conversion for serial transmission




Pattern recognizer

 - Combinational function of input samples
 - in this case, recognizing the pattern 1001 on the single input signal




Counters

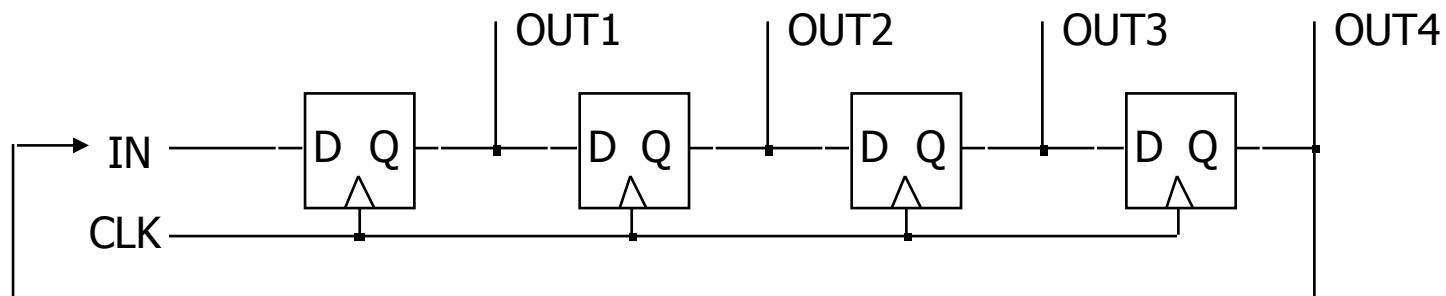- Sequences through a fixed set of patterns
 - in this case, 1000, 0100, 0010, 0001
 - if one of the patterns is its initial state (by loading or set/reset)




Mobius counter

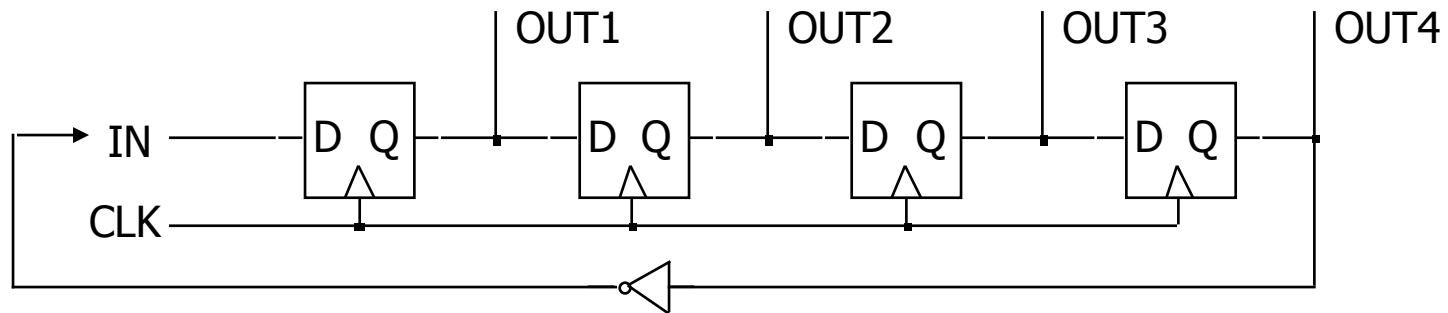- How does this counter work (assuming it starts in state 0000)?




Binary counter

 - Logic between registers (not just multiplexer)
 - XOR decides when bit should be toggled
 - always for low-order bit,
only when first bit is true for second bit,
and so on



How fast is our counter?

 
- $\text{Period} > T_{\text{propFF}} + T_{\text{propCL}} + T_{\text{setupFF}}$



- $\text{Period} > 3.6\text{ns} + \max(T_{\text{propCL}}) \{ \text{over all paths from Qs to Ds} \} + 1.8\text{ns}$
- $\text{Period} > 5.4\text{ns} + T_{\text{propXOR}} + T_{\text{propAND3}}$
- $\text{Frequency} < 1/\text{Period}$

Tug-of-War Game FSM (NOT the same as Lab #6)

 - Tug of War game
 - 7 LEDS, 2 push buttons (LPB, RPB)



Light Game FSM Verilog

```
module Light_Game (LEDS, LPB, RPB, CLK, RESET);
```

```
    input LPB ;
    input RPB ;
    input CLK ;
    input RESET;
    output [6:0] LEDS ;

    reg [6:0] position;
    reg left;
    reg right;
```


combinational logic and wires

```
    wire L, R;
    assign L = ~left && LPB;
    assign R = ~right && RPB;
    assign LEDS = position;
```

sequential logic

```
    always @(posedge CLK)
    begin
        left <= LPB;
        right <= RPB;
        if (RESET) position <= 7'b0001000;
        else if ((position == 7'b0000001) || (position == 7'b1000000)) ;
        else if (L) position <= position << 1;
        else if (R) position <= position >> 1;
    end
```

```
endmodule
```

 

Do you see a problem with this game?

Activity

- Where is the problem? What is the fix?


```
always @(posedge CLK) begin
    left <= LPB;
    right <= RPB;
    if (RESET) position <= 7'b0001000;
    else if ( (position == 7'b0000001) || (position == 7'b1000000) )
        position <= position;
    else if (L) position <= position << 1;
    else if (R) position <= position >> 1;
end
```

```
always @(posedge CLK) begin // no longer biased in favor of L player
    left <= LPB;
    right <= RPB;
    if (RESET) position <= 7'b0001000;
    else if ( (position == 7'b0000001) || (position == 7'b1000000) )
        position <= position;
    else if (L & ~R) position <= position << 1; // correct error in state diag.
    else if (R & ~L) position <= position >> 1; // favoring L player
    else
        position <= position; // otherwise, just hold
```

Lab #6





- 2 user-input FSMs for push buttons
 - ❑ One cycle pulse every time a button is pressed
- Tug-of-war game with a separate FSM for each LED (9 of them)
 - ❑ 1 center-light (lights up on reset)
 - ❑ 8 normal-lights (goes dark on reset)
- Victory logic
 - ❑ Input from first and last FSM and two buttons
 - ❑ If left-most light is on and left button pressed, then left wins
 - ❑ Similarly for right
 - ❑ Control HEX0 to display winner: 0 or 1, L or R, etc.
- Consider how a game ends
 - ❑ Do you want both push buttons still working after a player wins?

Input FSM – simple shift register

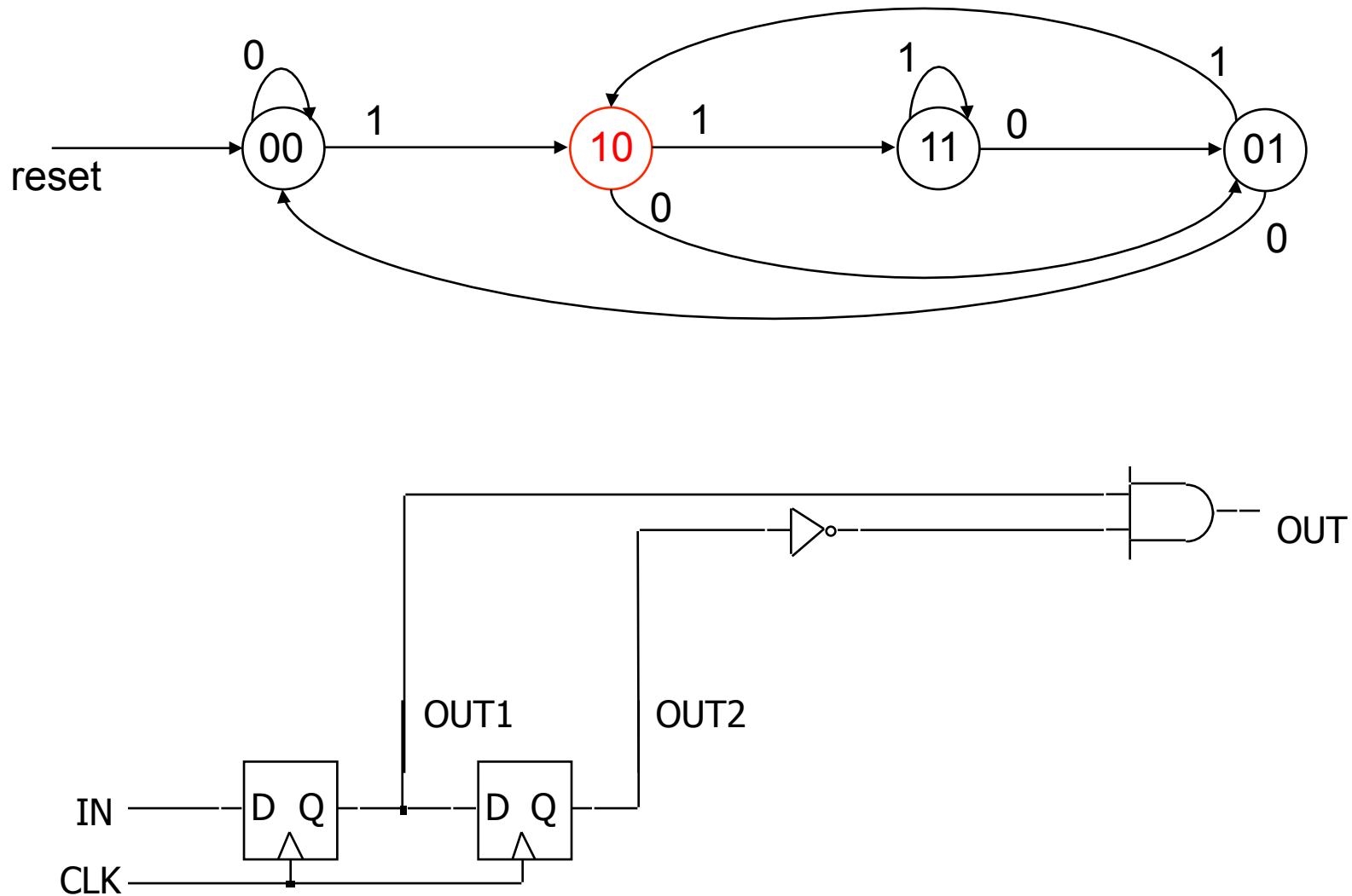

Communicating finite state machines

    - One machine's output is another machine's input



machines advance in lock step
initial inputs/outputs: $X = 0$, $Y = 0$