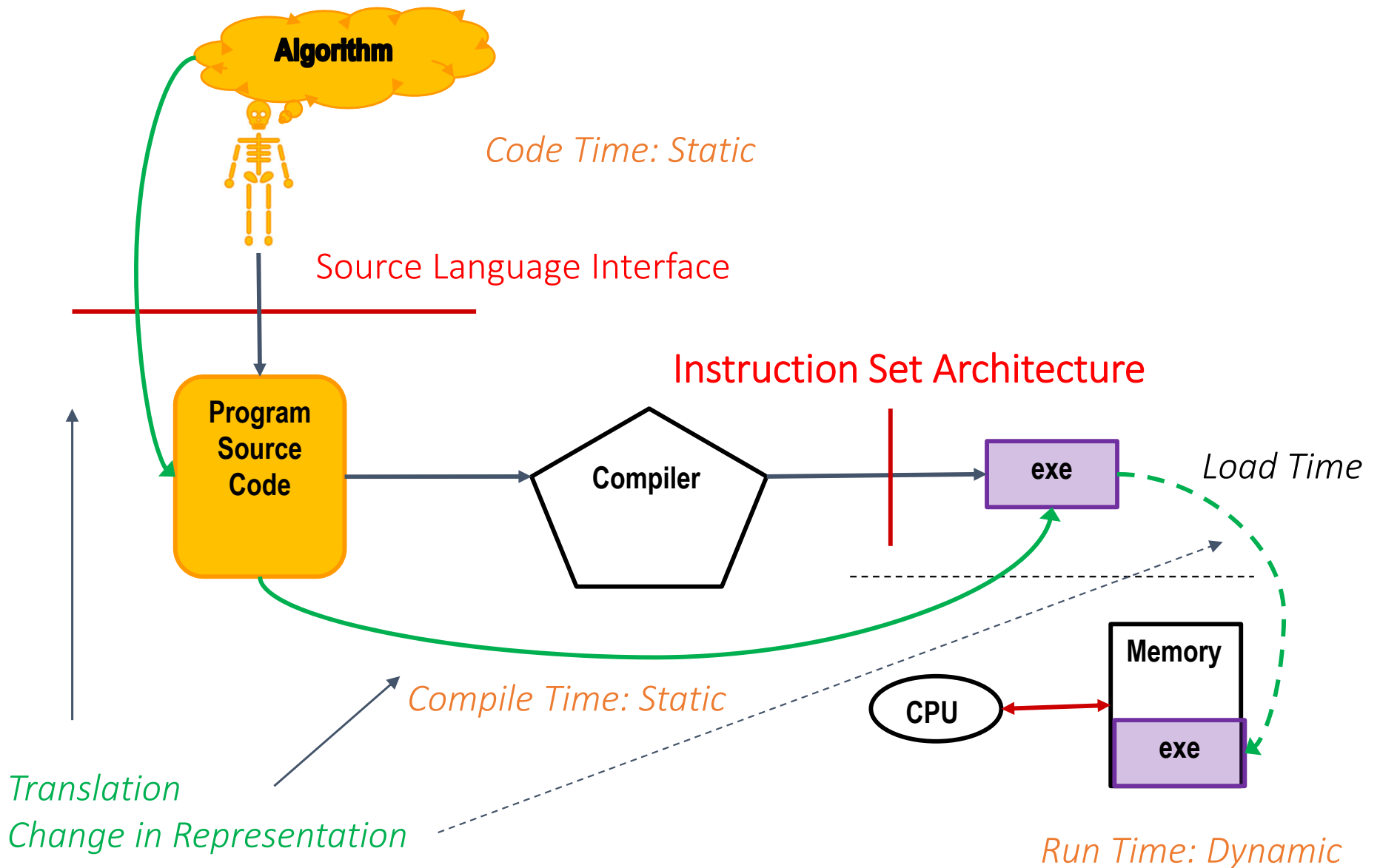


Boolean Circuits


CSE 410

Lecture 7

The Course So Far




What This Course is About

 


Software in Execution


Instruction Set Architecture

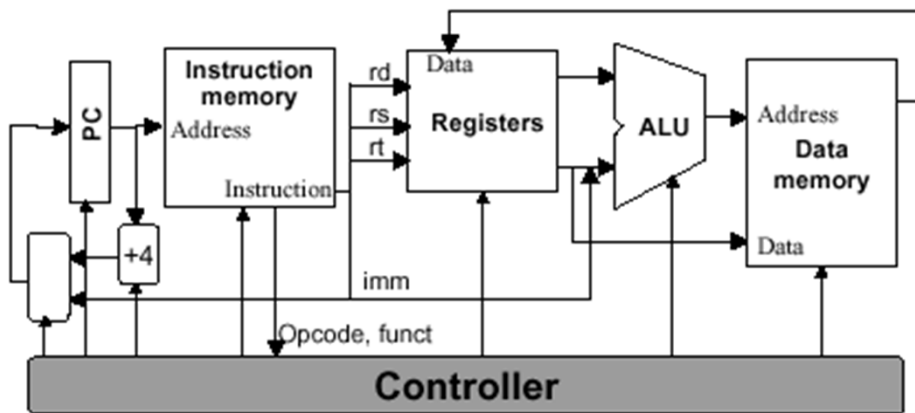

Machine Organization

 

Logic Implementation

 

Hardware

Lecture Outline

- **Boolean Functions, Logic Gates, and Boolean Circuits**
- **Example Combinational Components**
 - Adder
 - Multiplexor
- **Sequential Component**
 - example gated d latch

Boolean Functions

- A function where the inputs and output have value 0 or 1
- Represented by a **truth table**
 - 0 is false
 - 1 is true
- There are 2^{2^k} distinct Boolean functions with k inputs

Not ($\neg x$)

Input	Output
0	1
1	0


Or ($X + Y$)

Inputs		Output
0	0	0
0	1	1
1	0	1
1	1	1

AND/ OR/ NOT gates

- Digital circuits are built out of digital **gates**
- Each gate implements some logic function

NOT

 

Input	Output
A	C
0	1
1	0

AND



Inputs		Output
A	B	C
0	0	0
0	1	0
1	0	0
1	1	1


OR




Inputs		Output
A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

Combinational Circuit

 - We can connect these components together into circuits
- What function does this two-input circuit compute?



Example Circuit

 

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	0

$$(\neg A \wedge B) \vee (A \wedge \neg B)$$

Exclusive Or


Other Gates

Exclusive-OR gate




A	B	Output
0	0	0
0	1	1
1	0	1
1	1	0

NAND gate

 


A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0

NOR

 

A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0

Exclusive NOR (XNOR)

 

A	B	Output
0	0	1
0	1	0
1	0	0
1	1	1

Computing: Binary Addition


Examples:

0	1
<u>1</u>	<u>1</u>
01	10

Inputs		Outputs	
P	Q	CO	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


1-bit (half) adder

Inputs		Outputs	
P	Q	CO	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 


4-bit adder

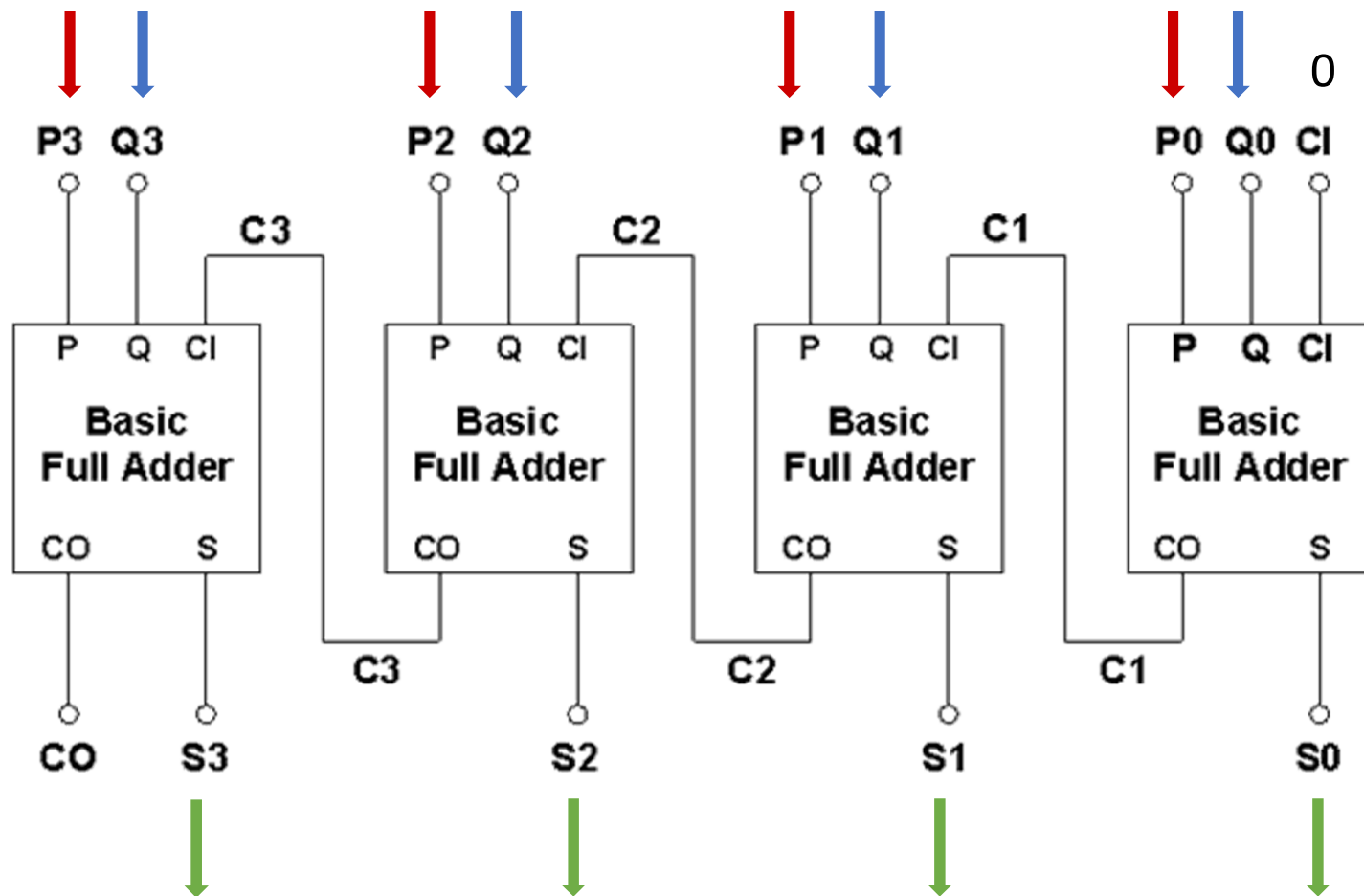If we had as a component a 3-input 1-bit adder (a “full adder”) we could use it to build an n-bit adder




1-bit full adder

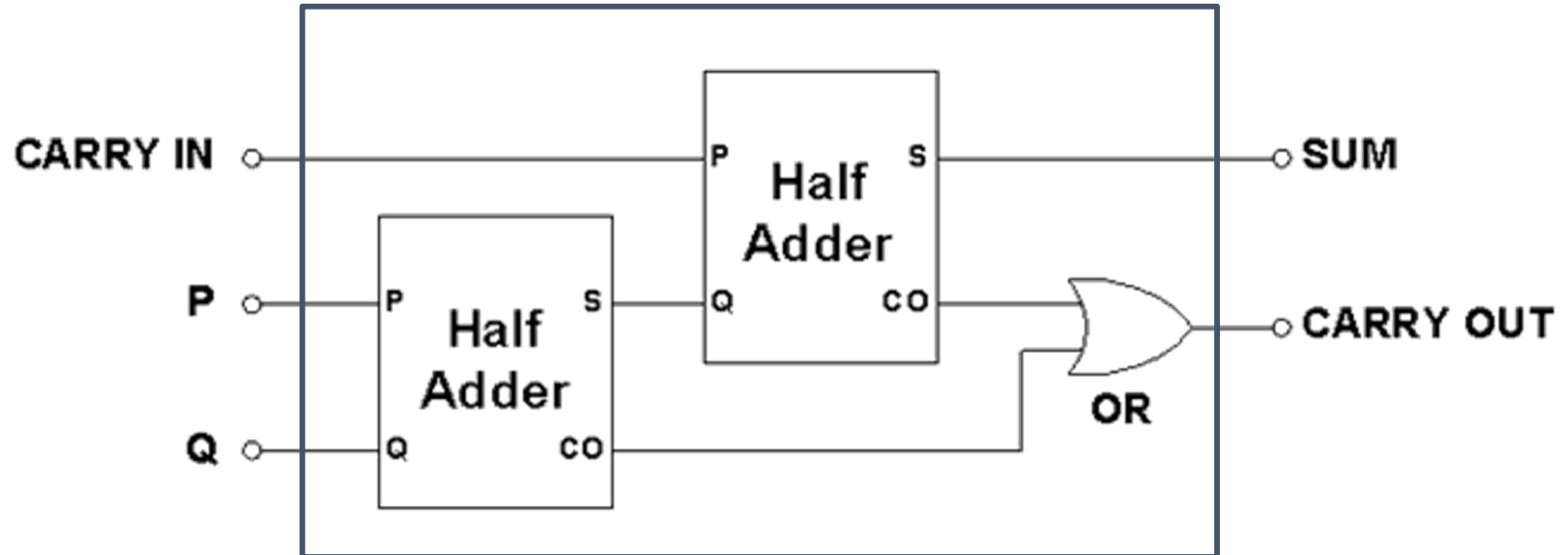


Direct Implementation in Gates

Input			Output	
A	B	Cin	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 


4-bit full (ripple carry) adder

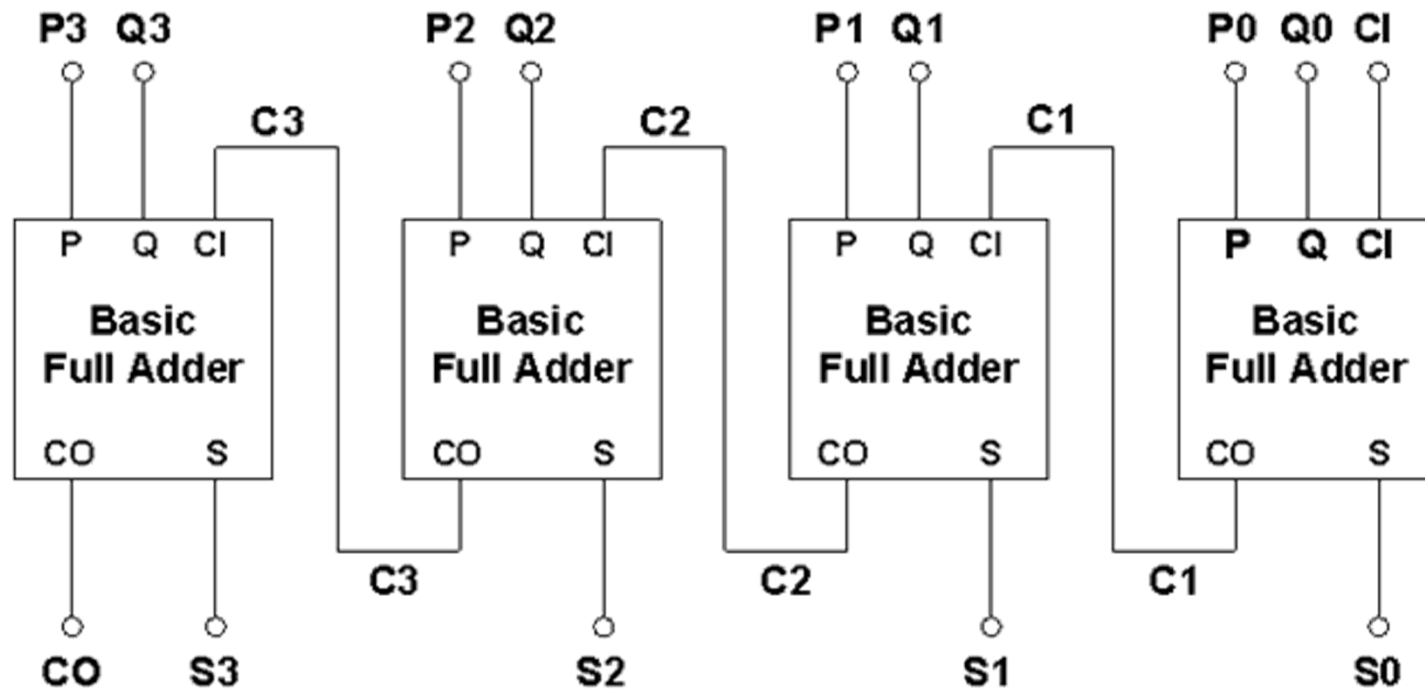

Sequential component: storage


- The outputs of combinational components is a function of their inputs (after some delay)
- Combinational circuits can have no loops
 - Loops create instability
- Sequential circuits can have loops
- How?
 - Components whose output is stable even when inputs are changing
 - Storage

Sequential Circuit: Operation

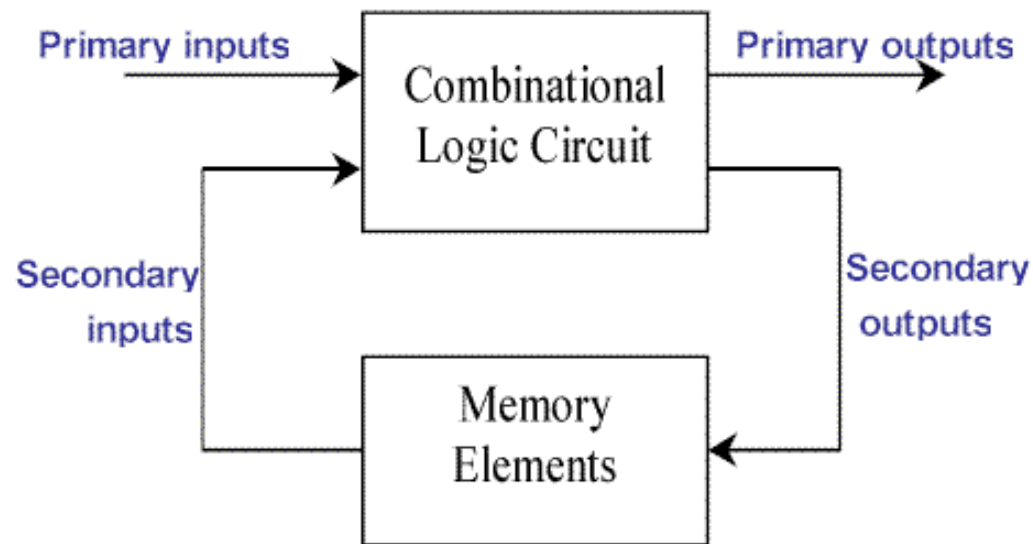


- At time n the memory elements have some values
 - The combinational circuit has “settled” and its output are stable (unchanging)
 - If we update the memory elements values, though, the outputs of the combinational circuit change

Example: Accumulator Circuit

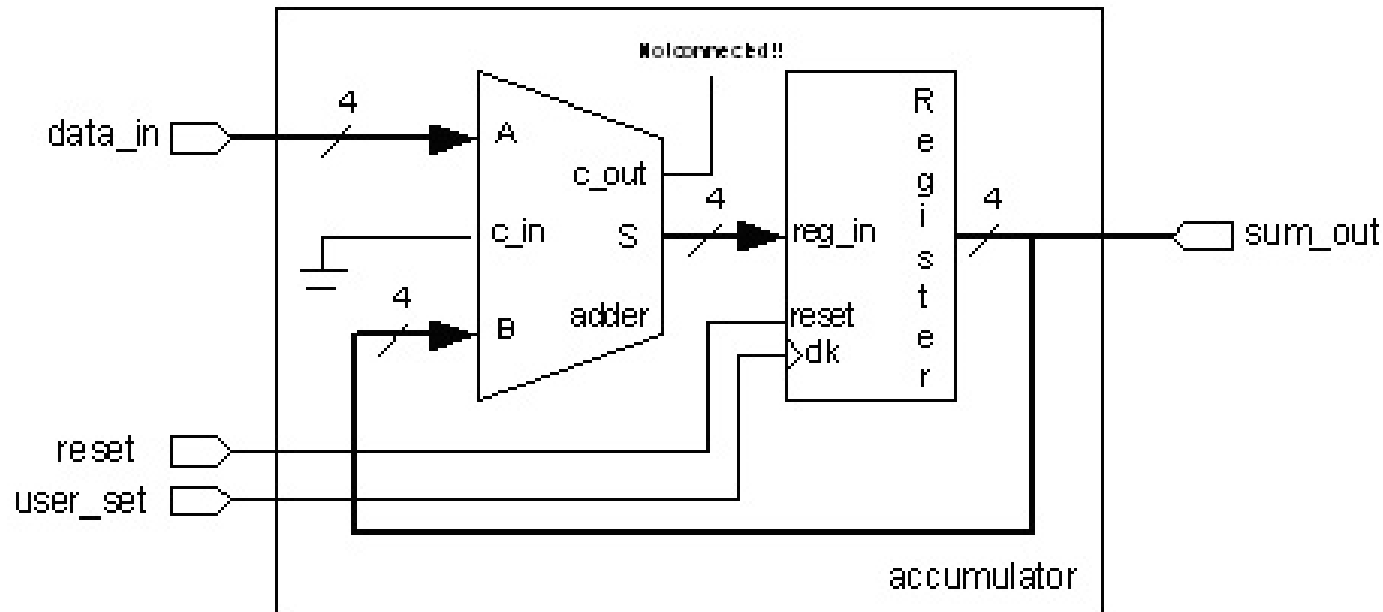


- Here the inputs are 4 bits wide (“/4”)
- If $\text{data_in} == 0001$ and the register holds 0010, the output of the adder will eventually be 0011
- When we update the register, the adder will eventually output 0011

Sequential Circuit: Clocks

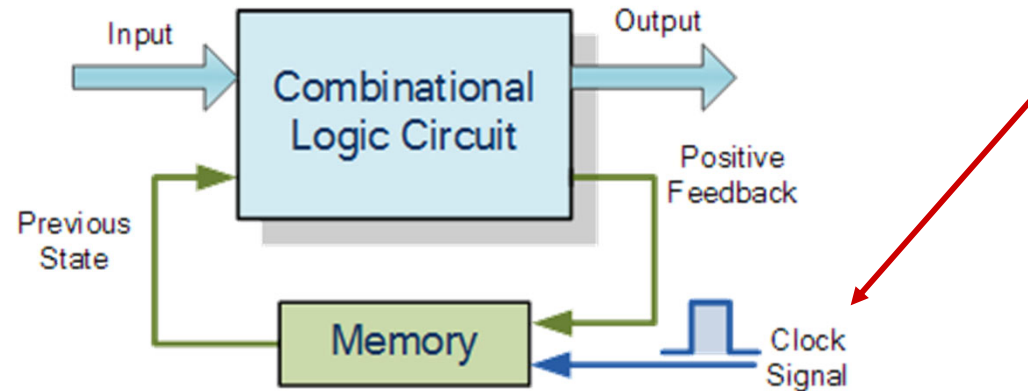

- It takes time for the combinational circuit to “settle” when its inputs change
- We don’t want to update the memory component while the combinational circuit is settling
- We control the rate of update using a “clock signal”
 - This is what’s behind processor specifications like “3.6GHz i5-8600K” versus “2.8GHz i5-8400”
 - Warning: A 4.0GHz processor is very unlikely to be anywhere near twice as fast as a 2GHz processor

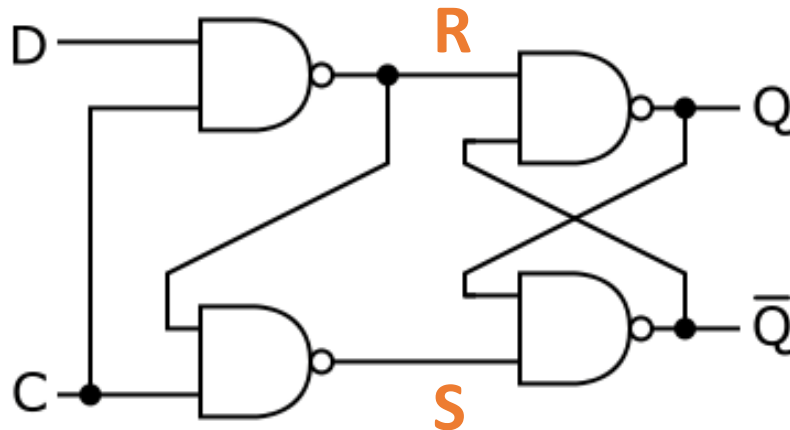
Implementing sequential components: the gated d-latch



- Component stores 1 bit, and advertises both its value (Q) and the negation of its value (\bar{Q})
- When $C(\text{lock})=1$ the output Q records the value of D
 - if $D=1$ then $R=0$ and $S=1$. $R=0$ makes $Q=1$. $Q=1$ makes $\bar{Q}=0$.
 - if $D=0$ then $R=1$ and $S=0$. $S=0$ makes $\bar{Q}=1$, which makes $Q=0$.
- When $C=0$ the output ignores the value of D
 - both R and S are 1. If $Q=1$ then \bar{Q} is 0 – no change. If $Q=0$, then \bar{Q} is 1 – no change.

Other combinational components

 - **Multiplexor** – select one of two inputs




- We can expand this implementation by
 - Allowing the inputs (I0 and I1) to be n bits wide
 - Cascading the two-input multiplexor to make allow more inputs
 - Implies widening the selector input, S


Looking ahead: CPU data path

Instruction Format

RD	RI ₀	RI ₁
2 bits	2 bits	2 bits

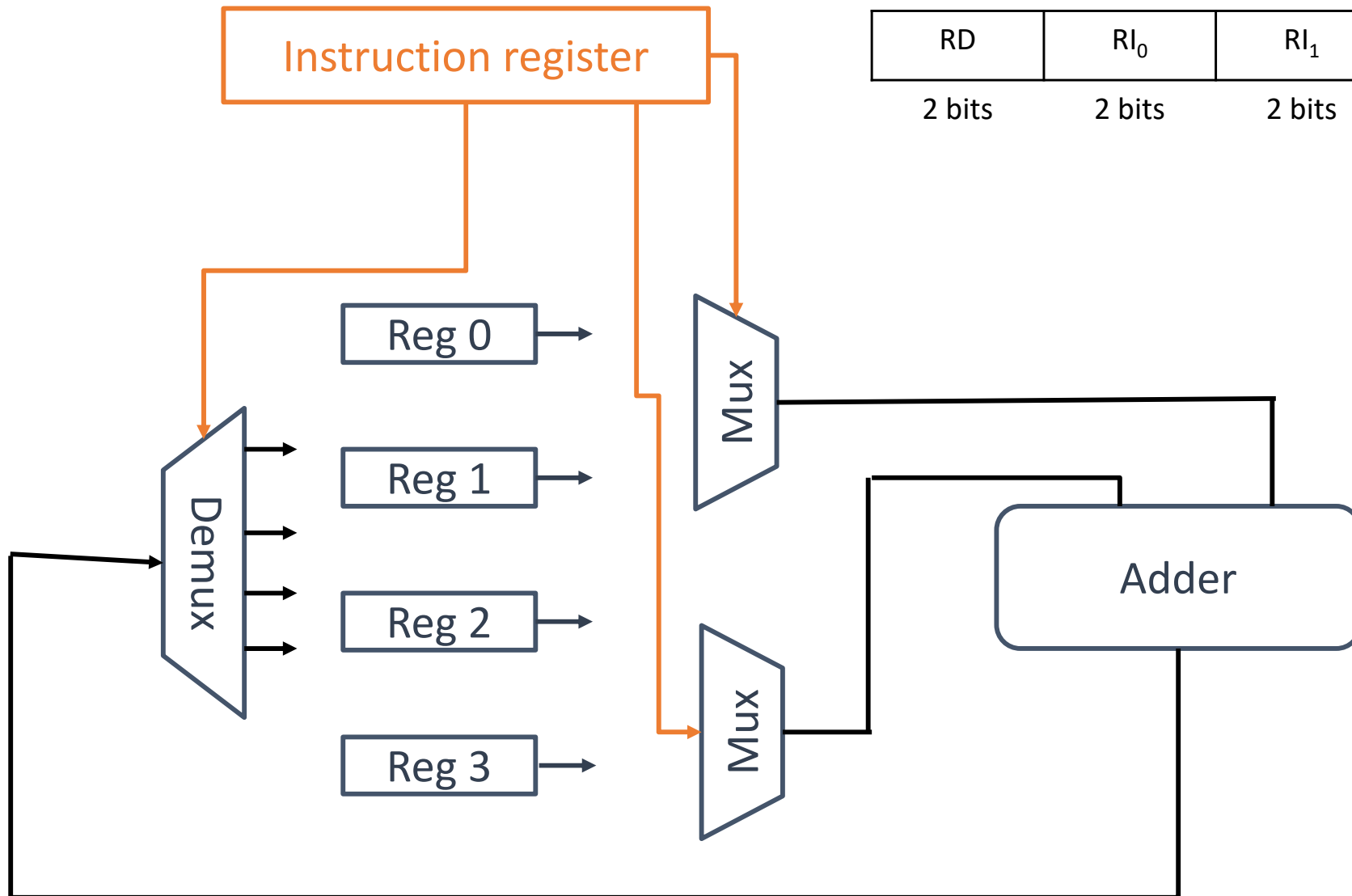



Lecture/Course Summary

 


Software in Execution

Instruction Set Architecture

Machine Organization

 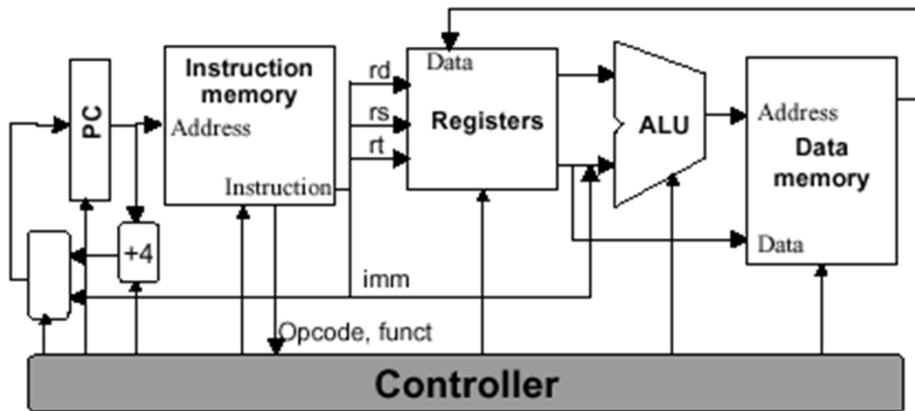

Logic Implementation

 

Hardware