

Datapath / Machine Organization

CSE 410

Lecture 08


Lecture Outline

- **The Datapath**
 - **Basic Components**
 - **Basic Datapath Layout**
 - **Basic Datapath Operation**

Datapath

- We've looked at how to create circuits composed of logic (gates) that perform some computing functions
- We now move up a level of abstraction – the basic components are not gates, but rather small circuits that perform more powerful functions, for example
 - adder
 - multiplexor
- This level of design is called “machine organization”


Single-Cycle Datapath

 

18-447-S19-L03-S27, James C. Hoe, CMU/ECE/CALCM, ©2019


[Figure 4.17 from book, Copyright © 2018 Elsevier Inc. All rights reserved.]

Components: Instruction Fetch

 


- A hardware register holds the PC
- An instruction fetch component can retrieve words of memory
 - Takes as an input the address to be fetched
 - We'll use the PC
 - Gives as an output the 32-bits at that memory address

Components: Register File

 


- Contains 32 32-bit registers
- Inputs:
 - Two register numbers, to be read
 - A one-bit “control” input indicating whether or not to write a register
 - A write register number
 - Write register data
- Outputs:
 - Contents of read registers whose numbers were given as inputs

Components: ALU

 

- Performs add, subtract, mul, div, and, or, etc.
- Inputs:
 - 2 32-bit data items
 - Control line indicating what operation to perform
- Output:
 - Result of the operation on the input values

Components: Memory Interface

 

- Inputs:
 - An address to be (possibly) read or written
 - Data to be written
 - Control lines indicating whether to do a read or a write (or neither)
- Output
 - Word read from memory, if a read is done

The Control Component



- Control is in charge of making sure the correct items are written (to memory ,register, or PC), depending on what the instruction is
- There is no incentive to not compute something that will not be written
 - E.g., don't care what data is fed to the register file as the write data if the register file won't be written


Reminder: Instruction Formats

CORE INSTRUCTION FORMATS

	31	27	26	25	24	20	19	15	14	12	11	7	6	0
R	funct7				rs2		rs1		funct3		rd		Opcode	
I	imm[11:0]						rs1		funct3		rd		Opcode	
S	imm[11:5]				rs2		rs1		funct3		imm[4:0]		opcode	
SB	imm[12 10:5]				rs2		rs1		funct3		imm[4:1 11]		opcode	
U	imm[31:12]										rd		opcode	
UJ	imm[20 10:1 11 19:12]										rd		opcode	


- If a register will be written, reg number in bits 11:7
- If one register read, number in bits 19:15
- If two registers read, second number in bits 24:20
- If there's an immediate:
 - sign bit in bit 31
 - bits 10:5 of immediate in bits 30:25 of instruction

Single-Cycle Datapath

 


[Figure 4.17 from book, Copyright © 2018 Elsevier Inc. All rights reserved.]

add x3, x2, x1 – PC update

 


[Figure 4.17 from book, Copyright © 2018 Elsevier Inc. All rights reserved.]

add x3, x2, x1 – fetch x2, x1

 


[Figure 4.17 from book, Copyright © 2018 Elsevier Inc. All rights reserved.]

add x3, x2, x1 – perform addition

 


[Figure 4.17 from book, Copyright © 2018 Elsevier Inc. All rights reserved.]

  add x3, x2, x1 – write result into x3

 


[Figure 4.17 from book, Copyright © 2018 Elsevier Inc. All rights reserved.]


addi x3, x2, 1 – differences from add



[Figure 4.17 from book, Copyright © 2018 Elsevier Inc. All rights reserved.]


$$|w_{x3,12(x2)}$$


beq x2, x3, 128

 


[Figure 4.17 from book, Copyright © 2018 Elsevier Inc. All rights reserved.]

sl x4, x3, 29 – what are control values?

 


[Figure 4.17 from book, Copyright © 2018 Elsevier Inc. All rights reserved.]

jalr x2, 64(x6) – what's missing in datapath?

 

[Figure 4.17 from book, Copyright © 2018 Elsevier Inc. All rights reserved.]

Datapath Summary

 

18-447-519-L03-S27, James C. Hoe, CMU/ECE/CALCM, ©2019

[Figure 4.17 from book, Copyright © 2018 Elsevier Inc. All rights reserved.]

- Major Components:
 - Control
 - Instruction Fetch & PC Control
 - Register File
 - ALU operation
 - Memory Read/Write
 - Register Write Data