


Interfacing

- Connecting the computation capabilities of a microcontroller to external signals
 - Transforming variable values into voltages and vice-versa
 - Digital and analog
- Issues
 - How many signals can be controlled?
 - How can digital and/or analog inputs be used to measure different physical phenomena?
 - How can digital and/or analog outputs be used to control different physical phenomena?

Controlling and reacting to the environment


- To control or react to the environment we need to interface the microcontroller to peripheral devices
 - Microcontroller may contain specialized interfaces to sensors and actuators
- Things we want to measure or control
 - light, temperature, sound, pressure, velocity, position
- Sensors
 - e.g., switches, photoresistors, accelerometers, compass, sonar
- Actuators
 - e.g., motors, relays, LEDs, sonar, displays, buzzers

Typical control system

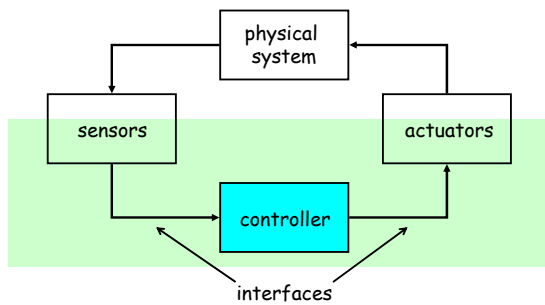


Analog to digital conversion

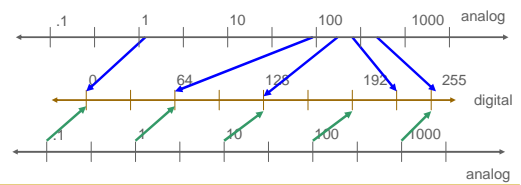- Map analog inputs to a range of binary values
 - 8-bit A/D has outputs in range 0-255
- What if we need more information?
 - linear vs. logarithmic mappings
 - larger range of outputs (16-bit a/d)




Logarithm of a signal

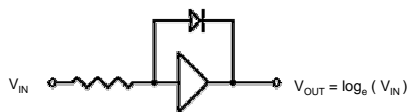- Usually use an op-amp circuit
- Often found as a pre-amplifier to ADC circuitry
- Simple circuit to compute natural logarithm




Digital to analog conversion

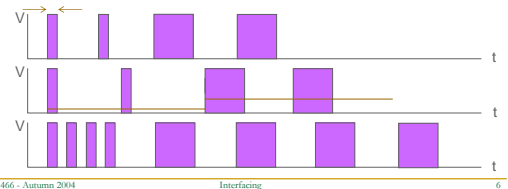- Map binary values to analog outputs (voltages)
- Most devices have a digital interface – use time to encode value
- Time-varying digital signals – almost arbitrary resolution
 - pulse-code modulation (data = number or width of pulses)
 - pulse-width modulation (data = duty-cycle of pulses)
 - frequency modulation (data = rate at which pulses occur)



Pulse-width modulation

- Pulse a digital signal to get an average “analog” value
- The longer the pulse width, the higher the voltage

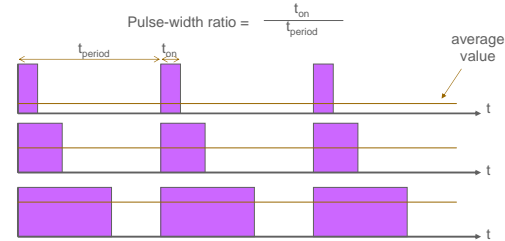

CSE 466 - Autumn 2004

Interfacing

7

Why pulse-width modulation works

- Most mechanical systems are low-pass filters
 - Consider frequency components of pulse-width modulated signal
 - Low frequency components affect components
 - They pass through
 - High frequency components are too fast to fight inertia
 - They are “filtered out”
- Electrical RC-networks are low-pass filters
 - Time constant ($\tau = RC$) sets “cutoff” frequency that separates low and high frequencies

CSE 466 - Autumn 2004

Interfacing

8

Anti-lock brake system


- Rear wheel controller/anti-lock brake system
 - Normal operation
 - Regulate velocity of rear wheel
 - Brake pressed
 - Gradually increase amount of breaking
 - If skidding (front wheel is moving much faster than rear wheel) then temporarily reduce amount of breaking
- Inputs
 - Brake pedal
 - Front wheel speed
 - Rear wheel speed
- Outputs
 - Pulse-width modulation rear wheel velocity
 - Pulse-width modulation brake on/off

CSE 466 - Autumn 2004

Interfacing

9

Rear wheel controller/anti-lock brake system

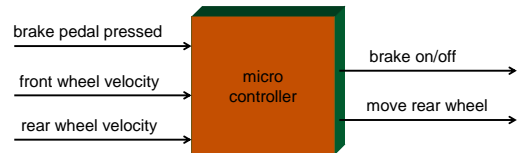


CSE 466 - Autumn 2004

Interfacing

10

Basic I/O ports (brakes)

- Check if brake pedal pressed – or interrupt
 - brakePressed = read (brakePedalPort)
- Turn brake on/off
 - write (brakePort, onOff)
- Move rear wheel
 - write (rearWheel, onOff)

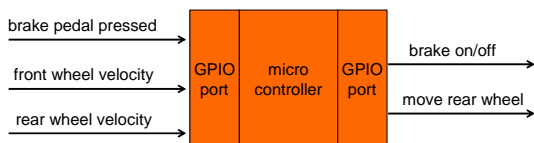


CSE 466 - Autumn 2004

Interfacing

11

Polling vs. interrupts

- Software must repeatedly check
 - Brake pedal port
 - How often?
 - Need to make sure not to forget to do so (use timer)
- Use automatic detection capability of processor
 - Connect brake pedal to input capture or external interrupt pin
 - Interrupt on level change
 - Interrupt handler for brake pedal

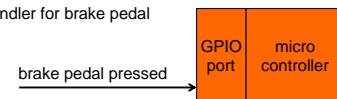


CSE 466 - Autumn 2004

Interfacing

12

Pulse-width modulation for brakes

- To pump the brakes gradually increase the duty-cycle (t_{on}) until car stops

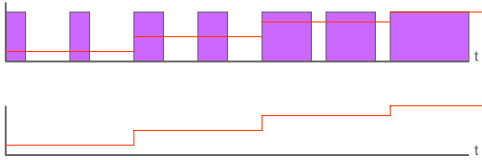

CSE 466 - Autumn 2004

Interfacing

13

Brake pump setup

- Use timer to turn brake on and off
 - Apply brake
 - Set timer to interrupt after "on" time
 - Disengage brake
 - Set time to interrupt after "off" time
 - Repeat
- How do we tell which interrupt is which?




CSE 466 - Autumn 2004

Interfacing

14

Brake pump setup (cont'd)

- Change value of "on" time to change analog average
 - average output = (on + off) / (period)
- How do we decide on the period of the pulses?
- Using two timers
 - One to set period (auto-reload)
 - One to turn it off at the right duty cycle

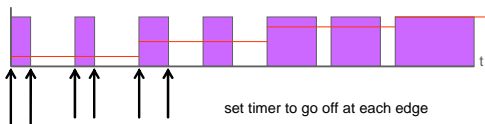


CSE 466 - Autumn 2004

Interfacing

15

Shaft encoders

- Need to determine the rear wheel velocity
 - Use sensor to detect wheel moving
- Determine speed of a bicycle
 - Attach baseball card so it pokes through spokes
 - Number of spokes is known
 - Count clicks per unit time to get velocity
- Baseball card sensor is a shaft encoder

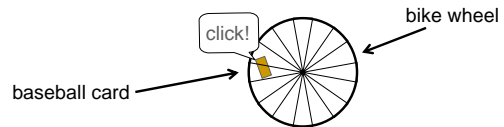


CSE 466 - Autumn 2004

Interfacing

16

Shaft encoders

- Instead of spokes we'll use black and white segments
- Black segments absorb infrared light, white reflects
- Count pulses instead of clicks

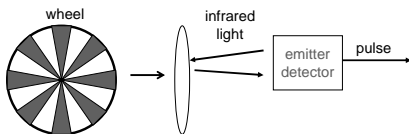


CSE 466 - Autumn 2004

Interfacing

17

IR reflective patterns

- How many segments should be used?
 - More segments give finer resolution
 - Fewer segments require less processing
 - Tradeoff resolution and processing

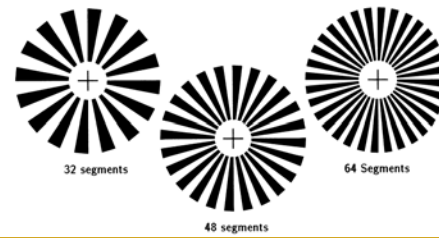

CSE 466 - Autumn 2004

Interfacing

18

Interfacing shaft encoders

- Use interrupt on GPIO pin
 - Every interrupt, increment counter
- Use timer to set period for counting
 - When timer interrupts, read GPIO pin counter
 - velocity = counter * "known distance per click" / "judiciously chosen period"
 - Reset counter
- Pulse accumulator function
 - Common function
 - Some microcontrollers have this in a single peripheral device
 - Basically a counter controlled by an outside signal
 - Signal might enable counter to count at rate of internal clock – to measure time
 - Signal might be the counter's clock – to measure pulses
 - ATmega16 has external clock source for timer/counter

General interfaces to microcontrollers


- Microcontrollers come with built-in I/O devices
 - Timers/counters
 - GPIO
 - ADC
 - Etc.
- Sometimes we need more . . .
- Options
 - Get a microcontroller with a different mix of I/O
 - Get a microcontroller with expansion capability
 - Parallel memory bus (address and data) exposed to the outside world
 - Serial communication to the outside world

I/O ports

- There are never enough I/O ports
- Techniques for creating more ports
 - port sharing with simple glue logic
 - decoders/multiplexors
 - memory-mapped I/O
 - port expansion units
- Direction of ports is important
 - single direction port easier to implement
 - timing important for bidirectional ports


Port sharing

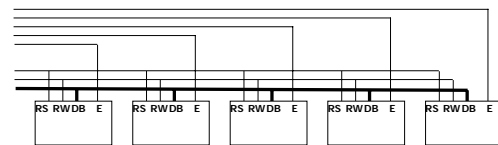- If signals all in same direction and have a separate guard signal, then able to share without glue logic
- Example: connect 5 LCD displays to microcontroller
 - can share connections to RS, RW, and DB but not E
 - changes on E affect display – must guarantee only one is active




Forced sharing

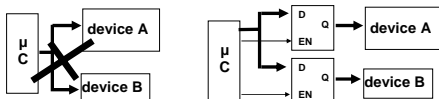- Conflict on device signals (e.g., one signal affects both)
 - solution is to insert intervening registers that keep signals stable
 - registers require enable signals which now need ports as well




Decoders and multiplexors

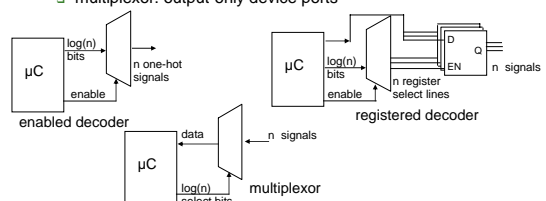- Encode n single-bit device ports using $\log n$ bits of a controller port
 - enabled decoder: one-hot, input-only device ports
 - registered decoder: input-only (but not one-hot) device ports
 - multiplexor: output-only device ports




Memory-mapped I/O

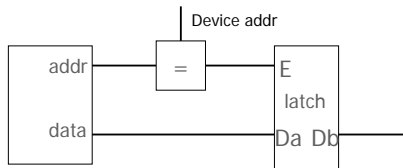- Address bus selects device
- Data bus contains data




Memory-mapped I/O

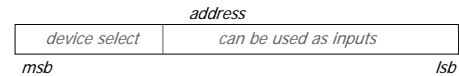- Partition the address space
- Assign memory-mapped locations
- Software
 - loads read from the device
 - stores write to the device
- Can exploit unused bits for device input-only ports



Port expansion units

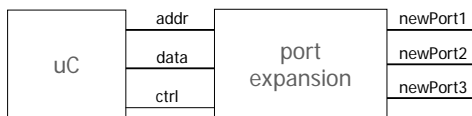- Problem of port shortage so common port expansion chips exist
- Easily connect to the microprocessor
- Timing on ports may be slightly different
- May not support interrupts




Connecting to the outside world

- Exploit specialized functions (e.g., UART, timers)
- Attempt to connect directly to a device port without adding interface hardware (e.g., registers), try to share registers if possible but beware of unwanted interactions if a signal goes to more than one device
- If out of ports, must force sharing by adding hardware to make a dedicated port sharable (e.g., adding registers and enable signals for the registers)
- If still run out of ports, then most encode signals to increase bandwidth (e.g., use decoders)
- If all else fails, then backup position is memory-mapped I/O, i.e., what we would have done if we had a bare microprocessor

64-bit General-purpose I/O port

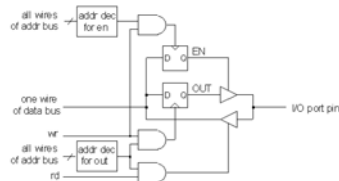- Suppose we wanted a 64-bit I/O port
- If EN is true, then we have an output pin
- If EN is false, then we have an input pin




64-bit I/O port software

- We need 8 8-bit registers to store/write the 64 bits
 - Select the EN addresses to be \$...000 to \$...007
 - Select OUT addresses to be \$...010 to \$...017
- Read 15th bit
 - load value at address \$...011 (2nd set of OUT regs)
 - logical AND with 0x80
 - bit position 7 of result is 15th bit
- Write the 47th bit
 - read OUT register at \$...015
 - set bit position 7 to desired value (or with 0x80)
 - store in \$...015
 - load EN register at \$...005
 - set bit to output
 - store value back to \$...005

External PWM Unit

- Design a system to control a digital
- Solution: design a PWM unit

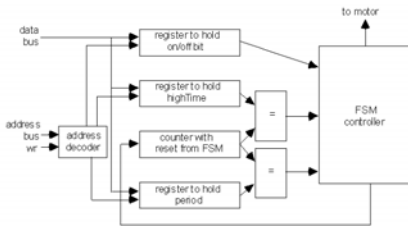


CSE 466 - Autumn 2004

Interfacing

31

External PWM FSM Controller

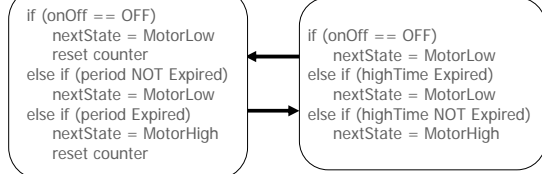

Motor Low State

Motor High State

CSE 466 - Autumn 2004

Interfacing

32

External PWM software

```
// in initialization code
Write off to onOff register

// do some stuff

// set up PWM
Repeat for each motor
  Write highTime and period registers

// turn motors on
Repeat for each motor
  Write on to the onOFF register

// more stuff
```

CSE 466 - Autumn 2004

Interfacing

33

Some example I/O devices

- Sonar range finder
- Compass
- IR proximity detector
- Accelerometer
- Bright LED

CSE 466 - Autumn 2004

Interfacing

34

Sonar range finder

- Uses ultra-sound (not audible) to measure distance
- Time echo return
 - Sound travels at approximately 343m/sec
 - need at least a 34.3kHz timer for cm resolution
- One simple echo not enough
 - many possible reflections
 - want to take multiple readings for high accuracy


CSE 466 - Autumn 2004

Interfacing

35

Polaroid 6500 sonar range finder

- Commonly found on old Polaroid cameras, now a frequently used part in mobile robots
- Transducer (gold disc)
 - charged up to high voltage and "snapped"
 - disc stays sensitized so it can detect echo (acts as microphone)
- Controller board
 - high-voltage circuitry to prepare disc for transmitting and then receiving

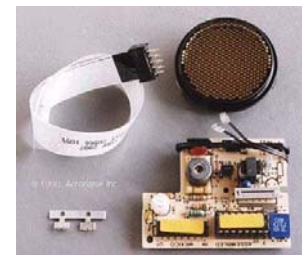

CSE 466 - Autumn 2004


Interfacing

36

Polaroid 6500 sonar range finder (cont'd)

- Only need to connect two pins to microcontroller
 - INIT - start transmitting
 - ECHO - return signal
- Some important information from data sheet

- INIT requires large current (greater than microcontroller can provide - add external buffer/amplifier)
- ECHO requires a pull-up resistor (determine current that needs to flow into microcontroller pin - size resistor so proper voltage is on pin)

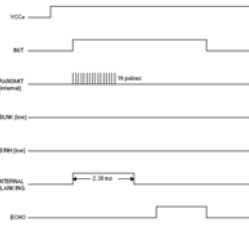



CSE 466 - Autumn 2004

Interfacing

37

Compass

- Four compass directions (each has three pins)
- One-hot/two-hot encoding
 - one-hot for N, E, S, W
 - two-hot for NE, SE, SW, NW

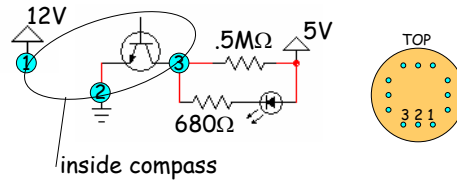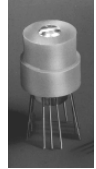


CSE 466 - Autumn 2004

Interfacing

38

Compass (cont'd)

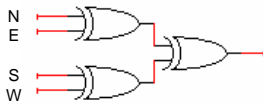- Detecting a change in compass direction
 - 4 bits change from 0001 to 0011 to 0010 to 0110 to 0100 ...
 - Always alternating between one bit on and two bits on
- Parity tree can detect difference between one and two bits being asserted
 - XOR tree of four bits (one TTL SSI package)
 - Output must change at least once for every change in orientation
 - Use interrupts to detect changes



e.g.,
NE → E → SE
1100 → 0100 → 0110
0 → 1 → 0


CSE 466 - Autumn 2004

Interfacing

39

IR proximity detector

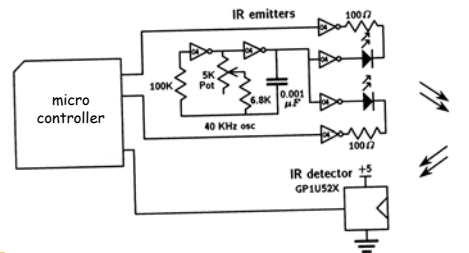
- Oscillator must be set to match detector



CSE

40

IR frequency modulation

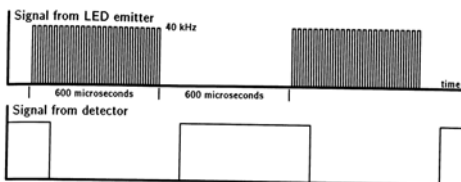

CSE 466 - Autumn 2004

Interfacing

41

Proximity code

```

turn on emitter
sleep for 600us
val_on = read detector
turn off emitter
sleep for 600us
val_off = read detector
return ( val_on & ~val_off )
    
```

timer goes off
wake
timer goes off
wake
Mostly in main

```

turn on emitter
set timer
sleep
    timer goes off
    val_on = read detector
    turn off emitter
    reset timer
    sleep
    timer goes off (again)
    val_off = read detector
return ( val_on & ~val_off )
    
```

Using interrupt handlers
wake


CSE 466 - Autumn 2004

Interfacing

42

More integrated proximity detector

- Always sending out IR
- Detector drives LED (guaranteed to match frequency)

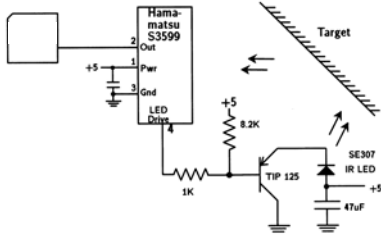


CSE 466 - Autumn 2004

Interfacing

43

Accelerometer

- Micro-electro-mechanical system that measures force
 - $F = ma$ (1. Newton)
 - Measured as change in capacitance between moving plates
 - Designed for a maximum g-force (e.g., 2-10g)
 - 2-axis and 3-axis versions
 - Used in airbags, laptop disk drives, etc.

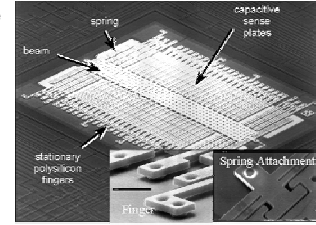

CSE 466 - Autumn 2004

Interfacing

44

Accelerometer output

- Analog output too susceptible to noise
- Digital output requires many pins for precision
- Use pulse-width modulation
- What about gravity?


CSE 466 - Autumn 2004

Interfacing

45

Analog Devices ADXL202

- 2-axis accelerometer
 - Set 0g at 50% duty-cycle
 - Positive acceleration increases duty cycle
 - Negative acceleration decreases duty cycle
 - 12.5% per g in either direction

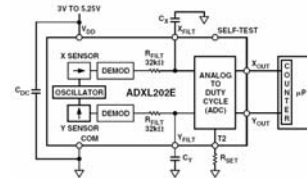


CSE 466 - Autumn 2004

Interfacing

46

Typical measurement for ADXL202

- Noisy data – all forces are aggregated by accelerometer
- Sample trace at 250Hz

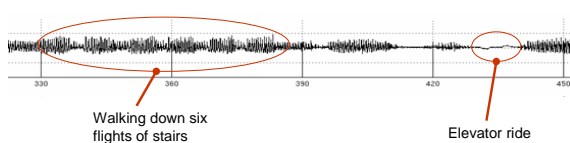


CSE 466 - Autumn 2004

Interfacing

47

Typical signal from ADXL202

- Cause interrupts at T_a , T_b , and T_c from X-axis output
 - Look for rising edge, reset counter: $T_a = 0$
 - Look for falling edge, record timer: $T_b =$ positive duty cycle
 - Look for rising edge, record timer, reset counter: $T_c =$ period
- Repeat from 2
- Same for Y-axis output (T_2 is the same for both axes)

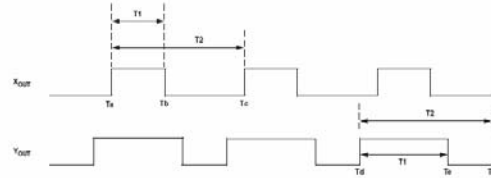

CSE 466 - Autumn 2004

Interfacing


48

What to do about noise/jitter?

- Average over time – smoothing
 - Software filter – like switch debouncing
- Take several readings
 - use average for T_b and T_c or their ratio
- Running average so that a reading is available at all times
 - e.g., update running average of 4 readings
current average = $\frac{3}{4}$ * current average + $\frac{1}{4}$ * new reading
- Take readings of both T_b and T_c to be extra careful
 - T_c changes with temperature
 - Usually can do T_c just once

Built-in filter

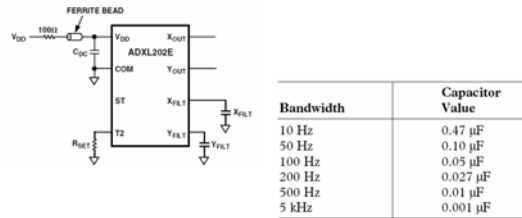- Filter capacitors limited noise frequency
 - bandwidth limiting



ADXL202 Output

- Accelerometer duty cycle varies with force
- 12.5% for each g
- R_{SET} determines duration of period
- At 1g duty-cycle will be 62.5% (37.5%)



$$A(g) = (T1/T2 - 0.5)/12.5\%$$

$$0g = 50\% \text{ DUTY CYCLE}$$

$$T2(s) = R_{SET}(\Omega)/125M\Omega$$

$T2$	R_{SET}
1 ms	125 k Ω
2 ms	250 k Ω
5 ms	625 k Ω
10 ms	1.25 M Ω

ADXL202 Orientation

- Sensitivity (maximum duty cycle change per degree) is highest when accelerometer is perpendicular to gravity

X Axis Orientation to Horizon ($^{\circ}$)	X Output (μ)		Y Output (μ)	
	X Output (μ)	Δ per Degree of Tilt (mg)	Y Output (μ)	Δ per Degree of Tilt (mg)
-90	-1.000	-4.2	0.000	17.5
-75	-0.866	-4.4	0.259	16.9
-60	-0.866	-4.6	0.500	15.2
-45	-0.707	-12.2	0.707	13.4
-30	-0.500	-15.9	0.866	8.9
-15	-0.259	-16.9	0.866	4.7
0	0.000	-17.5	1.000	0.2
15	0.259	-16.9	0.866	-4.4
30	0.500	-15.2	0.866	-8.6
45	0.707	-12.4	0.707	-13.2
60	0.866	-8.9	0.500	-15.9
75	0.866	-4.7	0.259	-16.8
90	1.000	0.2	0.000	-17.5

PWM Calculations

- How big a counter do you need?
- Assume 7.37MHz clock
- 1ms period yields a count of 7370
 - This fits in a 16-bit timer/counter
- Should you use a prescaler for the counter?
- Bit precision issues

```

unsigned int positive;
unsigned int period;
unsigned int pos_duty_cycle;

BAD:
pos_duty_cycle = positive/period;
BAD:
pos_duty_cycle = ( positive * 1000 ) / period;
OKAY:
pos_duty_cycle = ( (long) positive * 1000 ) / period;
    
```

Bright LED

- Easy to control intensity of light through pulse-width modulation
- Duty-cycle is averaged by human eye
 - Light is really turning on and off each period
 - Too quickly for human retina (or most video cameras)
 - Period must be short enough (< 1ms is a sure bet)
- LED output is low to turn on light, high to turn it off
 - Active low output

Sample code for LED

■ Varying PWM output

```
volatile uint8_t width; /* positive pulse width */
volatile uint8_t delay; /* used to slow the pulse width changing */

SIGNAL (SIG_OVERFLOW2)
{
    if(delay++ == 20) { OCR2 = width++; delay = 0; }
}


int main (void)
{
    /* must make OC2 pin an output for the PWM to visible */
    DDRD = _BV(DDD7);
    /* use Timer 2 FastPWM and the overflow interrupt to update duty-cycle */
    TCCR2 = _BV(WGM21) | _BV(WGM20) | _BV(COM21) | _BV(COM20) | _BV(CS21) | _BV(CS20);
    TIMSK = _BV(TOIE2);
    /* setup initial conditions */
    delay = 0;
    /* enable interrupts */
    sei ();
    for (;;)
    { /* LOOP FOREVER as the interrupt will make necessary adjustment */ }
    return (0);
}
```

CSE 466 - Autumn 2004

Interfacing

55

Fast PWM

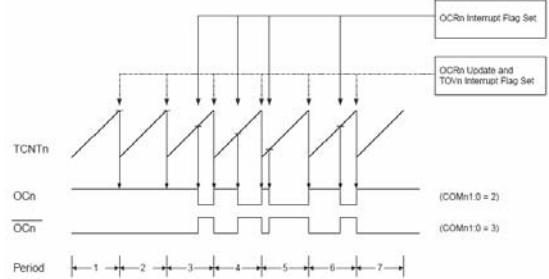


CSE 466 - Autumn 2004

Interfacing

56

Ball Lightning

- Use accelerometer to brighten/dim LED
- Think of it as a virtual knob with enabling button
 - Turn clockwise – brighten, turn counter-clockwise – dim
- Speed of turn
 - 3 different speeds
 - Fast – about 180 degrees of turn goes from off to brightest
 - Medium – about 360 degrees of turn (2 180 degree turns)
 - Slow – about 720 degrees of turn (4 180-degree turns)

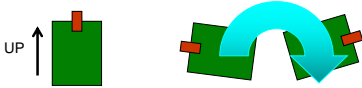

CSE 466 - Autumn 2004

Interfacing

57