 


Datapath & Control

Readings: 4.1-4.4




Datapath: System for performing operations on data, plus memory access.

Control: Control the datapath in response to instructions.


Simple CPU

Develop complete CPU for subset of instruction set


Memory: LDUR, STUR

 


Branch: B

 

Conditional Branch: CBZ

 


Arithmetic: ADD, SUB

 

Most other instructions similar

Execution Cycle

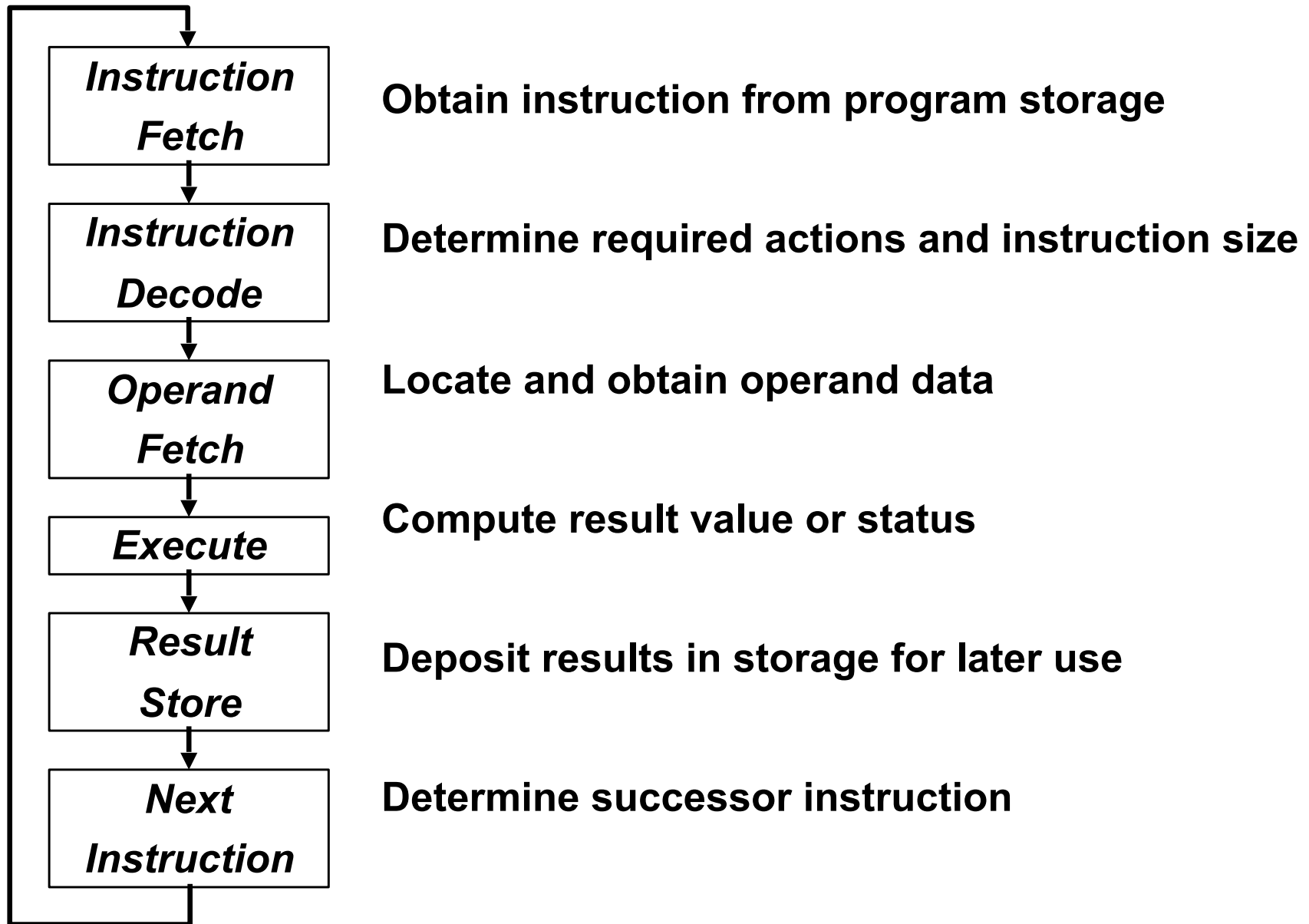

Processor Overview

Overall Dataflow


PC fetches instructions

Instructions select operand registers, ALU immediate values

ALU computes values

Load/Store addresses computed in ALU

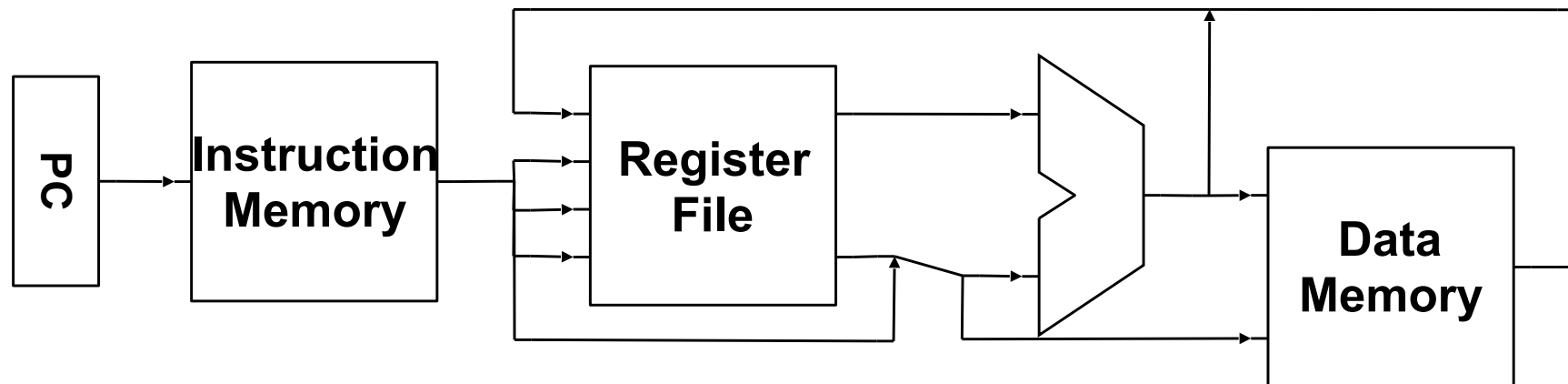Result goes to register file or Data memory



RTL & Processor Design

Convert instructions to Register Transfer Level (RTL) specification

$\text{RegA} = \text{RegB} + \text{RegC};$

RTL specifies required interconnection of units, control

Math unit example:

(add): $A = A + B; I++;$



(hold): $A = A; I++;$

(mult): $A = A * B; I++;$

(init): $A = \text{Din}; I++;$




Instruction Fetch

  

Instruction Fetch

 
```
Instruction = Mem[PC];    // Fetch Instruction  
PC = PC + 4;             // Increment
```



Add/Subtract RTL

Add instruction: ADD Rd, Rn, Rm

Subtract instruction: SUB Rd, Rn, Rm

 

Add/Subtract RTL

Add instruction: ADD Rd, Rn, Rm

Instruction = Mem[PC];

Reg[Rd] = Reg[Rn] + Reg[Rm];


PC = PC + 4;

Subtract instruction: SUB Rd, Rn, Rm



Instruction = Mem[PC];

Reg[Rd] = Reg[Rn] - Reg[Rm];

PC = PC + 4;


 


Add/Subtract Datapath

  


Add/Subtract Datapath

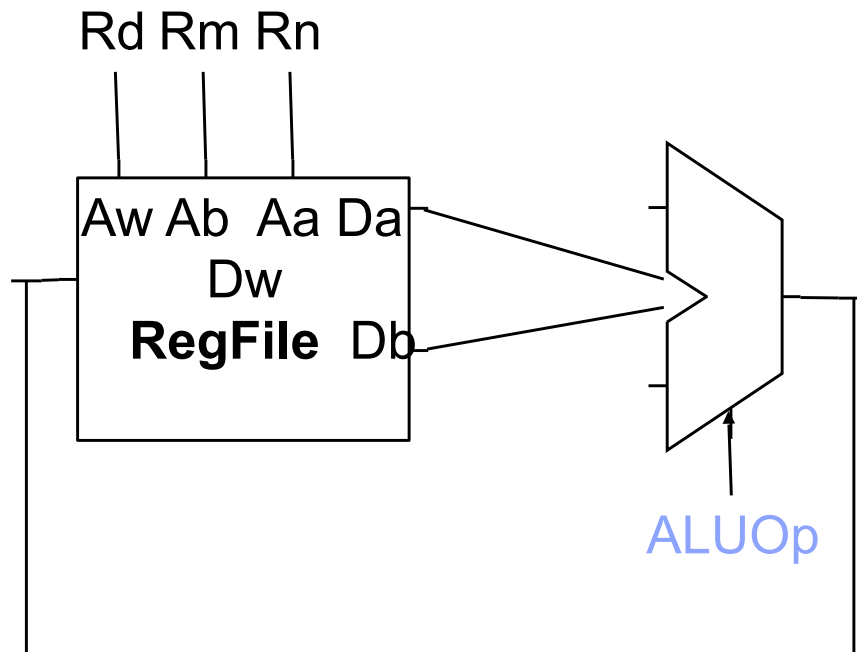 $\text{Reg}[\text{rd}] = \text{Reg}[\text{rn}] \text{ op } \text{Reg}[\text{rm}] ;$



Load RTL

Load Instruction: LDUR Rd, [Rn, DAddr9]

 

Load RTL


Load Instruction: LDUR Rd, [Rn, DAddr9]

Instruction = Mem[PC];





Addr = Reg[Rn] + SignExtend(DAddr9);

Reg[rd] = Mem[Addr];

PC = PC + 4;


 


Datapath + Load

    


Datapath + Load
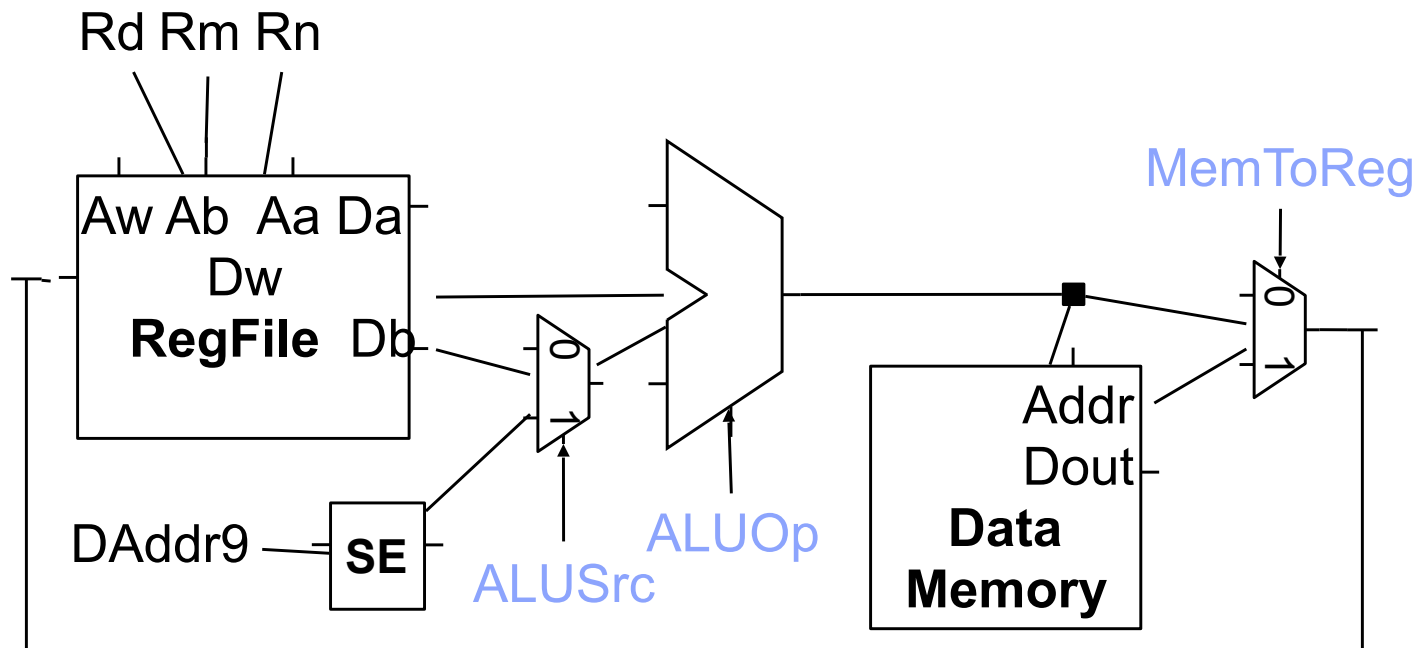 
```
Addr = Reg[Rn] + SignExtend(DAddr9);  
Reg[Rd] = Mem[Addr];
```



Store RTL

Store Instruction: STUR Rd, [Rn, DAddr9]

 

Store RTL


Store Instruction: STUR Rd, [Rn, DAddr9]

Instruction = Mem[PC];


Addr = Reg[Rn] + SignExtend(DAddr9);

Mem[Addr] = Reg[Rd];

PC = PC + 4;


 


Datapath + Store

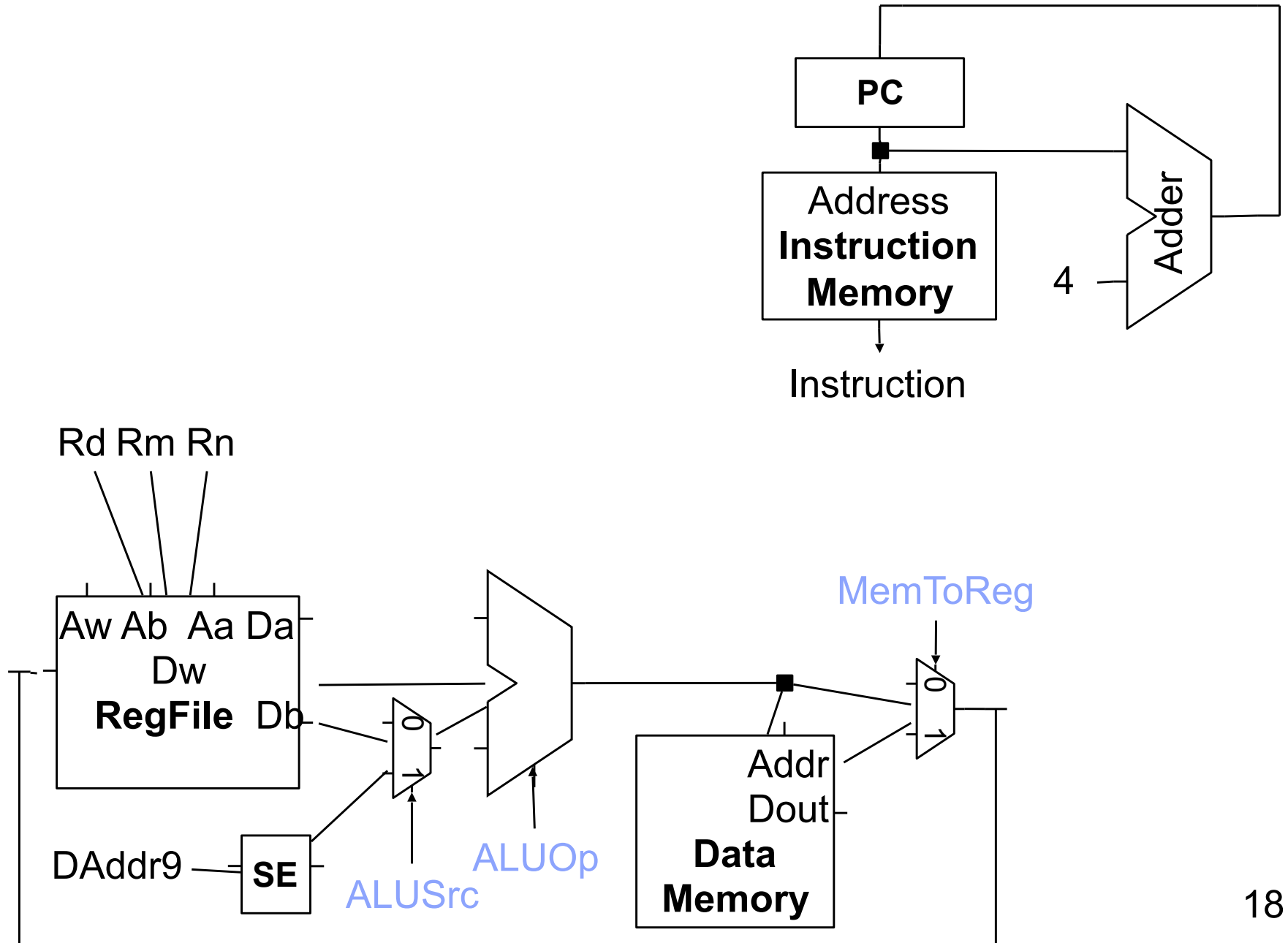


Datapath + Store
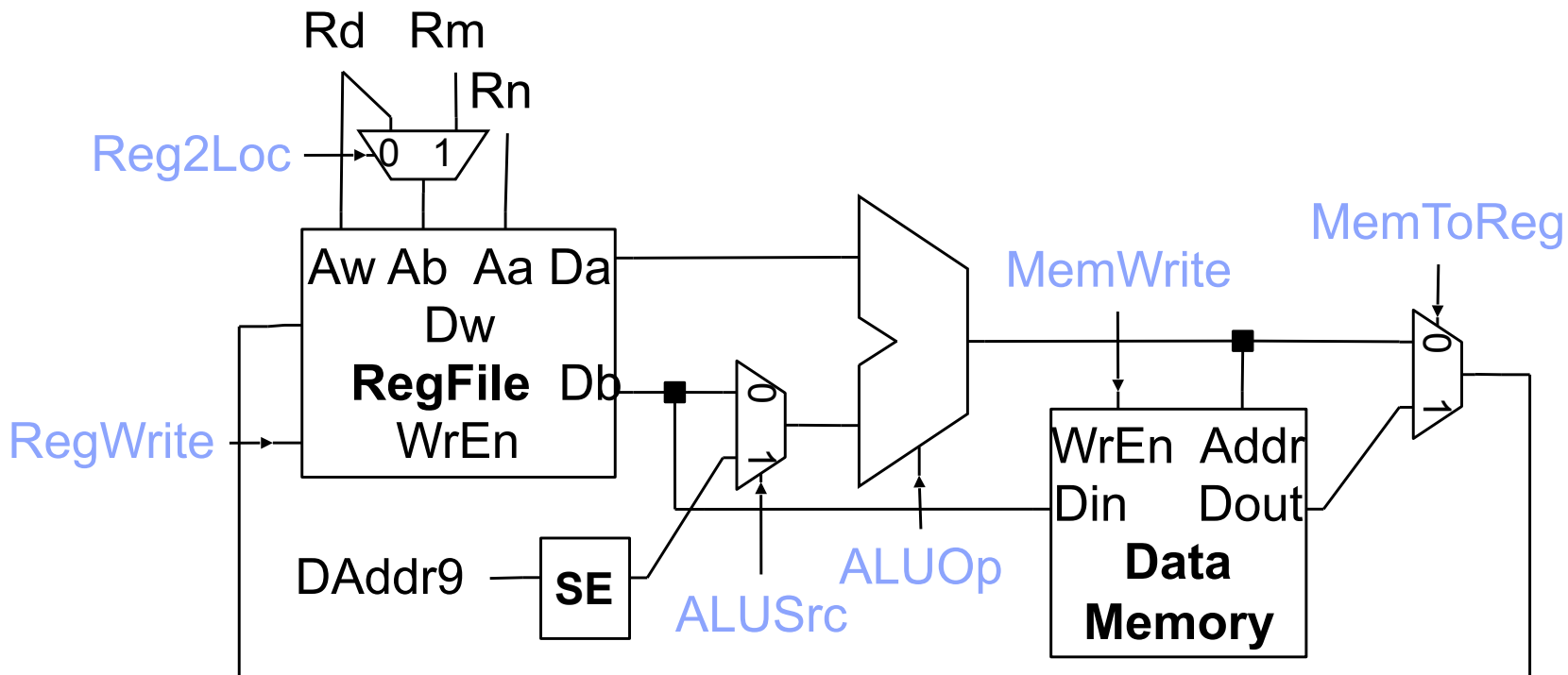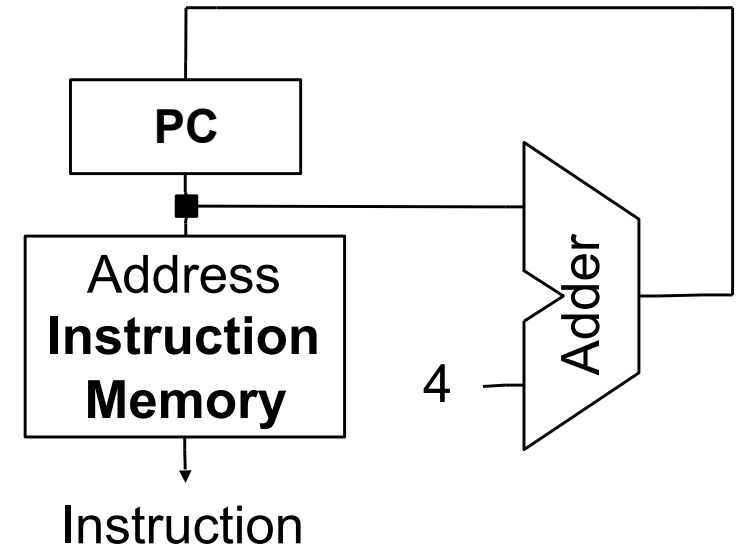
```
Addr = Reg[Rn] + SignExtend(DAddr9);  
Mem[Addr] = Reg[Rd];
```



Branch RTL

Branch Instruction: B BrAddr26

 


Branch RTL


Branch Instruction: B BrAddr26

Instruction = Mem[PC];

PC = PC + SignExtend(BrAddr26) << 2;

 


Datapath + Branch

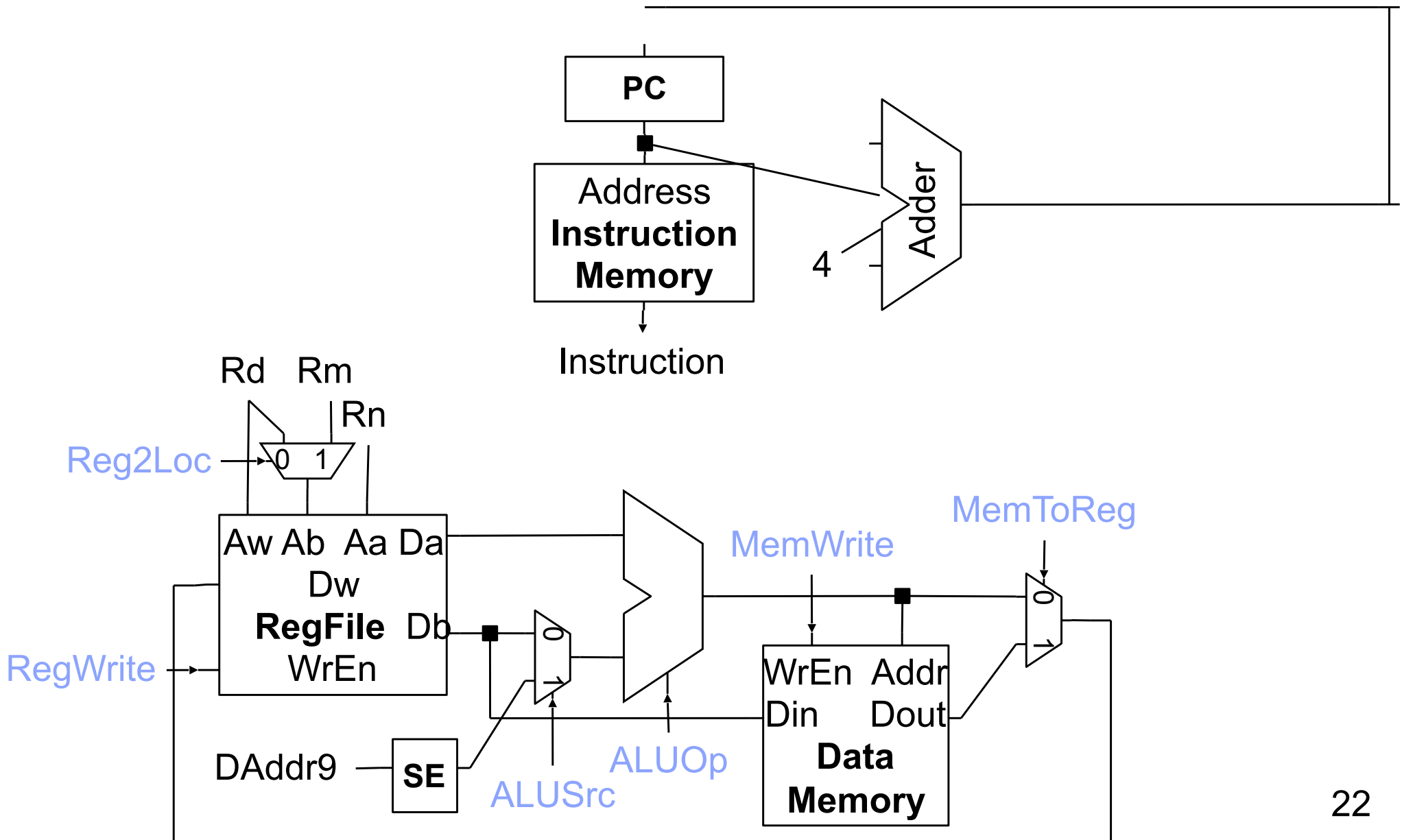


Datapath + Branch
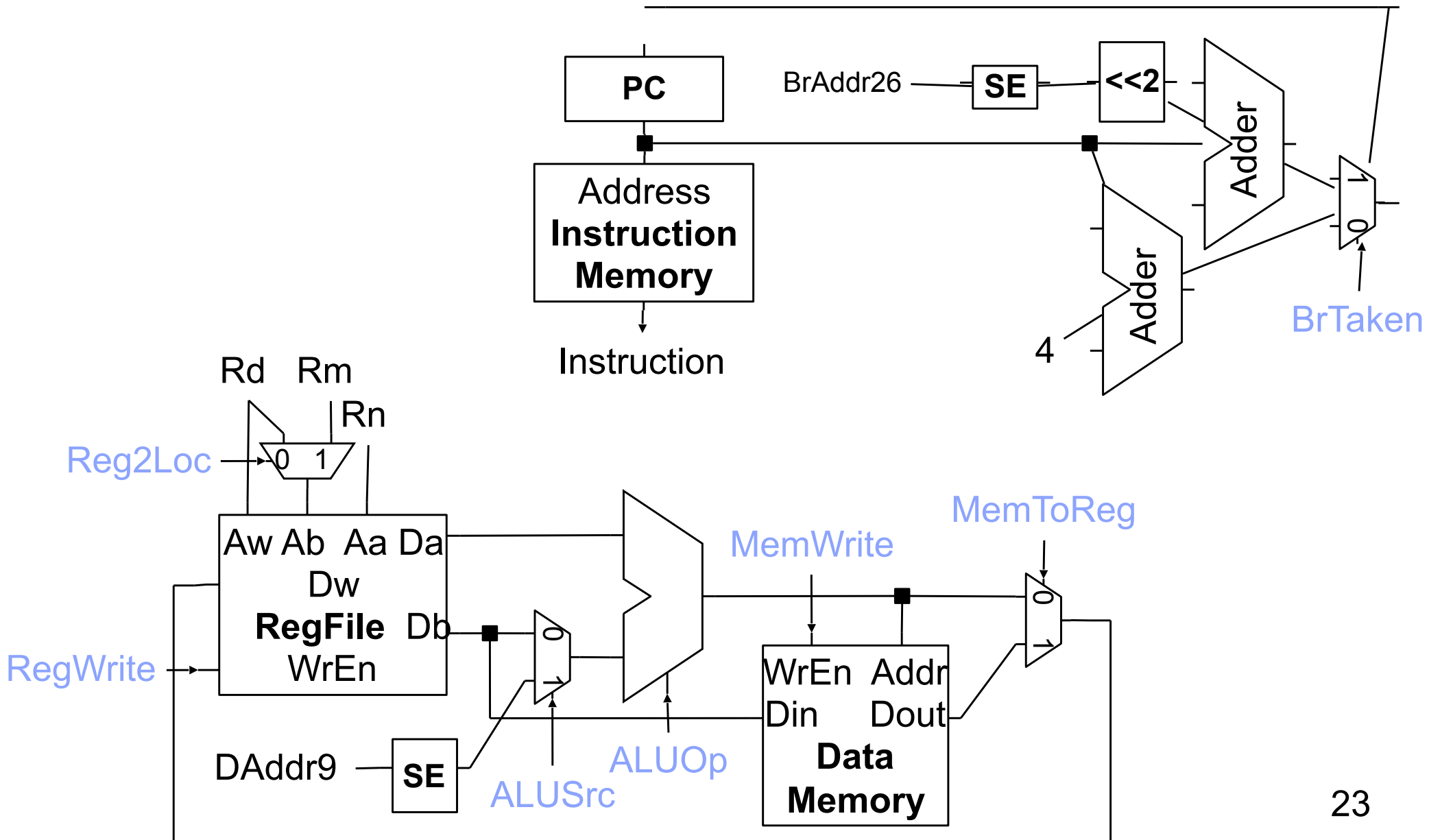
$$PC = PC + \text{SignExtend}(\text{BrAddr26}) \ll 2;$$



Conditional Branch RTL

 Conditional Branch Instruction: CBZ Rd, CondAddr19



Conditional Branch RTL

Conditional Branch Instruction: CBZ Rd, CondAddr19

```
Instruction = Mem[PC];
```


```
Cond = (Reg[Rd] == 0);
```

```
if (Cond)
```

```
    PC = PC + SignExtend(CondAddr19) << 2;
```

```
else
```

```
    PC = PC + 4;
```

 

Datapath + Conditional Branch


Cond = (Reg[Rd] == 0)

if (Cond)


PC = PC + SE(CondAddr19) << 2;

else

PC = PC + 4;

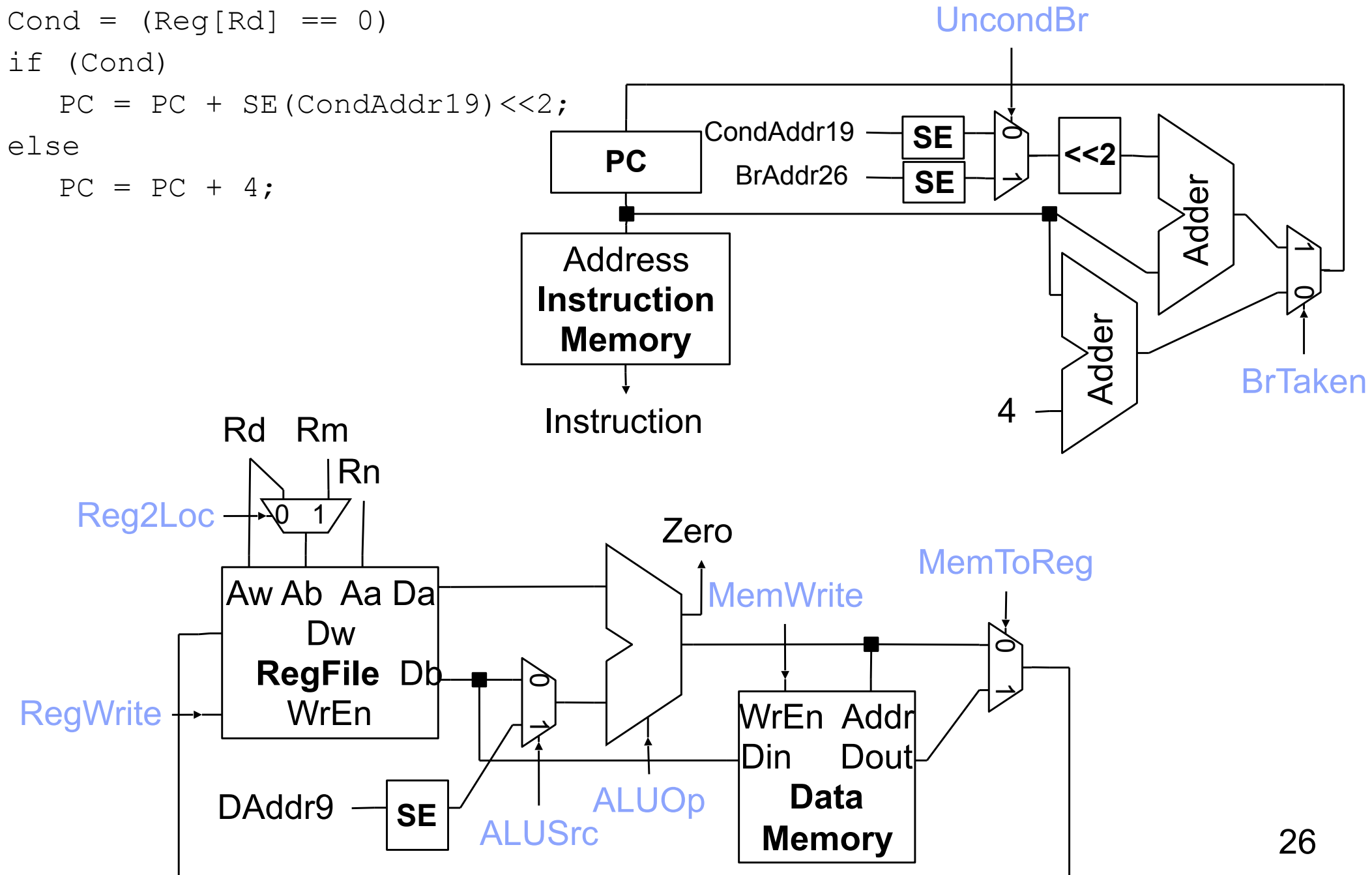

Datapath + Conditional Branch

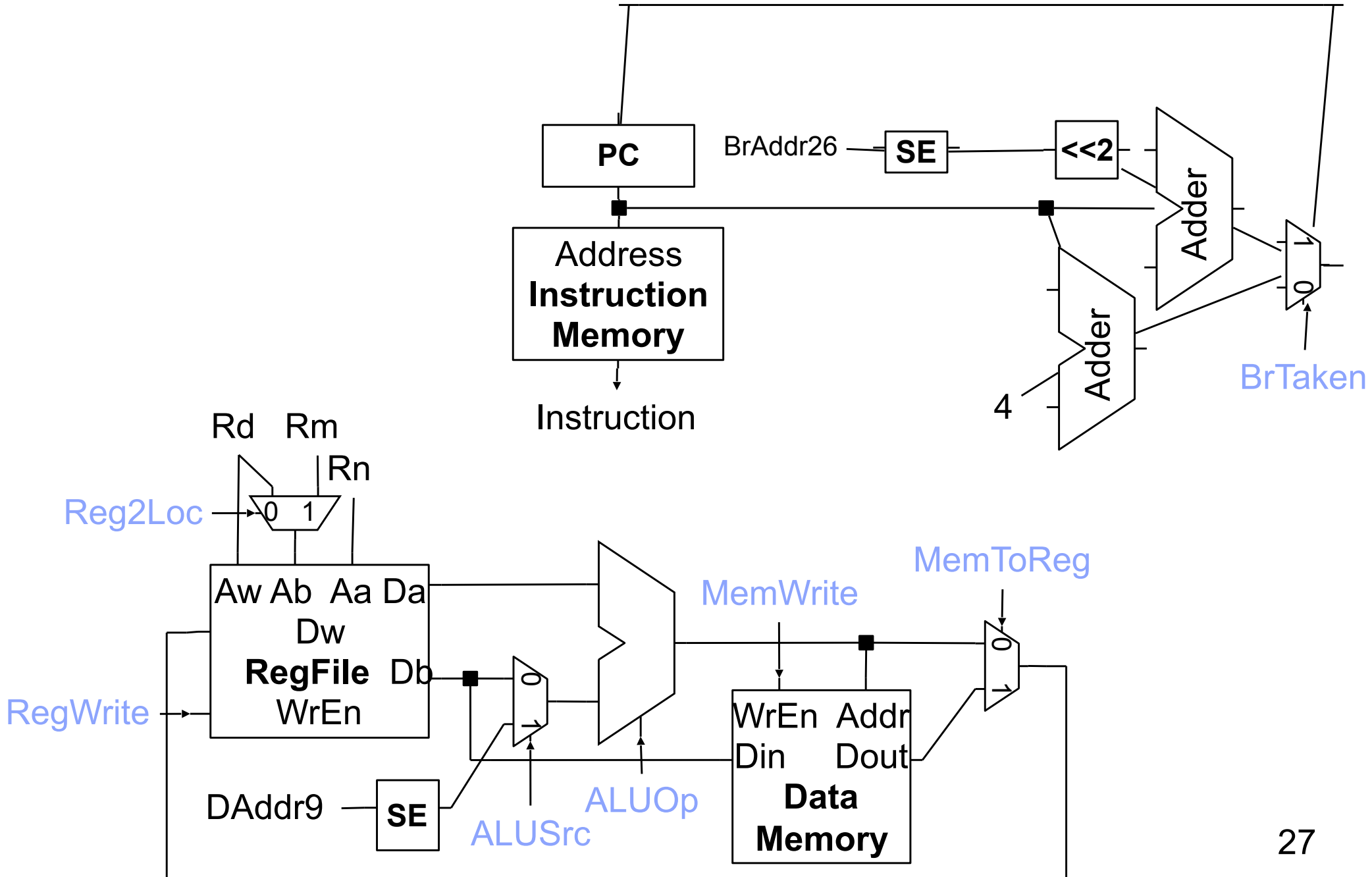

Control

Identify control points for pieces of datapath

- Instruction Fetch Unit

- ALU


- Memories

- Datapath muxes

- Etc.

Use RTL for determine per-instruction control assignments

Complete Datapath

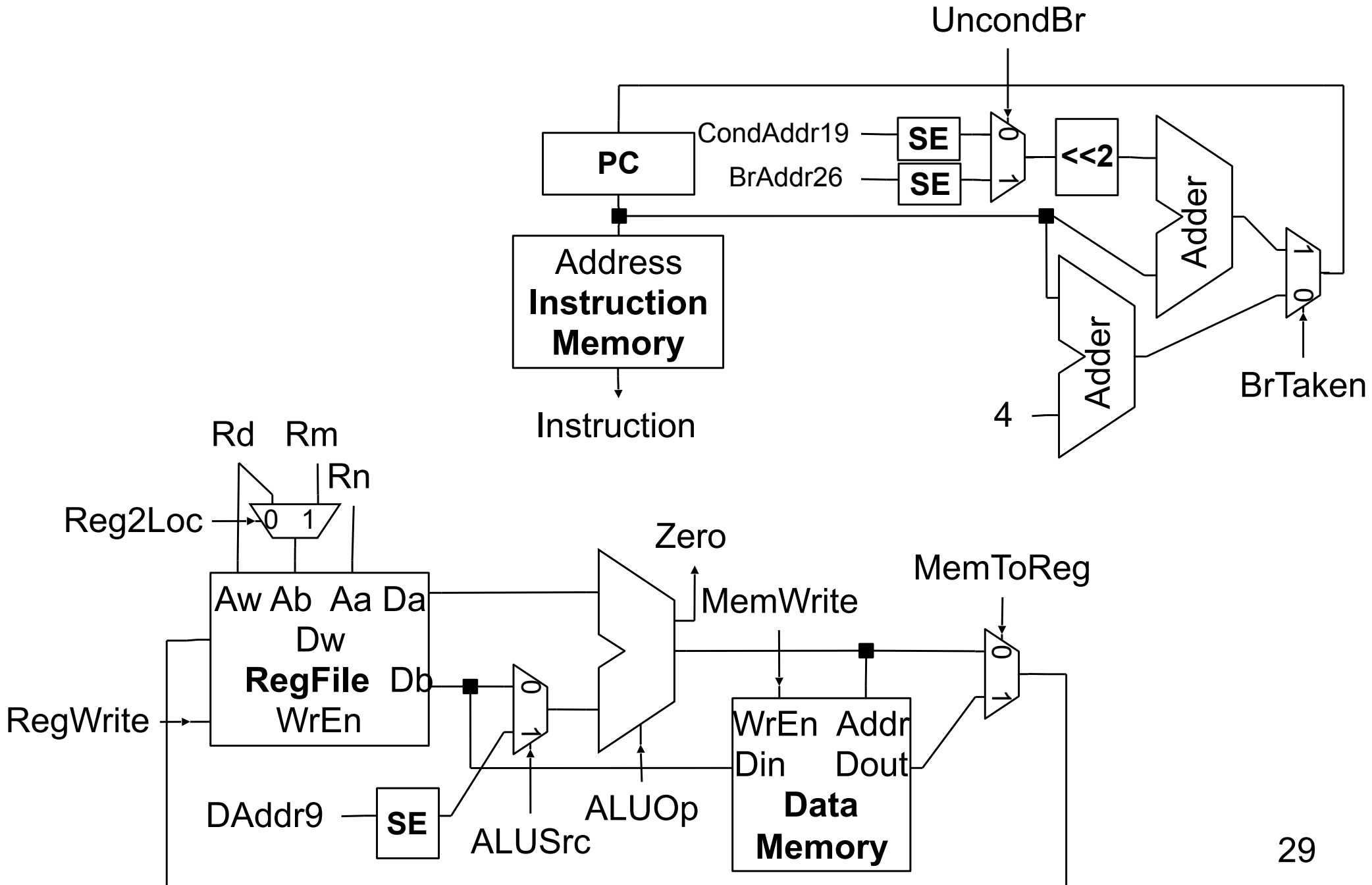

Control Signals

Opcode[31:26] Opcode[25:21]	1000101 1000	1100101 1000	111110 00010	111110 00000	000101x xxxx	1011010 0xxx
	ADD	SUB	LDUR	STUR	B	CBZ

Control Signals

Opcode[31:26]	1000101	1100101	111110	111110	000101x	1011010
Opcode[25:21]	1000	1000	00010	00000	xxxx	0xxx
	ADD	SUB	LDUR	STUR	B	CBZ
Reg2Loc						
ALUSrc						
MemToReg						
RegWrite						
MemWrite						
BrTaken						
UncondBr						
ALUOp						


Control Signals

Opcode[31:26] Opcode[25:21]	1000101	1100101	111110	111110	000101x	1011010
	1000	1000	00010	00000	xxxx	0xxx
	ADD	SUB	LDUR	STUR	B	CBZ
Reg2Loc	1	1	X	0	X	0
ALUSrc	0	0	1	1	X	0
MemToReg	0	0	1	X	X	X
RegWrite	1	1	1	0	0	0
MemWrite	0	0	0	1	0	0
BrTaken	0	0	0	0	1	(zero)
UncondBr	X	X	X	X	1	0
ALUOp	+	-	+	+	X	B==0?

ADD Control

```

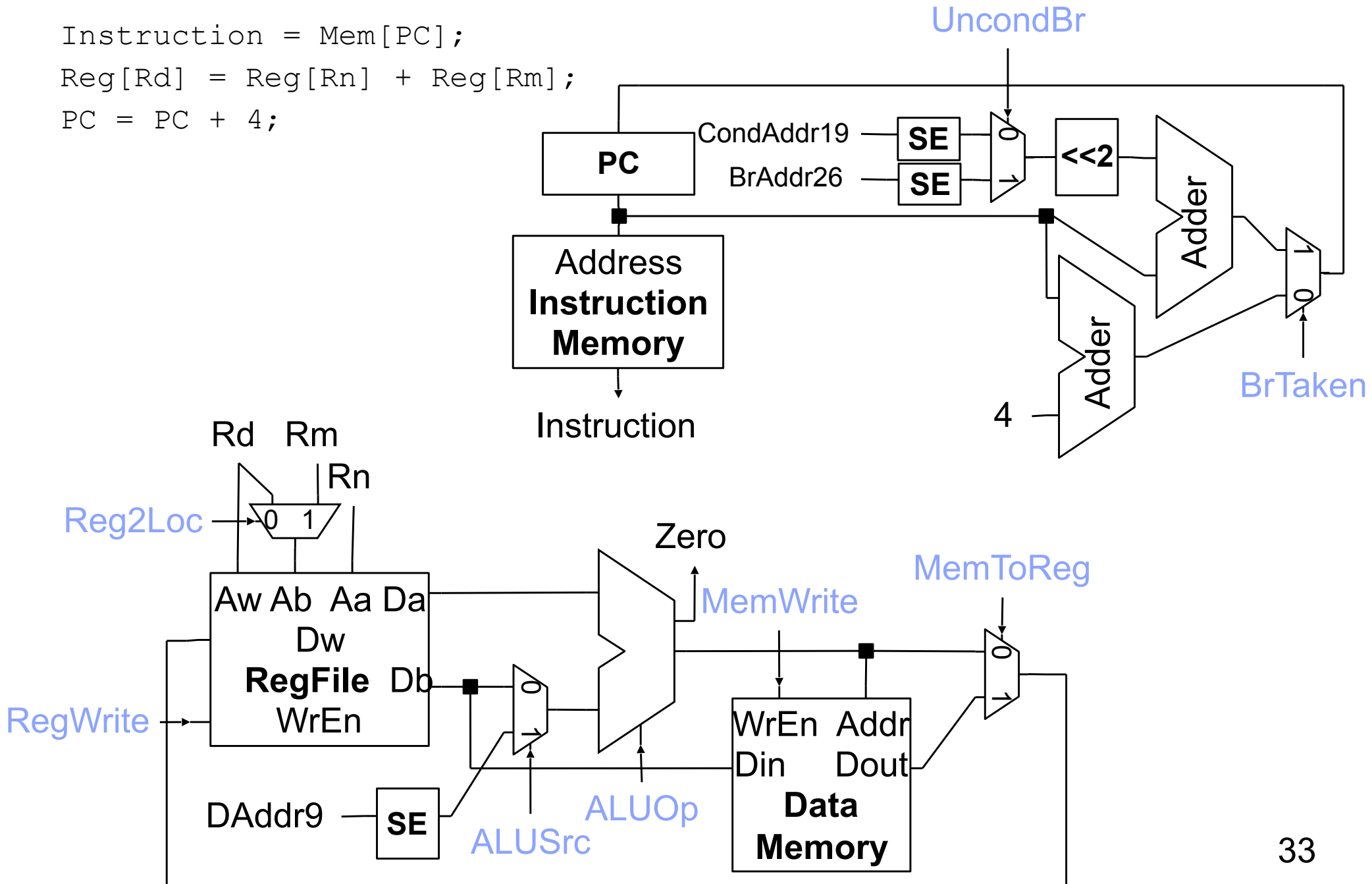
Instruction = Mem[PC];
Reg[Rd] = Reg[Rn] + Reg[Rm];
PC = PC + 4;
    
```



SUB Control

```

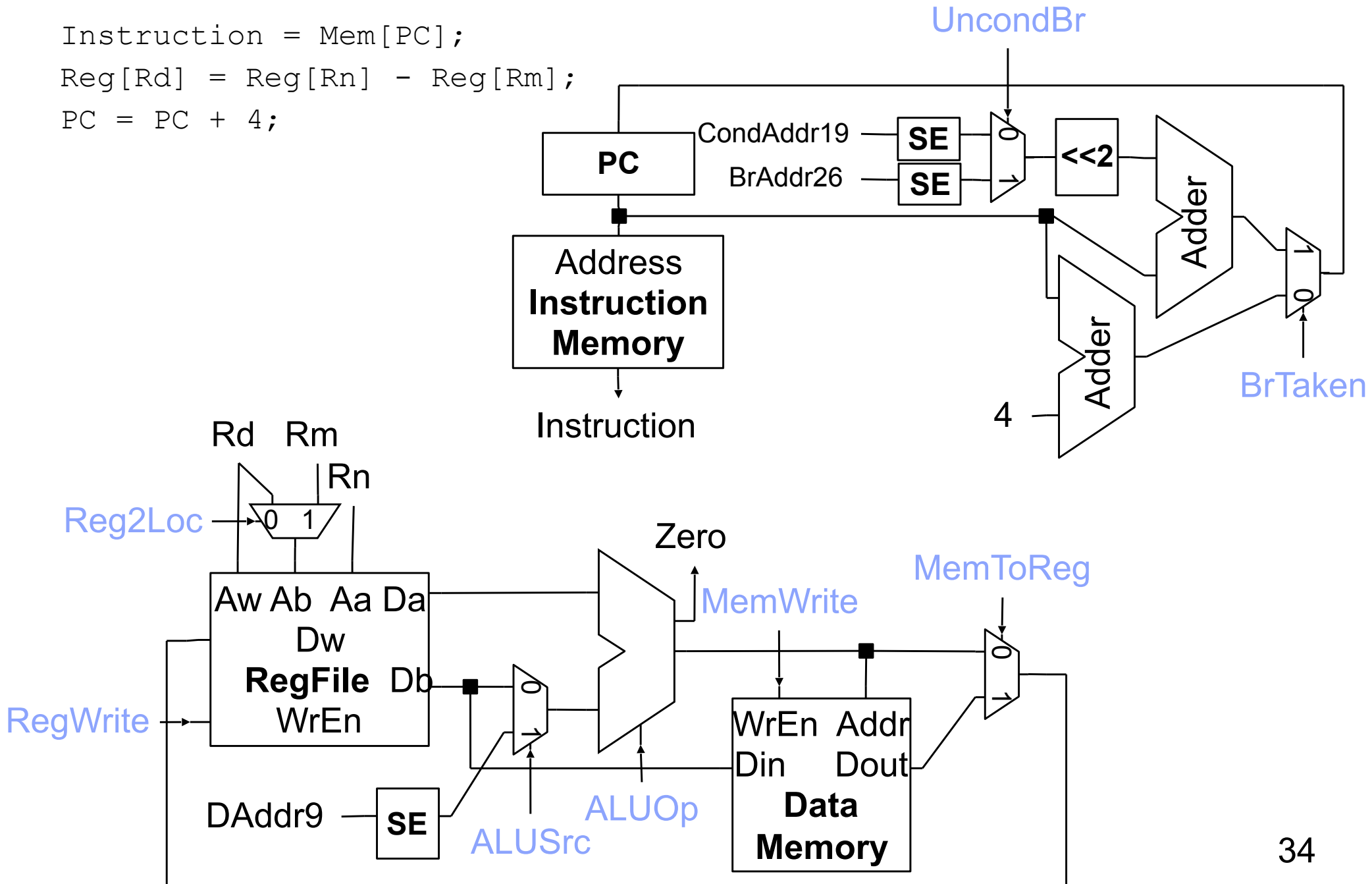Instruction = Mem[PC];
Reg[Rd] = Reg[Rn] - Reg[Rm];
PC = PC + 4;
    
```




LDUR Control

Instruction = Mem[PC];

Addr = Reg[Rn] + SignExtend(DAddr9);

Reg[Rd] = Mem[Addr];

PC = PC + 4;

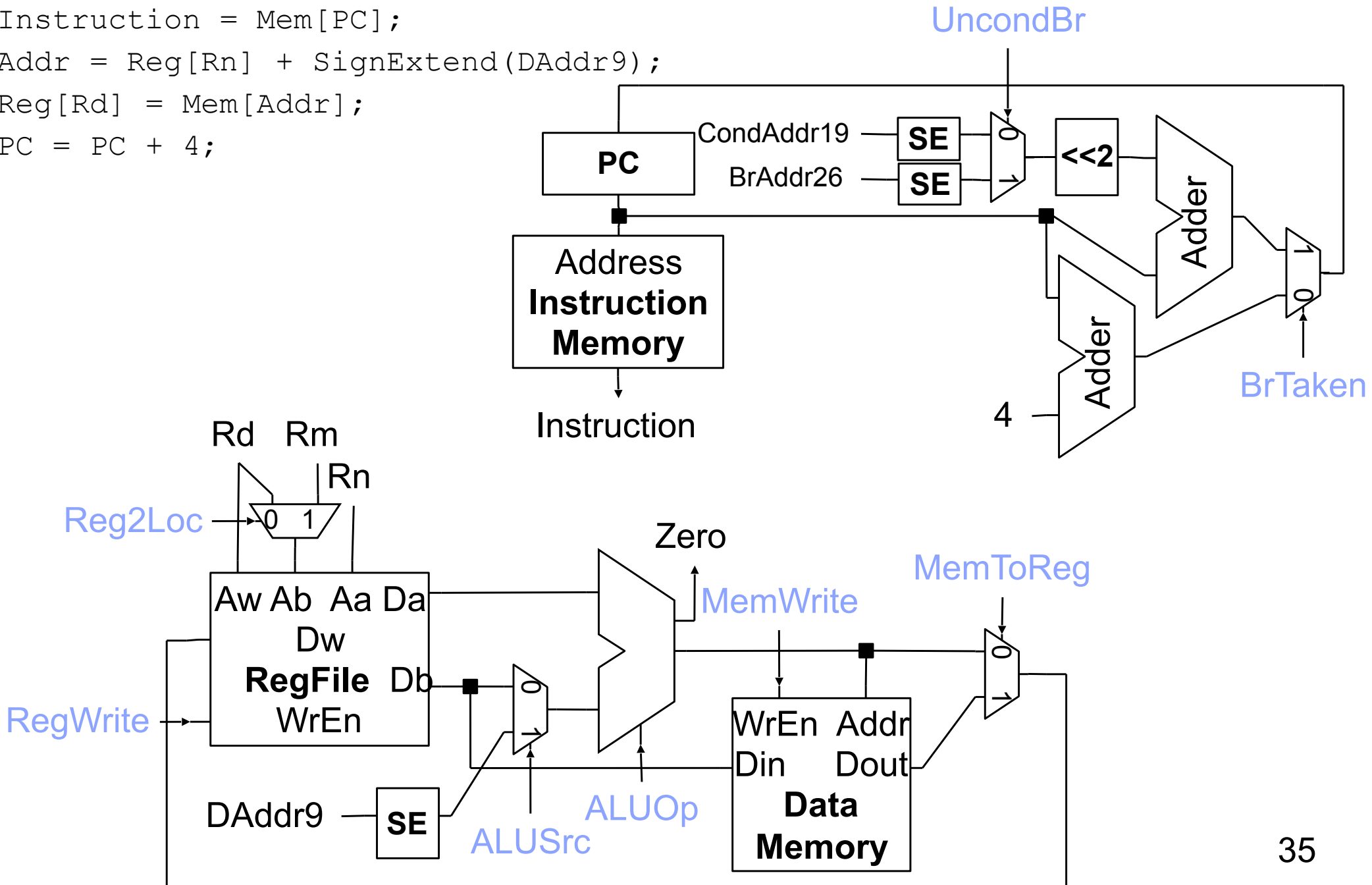


STUR Control

Instruction = Mem[PC];

Addr = Reg[Rn] + SignExtend(DAddr9);

Mem[Addr] = Reg[Rd];


PC = PC + 4;

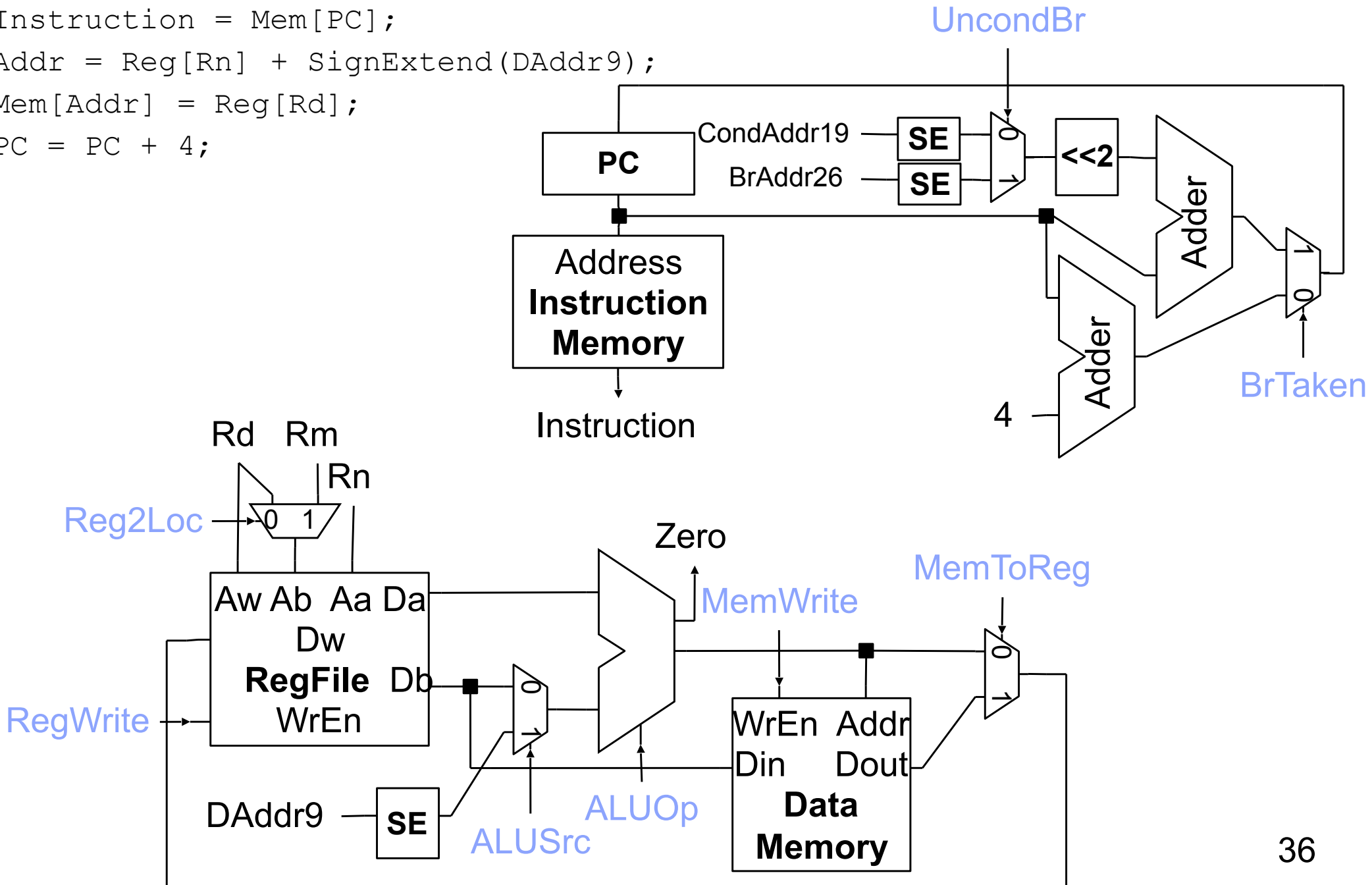

B Control

Instruction = Mem[PC];


PC = PC + SignExtend(BrAddr26) << 2;

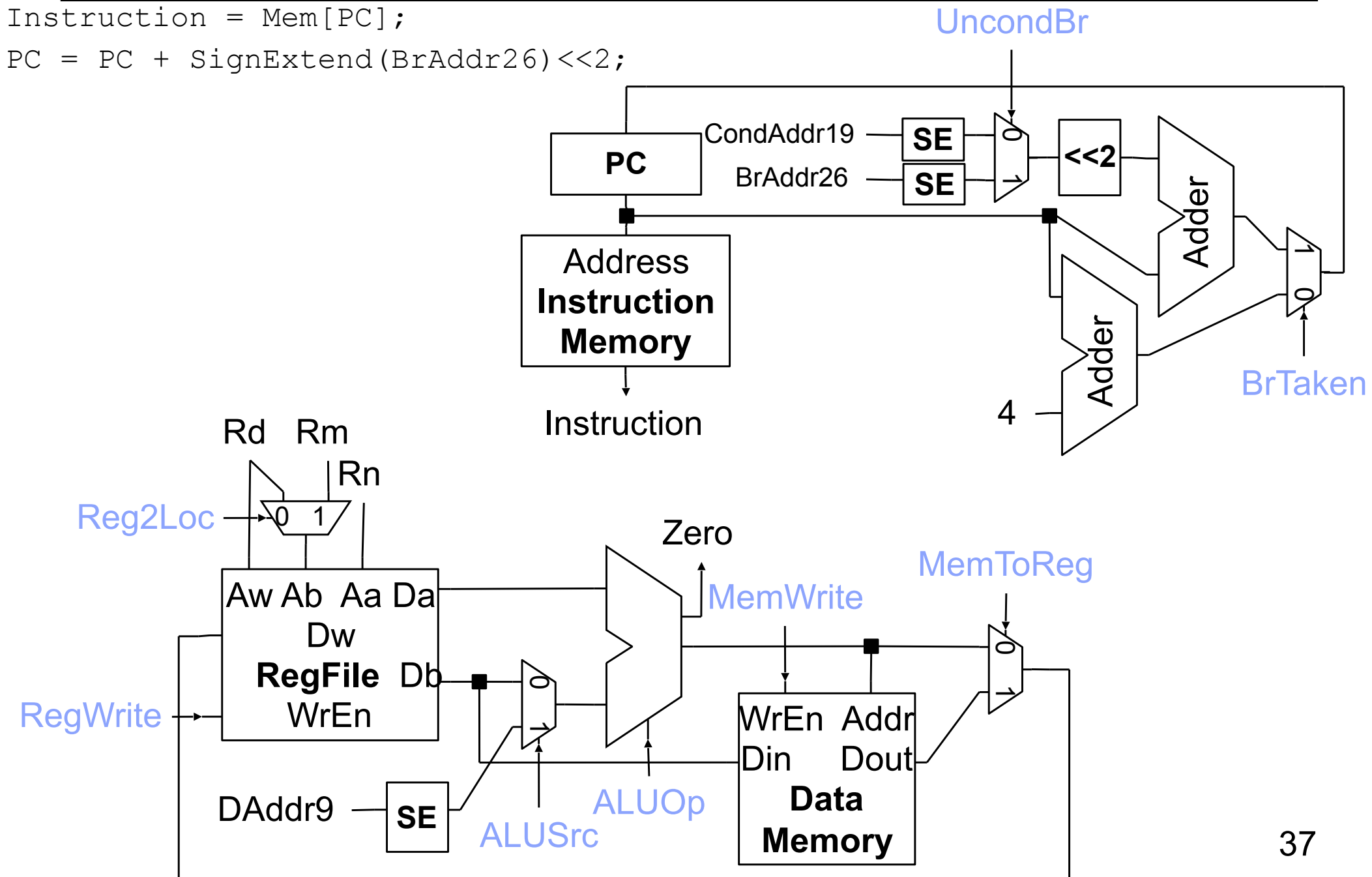


CBZ Control

```

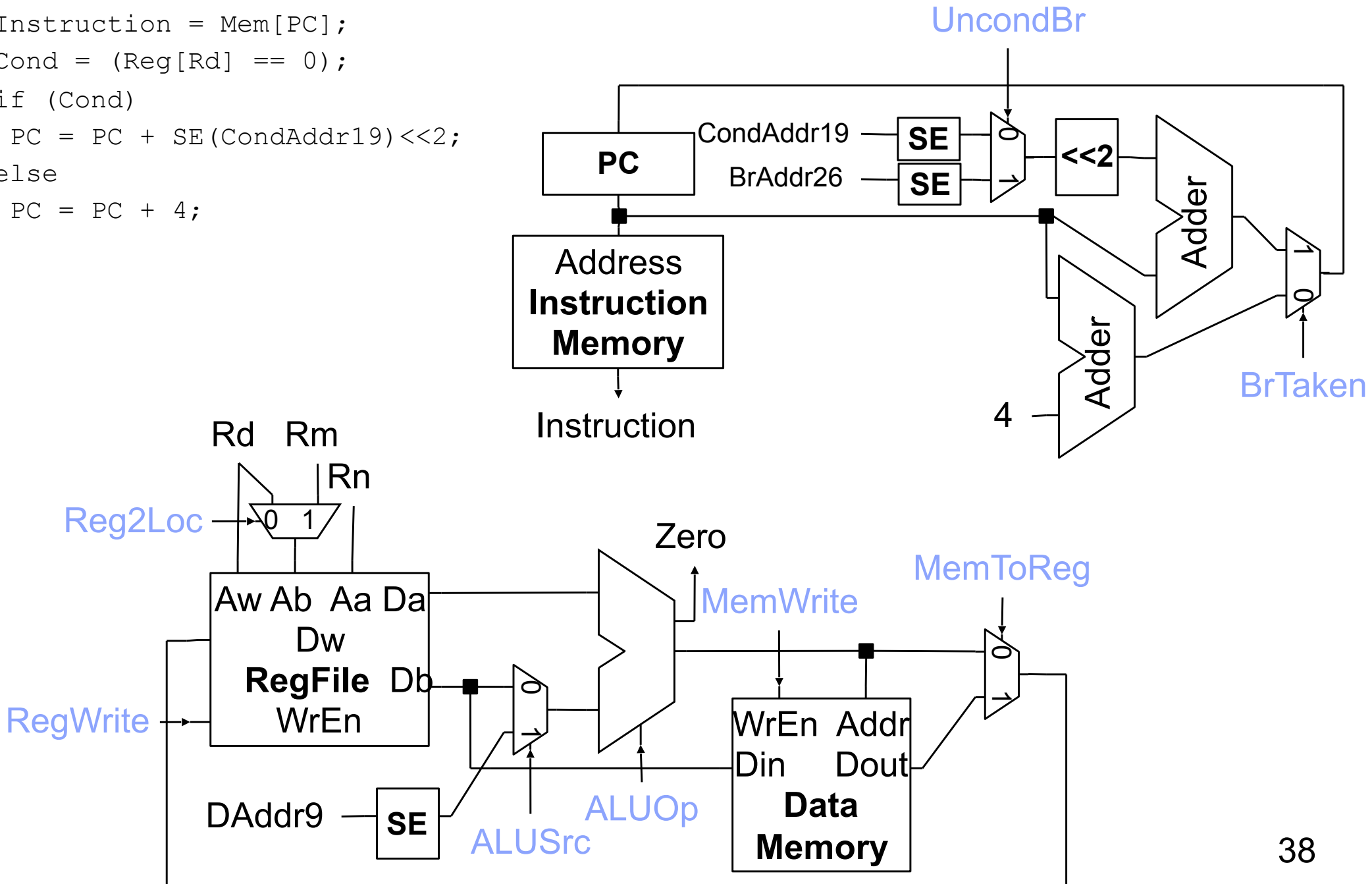Instruction = Mem[PC];
Cond = (Reg[Rd] == 0);
if (Cond)
  PC = PC + SE(CondAddr19) << 2;
else
  PC = PC + 4;
  
```




Complete Datapath

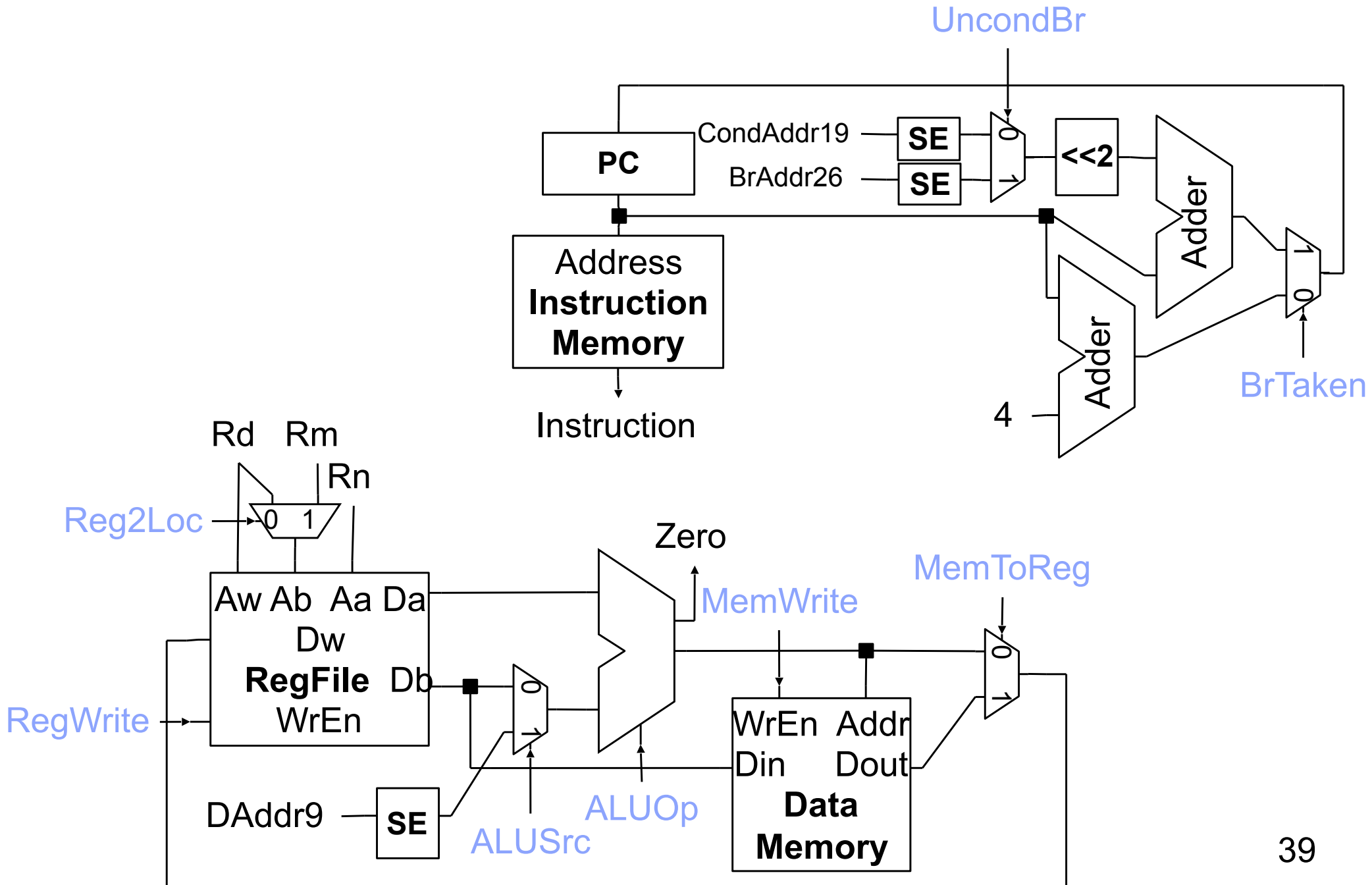

Advanced: Exceptions

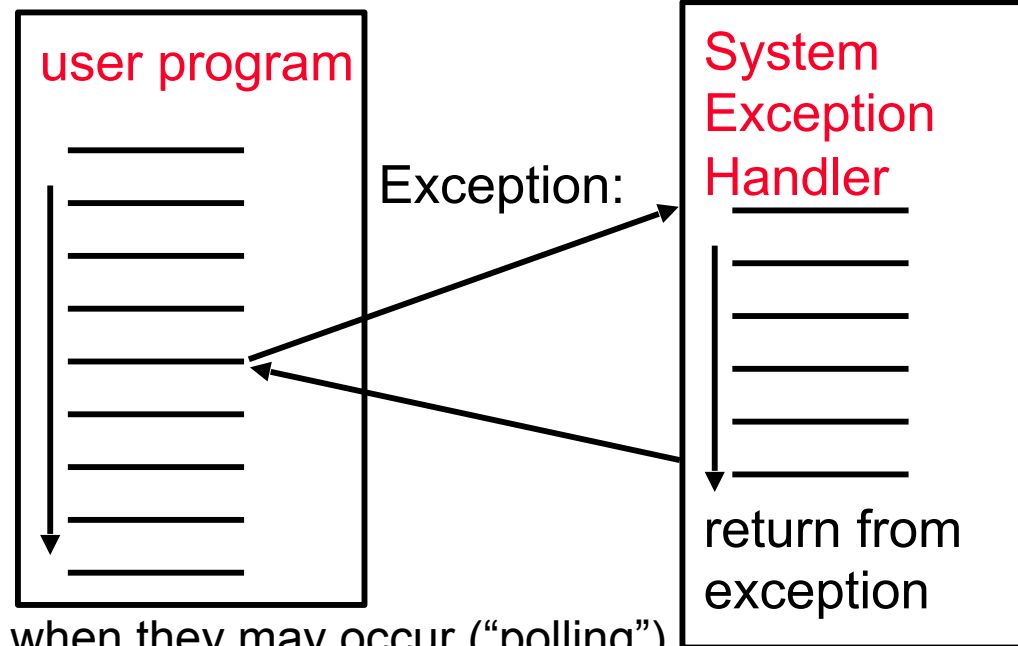Exception = unusual event in processor
Arithmetic overflow, divide by zero, ...
Call an undefined instruction
Hardware failure
I/O device request (called an "interrupt")



Approaches

Make software test for exceptional events when they may occur ("polling")

Have hardware detect these events & react:

Save state (Exception Program Counter, protect the GPRs, note cause)

Call Operating System

If (undef_instr) PC = C0000000

If (overflow) PC = C0000020

If (I/O) PC = C0000040

...

Performance of Single-Cycle Machine

CPI?

ADD, SUB



LDUR



STUR



CBZ




B



Reducing Cycle Time

Cut combinational dependency graph and insert register / latch

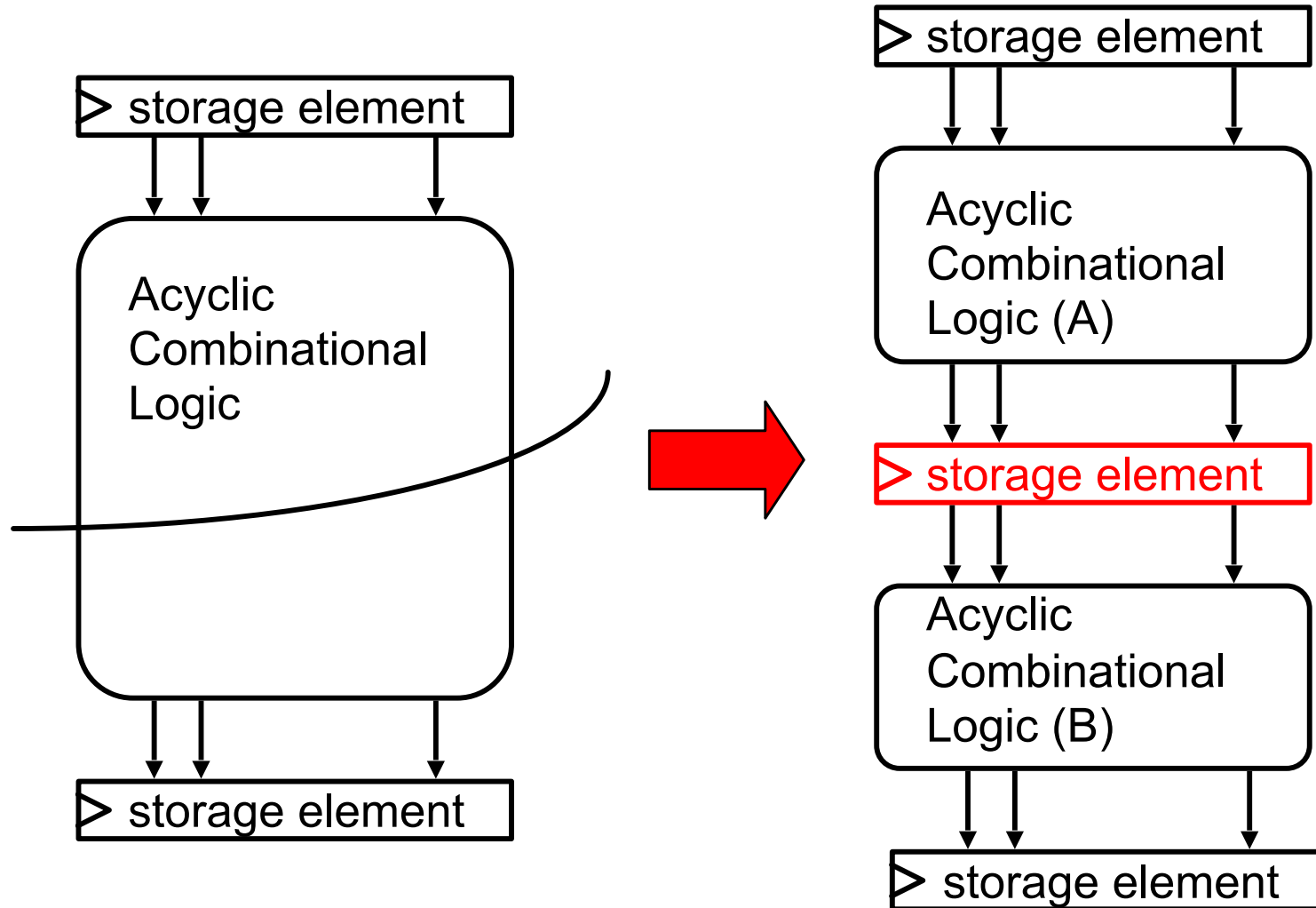Do same work in two fast cycles, rather than one slow one



Pipelined Processor Overview

Divide datapath into multiple stages

