

## Computer Design and Organization

**Problem Set #2**

Due: Friday January 21

This short assignment is to get you familiar with the basics of Verilog. How to **turnin** your programs will be posted on the Web page.

**Problem 1**

You will design an 8 by 3 decoder. There are two inputs, `in1`, `in2` respectively 2 and 6 bits long. The output `out` is 3 bits. You are strongly encouraged to use constructs such as `casex`.

The output of the decoder should have the following values:

`out` takes the value 0 if `in1 = 2` and `in2 = 4`, or 20, or 36, or 52.  
`out` takes the value 1 if `in1 = 2` and `in2 = 5`, or 21, or 37, or 53.  
`out` takes the value 2 if `in1 = 0`  
`out` takes the value 2 if `in1 = 2` and `in2 = 0`, or 16, or 32, or 48.  
`out` takes the value 6 if `in1 = 1`  
`out` takes the value 6 if `in1 = 2` and `in2 = 2`, or 18, or 34, or 50.  
`out` takes the value 7 if `in1 = 2` and `in2 = 10`, or 26, or 42, or 58.  
`out` is otherwise undefined.

You should test thoroughly your design by writing a test program in Verilog. **The decoder module should be called `dec8x3` and have parameters listed as: `module dec8x3(in1,in2,out)`. Turnin both the module and the test program.**

The code that you'll write should be at a level similar to the following example:

```
module decode2x4(in,z);
input [1:0]in;
output [3:0]z;
reg [3:0]z;
    always @ (in)
        case(in)
            0: z= 4'b0001;
            1: z= 4'b0010;
            etc.....
        endcase
    end
endmodule
```

### Problem 2

Design, at the functional level, an ALU that performs the operations listed below. The inputs **a** and **b** should be 32 bits. The third input is the **opcode** which is 3 bits with:

- opcode = 0 means “and”
- opcode = 1 means “or”
- opcode = 2 means “add”
- opcode = 3 means “sub”
- opcode = 4 means “slt”
- all other opcodes are undefined and should return undefined values **x** in the result

The outputs are a 32-bit result **r**, an overflow bit **v**, and a zero bit **z** which is equal to 1 if and only if all 32 bits of **r** are 0's.

**The module should be called `alu32` and have parameters listed as: `alu32(a,b,opcode,r,v,z)`. Turnin both the module and the test program.**

The code that you'll write should be at a level similar to the example below (which has not the same list of parameters, on purpose).

Of course you can (and will need to) use other statement types (e.g., **case**) and other operators (e.g., reduction operators).

You should also write, and turn in a test program which verifies your design. Be sure to include tests to see if the values generated for **v** and **z** (for example) are correct.

```
module alusim(a,b,Carryin,Result,Overflow,Operation);
    parameter width =1;
    input [width-1:0] a,b;
    input Carryin;
    output [width-1:0]Result;
    output Overflow;
    input Operation;
    reg Carryout, Overflow;
    reg [width-1:0]Result;

    always @(a or b or Carryin or Operation)
        if (Operation == 0)
            Result = a & b;
```


```

else if (Operation == 1)
begin
  {Carryout,Result}= a + b + Carryin;
  Overflow = ....
end
endmodule

```
 
### Problem 3

Design and test a Verilog program for a 2-bit saturating counter (finite state machine) with the following state diagram.



States are labelled 0, 1, 2, 3. Transitions are indicated by the arrows and occur everytime the input `in` is assigned a value of either 0 or 1.

**The module should be called `satc` and have parameters listed as: `module satc(in,state)`. Turnin both the module and the test program.**