I. Switch Debouncing

CSEP567

A Switch is Pressed, So What???

Vcc

Problem: Switch Bounce


10K ohm
Pull-up

Initial
Connection
Contact Closed

Typically 10-20ms

Debouncing

- When a switch (any type) changes state (on -> off or off -> on), it presents a mechanical bouncing which generates a signal similar to the one shown at the right.
- The resistor R is needed because the signal S can not be left "floating" in an undefined state when the switch changes from state 1 to 2.
- Without debouncing the signal can generate several interrupts (or status changes) corresponding to just one action.
- Debouncing consists in "Filtering" the signal S so that a proper operation of the switch action is sensed.
- Debouncing can be done in hardware of software

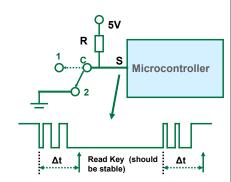

Techniques that can be used:

-If status loop: after first status change, program timer and after elapsed time read key status.

-If Interrupt: on first interrupt program timer which will interrupt after elapsed time. Then read key status.

CSEP567

3

Debouncing

```
1 Setup a counter variable, initialize to zero.
 2\ \mbox{Setup} a regular sampling event, perhaps using a timer. Use a period of about 1ms.
 3 On a sample event:
    if switch signal is high then
                                                                                 - Vcc
       Reset the counter variable to zero
                                                                                Or
       Set internal switch state to {\tt released}
     else
                                                                                Internal
      Increment the counter variable to a maximum of 10
                                                                                pullup
     end if
10
    if counter=10 then
                                                                                      Vout
11
      Set internal switch state to pressed
kevDown event occurs on the state transition of released to pressed
                                                                                  GND
void setup() {
  //configure pin2 as an input and enable the internal pull-up resistor
  pinMode(2, INPUT_PULLUP);
 CSEP567
```

Debouncing

- A Better Way:
 - □ Use the **Bounce** library, check examples
- Remember that debouncing is not the same as one event per button press:

keyDown event occurs on the state transition of released to pressed

