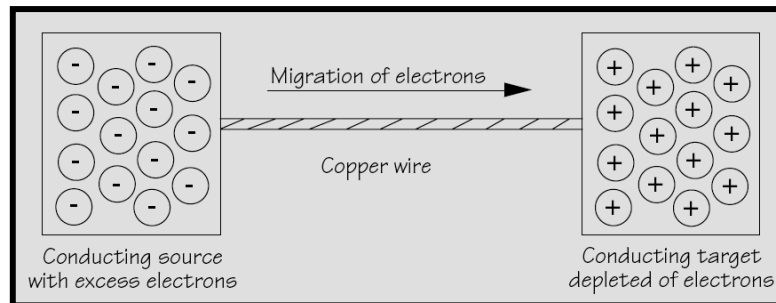




## Basic Concepts of Electricity

- Voltage
- Current
- Resistance



1




## Electric Fields

- An electric field applies a force to a charge
  - Force on positive charge is in direction of electric field, negative is opposite
- Charges move if they are mobile
- An electric field is produced by charges (positive and negative charges)
- Electric fields can be produced by time varying magnetic fields (generator, antenna radiation)

2
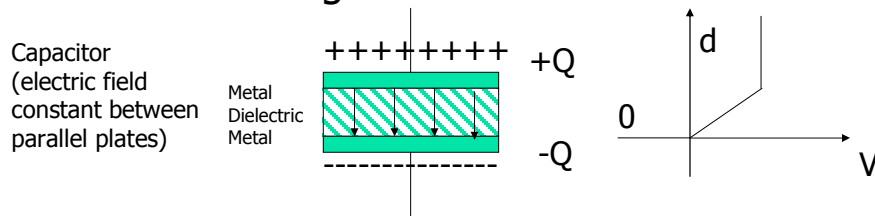
## Voltage Difference

- Voltage difference is the difference in potential energy in an electric field
- $E = V/d$
- As you move closer to a positive charge the voltage increases



## Current

- An electric current is produced by the flow of electric charges
- Current = rate of charge movement  
= amount of charge crossing a surface per unit time
- In conductors, current flow is due to electrons
- Conventional current is defined by the direction positive charges will flow
- Direction of electron flow is opposite to direction of conventional current


## Resistance

- In materials electrons accelerate in an electric field
- Electrons lose energy when they hit atoms - lost energy appears as heat and light
- The result is that electrons drift with constant velocity (superimposed on random thermal motion)
- Resistance is the ratio Voltage/current

$$R = V/I$$

5

## Voltage, Current, and Resistance

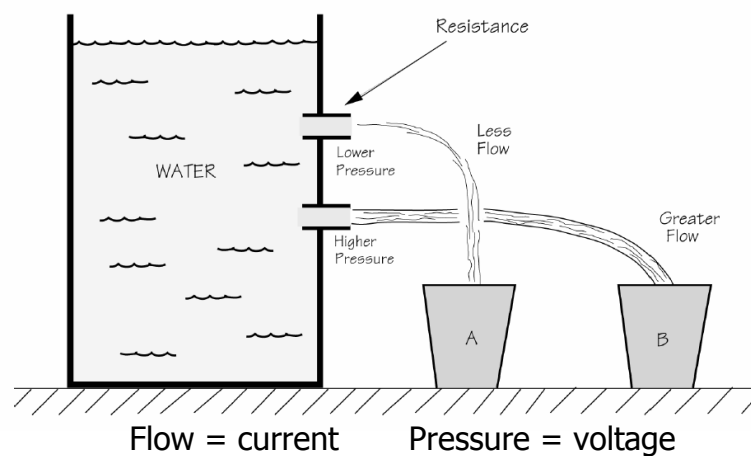

6


## Material Conductivity

- Conductors - negligible resistance
- Insulators - extremely large resistance
- Semiconductors - some resistance
- Resistors - are devices designed to have constant resistance across a range of voltages


7

## Resistor Combination

Series resistance

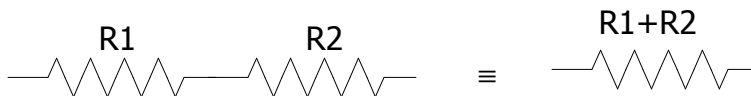

Parallel resistance

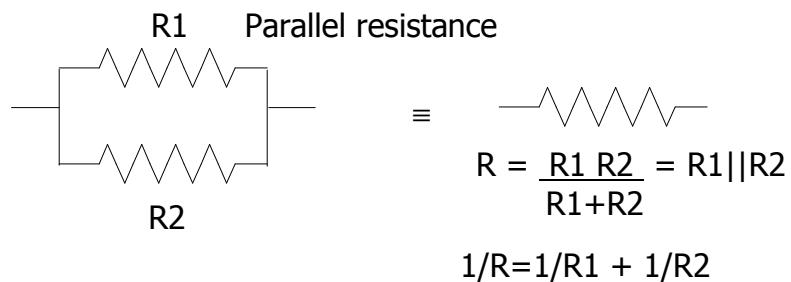


8

## Kirchoff's Voltage Law

- Kirchoff's voltage law (KVL)
  - The sum of voltage differences around any loop in a circuit equals 0
  - Equivalently, the voltage between two points is the same no matter what path is traversed

9

## Voltage Divider

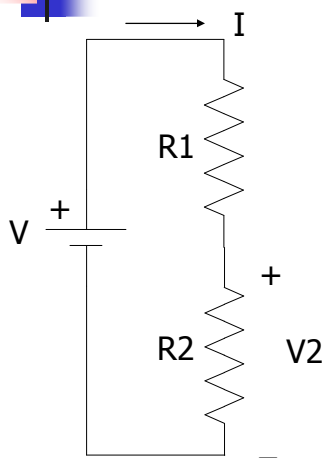

$$V_2 = \frac{V R_2}{R_1 + R_2}$$

Solution:


Goal: Find  $V_2$  given  $V$

- Find  $V_2$  in terms of  $I$
- Current through  $R_2$  in terms of  $I$
- Voltage across  $R_1$
- Find voltage across  $R_1$  and  $R_2$  using two different methods

10



## Potentiometer (Variable Resistor)

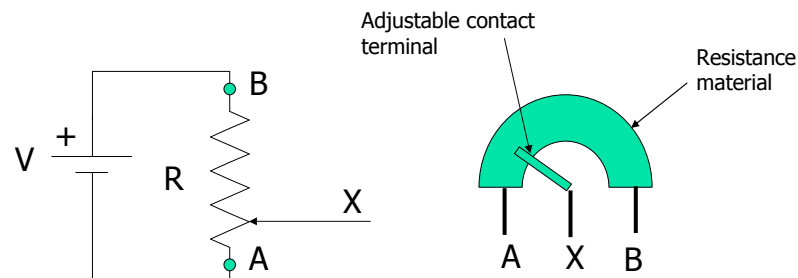

$$V_X = V * \text{Distance AX} / \text{Distance AB}$$

(linear potentiometer)

A trimpot is a small variable resistor mounted on a printed circuit board that can be adjusted by a small screwdriver to make semi-permanent adjustments to a circuit

11



## Input Transducers

- These are devices that produce electric signals in accordance with changes in some physical effect e.g. convert temperature, light level to a voltage level or resistance
- e.g. microphones, strain gauge, photo-detectors, ion-selective membranes, thermistors
- Sometimes the definition of transducer is that of a device that converts non-electrical energy to electrical energy

12



## Output Transducers

- Devices which convert an electrical quantity into some other physical quantity or effect e.g. relay, loudspeaker, solenoid

13



## Light Dependent Resistors (LDRs)

- Devices whose resistance changes (usually decreases) with light striking it
- (also called photocells, photoconductors)
- Light striking a semiconducting material can provide sufficient energy to cause electrons to break away from atoms.
- Free electrons and holes can be created which causes resistance to be reduced


14




## LDRs

- Typical materials used are Cadmium Sulphide (CdS), Cadmium Selenide (CdSe), Lead Sulphide
- With no illumination, resistance can be greater than  $1\text{ M}\Omega$  (dark resistance).
- Resistance varies inversely proportional to light intensity.
- Reduces down to 10-100s ohms
- 100ms/10ms response time

15

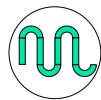

CdS LDR  
Top view

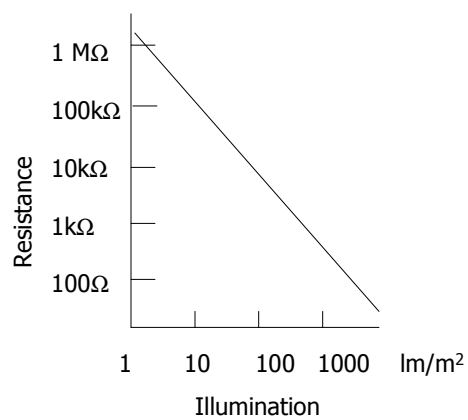

16





- LDRs have a low energy gap
- Operate over a wide wavelengths (some, into infrared)
- Indium antimonide is good for IR. When cooled is very sensitive, used for thermal scanning of earth's surface

17



## Capacitors


- A component constructed from two conductors separated by an insulating material (dielectric) that stores electric charge (+Q, -Q)
- As a consequence there is a voltage difference across the capacitor, V
- Capacitance =  $C = Q/V$
- The dielectric material operates to reduce the electric field between the conductors and so allow more charge to be stored for a given voltage

18




# Capacitors

## Bucket analogy

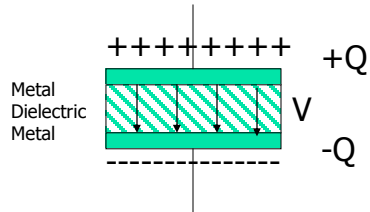

$$C = Q/V$$


$$(Q = CV)$$

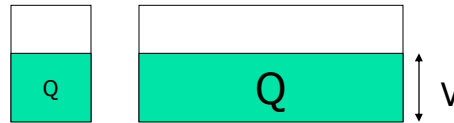


A small bucket (capacitor,  $C$ ) holds less charge ( $Q$ ) for given level (voltage  $V$ ) than a large bucket



# Charging a Capacitor

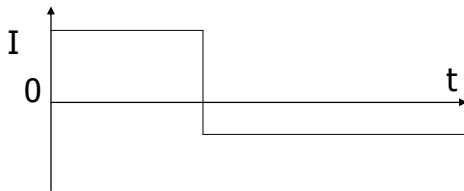

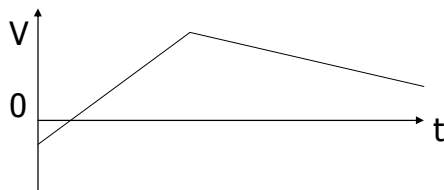The bucket analogy can be used to describe capacitor charging




When current flows in at a constant rate the voltage increases linearly and vice versa for current flowing out


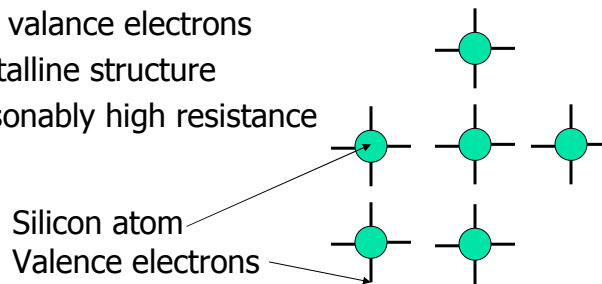
## Semiconductors

- Silicon is used as an example (other semiconductors include Germanium, Gallium Arsenide, Gallium phosphide, indium arsenide, indium phosphide)
- Pure silicon (intrinsic semiconductor)
  - Four valance electrons
  - Crystalline structure
  - Reasonably high resistance



21




## Electrons and holes

- Due to thermal energy some electrons in the valance shell become free
- Create:
  - One free electron +
  - One hole in the valance band that can be filled by electrons from the valance band in an adjacent silicon atom
- Current in silicon can flow due to both movement of electrons and holes

22
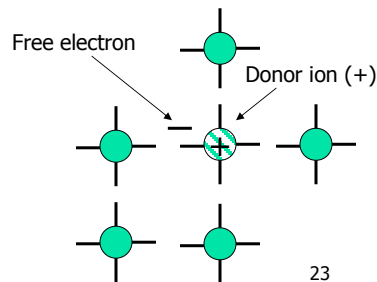
## n-type silicon


- Add donor impurities (e.g. Phosphorus, arsenic, indium) with 5 electrons in the valance band
- As only four electrons can bond with neighbouring silicon atoms one free electron is left
- Increases concentration of free electrons
- Reduces concentration of holes (due to increased chance of recombination)
- Resistance reduced



23
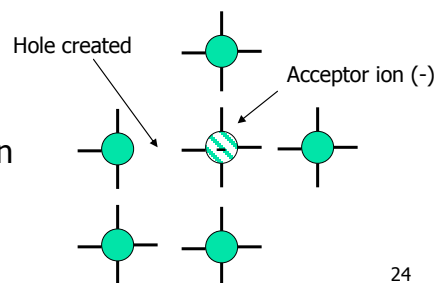
## p-type silicon

- p-type silicon is created by adding acceptor impurities which have three valance electrons (e.g. boron)
- This leaves an unbound valance electron in an adjacent silicon atom creating a hole
- Increases concentration of holes
- Reduces concentration of free electrons
- P-type silicon has lower resistance than pure silicon



24

## Diodes

- If a piece of n-type silicon and p-type silicon are joined directly together a diode (di - electrode) device is created



25

## Macro-behaviour


- A diode is a device that allows current flow easily in one direction easily and allows hardly any current flow in the opposite direction

26


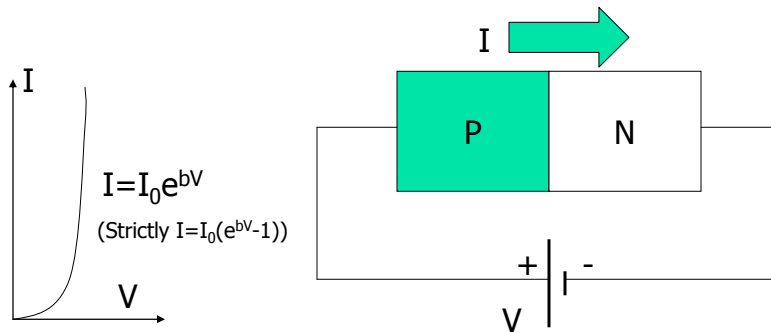
## Forward bias

- Current flows easily if the P region is positive with respect to the N region




27


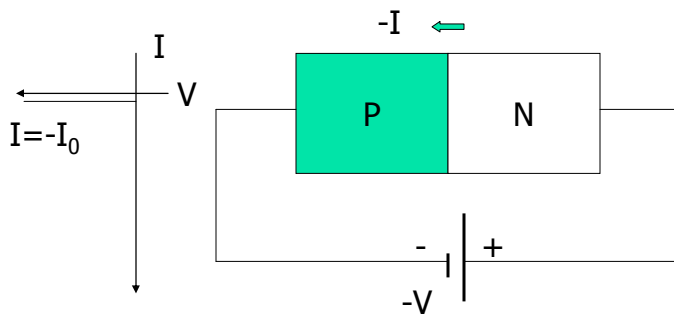
## Reverse bias


- Current hardly flows if the P region is negative with respect to the N region



28



## Diode and resistor circuit

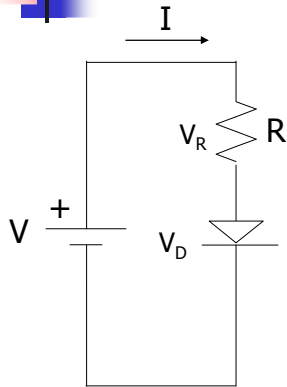

Currents and voltages determined by:  
(work backwards to find  $V_D$  )

1.  $V_D$  related to  $I$  by diode equation
2. Current in resistor and diode equal
3.  $V_R = IR$
4. voltage across diode and voltage resistor add up to voltage source  $V$


Short cut rule of thumb,  $V_D$  is approx 0.6-0.7 volts and  $V_R \approx V - 0.6$   
For LEDs  $V_D$  is about 1.8 - 4.0 V, depending on colour

Forward biased diode

29



## Diode and resistor circuit

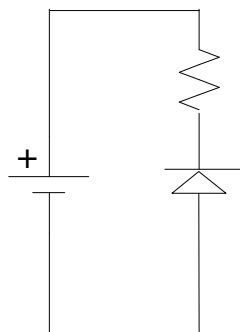

Assume no reverse-bias current flows (ideal case)

Therefore no voltage occurs across the resistor

Therefore the full supply voltage appears across the diode

Reverse biased diode

30



## LEDs

---

- Light emitting diode
- When an electron moves down from the conduction band to the valence band it loses energy
- In silicon and germanium the energy-momentum relationships mean that this energy is lost heat
- In gallium arsenide it produces a photon

31



## LEDs

---

- The light intensity is proportional to current
- Pure gallium arsenide produces infrared light
- GaAsP produces red or yellow light
- GaP produces red or green

32




## Circuit design using LEDs

- LEDs behave just like normal diodes except that the forward bias voltages are greater (typically 1.8 - 4.0 V)
- A typical forward bias current of 10-20 mA is used.


33

## Example

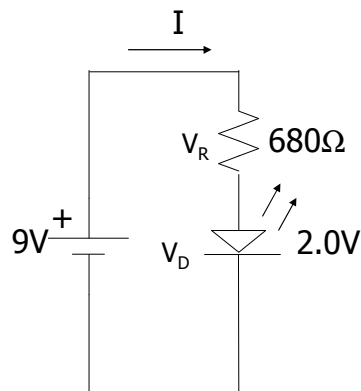

$$I = \frac{9 - 2.0}{680} \\ = 10.29 \text{ mA}$$

34




# Introduction to AVR

---

## Atmel AVR Microcontroller

35




# AVR Key Features

---

- High Performance 8-Bit MCU
- RISC Architecture
  - 32 Registers
  - 2-Address Instructions
  - Single Cycle Execution
- Low Power
- Large linear address spaces
- Efficient C Language Code Density
- On-chip in-system programmable memories

RISC Performance with CISC Code Density

36

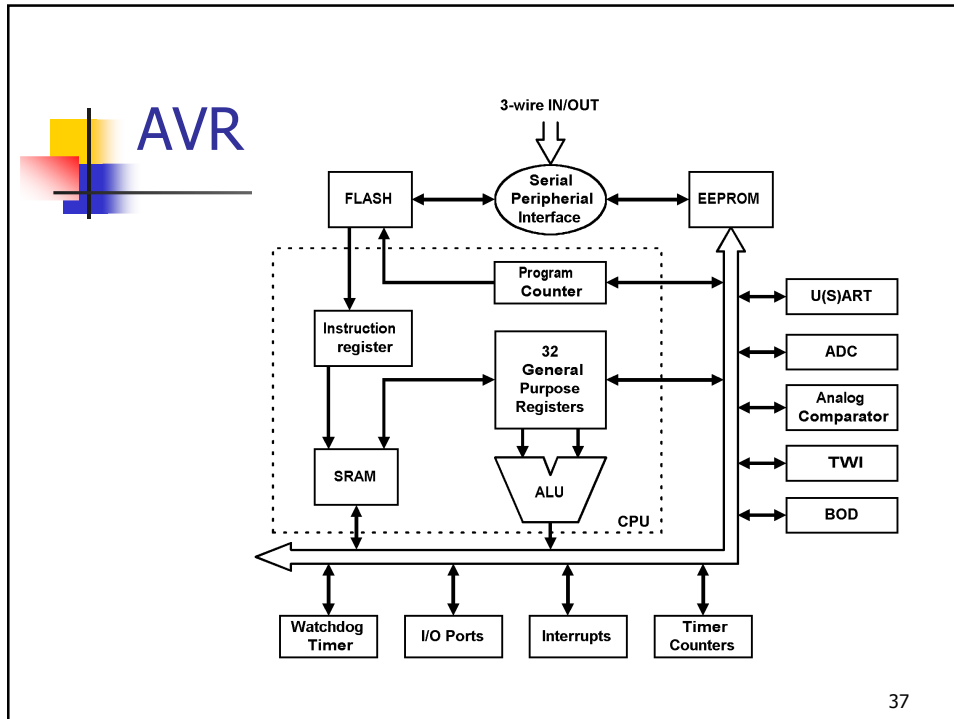

37

## ATmega16(L)

- 40/44 pin packages
- 16 KBytes ISP Flash, Self Programmable
- 512 Bytes ISP EEPROM
- 1 KBytes SRAM
- Full Duplex UART
- SPI – Serial Interface
- TWI – Serial Interface
- 8- and 16-bits Timer/Counters with PWM
- 2 External Interrupts
- 10-bit ADC with 8 Multiplexed Inputs
- RTC with Separate 32 kHz Oscillator
- Analog Comparator
- JTAG Interface with On-Chip Debugger

38



## Typical Applications, ATmega16(L)

---

- Smart Battery
- Advanced Battery Charger
- Power Meter
- Temperature Logger
- Voltage Logger
- Tension Control
- Touch Screen Sensor
- Metering Applications
- UPS
- 3 Phase Motor Controller
- Industrial Control
- Power Management

39



## I/O Ports General Features

---

- Push-Pull Drivers
- High Current Drive (sinks up to 40 mA)
- Pin-wise Controlled Pull-Up Resistors
- Pin-wise Controlled Data Direction
- Fully Synchronized Inputs
- Three Control/Status Bits per Bit/Pin
- Real Read-Modify-Write

40




## 3 Control/Status Bits per Pin

- DDx Data Direction Control Bit
- PORTx Output Data or Pull-Up Control Bit
- PINx Pin Level Bit

41





## Default Configuration

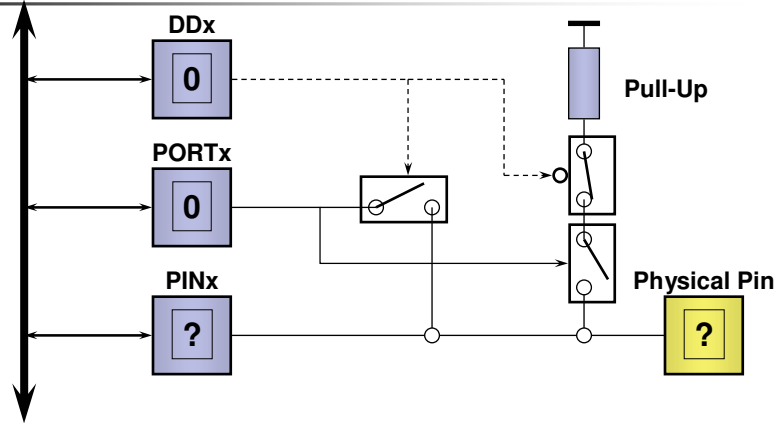

Direction: **INPUT**  
Pull-Up: **OFF**

42

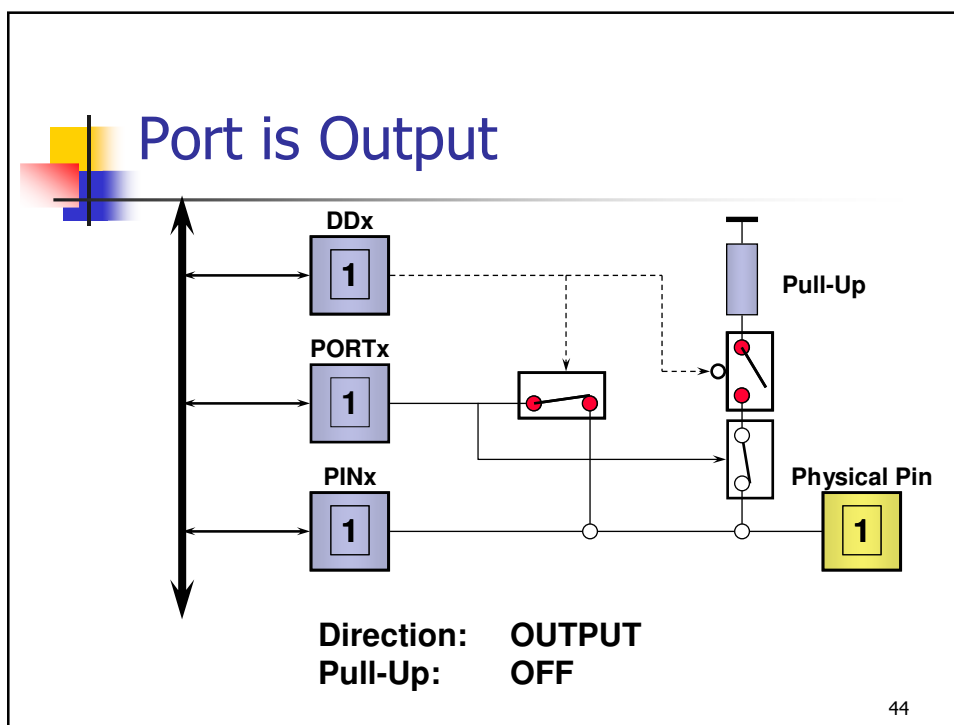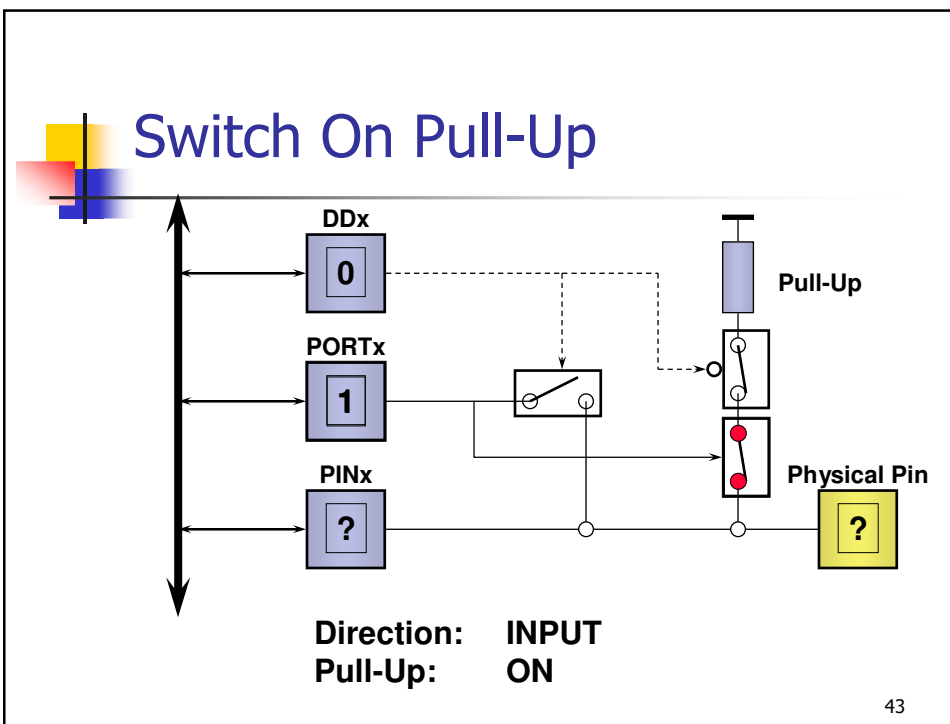



## General T/C Features

- Various Clock Prescaling Options
- Can Run at Undivided XTAL Frequency (High Resolution)
- Can be Set to Any Value at Any Time
- Can be Clocked Externally by Signals with Transition Periods down to XTAL/2
- Can be Clocked Externally on both Rising and Falling Edge
- The features vary from device to device, see datasheets for details

45




## 16 Bit Timer/Counter

- Prescaler
- Overflow Interrupt
- Output Compare Function with Interrupt
- Input Capture with Interrupt and Noise Cancler
- PWM

46

## 16 Bit T/C Block Diagram

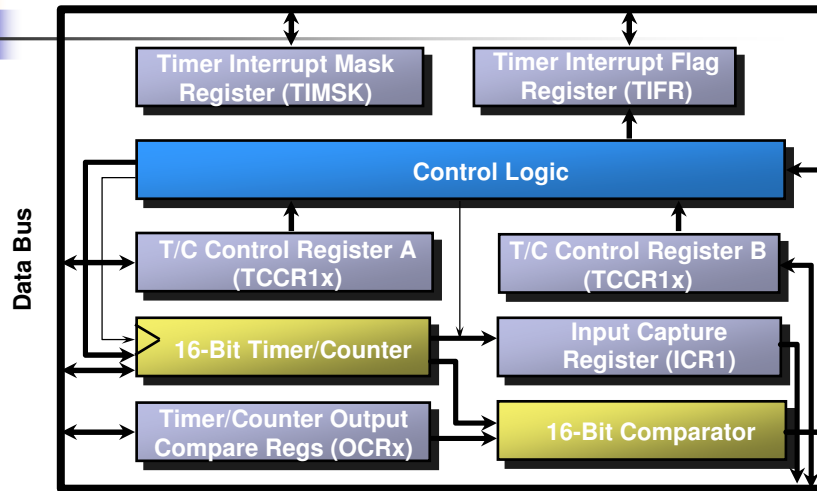

47

## Output Compare Features

- Compare match can control an external pin (Rise, Fall or Toggle) even if the Interrupt is disabled.
- As an option, the timer can be automatically cleared when a compare match occurs.

48






## PWM Features

- Selectable 8, 9 or 10-Bit Resolution.
- Frequency @ 10 MHz (8-bit): 19 KHz
- Centered Pulses
- Glitch-Free Pulse Width Change
- Selectable Polarity

49



## PWM Operation

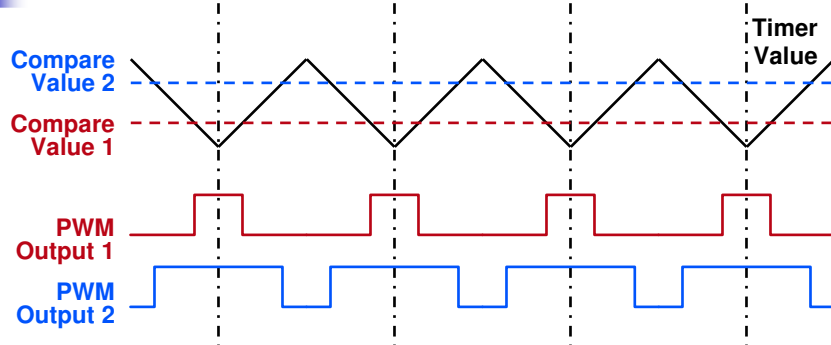


50
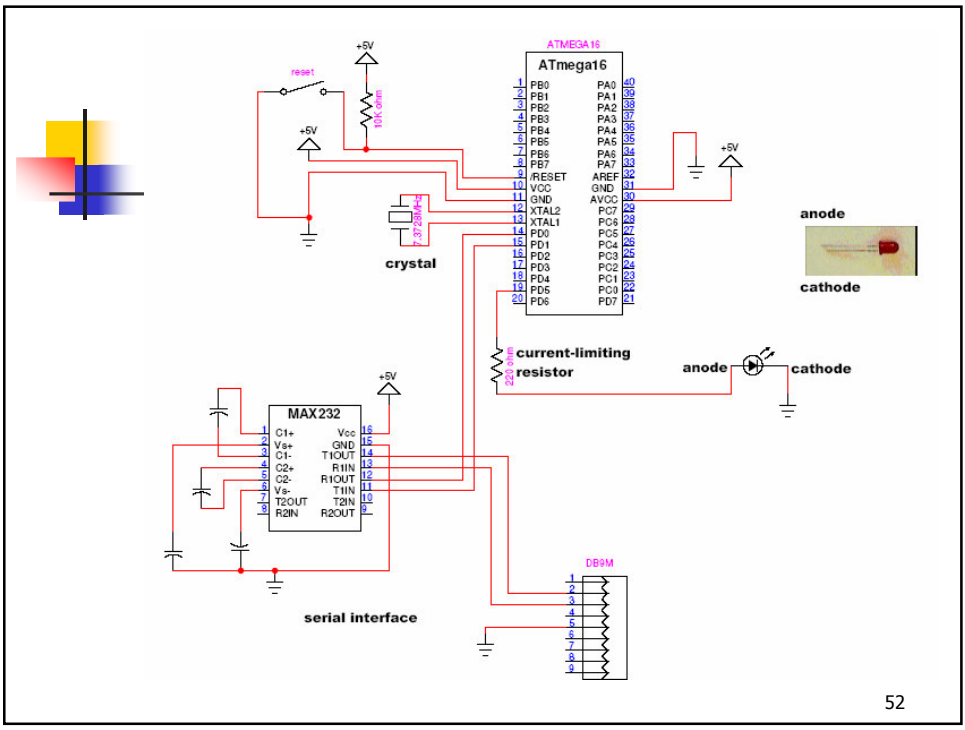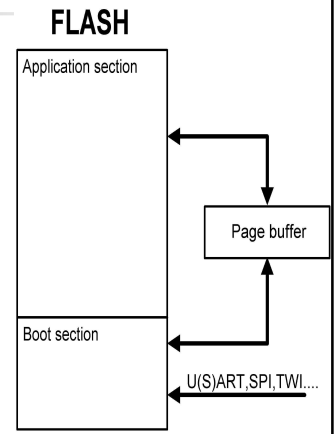
# Self Programming

- Dual memory areas
  - Application section
  - Boot section (optional)
- Read data from
  - Any communication interface
  - Application section
  - Boot section
- Write it to a page buffer
- Transfer the buffer to the Flash page in Application or Boot section



## MegaLoad

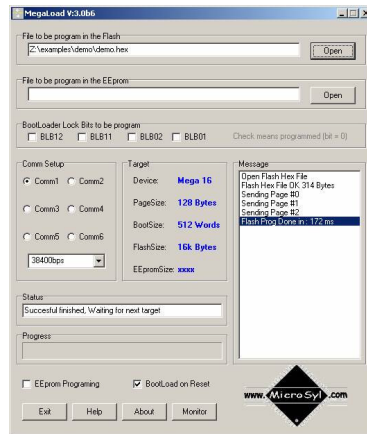

53

## AVR websites and mail

- ATMEL website [www.atmel.com](http://www.atmel.com)
  - Datasheets
  - Application Notes
  - FAQ
- Unofficial AVR websites
  - [www.avrfreaks.net](http://www.avrfreaks.net)
  - [www.avr-forum.com](http://www.avr-forum.com)

54