

Lecture 3 – System Timing and Case Studies

CSE P567

Summary: Verilog for Combinational Logic

- ▶ **Two alternatives:**
 - ▶ assign statement – simple logic equation
 - ▶ always block – allows complex program to describe function
- ▶ **Each assign and always block compiles into a component**
 - ▶ Combinational function with some inputs and outputs
- ▶ **All components operate in parallel, continuously**
 - ▶ If any input changes, the function is recomputed
 - ▶ This may change the output
 - ▶ Which will cause inputs of some components to change
- ▶ **Just like a circuit made up of gates!**



Verilog for

- ▶ for is similar to C
- ▶ for statement is executed at compile time
 - ▶ result is all that matters, not how result is calculated

```
// simple encoder
module encode
  (input  [7:0] A,      // 8-bit input vector
   output reg [2:0] Y); // 3-bit encoded output
  integer i;          // Temporary variables for program only
  reg [7:0] test;

  always @(*) begin
    test = 8b'00000001;
    Y = 3'bX;
    for (i = 0; i < 8; i = i + 1) begin
      if (A == test) Y = i;
      test = test << 1;
    end
  end
endmodule
```

Another Behavioral Example

- ▶ Combinational block that computes Conway's Game of Life rule

```
module life
  (input          self,
   input [7:0]    neighbors,
   output reg     out);
  integer        count;
  integer        i;

  always @(*) begin
    count = 0;
    for (i = 0; i < 8; i = i + 1) count = count + neighbors[i];
    out = 0;
    out = out | (count == 3);
    out = out | ((self == 1) & (count == 2));
  end
endmodule
```

Case Study – Division by Constant

- ▶ e.g. $\text{gray} = (\text{red} + \text{blue} + \text{green})/3$
- ▶ Division is very expensive in general
 - ▶ Area and Delay
 - ▶ Much more so than multiplication
- ▶ Convert division to multiplication
 - ▶ Multiply by the reciprocal
 - ▶ e.g. $(\text{red} + \text{blue} + \text{green}) * 0.33$
 - ▶ Floating-point??
 - ▶ Also expensive!
- ▶ Key idea: multiply & divide by 2^n is FREE



RGB to Grayscale

- ▶ $Y = 0.3 * R + 0.59 * G + 0.11 * B$
- ▶ $1024 * 0.3 = 307.2$
- ▶ $1024 * 0.59 = 604.16$
- ▶ $1024 * 0.11 = 112.64$

- ▶ $Y = (307 * R + 604 * G + 113 * B) \gg 10;$

- ▶ This works for multiplying/dividing with any number with fractions
 - ▶ Scale then re-scale



Converting Division to Multiplication

- ▶ Increase precision until it's good enough
 - ▶ FPGA has 18x18 multipliers – almost free
- ▶ Division by a variable?
 - ▶ Table lookup of reciprocal
 - ▶ Does not scale to large numbers
 - ▶ Use iterative solutions



Creating a Table in Verilog

```
////////// Sin Wave ROM Table //////////
always @(*) begin
  case(SIN_Cont)
    0 : Sin_Out = 0 ;
    1 : Sin_Out = 4276 ;
    2 : Sin_Out = 8480 ;
    3 : Sin_Out = 12539 ;
    4 : Sin_Out = 16383 ;
    5 : Sin_Out = 19947 ;
    6 : Sin_Out = 23169 ;
    7 : Sin_Out = 25995 ;
    8 : Sin_Out = 28377 ;
    9 : Sin_Out = 30272 ;
    10 : Sin_Out = 31650 ;
    11 : Sin_Out = 32486 ;
    12 : Sin_Out = 32767 ;
    13 : Sin_Out = 32486 ;
    14 : Sin_Out = 31650 ;
    15 : Sin_Out = 30272 ;
    16 : Sin_Out = 28377 ;
    17 : Sin_Out = 25995 ;
    18 : Sin_Out = 23169 ;
    19 : Sin_Out = 19947 ;
    20 : Sin_Out = 16383 ;
    21 : Sin_Out = 12539 ;
    22 : Sin_Out = 8480 ;
    23 : Sin_Out = 4276 ;
    24 : Sin_Out = 0 ;
    25 : Sin_Out = 61259 ;
    26 : Sin_Out = 57056 ;
    . . .
    default : Sin_Out = 0 ;
  endcase
end
```

- ▶ Generate this code using a program!
-



Summary: Verilog for Sequential Logic

- ▶ Use `always @ (posedge clk)` blocks
 - ▶ Executes only when clock “ticks” (rising edge)
 - ▶ All assignments are registered
 - ▶ Use `<=` (delayed assignment – implements parallel sample/hold)
- ▶ Styles
 - ▶ One `posedge clk` block
 - ▶ Computation and registers
 - ▶ Not general
 - ▶ Separate register block and combinational logic block
 - ▶ More general, more like hardware
 - ▶ Less intuitive



Shift Register Example

```
// 4 register shift register
module shiftReg
  (input      CLK,
   input      reset,    // initialize registers
   input      shift,
   input  [7:0] Din,    // Data input for load
   output [7:0] Dout);
  reg [7:0] D0, D1, D2, D3;
  assign Dout = D0;
  always @(posedge CLK) begin
    if (reset) begin
      D0 <= 0; D1 <= 0; D2 <= 0; D3 <= 0;
    end else if (shift) begin
      D3 <= Din; D2 <= D3; D1 <= D2; D0 <= D1;
    end
  end
end

endmodule    // shiftReg
```



FIR Filter Example

```
module fir
  (input      CLK,
   input      reset,    // initialize registers
   input  [7:0] Din,    // Data input for load
   output reg [7:0] Dout);
  reg [7:0]    D0, D1, D2, D3;
  localparam C0 = 4, C1 = 3, C2 = 2, C3 = 1;

  always @(posedge CLK) begin
    if (reset) begin
      D0 <= 0; D1 <= 0; D2 <= 0; D3 <= 0;
    end else begin
      D3 <= Din; D2 <= D3; D1 <= D2; D0 <= D1;
      Dout <= C0 * D0 + C1 * D1 + C2 * D2 + C3 * D3;
    end
  end
end
endmodule // fir
```



Case Study: Wavelet Computation #1

```
localparam INIT=4, State0=0, State1=1, State2=2, State3=3;
    reg [2:0] state;          // State register

    // This shift register captures the input
    reg [7:0] in0, in1, in2, in3;
    // These hold data while data is shifting in
    reg [7:0] D0, D1, D2, D3;

// We use this shift register to delay the input valid bit by
// up to 8 clock cycles to generate the output valid bit
reg [8:0] valid;
assign validOut = valid[5]; // 5 cycles for pipe to fill

// Valid data enters as soon as reset is turned off
wire      validIn = ~reset;

always @(posedge clk) begin
    if (reset) begin
        valid = 0;
        state <= INIT;
    end else begin

// Constantly shift input data
in0 <= in1;
in1 <= in2;
in2 <= in3;
in3 <= dataIn;
valid <= { valid[7:0], validIn };
case (state)
    INIT: begin
        state <= State0;
    end
    State0: begin
        dataOut <= D0-D1; // Q0
        state <= State1;
    end
    State1: begin
        dataOut <= D2-D3; // Q1
        state <= State2;
    end
    State2: begin
        dataOut <= D0+D1+D2+D3; // Q2
        state <= State3;
    end
    State3: begin
        dataOut <= D0+D1-D2-D3; // Q3
        // Latch inputs
        D0 <= in0;
        D1 <= in1;
        D2 <= in2;
        D3 <= in3;
        state <= State0;
    end // case: State3
endcase // case(state)

    end
end
```



Block Diagram for Wavelet Filter



Wavelet with Split Block Style

```
localparam      INIT=4, State0=0, State1=1, State2=2, State3=3;
reg [2:0] state, nextState; // State register

. . .

// Registers
always @(posedge clk) begin
    if (reset) begin
        valid <= 0;
        state <= INIT;
    end else begin
        // Input shift register
        in0 <= in1;
        in1 <= in2;
        in2 <= in3;
        in3 <= dataIn;
        valid <= { valid[7:0], validIn }; // Shift left
        if (state == State3) begin
            D0 <= in0;
            D1 <= in1;
            D2 <= in2;
            D3 <= in3;
        end
        state <= nextState;
    end // else: !if(reset)
end // always @ (posedge clk)

// Combinational logic
always @(*) begin
    case (state)
        INIT: begin
            nextState = State0;
        end
        State0: begin
            dataOut = D0-D1; // Q0
            nextState = State1;
        end
        State1: begin
            dataOut = D2-D3; // Q1
            nextState = State2;
        end
        State2: begin
            dataOut = D0+D1+D2+D3; // Q2
            nextState = State3;
        end
        State3: begin
            dataOut = D0+D1-D2-D3; // Q3
            nextState = State0;
        end // case: State3
    endcase // case(state)
end
```



Case Study: Complex Wavelet

```
localparam INIT=4, State0=0, State1=1, State2=2, State3=3;
reg [2:0] state; // State register
reg [9:0] D0D1, D2D3; // Temp registers

// This shift register captures the input
// oldest newest
reg [7:0] in0, in1, in2, in3;

reg [8:0] valid;
assign validOut = valid[3];

// Valid data enters as soon as reset is turned off
wire validIn = ~reset;

always @(posedge clk) begin
    if (reset) begin
        valid = 0;
        state <= INIT;
    end else begin

in0 <= in1;
in1 <= in2;
in2 <= in3;
in3 <= dataIn;
valid <= { valid[7:0], validIn };
case (state)
    INIT: begin
        state <= State0;
    end
    State0: begin
        dataOut <= D0D1 + D2D3; // Q2
        state <= State1;
    end
    State1: begin
        dataOut <= D0D1 - D2D3; // Q3
        state <= State2;
    end
    State2: begin
        dataOut <= in1 - in2; // Q0: D0 - D1
        D0D1 <= in1 + in2; // D0 + D1
        state <= State3;
    end
    State3: begin
        dataOut <= in2 - in3; // Q1: D2 - D3
        D2D3 <= in2 + in3; // D2 + D3
        state <= State0;
    end // case: State3
endcase // case(state)

end
end
endmodule
```



Block Diagram for Complex Wavelet



Case Study: Camera Input

```
module camera(  
    input          clk,          // clock  
    input          reset,       // reset  
    input  [11:0]  CCD_DATA,    // Input from camera  
    input          CCD_FVAL,    // In Frame signal  
    input          CCD_LVAL,    // In Line signal  
    input          iSTART,     // Start button  
    input          iEND,       // Stop button  
    output [11:0]  pixelOut,    // Output pixel data  
    output reg [15:0] colAddr,  // Pixel address  
    output reg [15:0] lineAddr, // Line address  
    output         newFrame,   // Done with frame  
    output         pixelValid); // Pixel valid  
  
    // Registers  
    reg fvalPrev;  
    reg lvalPrev;  
    reg [11:0] CCD_DATA_L0;  
    reg [11:0] CCD_DATA_L1;  
  
    // Control signals  
    reg outputEnableSignal;  
    reg outputEnable;  
    wire isNewPixel;  
    wire isNewFrame;  
    wire isNewLine;  
  
    // Control signals  
    assign isNewPixel = CCD_FVAL && CCD_LVAL;  
    assign isNewFrame = fvalPrev && !CCD_FVAL;  
    assign isNewLine = lvalPrev && !CCD_LVAL;  
  
    assign pixelOut = CCD_DATA_L1;  
    assign pixelValid = isNewPixel && outputEnable;  
    assign newFrame = isNewFrame && outputEnable;  
  
    // Latch signals  
    always @(posedge clk) begin  
        fvalPrev <= CCD_FVAL;  
        lvalPrev <= CCD_LVAL;  
        CCD_DATA_L0 <= CCD_DATA;  
        CCD_DATA_L1 <= CCD_DATA_L0;  
    end  
  
    // Calculate addresses  
    always @(posedge clk) begin  
        if (reset || isNewLine) colAddr <= 0;  
        else if (isNewPixel) colAddr <= colAddr + 1;  
        if (reset || isNewFrame) lineAddr <= 0;  
        else if (isNewLine) lineAddr <= lineAddr + 1;  
    end  
  
    // Implement START/STOP picture  
    always @(posedge clk) begin  
        if (reset || iSTART) outputEnableSignal <= 1;  
        else if (iEND) outputEnableSignal <= 0;  
        if (isNewFrame) outputEnable <= outputEnableSignal;  
    end  
end
```



Case Study: Camera Input

```
// Calculate addresses
always @(posedge clk) begin
    if (reset || isNewLine) colAddr <= 0;
    else if (isNewPixel) colAddr <= colAddr + 1;
    if (reset || isNewFrame) lineAddr <= 0;
    else if (isNewLine) lineAddr <= lineAddr + 1;
end

// Implement START/STOP picture
always @(posedge clk) begin
    if (reset || iSTART) outputEnableSignal <= 1;
    else if (iEND) outputEnableSignal <= 0;
    if (isNewFrame) outputEnable <= outputEnableSignal;
end
```



Case Study: Camera Input

```
// Control signals
assign isNewPixel = CCD_FVAL && CCD_LVAL;
assign isNewFrame = fvalPrev && !CCD_FVAL;
assign isNewLine = lvalPrev && !CCD_LVAL;

assign pixelOut = CCD_DATA_L1;
assign pixelValid = isNewPixel && outputEnable;
assign newFrame = isNewFrame && outputEnable;

// Latch signals
always @(posedge clk) begin
    fvalPrev <= CCD_FVAL;
    lvalPrev <= CCD_LVAL;
    CCD_DATA_L0 <= CCD_DATA;
    CCD_DATA_L1 <= CCD_DATA_L0;
end
```



Case Study: Camera Input

```
// Control signals
assign isNewPixel = CCD_FVAL && CCD_LVAL;
assign isNewFrame = fvalPrev && !CCD_FVAL;
assign isNewLine = lvalPrev && !CCD_LVAL;


assign pixelOut = CCD_DATA_L1;
assign pixelValid = isNewPixel && outputEnable;
assign newFrame = isNewFrame && outputEnable;

// Latch signals
always @(posedge clk) begin
    fvalPrev <= CCD_FVAL;
    lvalPrev <= CCD_LVAL;
    CCD_DATA_L0 <= CCD_DATA;
    CCD_DATA_L1 <= CCD_DATA_L0;
end
```



Design Problem – Run-Length Encoder

 - ▶ 7-bit input stream
- ▶ 8-bit output stream
 - ▶ high-order bit == 0: Data value
 - ▶ high-order bit == 1: Repeat count of previous data value
- ▶ Valid bit set when 8-bit output is data or count




RLE Design

- ▶ Split design into datapath and control
- ▶ Datapath
 - ▶ Registers for data values, count
 - ▶ Multiplexors
- ▶ Control
 - ▶ Keep track of what's happening
 - ▶ clear count, increment count, send data value, send count
- ▶ Control will be an FSM


Start with Datapath

- ▶ We need to know what to control

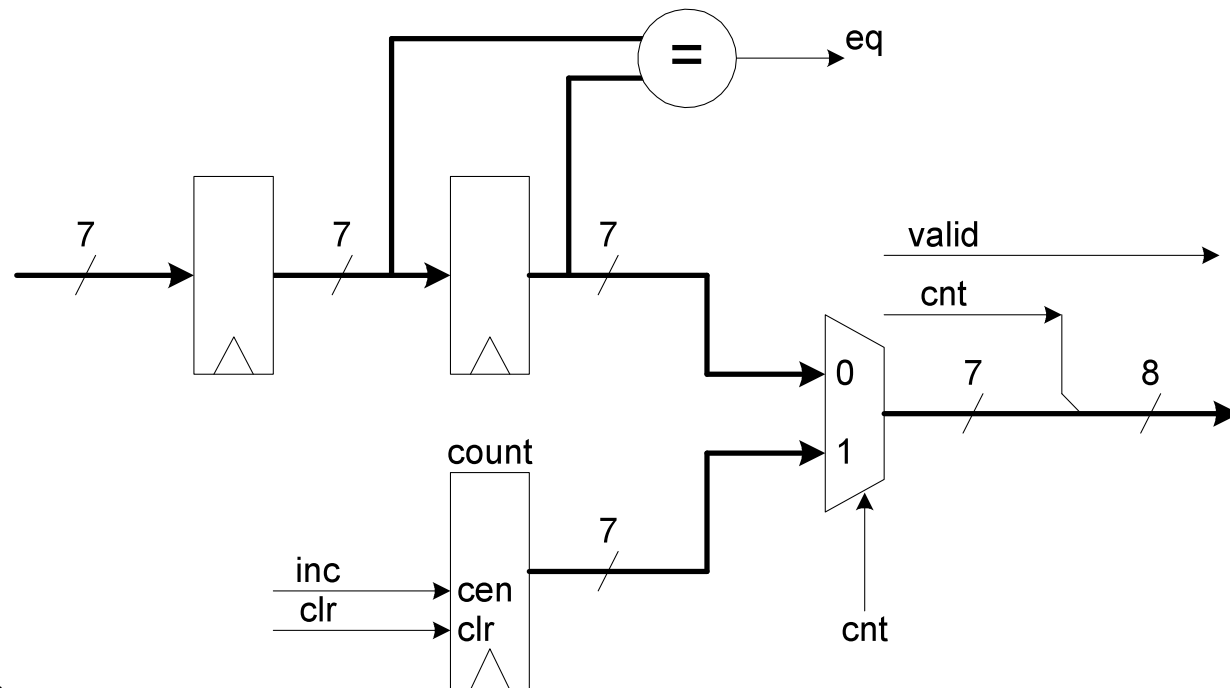


- ▶ **FSM inputs**
 - ▶ eq
- ▶ **FSM outputs**
 - ▶ clr, inc, valid, cnt,

FSM Controller

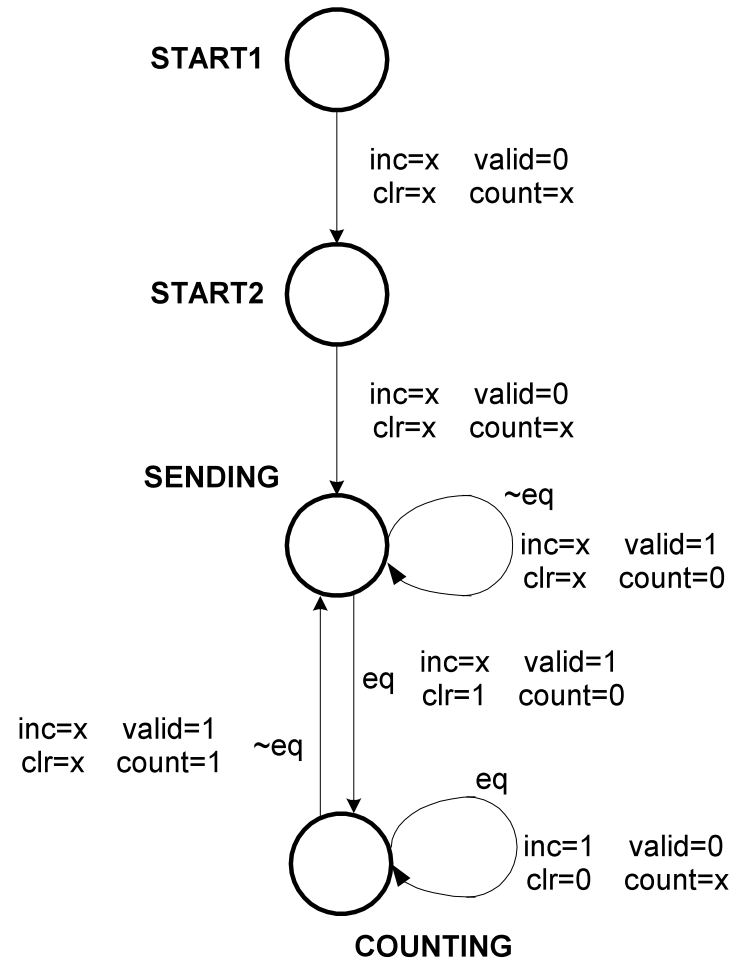

Verilog For State Machines

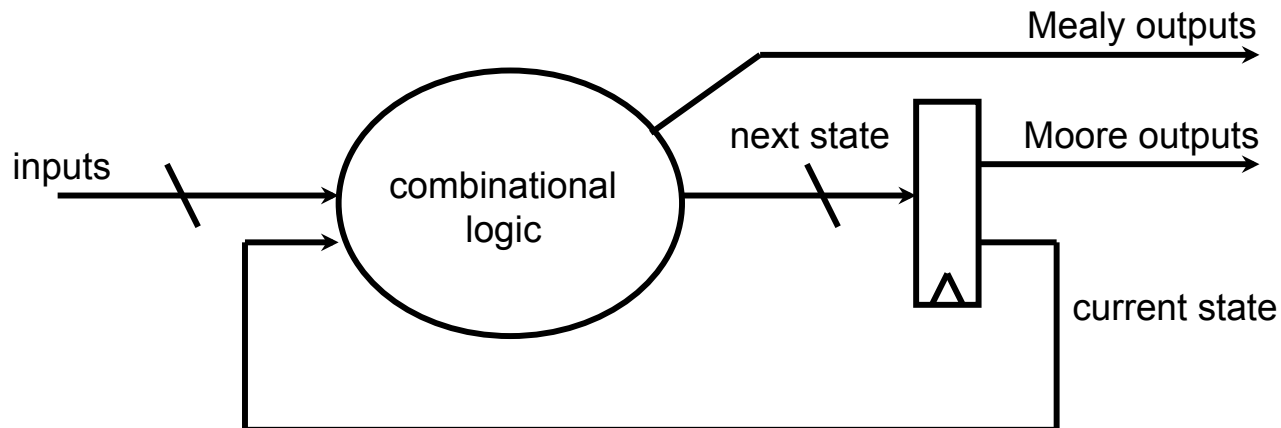- ▶ State machine has two parts
 - ▶ State register
 - ▶ Combinational Logic
 - ▶ Next state function
 - ▶ Output function
- ▶ Each in a different always block



RLE Module – Datapath + Control

```
module rleFSM (clk, reset, eq, clr, inc, valid, cnttag);
  input clk, reset;
  input eq;           // current data value == previous data value
  output clr;        // clear count value (0 means 2, . . .)
  output inc;        // increment count value (clr overrides)
  output valid;      // output value is valid
  output cnttag;     // select the count for the output value

  // Use parameter to define symbolic states
  localparam START1 = 0, START2 = 1, SENDING = 2, COUNTING = 3;
  reg [1:0] state,    // current state
           nextState; // next state

  always @(posedge CLK) begin
    if (reset)
      state <= START1;
    else
      state <= nextState;
  end
end
```

Combinational Logic for FSM

```
always @(*) begin
    // Set defaults
    valid = 0; inc = x; clr = x; cnttag = x;
    case (state)
    START1:
        nextState = START2;
    START2:
        nextState = SENDING;
    SENDING: begin
        valid = 1;
        cnttag = 0;
        if (eq) begin
            nextState = COUNTING;
        end else begin
            nextState = SENDING;
        end
    end
    COUNTING: begin
        if (eq) begin
            clr = 0;
            inc = 1;
            nextState = COUNTING;
        end else begin
            valid = 1;
            cnttag = 1;
            nextState = SENDING;
        end
    end
end
```

Combinational Logic Design

- ▶ We can translate a Boolean function into logic gates
 - ▶ AND, OR, INVERT
- ▶ e.g. Homework problem
 - ▶ $g_0 = r_0$
 - ▶ $g_1 = r_1 * r_0'$
 - ▶ $g_2 = r_2 * r_0' * r_1'$
 - ▶ $g_2 = r_3 * r_0' * r_1' * r_2'$
 - ▶ $g_2 = r_4 * r_0' * r_1' * r_2' * r_3'$
 - ▶ $g_2 = r_5 * r_0' * r_1' * r_2' * r_3' * r_4$
- ▶ This is a “scan” computation from parallel computing



Reduce and Scan Operators

- ▶ **Reduce:** Reduce a vector of values to a single value
 - ▶ e.g. sum, max, min, ...
- ▶ **Scan:** Convert a vector of values to a new vector
 - ▶ output_k is reduction applied to the first k inputs
 - ▶ e.g. sum, max, min, ...
- ▶ **Reduce can be done in $O(\log)$ time**
 - ▶ Simple n -ary tree
- ▶ **Scan can also be done in $O(\log)$ time**
 - ▶ Double the time for Reduce
 - ▶ A “down” tree and an “up” tree




A Real Example of Scan

- ▶ Histogram equalization – contrast enhancement
 - ▶ (see Wikipedia)
- ▶ Step 1 – Create a histogram of all pixel values
 - ▶ Bin 0 – 255
- ▶ Step 2 – Compute the Cumulative Distribution Function
 - ▶ $\text{cdf}[i] = \text{SUM}_{j <= i} (\text{bin}[j]) / \text{totalPixelCount}$
- ▶ Step 3 – Convert pixels using the cdf
 - ▶ $\text{out} = 255 * \text{cdf}(\text{in})$
- ▶ CDF can be computed in $O(\log)$ time
 - ▶ For large dynamic range, this can be important




Histogram Equalization

 - ▶ a) Histogram and cdf
- ▶ b) Equalized histogram and cdf



a

 

b



Carry-Lookahead Adder

- ▶ Recall: $\text{Sum}_i = A_i \text{ xor } B_i \text{ xor } C_i$
 - ▶ where C_i is the carry in from the next bit position
- ▶ If we can compute carry using scan, we can compute add in $O(\log)$ time
- ▶ Problem: Parallel scan only works for associative functions
 - ▶ Carry is not associative
- ▶ We will use two other functions that are associative
 - ▶ Carry Generate (G)
 - ▶ Carry Propagate (P)



Carry-Lookahead Adder

- ▶ Generate – true, if an adder “block” generates a carry regardless of the carry in
- ▶ Propagate – true, if an adder “block” propagates a carry in to the carry out
- ▶ Example: 1-bit adder
- ▶ Example: 2-bit adder
- ▶ Associativity: Combining Generates and Propagates



Carry-Lookahead Adder

- ▶ $C_i = G_{i:0} + C_{in} * P_{i:0}$
- ▶ That is, if we compute $G_{i:0}$ and $P_{i:0}$ fast, then we can compute C_i fast
- ▶ And we can use parallel scan (aka parallel prefix) to compute $G_{i:0}$ and $P_{i:0}$ fast




System Timing

- ▶ **Register Timing Constraints**
 - ▶ Setup time
 - ▶ Hold time
- ▶ **Clock Generation and Distribution**
 - ▶ Clock skew
 - ▶ Multiple clocks
 - ▶ PLLs & DLLs
- ▶ **Asynchronous communication**
 - ▶ Not all modules can have the same clock
 - ▶ Distance and too much clock skew
- ▶ **Synchronous communication**
 - ▶ Source-synchronous signaling



Registers

 
- ▶ Sample data using clock
- ▶ Hold data between clock cycles
- ▶ Computation (and delay) occurs between registers




Timing Methodologies (cont'd)

▶ Definition of terms

 - ▶ setup time: minimum time before the clocking event by which the input must be stable (T_{su})
- ▶ hold time: minimum time after the clocking event until which the input must remain stable (T_h)




 there is a timing "window" around the clocking event during which the input must remain stable and unchanged in order to be recognized



Typical timing specifications

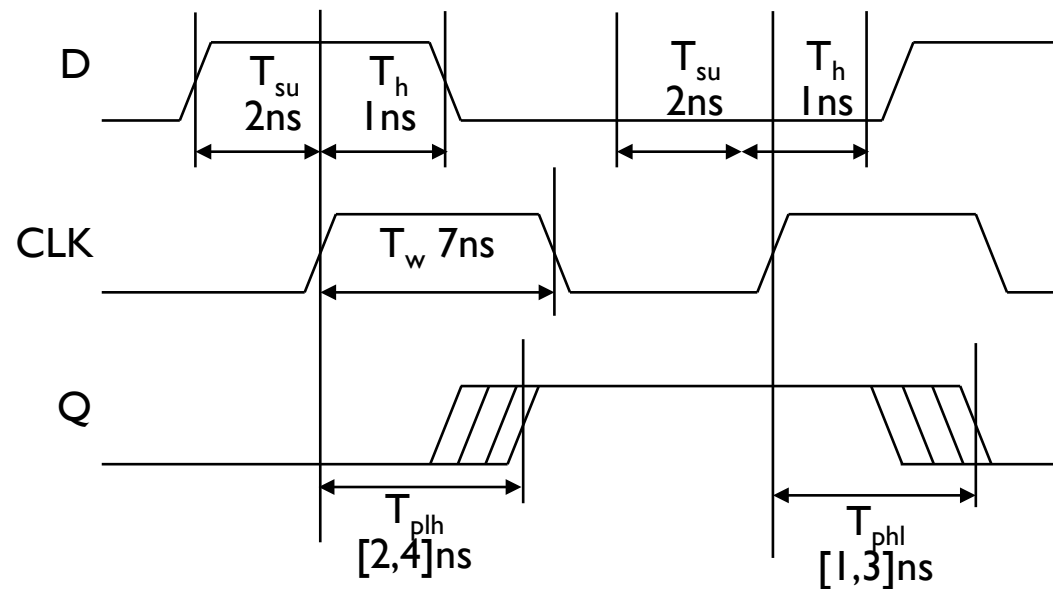
- ▶ Positive edge-triggered D flip-flop
 - ▶ setup and hold times
 - ▶ minimum clock width
 - ▶ propagation delays (low to high, high to low, max and typical)



all measurements are made from the clocking event that is,
the rising edge of the clock


Synchronous System Model

 - ▶ Register-to-register operation
- ▶ Perform operations during transfer
- ▶ Many transfers/operations occur simultaneously




System Clock Frequency

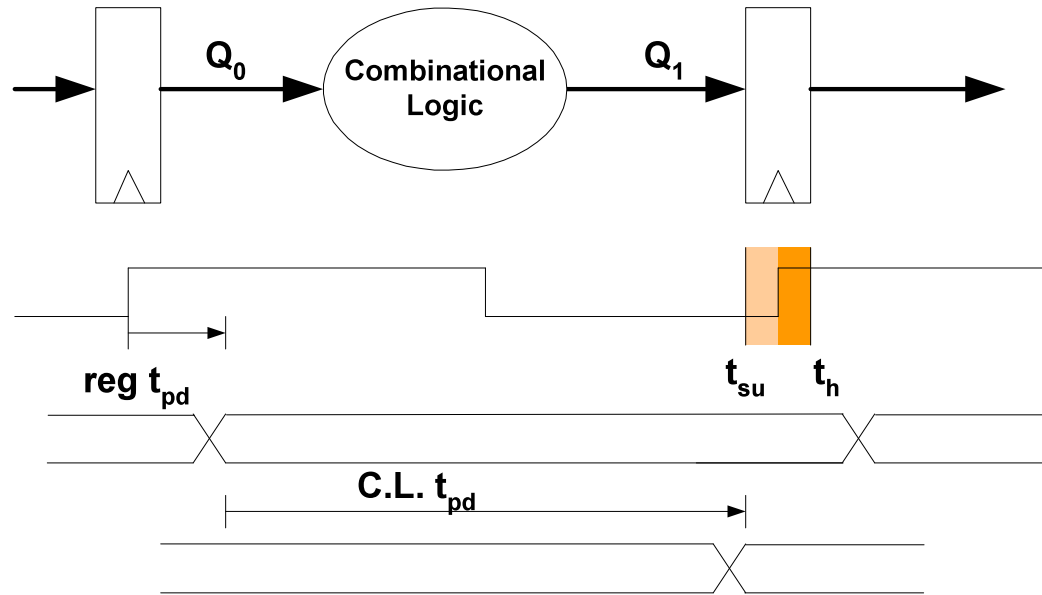- ▶ Register transfer must fit into one clock cycle
 - ▶ $\text{reg } t_{pd} + \text{C.L. } t_{pd} + \text{reg } t_{su} < T_{\text{clk}}$
 - ▶ Use maximum delays
 - ▶ Find the “critical path”
 - ▶ Longest register-register delay




Short Paths

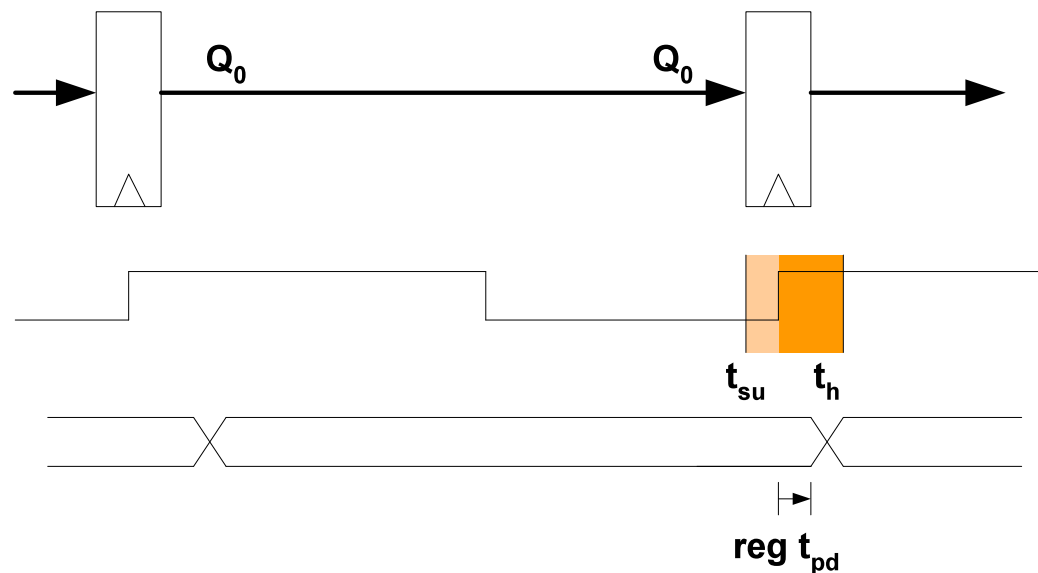- ▶ Can a path have too little delay?
 - ▶ Yes: Hold time can be violated
 - ▶ $t_{pd} > t_h$
 - ▶ Use min delay (contamination delay)
- ▶ Fortunately, most registers have hold time = 0
 - ▶ But there can still be a problem! Clock skew...




Clock Skew

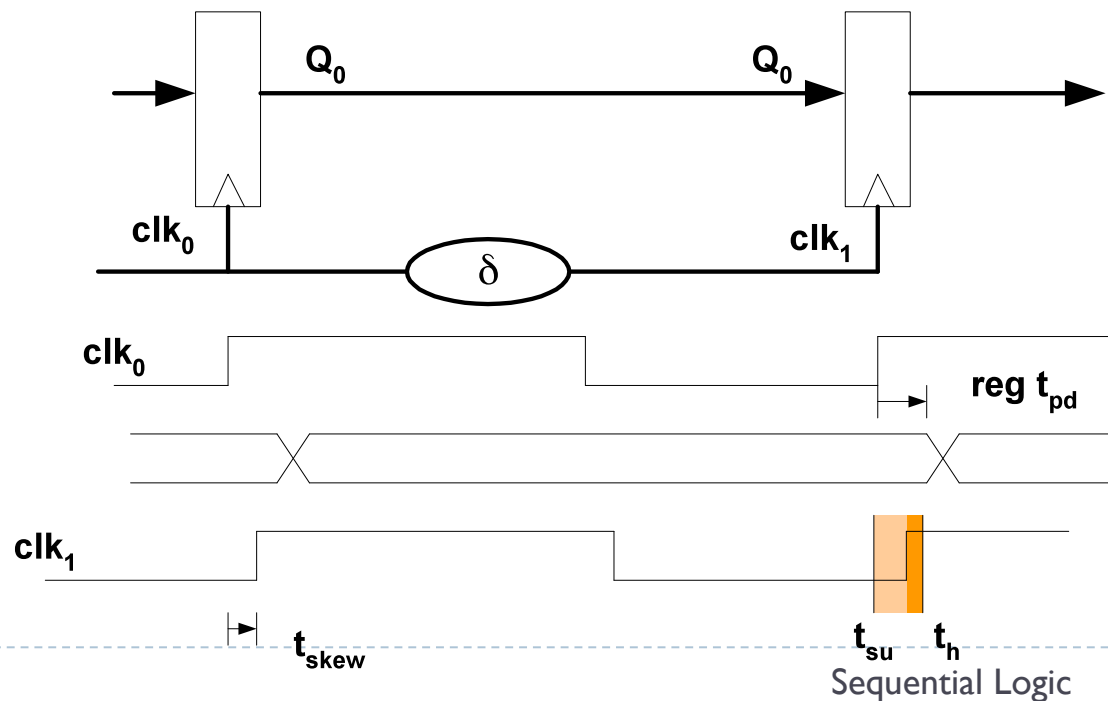- ▶ Cannot make clock arrive at registers at the same time
- ▶ If skew > 0 :
 - ▶ $t_{pd} > t_h + t_{skew}$
 - ▶ Clock skew can cause system failure
 - ▶ Can you fix this after you've fabbed the chip?



Clock Skew

 
- ▶ Cannot make clock arrive at registers at the same time
- ▶ If skew > 0 :
 - ▶ $t_{pd} > t_h + t_{skew}$
 - ▶ Clock skew can cause system failure
 - ▶ Can you fix this after you've fabbed the chip?



Clock Skew

- ▶ If skew < 0:


- ▶ $t_{clk} > reg\ t_{pd} + CL\ t_{pd} + reg\ t_{SU} + |t_{skew}|$
- ▶ Can you fix this after fab?

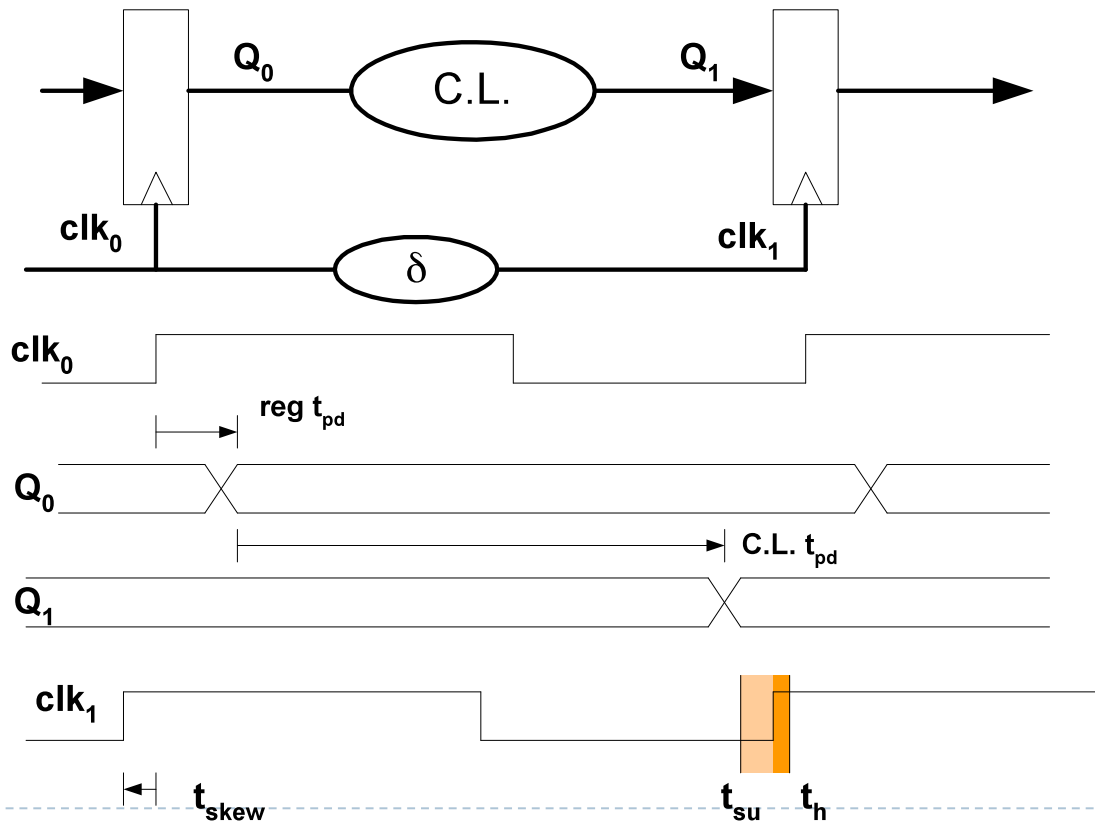

Clock Skew

- ▶ If skew < 0:

- ▶ $t_{clk} > reg\ t_{pd} + CL\ t_{pd} + reg\ t_{SU} + |t_{skew}|$
- ▶ Can you fix this after fab?

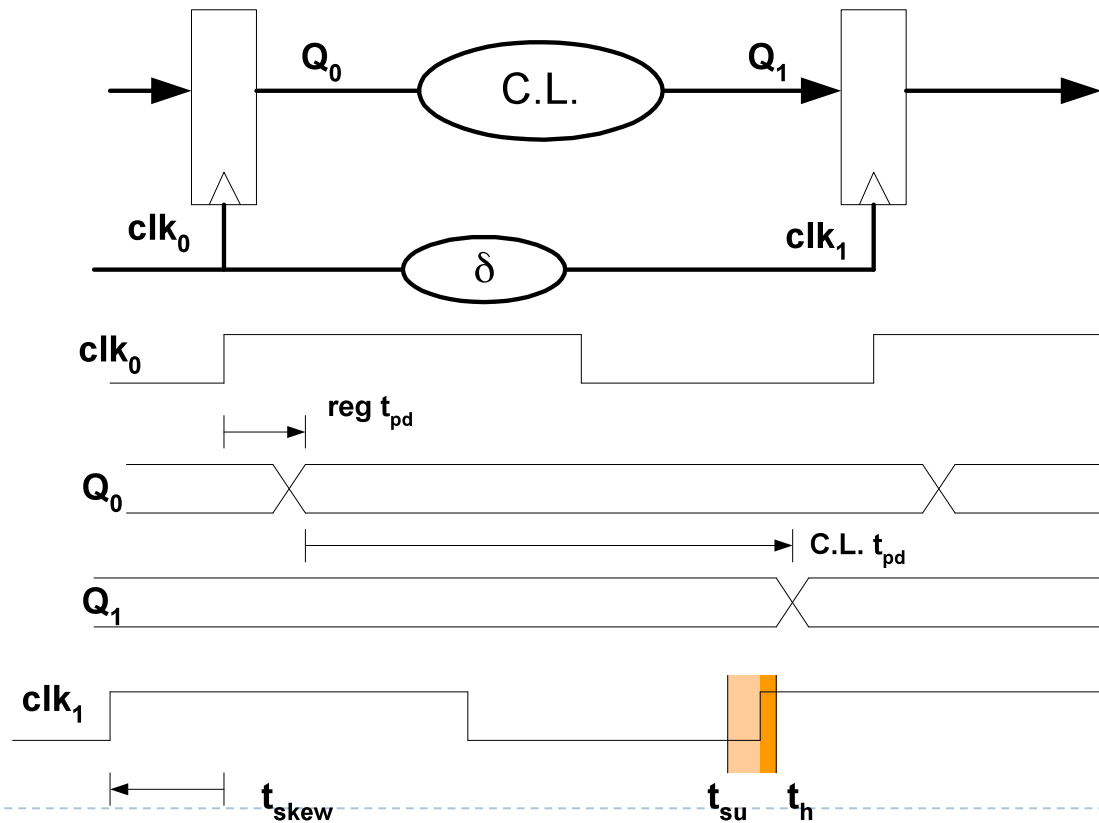


Clock Skew

- ▶ Correct behavior assumes that all storage elements sample at exactly the same time
- ▶ Not possible in real systems:
 - ▶ clock driven from some central location
 - ▶ different wire delay to different points in the circuit
- ▶ Problems arise if skew is of the same order as FF contamination delay
- ▶ Gets worse as systems get faster (wires don't improve as fast)
 - ▶ 1) distribute clock signals against the data flow
 - ▶ 2) wire carrying the clock between two communicating components should be as short as possible
 - ▶ 3) try to make all wires from the clock generator be the same length
=> clock tree


Altera FPGA PLL

Figure 2-16. Cyclone II PLL Note (1)

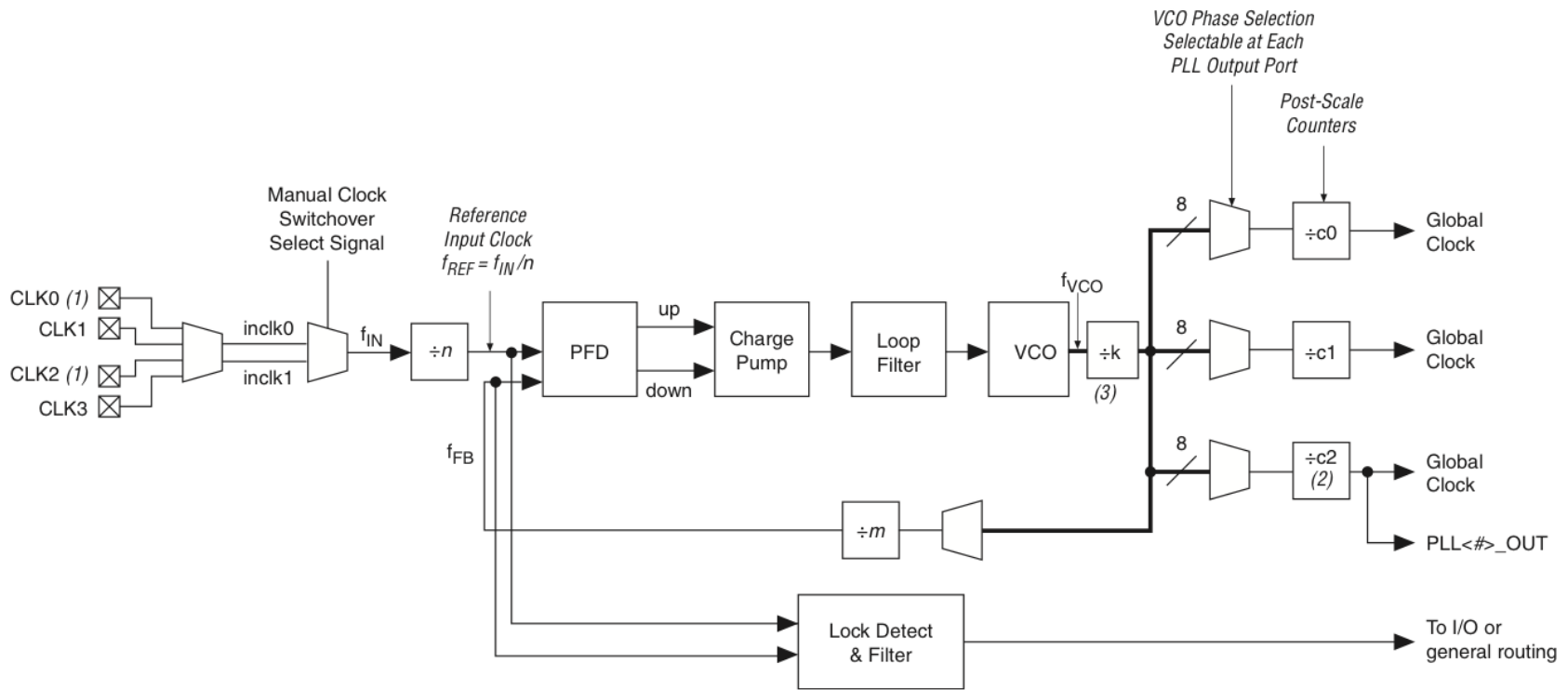


What About External Inputs?

 - ▶ **Internal signals are OK**
 - ▶ Can only change when clock changes
- ▶ **External signals can change at any time**
 - ▶ Asynchronous inputs
 - ▶ Truly asynchronous
 - ▶ Produced by a different clock
- ▶ **This means register may sample a signal that is changing**
 - ▶ Violates setup/hold time
 - ▶ What happens?




Sampling Asynchronous Inputs

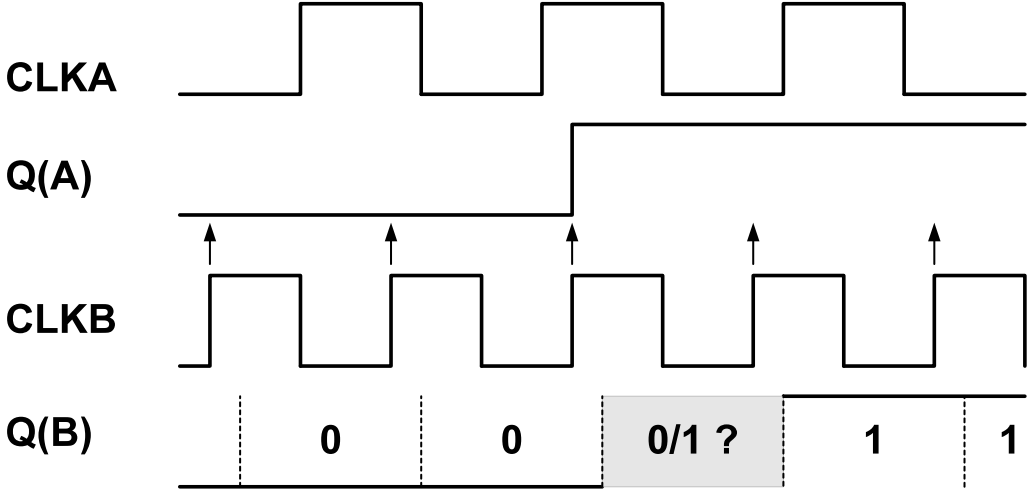


Sampling Rate

 - ▶ How fast does your sample clock need to be?




Sampling Rate

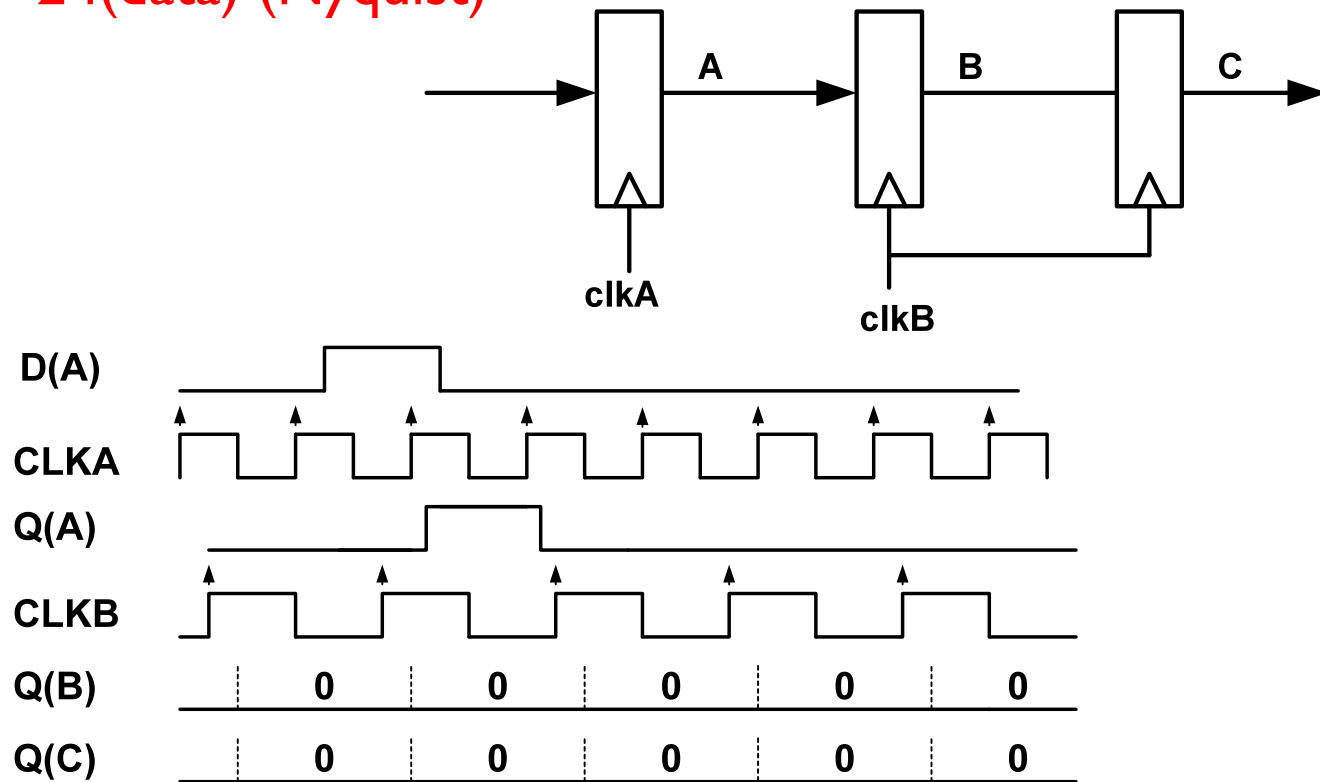- ▶ How fast does your sample clock need to be?
 - ▶ $f(\text{clkB}) > f(\text{clkA})$
 - ▶ $f(\text{clkB}) > 2 f(\text{data})$ (Nyquist)



Another Problem with Asynchronous inputs

 - ▶ What goes wrong here?
- ▶ What is the fix?




Think About the Reset Signal!

- ▶ **Reset input is typically asynchronous**
 - ▶ Which edge do we care about?
 - ▶ Does it matter if the registers have synchronous or asynchronous resets?
- ▶ **Reset is broadcast to all registers in system**
- ▶ **What happens?**

- ▶ **Register input should be single-registered just like every other asynchronous input**


More Asynchronous inputs

 - ▶ What is the problem?
- ▶ What is the fix?




Important Rule!

 - ▶ Exactly one register makes the synchronizing decision





More Asynchronous inputs

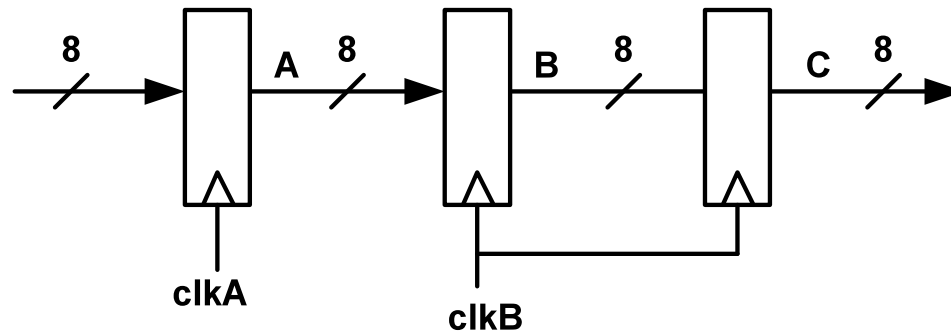- ▶ Can we input asynchronous data values with several bits?



More Asynchronous inputs

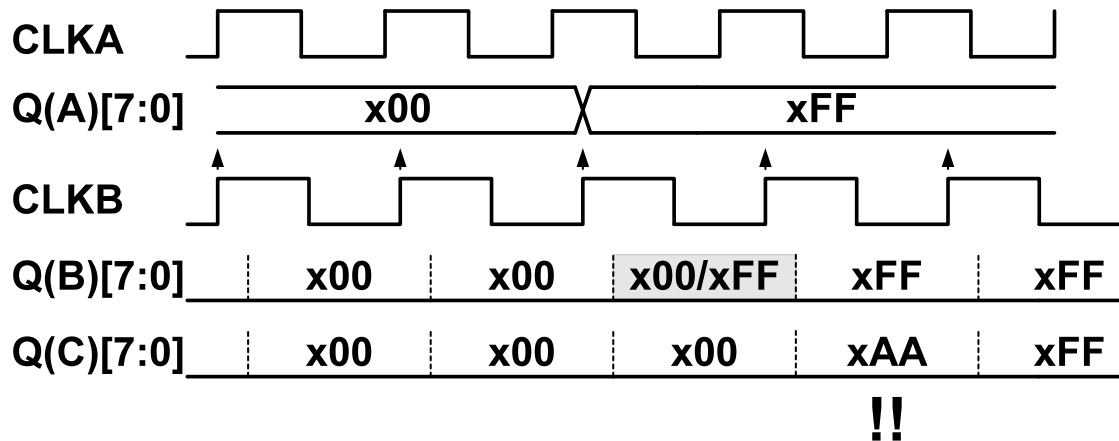 - ▶ How can we input asynchronous data values with several bits?




What Went Wrong?

- ▶ Each bit has a different delay
 - ▶ Wire lengths differ
 - ▶ Gate thresholds differ
 - ▶ Driver speeds are different
 - ▶ Register delays are different
 - ▶ Rise vs. Fall times
 - ▶ Clock skews to register bits
- ▶ Bottom line – “data skew” is inevitable
 - ▶ aka Bus Skew
 - ▶ Longer wires => More skew
- ▶ What is the solution??

Sending Multiple Data Bits

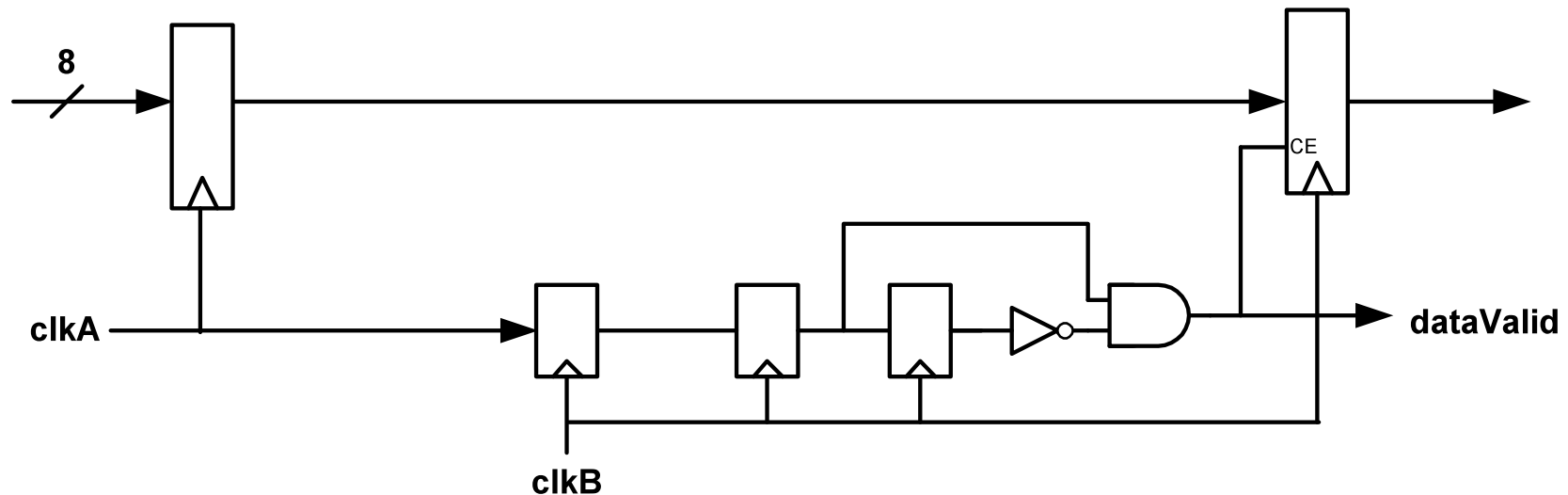- ▶ Must send a “clock” with the data – Source-Synchronous
 - ▶ Waits until data is stable
 - ▶ “Sample window”
 - ▶ De-skewing delay
- ▶ **$f(\text{clkB}) > 2 f(\text{clkA})$**




Crossing Clock Domain Boundaries is Tricky


- ▶ **Direct sampling of multiple asynchronous bits is impossible**
 - ▶ We can reliably sample only a single bit
- ▶ **But even worse: Synchronization Failure [Metastability]**
 - ▶ Non-zero probability that our system will fail
 - ▶ And there is nothing we can do about
 - ▶ Although we can reduce the probability to an extremely low value

Synchronization failure

 - ▶ Occurs when FF input changes close to clock edge
 - ▶ the FF may enter a metastable state – neither a logic 0 nor 1 –
 - ▶ it may stay in this state an indefinite amount of time
 - ▶ this is not likely in practice but has some probability



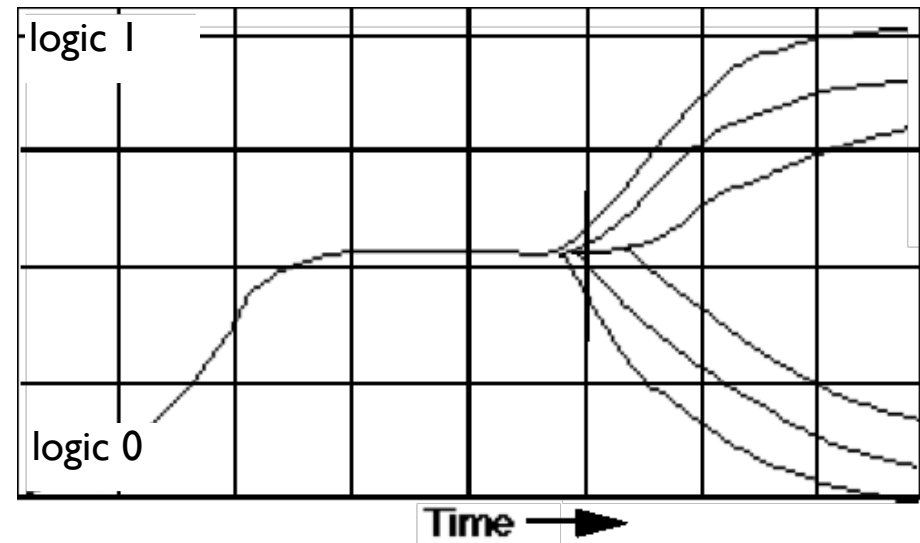
small, but non-zero probability
that the FF output will get stuck
in an in-between state



oscilloscope traces demonstrating
synchronizer failure and eventual
decay to steady state

Guarding against synchronization failure

 - ▶ Key idea – give the register as long as possible to make up its mind
 - ▶ Probability of failure cannot be reduced to 0, but low enough that we don't care
- ▶ Cascade two registers
- ▶ Use very fast registers
- ▶ Slow down the clock
 - ▶ Slows communication rate



Calculating probability of failure

- ▶ For a single synchronizer

$$\text{Mean-Time Between Failure (MTBF)} = \exp (t_r / \tau) / (T_0 \times f_c \times f_a)$$

where a failure occurs if metastability persists beyond time t_r

- ▶ t_r is the resolution time – slack time in the clock period for settling
 - ▶ $T_{\text{clk}} - (t_{\text{pd}} + T_{\text{CL}} + t_{\text{setup}})$
- ▶ f_c is the frequency of the FF clock
- ▶ f_a is the frequency of asynchronous events on the input of the FF
- ▶ T_0 and τ are constants that depend on the FF's electrical characteristics (e.g., gain or steepness of curve)
- ▶ Must add probabilities from all synchronizers in system
$$1/\text{MTBF}_{\text{system}} = \sum 1/\text{MTBF}_{\text{synch}}$$

Altera Stratix-3 Example Data

