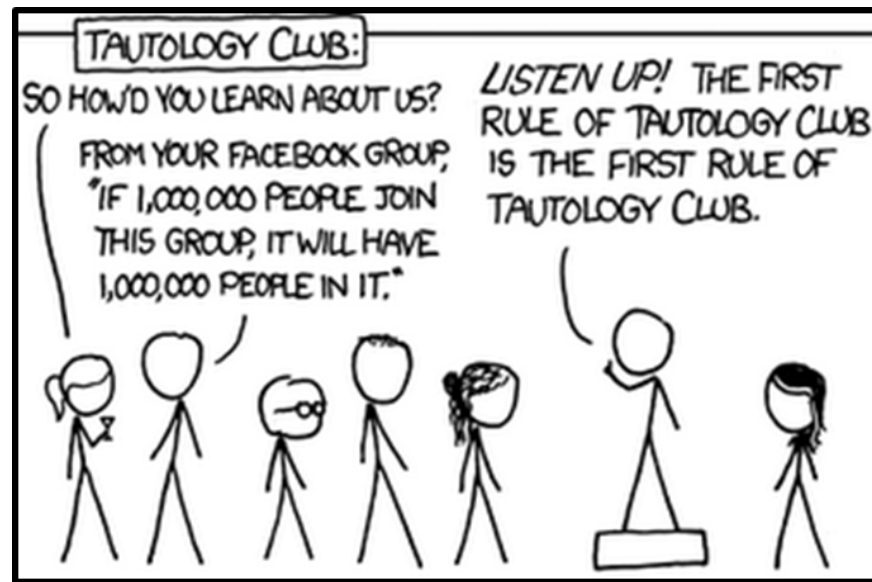


# CSE 311: Foundations of Computing

---

## Lecture 4: Boolean Algebra, Circuits, Canonical Forms



# Last Time: Proofs of Equivalence

---

## To show $A$ is equivalent to $B$

- Apply a series of logical equivalences to sub-expressions to convert  $A$  to  $B$

## To show $A$ is a tautology

- Apply a series of logical equivalences to sub-expressions to convert  $A$  to  $T$

# Prove this is a Tautology: Option 1

$$(p \wedge r) \rightarrow (r \vee p)$$

Use a series of equivalences like so:

$$\begin{aligned} (p \wedge r) \rightarrow (r \vee p) &\equiv \\ &\equiv \\ &\equiv \\ &\equiv \\ &\equiv \\ &\equiv \\ &\equiv \\ &\equiv \\ &\equiv \\ &\equiv \mathbf{T} \end{aligned}$$

## Identity

- $p \wedge \mathbf{T} \equiv p$
- $p \vee \mathbf{F} \equiv p$

## Domination

- $p \vee \mathbf{T} \equiv \mathbf{T}$
- $p \wedge \mathbf{F} \equiv \mathbf{F}$

## Idempotent

- $p \vee p \equiv p$
- $p \wedge p \equiv p$

## Commutative

- $p \vee q \equiv q \vee p$
- $p \wedge q \equiv q \wedge p$

## Associative

- $(p \vee q) \vee r \equiv p \vee (q \vee r)$
- $(p \wedge q) \wedge r \equiv p \wedge (q \wedge r)$

## Distributive

- $p \wedge (q \vee r) \equiv (p \wedge q) \vee (p \wedge r)$
- $p \vee (q \wedge r) \equiv (p \vee q) \wedge (p \vee r)$

## Absorption

- $p \vee (p \wedge q) \equiv p$
- $p \wedge (p \vee q) \equiv p$

## Negation

- $p \vee \neg p \equiv \mathbf{T}$
- $p \wedge \neg p \equiv \mathbf{F}$

# Prove this is a Tautology: Option 1

$$(p \wedge r) \rightarrow (r \vee p)$$

Use a series of equivalences like so:

$$\begin{aligned}(p \wedge r) \rightarrow (r \vee p) &\equiv \neg(p \wedge r) \vee (r \vee p) \\ &\equiv (\neg p \vee \neg r) \vee (r \vee p) \\ &\equiv \neg p \vee (\neg r \vee (r \vee p)) \\ &\equiv \neg p \vee ((\neg r \vee r) \vee p) \\ &\equiv \neg p \vee (p \vee (\neg r \vee r)) \\ &\equiv (\neg p \vee p) \vee (\neg r \vee r) \\ &\equiv (p \vee \neg p) \vee (r \vee \neg r) \\ &\equiv \mathbf{T} \vee \mathbf{T} \\ &\equiv \mathbf{T}\end{aligned}$$

## Associative

- $(p \vee q) \vee r \equiv p \vee (q \vee r)$
- $(p \wedge q) \wedge r \equiv p \wedge (q \wedge r)$

## Distributive

- $p \wedge (q \vee r) \equiv (p \wedge q) \vee (p \wedge r)$
- $p \vee (q \wedge r) \equiv (p \vee q) \wedge (p \vee r)$

## Absorption

- $p \vee (p \wedge q) \equiv p$
- $p \wedge (p \vee q) \equiv p$

## Negation

- $p \vee \neg p \equiv \mathbf{T}$
- $p \wedge \neg p \equiv \mathbf{F}$

Law of Implication

De Morgan

Associative

Associative

Commutative

Associative

Commutative (twice)

Negation (twice)

Domination/Identity

## Identity

- $p \wedge \mathbf{T} \equiv p$
- $p \vee \mathbf{F} \equiv p$

## Domination

- $p \vee \mathbf{T} \equiv \mathbf{T}$
- $p \wedge \mathbf{F} \equiv \mathbf{F}$

## Idempotent

- $p \vee p \equiv p$
- $p \wedge p \equiv p$

## Commutative

- $p \vee q \equiv q \vee p$
- $p \wedge q \equiv q \wedge p$

## Prove this is a Tautology: Option 2

---

$$(p \wedge r) \rightarrow (r \vee p)$$

Make a Truth Table and show:

$$(p \wedge r) \rightarrow (r \vee p) \equiv \mathbf{T}$$

$p$	$r$	$p \wedge r$	$r \vee p$	$(p \wedge r) \rightarrow (r \vee p)$
T	T	T	T	T
T	F	F	T	T
F	T	F	T	T
F	F	F	F	T

# Boolean Logic

---

## Combinational Logic

– output = F(input)

## Sequential Logic


- $\text{output}_t = F(\text{output}_{t-1}, \text{input}_t)$ 
  - output dependent on history
  - concept of a time step (clock, t)

# Boolean Logic

---

## Combinational Logic

– output =  $F(\text{input})$

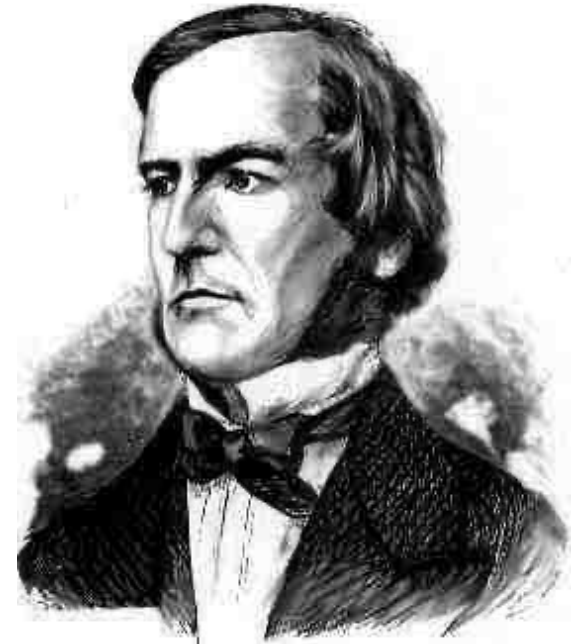

## Boolean Algebra: another notation for logic consisting of...

- a set of elements  $B = \{0, 1\}$
- binary operations  $\{ + , \cdot \}$  (OR, AND)
- and a unary operation  $\{ ' \}$  (NOT)

# Boolean Algebra

---

- Usual notation used in circuit design
- Boolean algebra
  - a set of elements  $B$  containing  $\{0, 1\}$
  - binary operations  $\{ + , \cdot \}$
  - and a unary operation  $\{ ' \}$
  - such that the following axioms hold:



For any  $a, b, c$  in  $B$ :

1. closure:

$$a + b \text{ is in } B$$

$$a \cdot b \text{ is in } B$$

2. commutativity:

$$a + b = b + a$$

$$a \cdot b = b \cdot a$$

3. associativity:

$$a + (b + c) = (a + b) + c$$

$$a \cdot (b \cdot c) = (a \cdot b) \cdot c$$

4. distributivity:

$$a + (b \cdot c) = (a + b) \cdot (a + c)$$

$$a \cdot (b + c) = (a \cdot b) + (a \cdot c)$$

5. identity:

$$a + 0 = a$$

$$a \cdot 1 = a$$

6. complementarity:

$$a + a' = 1$$

$$a \cdot a' = 0$$

7. null:

$$a + 1 = 1$$

$$a \cdot 0 = 0$$

8. idempotency:

$$a + a = a$$

$$a \cdot a = a$$

9. involution:

$$(a')' = a$$



# A Combinational Logic Example

---

## Sessions of Class:

We would like to compute the number of lectures or quiz sections remaining *at the start* of a given day of the week.

- **Inputs:** Day of the Week, Lecture/Section flag
- **Output:** Number of sessions left

Examples: Input: (Wednesday, Lecture) Output: **2**

Input: (Monday, Section) Output: **1**

# Implementation in Software

---


```
public int classesLeftInMorning(int weekday, boolean isLecture) {
    switch (weekday) {
        case SUNDAY:
        case MONDAY:
            return isLecture ? 3 : 1;
        case TUESDAY:
        case WEDNESDAY:
            return isLecture ? 2 : 1;
        case THURSDAY:
            return isLecture ? 1 : 1;
        case FRIDAY:
            return isLecture ? 1 : 0;
        case SATURDAY:
            return isLecture ? 0 : 0;
    }
}
```

# Implementation with Combinational Logic

---
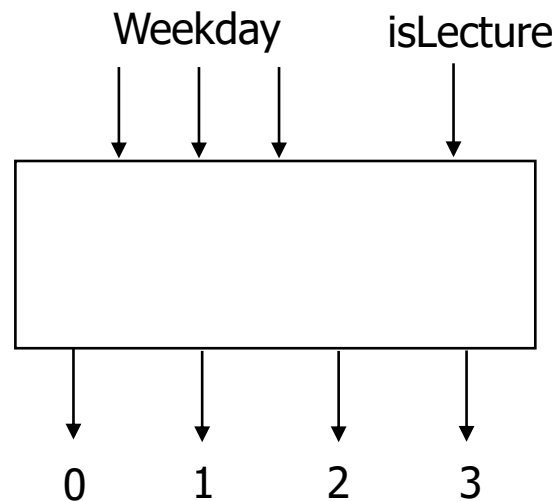
## Encoding:

- How many bits for each input/output?
- Binary number for weekday
- One bit for each possible output



# Defining Our Inputs!

---

## Weekday Input:

- Binary number for weekday
- Sunday = 0, Monday = 1, ...
- We care about these in binary:

Weekday	Number	Binary
Sunday	0	(000) <sub>2</sub>
Monday	1	(001) <sub>2</sub>
Tuesday	2	(010) <sub>2</sub>
Wednesday	3	(011) <sub>2</sub>
Thursday	4	(100) <sub>2</sub>
Friday	5	(101) <sub>2</sub>
Saturday	6	(110) <sub>2</sub>

# Converting to a Truth Table!

---

```
case SUNDAY or MONDAY:
    return isLecture ? 3 : 1;
case TUESDAY or WEDNESDAY:
    return isLecture ? 2 : 1;
case THURSDAY:
    return isLecture ? 1 : 1;
case FRIDAY:
    return isLecture ? 1 : 0;
case SATURDAY:
    return isLecture ? 0 : 0;
```

Weekday	isLecture	c <sub>0</sub>	c <sub>1</sub>	c <sub>2</sub>	c <sub>3</sub>
SUN	000	0			
SUN	000	1			
MON	001	0			
MON	001	1			
TUE	010	0			
TUE	010	1			
WED	011	0			
WED	011	1			
THU	100	-			
FRI	101	0			
FRI	101	1			
SAT	110	-			
-	111	-			

# Converting to a Truth Table!

---

```

case SUNDAY or MONDAY:
    return isLecture ? 3 : 1;
case TUESDAY or WEDNESDAY:
    return isLecture ? 2 : 1;
case THURSDAY:
    return isLecture ? 1 : 1;
case FRIDAY:
    return isLecture ? 1 : 0;
case SATURDAY:
    return isLecture ? 0 : 0;

```

Weekday	isLecture	c <sub>0</sub>	c <sub>1</sub>	c <sub>2</sub>	c <sub>3</sub>
SUN	000	0	1	0	0
SUN	000	1	0	0	1
MON	001	0	1	0	0
MON	001	1	0	0	1
TUE	010	0	1	0	0
TUE	010	1	0	1	0
WED	011	0	1	0	0
WED	011	1	0	1	0
THU	100	-	1	0	0
FRI	101	0	1	0	0
FRI	101	1	0	1	0
SAT	110	-	1	0	0
-	111	-	1	0	0

# Truth Table to Logic (Part 1)

	$d_2d_1d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

Let's begin by finding an expression for  $c_3$ . To do this, we look at the rows where  $c_3 = 1$  (true).

# Truth Table to Logic (Part 1)

	$d_2d_1d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

DAY == SUN && L == 1

DAY == MON && L == 1



# Truth Table to Logic (Part 1)

	$d_2d_1d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

$d_2d_1d_0 == 000 \ \&\& \ L == 1$

$d_2d_1d_0 == 001 \ \&\& \ L == 1$

Substituting DAY for the binary representation.

# Truth Table to Logic (Part 1)

	$d_2d_1d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

$d_2 == 0 \ \&\& \ d_1 == 0 \ \&\& \ d_0 == 0 \ \&\& \ L == 1$

$d_2 == 0 \ \&\& \ d_1 == 0 \ \&\& \ d_0 == 1 \ \&\& \ L == 1$

Splitting up the bits of the day;  
so, we can write a formula.

# Truth Table to Logic (Part 1)

	$d_2d_1d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0


$d_2' \cdot d_1' \cdot d_0' \cdot L$


$d_2' \cdot d_1' \cdot d_0 \cdot L$

Replacing with  
Boolean Algebra...

# Truth Table to Logic (Part 1)

	$d_2d_1d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0


 $d_2' \cdot d_1' \cdot d_0' \cdot L$


 $d_2' \cdot d_1' \cdot d_0 \cdot L$

How do we combine them?

# Truth Table to Logic (Part 1)

	$d_2d_1d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

$d_2' \cdot d_1' \cdot d_0' \cdot L$

$d_2' \cdot d_1' \cdot d_0 \cdot L$

Either situation causes  $c_3$  to be true. So, we "or" them.

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

# Truth Table to Logic (Part 2)

	$d_2d_1d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

Now, we do  $c_2$ .



# Truth Table to Logic (Part 3)

	$d_2d_1d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$	
SUN	000	0	0	1	0	0	→
SUN	000	1	0	0	0	1	
MON	001	0	0	1	0	0	→
MON	001	1	0	0	0	1	
TUE	010	0	0	1	0	0	→
TUE	010	1	0	0	1	0	
WED	011	0	0	1	0	0	→
WED	011	1	0	0	1	0	
THU	100	-	0	1	0	0	→
FRI	101	0	1	0	0	0	
FRI	101	1	0	1	0	0	→
SAT	110	-	1	0	0	0	
-	111	-	1	0	0	0	

Now, we do  $c_1$ :

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

# Truth Table to Logic (Part 3)

	$d_2d_1d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$	
SUN	000	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0' \cdot L'$
SUN	000	1	0	0	0	1	
MON	001	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0 \cdot L'$
MON	001	1	0	0	0	1	
TUE	010	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0' \cdot L'$
TUE	010	1	0	0	1	0	
WED	011	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0 \cdot L'$
WED	011	1	0	0	1	0	
THU	100	-	0	1	0	0	???
FRI	101	0	1	0	0	0	
FRI	101	1	0	1	0	0	$d_2 \cdot d_1' \cdot d_0 \cdot L$
SAT	110	-	1	0	0	0	
-	111	-	1	0	0	0	

Now, we do  $c_1$ :

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$



# Truth Table to Logic (Part 3)

	$d_2d_1d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$	
SUN	000	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0' \cdot L'$
SUN	000	1	0	0	0	1	
MON	001	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0 \cdot L'$
MON	001	1	0	0	0	1	
TUE	010	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0' \cdot L'$
TUE	010	1	0	0	1	0	
WED	011	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0 \cdot L'$
WED	011	1	0	0	1	0	
THU	100	-	0	1	0	0	$d_2 \cdot d_1' \cdot d_0'$
FRI	101	0	1	0	0	0	
FRI	101	1	0	1	0	0	$d_2 \cdot d_1' \cdot d_0 \cdot L$
SAT	110	-	1	0	0	0	
-	111	-	1	0	0	0	

Now, we do  $c_1$ :

No matter what L is, we always say it's 1. So, we don't need L in the expression.

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

# Truth Table to Logic (Part 3)

	$d_2d_1d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$	
SUN	000	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0' \cdot L'$
SUN	000	1	0	0	0	1	
MON	001	0	0	1	0	0	$d_2' \cdot d_1' \cdot d_0 \cdot L'$
MON	001	1	0	0	0	1	
TUE	010	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0' \cdot L'$
TUE	010	1	0	0	1	0	
WED	011	0	0	1	0	0	$d_2' \cdot d_1 \cdot d_0 \cdot L'$
WED	011	1	0	0	1	0	
THU	100	-	0	1	0	0	$d_2 \cdot d_1' \cdot d_0'$
FRI	101	0	1	0	0	0	
FRI	101	1	0	1	0	0	$d_2 \cdot d_1' \cdot d_0 \cdot L$
SAT	110	-	1	0	0	0	
-	111	-	1	0	0	0	

Now, we do  $c_1$ :

No matter what L is, we always say it's 1. So, we don't need L in the expression.

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

$$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L + d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L + d_2 \cdot d_1' \cdot d_0' + d_2 \cdot d_1' \cdot d_0 \cdot L$$

# Truth Table to Logic (Part 4)

	$d_2d_1d_0$	L	$c_0$	$c_1$	$c_2$	$c_3$
SUN	000	0	0	1	0	0
SUN	000	1	0	0	0	1
MON	001	0	0	1	0	0
MON	001	1	0	0	0	1
TUE	010	0	0	1	0	0
TUE	010	1	0	0	1	0
WED	011	0	0	1	0	0
WED	011	1	0	0	1	0
THU	100	-	0	1	0	0
FRI	101	0	1	0	0	0
FRI	101	1	0	1	0	0
SAT	110	-	1	0	0	0
-	111	-	1	0	0	0

$$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L' + d_2' \cdot d_1' \cdot d_0 \cdot L' + d_2' \cdot d_1 \cdot d_0' \cdot L' + d_2' \cdot d_1 \cdot d_0 \cdot L' + d_2 \cdot d_1' \cdot d_0' + d_2 \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$

Finally, we do  $c_0$ :

$$d_2 \cdot d_1' \cdot d_0 \cdot L'$$

$$d_2 \cdot d_1 \cdot d_0'$$

$$d_2 \cdot d_1 \cdot d_0$$

# Truth Table to Logic (Part 4)

---


$$c_0 = d_2 \cdot d_1' \cdot d_0 \cdot L' + d_2 \cdot d_1 \cdot d_0' + d_2 \cdot d_1 \cdot d_0$$

$$c_1 = d_2' \cdot d_1' \cdot d_0' \cdot L' + d_2' \cdot d_1' \cdot d_0 \cdot L' + d_2' \cdot d_1 \cdot d_0' \cdot L' + d_2' \cdot d_1 \cdot d_0 \cdot L' + d_2 \cdot d_1' \cdot d_0' + d_2 \cdot d_1' \cdot d_0 \cdot L$$

$$c_2 = d_2' \cdot d_1 \cdot d_0' \cdot L + d_2' \cdot d_1 \cdot d_0 \cdot L$$

$$c_3 = d_2' \cdot d_1' \cdot d_0' \cdot L + d_2' \cdot d_1' \cdot d_0 \cdot L$$


Here's  $c_3$  as a circuit:

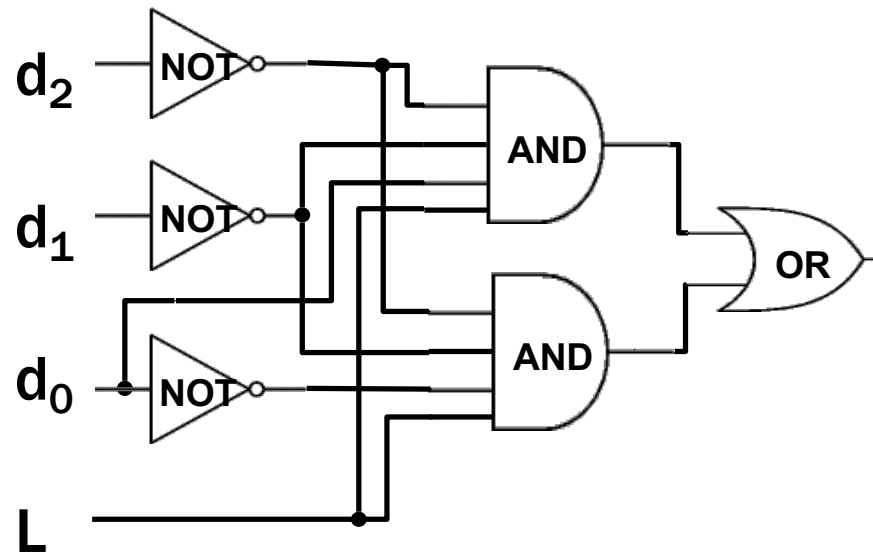
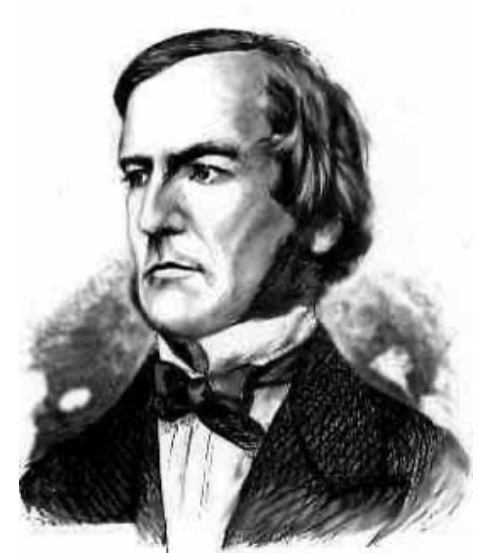
# Boolean Algebra

---

- Usual notation used in circuit design
- Boolean algebra
  - a set of elements  $B$  containing  $\{0, 1\}$
  - binary operations  $\{ + , \cdot \}$
  - and a unary operation  $\{ ' \}$
  - such that the following axioms hold:



For any  $a, b, c$  in  $B$ :

1. closure:

$$a + b \text{ is in } B$$

$$a \cdot b \text{ is in } B$$

2. commutativity:

$$a + b = b + a$$

$$a \cdot b = b \cdot a$$

3. associativity:

$$a + (b + c) = (a + b) + c$$

$$a \cdot (b \cdot c) = (a \cdot b) \cdot c$$

4. distributivity:

$$a + (b \cdot c) = (a + b) \cdot (a + c)$$

$$a \cdot (b + c) = (a \cdot b) + (a \cdot c)$$

5. identity:

$$a + 0 = a$$

$$a \cdot 1 = a$$

6. complementarity:

$$a + a' = 1$$

$$a \cdot a' = 0$$

7. null:

$$a + 1 = 1$$

$$a \cdot 0 = 0$$

8. idempotency:

$$a + a = a$$

$$a \cdot a = a$$

9. involution:

$$(a')' = a$$

# Simplification using Boolean Algebra

---

## uniting:

$$10. a \cdot b + a \cdot b' = a$$

$$10D. (a + b) \cdot (a + b') = a$$

## absorption:

$$11. a + a \cdot b = a$$

$$11D. a \cdot (a + b) = a$$

$$12. (a + b') \cdot b = a \cdot b$$

$$12D. (a \cdot b') + b = a + b$$

## factoring:

$$13. (a + b) \cdot (a' + c) = \\ a \cdot c + a' \cdot b$$

$$13D. a \cdot b + a' \cdot c = \\ (a + c) \cdot (a' + b)$$

## consensus:

$$14. (a \cdot b) + (b \cdot c) + (a' \cdot c) = \\ a \cdot b + a' \cdot c$$

$$14D. (a + b) \cdot (b + c) \cdot (a' + c) = \\ (a + b) \cdot (a' + c)$$

## de Morgan's:

$$15. (a + b + \dots)' = a' \cdot b' \cdot \dots$$

$$15D. (a \cdot b \cdot \dots)' = a' + b' + \dots$$

# Proving Theorems

---

- 2. commutativity:
- 3. associativity:
- 4. distributivity:
- 5. identity:
- 6. complementarity:
- 7. null:
- 8. idempotency:
- 9. involution:

$$\begin{aligned}a + b &= b + a \\ a + (b + c) &= (a + b) + c \\ a + (b \cdot c) &= (a + b) \cdot (a + c) \\ a + 0 &= a \\ a + a' &= 1 \\ a + 1 &= 1 \\ a + a &= a \\ (a')' &= a\end{aligned}$$

$$\begin{aligned}a \cdot b &= b \cdot a \\ a \cdot (b \cdot c) &= (a \cdot b) \cdot c \\ a \cdot (b + c) &= (a \cdot b) + (a \cdot c) \\ a \cdot 1 &= a \\ a \cdot a' &= 0 \\ a \cdot 0 &= 0 \\ a \cdot a &= a\end{aligned}$$

## Using the laws of Boolean Algebra:

prove the **Uniting theorem**:

$$X \cdot Y + X \cdot Y' = X$$

$$X \cdot Y + X \cdot Y' =$$

prove the **Absorption theorem**:

$$X + X \cdot Y = X$$

$$X + X \cdot Y =$$

# Proving Theorems

---

2. commutativity:
3. associativity:
4. distributivity:
5. identity:
6. complementarity:
7. null:
8. idempotency:
9. involution:

$$\begin{aligned}a + b &= b + a \\ a + (b + c) &= (a + b) + c \\ a + (b \cdot c) &= (a + b) \cdot (a + c) \\ a + 0 &= a \\ a + a' &= 1 \\ a + 1 &= 1 \\ a + a &= a \\ (a')' &= a\end{aligned}$$

$$\begin{aligned}a \cdot b &= b \cdot a \\ a \cdot (b \cdot c) &= (a \cdot b) \cdot c \\ a \cdot (b + c) &= (a \cdot b) + (a \cdot c) \\ a \cdot 1 &= a \\ a \cdot a' &= 0 \\ a \cdot 0 &= 0 \\ a \cdot a &= a\end{aligned}$$

## Using the laws of Boolean Algebra:

**prove the Uniting theorem:**

$$X \cdot Y + X \cdot Y' = X$$

distributivity  
complementarity  
identity

$$\begin{aligned}X \cdot Y + X \cdot Y' &= X \cdot (Y + Y') \\ &= X \cdot 1 \\ &= X\end{aligned}$$

**prove the Absorption theorem:**

$$X + X \cdot Y = X$$

identity  
distributivity  
commutativity  
null  
identity

$$\begin{aligned}X + X \cdot Y &= X \cdot 1 + X \cdot Y \\ &= X \cdot (1 + Y) \\ &= X \cdot (Y + 1) \\ &= X \cdot 1 \\ &= X\end{aligned}$$



# Proving Theorems

---

## Using truth table:

For example, de Morgan's Law:

$(X + Y)' = X' \cdot Y'$   
NOR is equivalent to AND  
with inputs complemented

X	Y	X'	Y'	$(X + Y)'$	$X' \cdot Y'$
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

$(X \cdot Y)' = X' + Y'$   
NAND is equivalent to OR  
with inputs complemented

X	Y	X'	Y'	$(X \cdot Y)'$	$X' + Y'$
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0

# Simplifying using Boolean Algebra

---

$$\begin{aligned}c3 &= d2' \cdot d1' \cdot d0' \cdot L + d2' \cdot d1' \cdot d0 \cdot L \\ &= d2' \cdot d1' \cdot (d0' + d0) \cdot L \\ &= d2' \cdot d1' \cdot 1 \cdot L \\ &= d2' \cdot d1' \cdot L\end{aligned}$$

