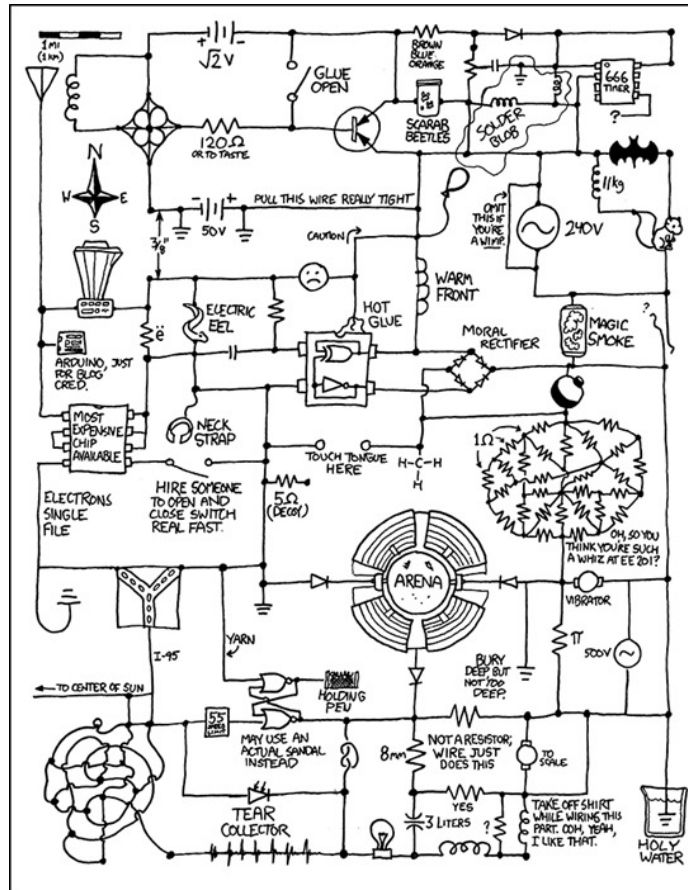


CSE 311: Foundations of Computing

Lecture 5: DNF, CNF and Predicate Logic



Administrivia

HW1 due tonight

HW2 posted tomorrow

- **some tools available for testing equivalence chains**
 - one is <http://homes.cs.washington.edu/~kevinz/equiv-test/>
 - another mentioned in the HW
- **both are optional**
 - also “beta” software

Last Time: Building Circuits

“Turn the Crank” Process:

1. write down a table showing desired 0/1 outputs
2. construct a Boolean algebra expression
 - term for each 1 in the column
 - sum (or) them to get all 1s
3. simplify the expression using equivalences
4. translate Boolean algebra to a circuit

(Since it's “turn the crank”, software can do this for you.)

Warm-up Exercise

- Create a Boolean Algebra expression for “*c*” below in terms of the variables *a* and *b*

<i>a</i>	<i>b</i>	<i>c</i>
1	1	0
1	0	1
0	1	1
0	0	0

$$c = ab' + a'b$$

Warm-up Exercise

- Create a Boolean Algebra expression for “*c*” below in terms of the variables *a* and *b*

$$c = ab' + a'b$$

- Draw this as a circuit (using AND, OR, NOT)

1-bit Binary Adder

A	$0 + 0 = 0$ (with $C_{OUT} = 0$)
<u>+ B</u>	$0 + 1 = 1$ (with $C_{OUT} = 0$)
S	$1 + 0 = 1$ (with $C_{OUT} = 0$)
(C_{OUT})	$1 + 1 = 0$ (with $C_{OUT} = 1$)

1-bit Binary Adder

A	$0 + 0 = 0$ (with $C_{OUT} = 0$)
<u>+ B</u>	$0 + 1 = 1$ (with $C_{OUT} = 0$)
S	$1 + 0 = 1$ (with $C_{OUT} = 0$)
(C_{OUT})	$1 + 1 = 0$ (with $C_{OUT} = 1$)

Idea: chain these together to add larger numbers


Recall from
elementary school:

$$\begin{array}{r} 248 \\ + 375 \\ \hline \end{array}$$

1-bit Binary Adder

A	$0 + 0 = 0$ (with $C_{OUT} = 0$)
+ B	$0 + 1 = 1$ (with $C_{OUT} = 0$)
S	$1 + 0 = 1$ (with $C_{OUT} = 0$)
(C_{OUT})	$1 + 1 = 0$ (with $C_{OUT} = 1$)

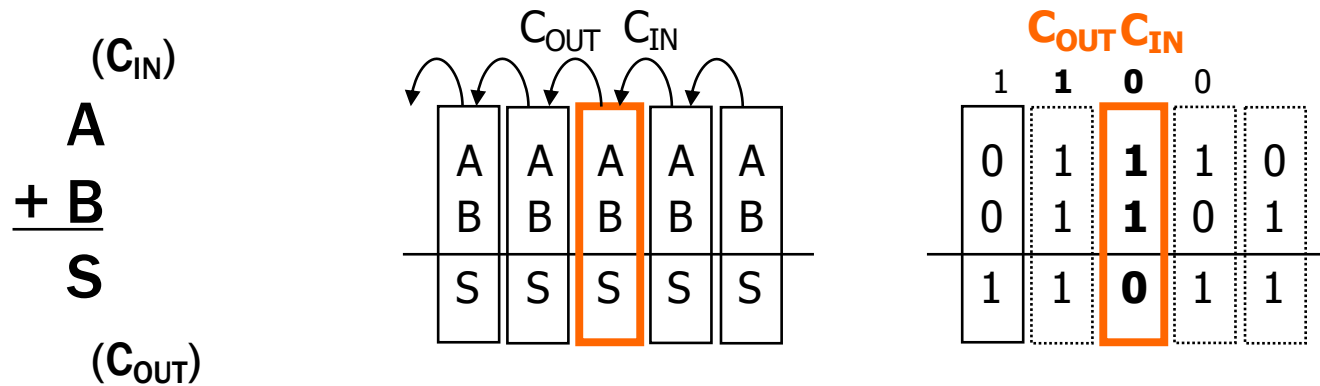
Idea: These are chained together with a carry-in



1-bit Binary Adder


- **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out

A	B	C _{IN}	C _{OUT}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

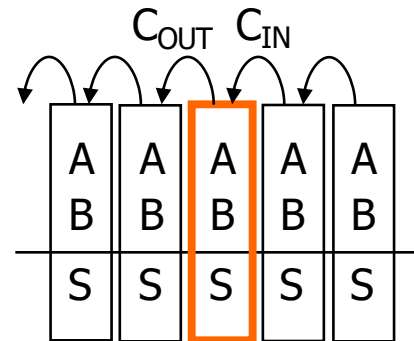


1-bit Binary Adder

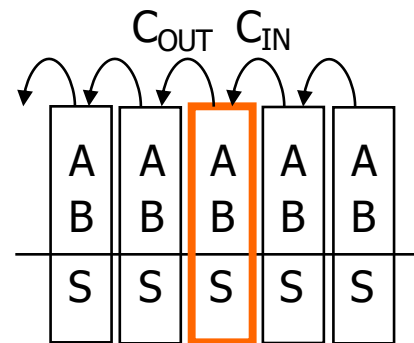- **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out



A	B	C _{IN}	C _{OUT}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


Derive an expression for S

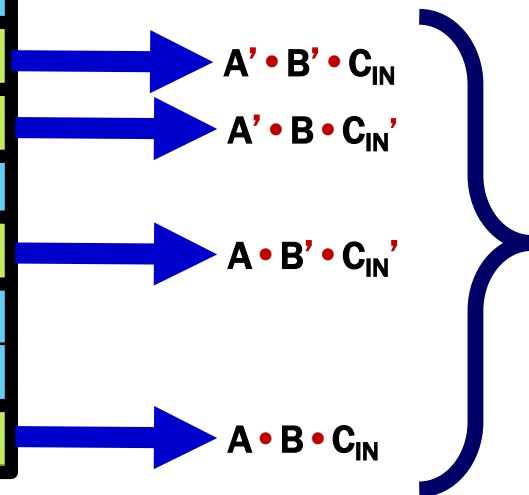

$$S = A' \cdot B' \cdot C_{IN} + A' \cdot B \cdot C_{IN}' + A \cdot B' \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$

1-bit Binary Adder

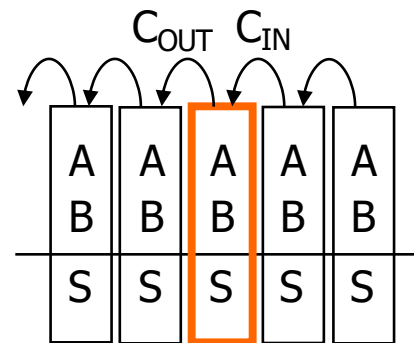- **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out



A	B	C _{IN}	C _{OUT}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


Derive an expression for C_{OUT}

$$\begin{aligned}
 & \left. \begin{aligned}
 & \rightarrow A' \cdot B \cdot C_{IN} \\
 & \rightarrow A \cdot B' \cdot C_{IN} \\
 & \rightarrow A \cdot B \cdot C_{IN}' \\
 & \rightarrow A \cdot B \cdot C_{IN}
 \end{aligned} \right\} C_{OUT} = A' \cdot B \cdot C_{IN} + A \cdot B' \cdot C_{IN} + \\
 & \quad A \cdot B \cdot C_{IN}' + A \cdot B \cdot C_{IN}
 \end{aligned}$$

$$S = A' \cdot B' \cdot C_{IN} + A' \cdot B \cdot C_{IN}' + A \cdot B' \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$

1-bit Binary Adder

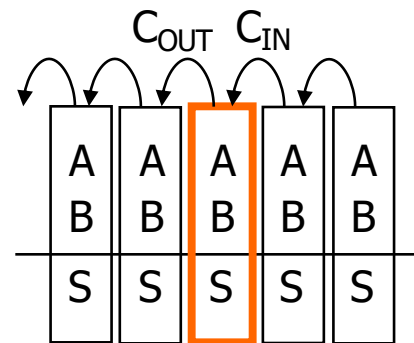- **Inputs:** A, B, Carry-in
- **Outputs:** Sum, Carry-out



A	B	C _{IN}	C _{OUT}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A' \cdot B' \cdot C_{IN} + A' \cdot B \cdot C_{IN}' + A \cdot B' \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$

$$C_{OUT} = A' \cdot B \cdot C_{IN} + A \cdot B' \cdot C_{IN} + A \cdot B \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$

Apply Theorems to Simplify Expressions

The theorems of Boolean algebra can simplify expressions

– e.g., full adder's carry-out function

$$\begin{aligned} \text{Cout} &= A' B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= A' B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} + A B \text{Cin} \\ &= A' B \text{Cin} + A B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= (A' + A) B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= (1) B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} + A B \text{Cin} \\ &= B \text{Cin} + A B' \text{Cin} + A B \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= B \text{Cin} + A (B' + B) \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= B \text{Cin} + A (1) \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= B \text{Cin} + A \text{Cin} + A B (\text{Cin}' + \text{Cin}) \\ &= B \text{Cin} + A \text{Cin} + A B (1) \\ &= B \text{Cin} + A \text{Cin} + A B \end{aligned}$$

Apply Theorems to Simplify Expressions


The theorems of Boolean algebra can simplify expressions

– e.g., full adder's carry-out function

$$\begin{aligned} \text{Cout} &= A' B C_{in} + A B' C_{in} + A B C_{in}' + A B C_{in} \\ &= A' B C_{in} + A B' C_{in} + A B C_{in}' + \boxed{A B C_{in} + A B C_{in}} \\ &= A' B C_{in} + A B C_{in} + A B' C_{in} + A B C_{in}' + A B C_{in} \\ &= (A' + A) B C_{in} + A B' C_{in} + A B C_{in}' + A B C_{in} \\ &= (1) B C_{in} + A B' C_{in} + A B C_{in}' + A B C_{in} \\ &= B C_{in} + A B' C_{in} + A B C_{in}' + \boxed{A B C_{in} + A B C_{in}} \\ &= B C_{in} + A B' C_{in} + A B C_{in} + A B C_{in}' + A B C_{in} \\ &= B C_{in} + A (B' + B) C_{in} + A B C_{in}' + A B C_{in} \\ &= B C_{in} + A (1) C_{in} + A B C_{in}' + A B C_{in} \\ &= B C_{in} + A C_{in} + A B (C_{in}' + C_{in}) \\ &= B C_{in} + A C_{in} + A B (1) \\ &= B C_{in} + A C_{in} + A B \end{aligned}$$

adding extra terms
creates new factoring
opportunities

A 2-bit Ripple-Carry Adder

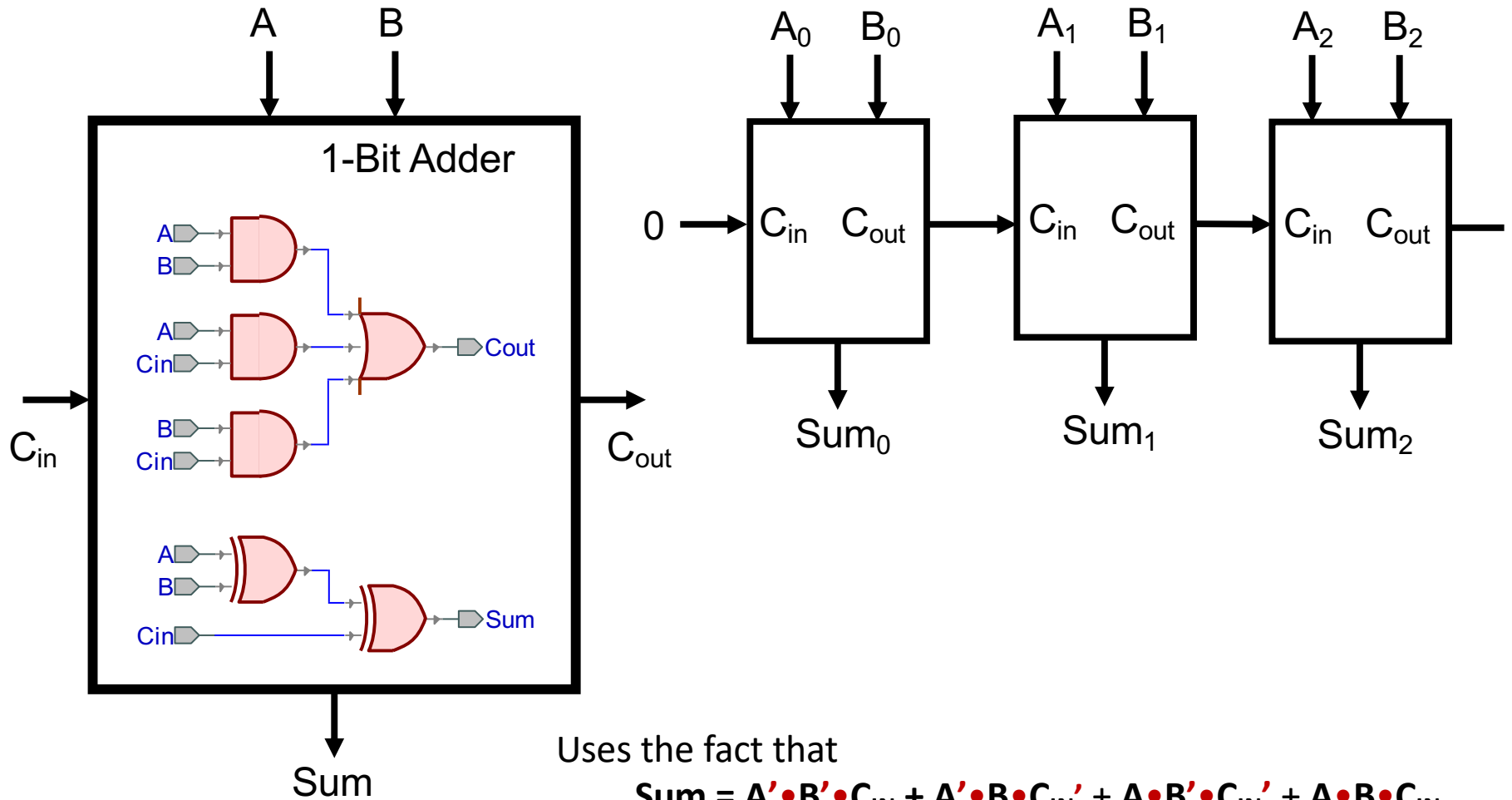

Uses the fact that

$$\text{Sum} = A' \cdot B' \cdot C_{IN} + A' \cdot B \cdot C_{IN}' + A \cdot B' \cdot C_{IN}' + A \cdot B \cdot C_{IN}$$

is equivalent to $\text{Sum} = (A \oplus B) \oplus C_{IN}$

Mapping Truth Tables to Logic Gates



Given a truth table:

1. Write the output in a table
2. Write the Boolean expression
3. Minimize the Boolean expression
4. Draw as gates
5. Map to available gates

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

③
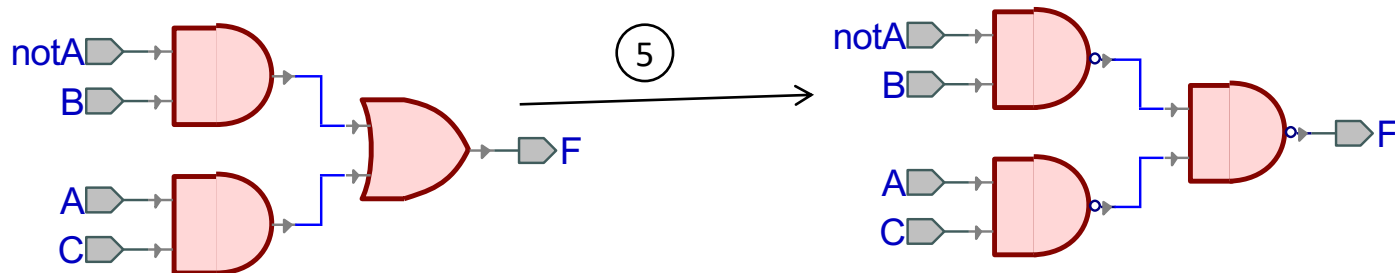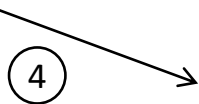
$$\begin{aligned} F &= A'BC' + A'BC + AB'C + ABC \\ &= A'B(C' + C) + AC(B' + B) \\ &= A'B + AC \end{aligned}$$



Canonical Forms

- **Truth table is the unique signature of a 0/1 function**
- **The same truth table can have many gate realizations**
 - We've seen this already
 - Depends on how good we are at Boolean simplification
- **Canonical forms**
 - Standard forms for a Boolean expression
 - We all produce the same expression


Sum-of-Products Canonical Form

- AKA **Disjunctive Normal Form (DNF)**
- AKA **Minterm Expansion**

③

Add the minterms together

$$F = A'B'C + A'BC + AB'C + ABC' + ABC$$

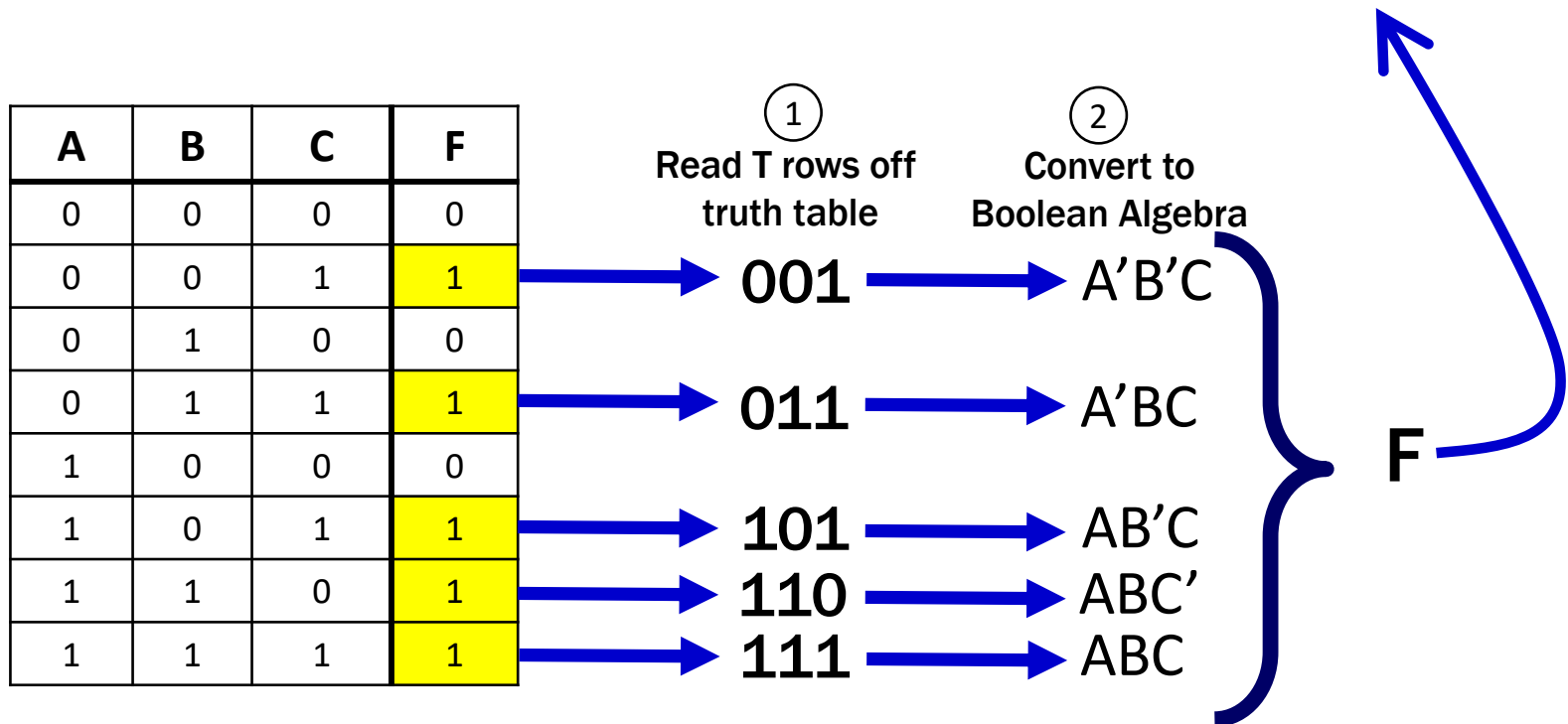

Sum-of-Products Canonical Form

Product term (or minterm)

- ANDed product of literals – input combination for which output is true
- each variable appears exactly once, true or inverted (but not both)

A	B	C	minterms
0	0	0	A'B'C'
0	0	1	A'B'C
0	1	0	A'BC'
0	1	1	A'BC
1	0	0	AB'C'
1	0	1	AB'C
1	1	0	ABC'
1	1	1	ABC

F in canonical form:


$$F(A, B, C) = A'B'C + A'BC + AB'C + ABC' + ABC$$

canonical form \neq minimal form

$$\begin{aligned} F(A, B, C) &= A'B'C + A'BC + AB'C + ABC + ABC' \\ &= (A'B' + A'B + AB' + AB)C + ABC' \\ &= ((A' + A)(B' + B))C + ABC' \\ &= C + ABC' \\ &= ABC' + C \\ &= AB + C \end{aligned}$$


Product-of-Sums Canonical Form

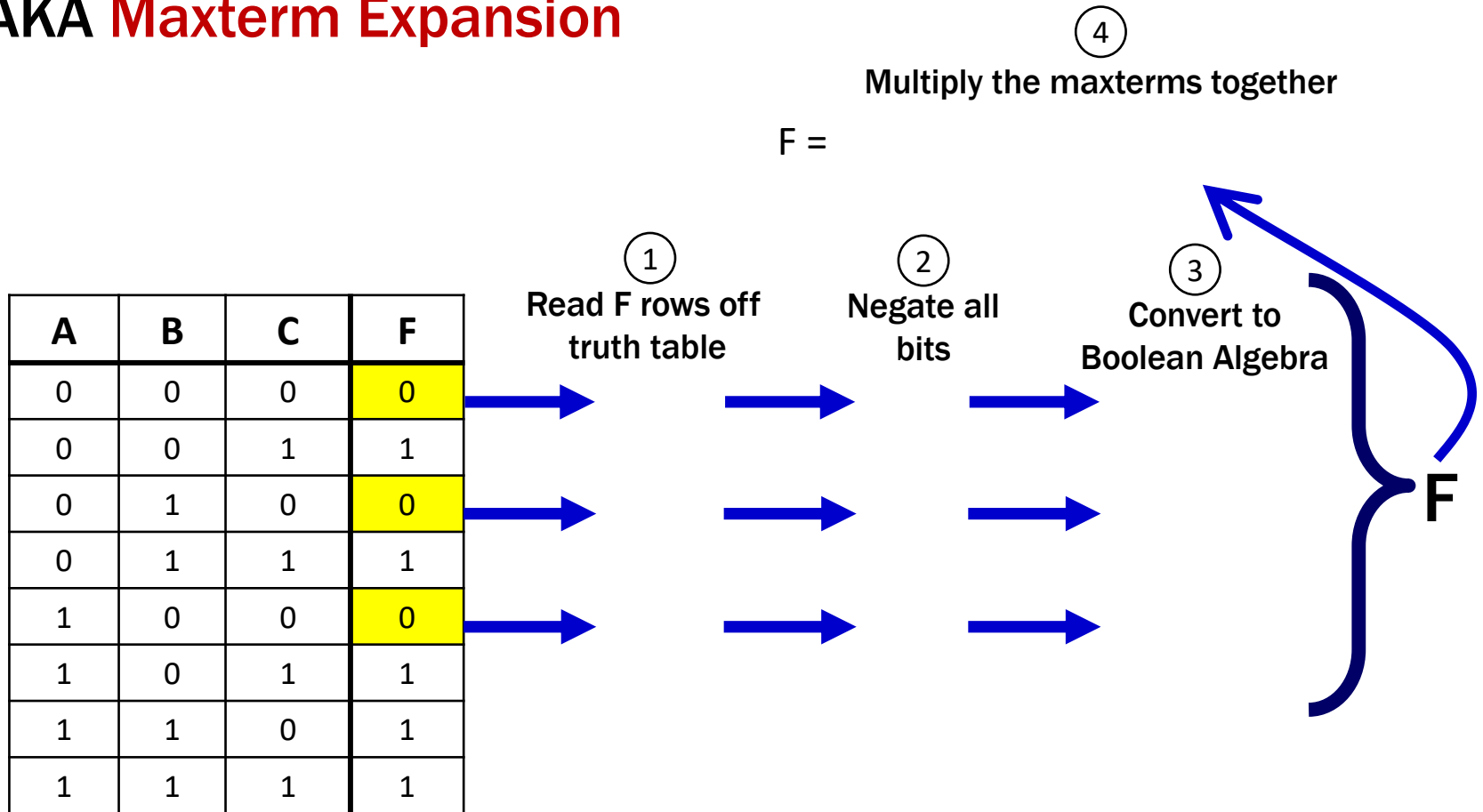- AKA **Conjunctive Normal Form (CNF)**
- AKA **Maxterm Expansion**



Product-of-Sums Canonical Form

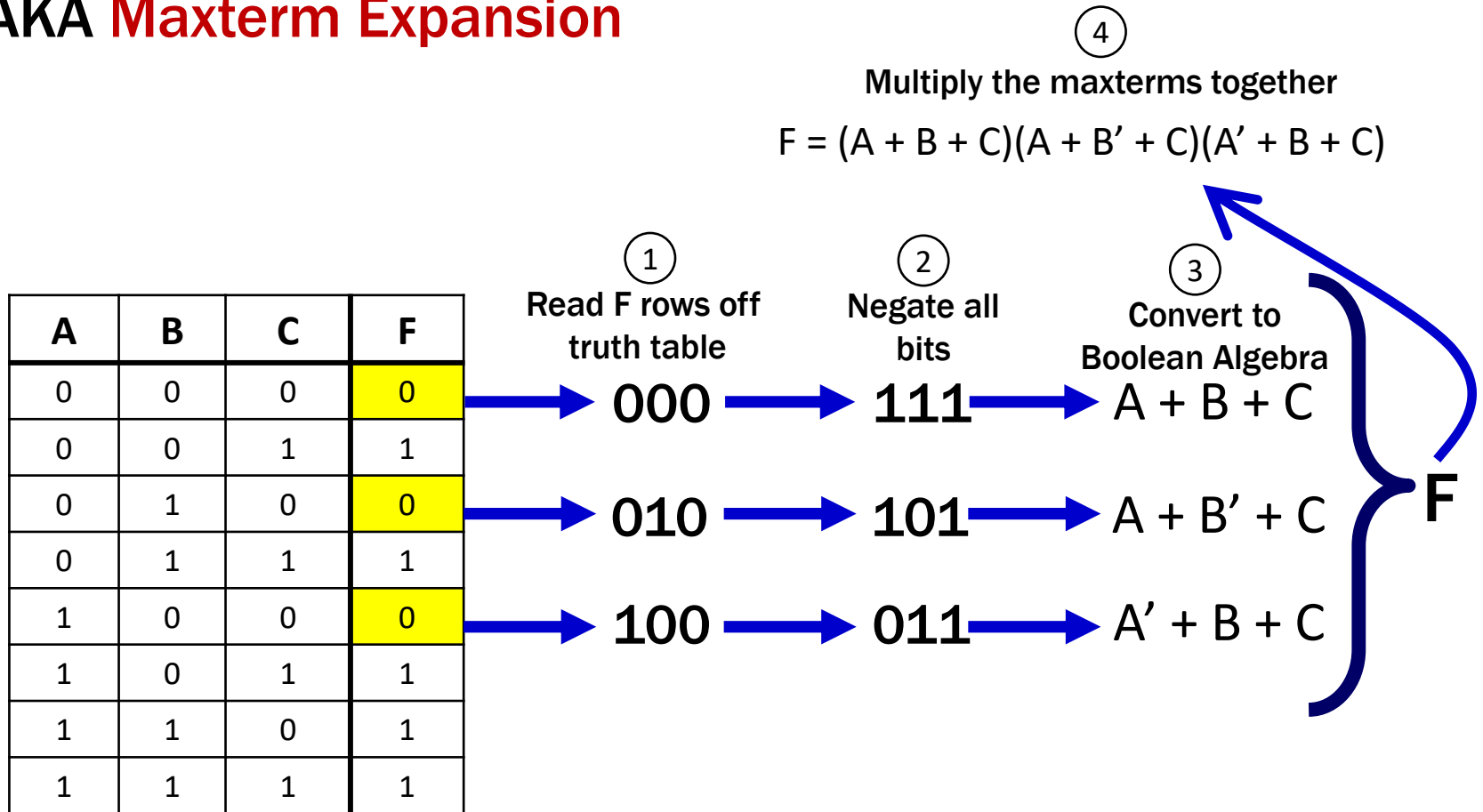- AKA **Conjunctive Normal Form (CNF)**
- AKA **Maxterm Expansion**




Product-of-Sums: Why does this procedure work?

Useful Facts:

- We know $(F')' = F$
- We know how to get a minterm expansion for F'

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

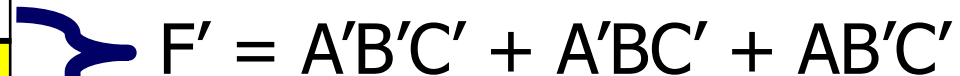
$$F' = A'B'C' + A'BC' + AB'C'$$

Product-of-Sums: Why does this procedure work?

Useful Facts:

- We know $(F')' = F$
- We know how to get a minterm expansion for F'

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


$$F' = A'B'C' + A'BC' + AB'C'$$

Taking the complement of both sides...

$$(F')' = (A'B'C' + A'BC' + AB'C')'$$

And using DeMorgan/Comp....

$$F = (A'B'C')' (A'BC')' (AB'C')'$$

$$F = (A + B + C)(A + B' + C)(A' + B + C)$$

Product-of-Sums Canonical Form

Sum term (or maxterm)

- ORed sum of literals – input combination for which output is false
- each variable appears exactly once, true or inverted (but not both)

A	B	C	maxterms
0	0	0	$A+B+C$
0	0	1	$A+B+C'$
0	1	0	$A+B'+C$
0	1	1	$A+B'+C'$
1	0	0	$A'+B+C$
1	0	1	$A'+B+C'$
1	1	0	$A'+B'+C$
1	1	1	$A'+B'+C'$

F in canonical form:

$$F(A, B, C) = (A + B + C) (A + B' + C) (A' + B + C)$$

canonical form \neq minimal form

$$\begin{aligned} F(A, B, C) &= (A + B + C) (A + B' + C) (A' + B + C) \\ &= (A + B + C) (A + B' + C) \\ &\quad (A + B + C) (A' + B + C) \\ &= (A + C) (B + C) \end{aligned}$$

Predicate Logic

Predicate Logic

- **Propositional Logic**

“If you take the high road and I take the low road then I’ll arrive in Scotland before you.”

- **Predicate Logic**

“All positive integers x , y , and z satisfy $x^3 + y^3 \neq z^3$.”

Predicate Logic

- **Propositional Logic**

- Allows us to analyze complex propositions in terms of their simpler constituent parts (a.k.a. atomic propositions) joined by connectives

- **Predicate Logic**

- Lets us analyze them at a deeper level by expressing how those propositions depend on the objects they are talking about

Predicate Logic

Adds two key notions to propositional logic

- **Predicates**

- **Quantifiers**

Predicates

Predicate

– A function that returns a truth value, e.g.,

$\text{Cat}(x) ::= \text{“}x \text{ is a cat”}$

$\text{Prime}(x) ::= \text{“}x \text{ is prime”}$

$\text{HasTaken}(x, y) ::= \text{“student } x \text{ has taken course } y\text{”}$

$\text{LessThan}(x, y) ::= \text{“}x < y\text{”}$

$\text{Sum}(x, y, z) ::= \text{“}x + y = z\text{”}$

$\text{GreaterThan5}(x) ::= \text{“}x > 5\text{”}$

$\text{HasNChars}(s, n) ::= \text{“string } s \text{ has length } n\text{”}$

Predicates can have varying numbers of arguments and input types.

Domain of Discourse

For ease of use, we define one “type”/“domain” that we work over. This non-empty set of objects is called the “**domain of discourse**”.

For each of the following, what might the domain be?

(1) “x is a cat”, “x barks”, “x ruined my couch”

“mammals” or “sentient beings” or “cats and dogs” or ...

(2) “x is prime”, “ $x = 0$ ”, “ $x < 0$ ”, “x is a power of two”

“numbers” or “integers” or “integers greater than 5” or ...

(3) “student x has taken course y” “x is a pre-req for z”

“students and courses” or “university entities” or ...