

Combinational logic design case studies

- General design procedure
- Examples
 - calendar subsystem
 - BCD to 7-segment display controller
 - process line controller
 - logical function unit
- Arithmetic
 - integer representations
 - addition/subtraction
 - arithmetic/logic units

CSE 370 - Spring 2000 - Combinational Examples - 1

General design procedure for combinational logic

- 1. Understand the problem
 - what is the circuit supposed to do?
 - write down inputs (data, control) and outputs
 - draw block diagram or other picture
- 2. Formulate the problem using a suitable design representation
 - truth table or waveform diagram are typical
 - may require encoding of symbolic inputs and outputs
- 3. Choose implementation target
 - ROM, PAL, PLA
 - mux, decoder and OR-gate
 - discrete gates
- 4. Follow implementation procedure
 - K-maps for two-level, multi-level
 - design tools and hardware description language (e.g., Verilog)

CSE 370 - Spring 2000 - Combinational Examples - 2

Calendar subsystem

- Determine number of days in a month (to control watch display)
 - used in controlling the display of a wrist-watch LCD screen


- inputs: month, leap year flag
- outputs: number of days

- Use software implementation to help understand the problem

```
integer number_of_days ( month, leap_year_flag) {
    switch (month) {
        case 1: return (31);
        case 2: if (leap_year_flag == 1)
                then return (29)
                else return (28);
        case 3: return (31);
        case 4: return (30);
        case 5: return (31);
        case 6: return (30);
        case 7: return (31);
        case 8: return (31);
        case 9: return (30);
        case 10: return (31);
        case 11: return (30);
        case 12: return (31);
        default: return (0);
    }
}
```

Formalize the problem

 - Encoding:
 - binary number for month: 4 bits
 - 4 wires for 28, 29, 30, and 31
one-hot – only one true at any time
- Block diagram:



month	leap	28	29	30	31
0000	-	-	-	-	-
0001	-	0	0	0	1
0010	0	1	0	0	0
0010	1	0	1	0	0
0011	-	0	0	0	1
0100	-	0	0	1	0
0101	-	0	0	0	1
0110	-	0	0	1	0
0111	-	0	0	0	1
1000	-	0	0	0	1
1001	-	0	0	1	0
1010	-	0	0	0	1
1011	-	0	0	1	0
1100	-	0	0	0	1
1101	-	-	-	-	-
111-	-	-	-	-	-

Choose implementation target and perform mapping

- Discrete gates

- $28 = m8' m4' m2 m1' \text{ leap}'$

- $29 = m8' m4' m2 m1' \text{ leap}$

- $30 = m8' m4 m1' + m8 m1$

- $31 = m8' m1 + m8 m1'$

- Can translate to S-o-P or P-o-S

month	leap	28	29	30	31
0000	-	-	-	-	-
0001	-	0	0	0	1
0010	0	1	0	0	0
0011	1	0	1	0	0
0011	-	0	0	0	1
0100	-	0	0	1	0
0101	-	0	0	0	1
0110	-	0	0	1	0
0111	-	0	0	0	1
1000	-	0	0	0	1
1001	-	0	0	1	0
1010	-	0	0	0	1
1011	-	0	0	1	0
1100	-	0	0	0	1
1101	-	-	-	-	-
111-	-	-	-	-	-


BCD to 7-segment display controller

- Understanding the problem

- input is a 4 bit bcd digit (A, B, C, D)

- output is the control signals for the display (7 outputs C0 – C6)

- Block diagram

 

Formalize the problem

- Truth table
 - show don't cares
- Choose implementation target
 - if ROM, we are done
 - don't cares imply PAL/PLA may be attractive
- Follow implementation procedure
 - minimization using K-maps

A	B	C	D	C0	C1	C2	C3	C4	C5	C6
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	0	1	1
1	0	1	-	-	-	-	-	-	-	-
1	1	-	-	-	-	-	-	-	-	-

CSE 370 - Spring 2000 - Combinational Examples - 7

Implementation as minimized sum-of-products

- 15 unique product terms when minimized individually

<table border="1" style="font-size: small;"> <tr><td></td><td colspan="4">A</td><td></td></tr> <tr><td></td><td>1</td><td>0</td><td>X</td><td>1</td></tr> <tr><td></td><td>0</td><td>1</td><td>X</td><td>1</td></tr> <tr><td>C</td><td>1</td><td>1</td><td>X</td><td>X</td></tr> <tr><td></td><td>1</td><td>1</td><td>X</td><td>X</td></tr> <tr><td></td><td colspan="4">B</td><td></td></tr> </table>		A						1	0	X	1		0	1	X	1	C	1	1	X	X		1	1	X	X		B					<table border="1" style="font-size: small;"> <tr><td></td><td colspan="4">A</td><td></td></tr> <tr><td></td><td>1</td><td>1</td><td>X</td><td>1</td></tr> <tr><td></td><td>1</td><td>0</td><td>X</td><td>1</td></tr> <tr><td>C</td><td>1</td><td>1</td><td>X</td><td>X</td></tr> <tr><td></td><td>1</td><td>0</td><td>X</td><td>X</td></tr> <tr><td></td><td colspan="4">B</td><td></td></tr> </table>		A						1	1	X	1		1	0	X	1	C	1	1	X	X		1	0	X	X		B					<table border="1" style="font-size: small;"> <tr><td></td><td colspan="4">A</td><td></td></tr> <tr><td></td><td>1</td><td>1</td><td>X</td><td>1</td></tr> <tr><td></td><td>1</td><td>1</td><td>X</td><td>1</td></tr> <tr><td>C</td><td>1</td><td>1</td><td>X</td><td>X</td></tr> <tr><td></td><td>0</td><td>1</td><td>X</td><td>X</td></tr> <tr><td></td><td colspan="4">B</td><td></td></tr> </table>		A						1	1	X	1		1	1	X	1	C	1	1	X	X		0	1	X	X		B					<table border="1" style="font-size: small;"> <tr><td></td><td colspan="4">A</td><td></td></tr> <tr><td></td><td>1</td><td>0</td><td>X</td><td>1</td></tr> <tr><td></td><td>0</td><td>1</td><td>X</td><td>0</td></tr> <tr><td>C</td><td>1</td><td>0</td><td>X</td><td>X</td></tr> <tr><td></td><td>1</td><td>1</td><td>X</td><td>X</td></tr> <tr><td></td><td colspan="4">B</td><td></td></tr> </table>		A						1	0	X	1		0	1	X	0	C	1	0	X	X		1	1	X	X		B					<table border="1" style="font-size: small;"> <tr><td></td><td colspan="4">A</td><td></td></tr> <tr><td></td><td>1</td><td>0</td><td>X</td><td>1</td></tr> <tr><td></td><td>0</td><td>0</td><td>X</td><td>0</td></tr> <tr><td>C</td><td>0</td><td>0</td><td>X</td><td>X</td></tr> <tr><td></td><td>1</td><td>1</td><td>X</td><td>X</td></tr> <tr><td></td><td colspan="4">B</td><td></td></tr> </table>		A						1	0	X	1		0	0	X	0	C	0	0	X	X		1	1	X	X		B				
	A																																																																																																																																																																			
	1	0	X	1																																																																																																																																																																
	0	1	X	1																																																																																																																																																																
C	1	1	X	X																																																																																																																																																																
	1	1	X	X																																																																																																																																																																
	B																																																																																																																																																																			
	A																																																																																																																																																																			
	1	1	X	1																																																																																																																																																																
	1	0	X	1																																																																																																																																																																
C	1	1	X	X																																																																																																																																																																
	1	0	X	X																																																																																																																																																																
	B																																																																																																																																																																			
	A																																																																																																																																																																			
	1	1	X	1																																																																																																																																																																
	1	1	X	1																																																																																																																																																																
C	1	1	X	X																																																																																																																																																																
	0	1	X	X																																																																																																																																																																
	B																																																																																																																																																																			
	A																																																																																																																																																																			
	1	0	X	1																																																																																																																																																																
	0	1	X	0																																																																																																																																																																
C	1	0	X	X																																																																																																																																																																
	1	1	X	X																																																																																																																																																																
	B																																																																																																																																																																			
	A																																																																																																																																																																			
	1	0	X	1																																																																																																																																																																
	0	0	X	0																																																																																																																																																																
C	0	0	X	X																																																																																																																																																																
	1	1	X	X																																																																																																																																																																
	B																																																																																																																																																																			
<table border="1" style="font-size: small;"> <tr><td></td><td colspan="4">A</td><td></td></tr> <tr><td></td><td>1</td><td>1</td><td>X</td><td>1</td></tr> <tr><td></td><td>0</td><td>1</td><td>X</td><td>1</td></tr> <tr><td>C</td><td>0</td><td>0</td><td>X</td><td>X</td></tr> <tr><td></td><td>0</td><td>1</td><td>X</td><td>X</td></tr> <tr><td></td><td colspan="4">B</td><td></td></tr> </table>		A						1	1	X	1		0	1	X	1	C	0	0	X	X		0	1	X	X		B					<table border="1" style="font-size: small;"> <tr><td></td><td colspan="4">A</td><td></td></tr> <tr><td></td><td>0</td><td>1</td><td>X</td><td>1</td></tr> <tr><td></td><td>0</td><td>1</td><td>X</td><td>1</td></tr> <tr><td>C</td><td>1</td><td>0</td><td>X</td><td>X</td></tr> <tr><td></td><td>1</td><td>1</td><td>X</td><td>X</td></tr> <tr><td></td><td colspan="4">B</td><td></td></tr> </table>		A						0	1	X	1		0	1	X	1	C	1	0	X	X		1	1	X	X		B					$C0 = A + B D + C + B' D'$ $C1 = C' D' + C D + B'$ $C2 = B + C' + D$ $C3 = B' D' + C D' + B C' D + B' C$ $C4 = B' D' + C D'$ $C5 = A + C' D' + B D' + B C'$ $C6 = A + C D' + B C' + B' C$																																																																																																		
	A																																																																																																																																																																			
	1	1	X	1																																																																																																																																																																
	0	1	X	1																																																																																																																																																																
C	0	0	X	X																																																																																																																																																																
	0	1	X	X																																																																																																																																																																
	B																																																																																																																																																																			
	A																																																																																																																																																																			
	0	1	X	1																																																																																																																																																																
	0	1	X	1																																																																																																																																																																
C	1	0	X	X																																																																																																																																																																
	1	1	X	X																																																																																																																																																																
	B																																																																																																																																																																			

CSE 370 - Spring 2000 - Combinational Examples - 8

Implementation as minimized S-o-P (cont'd)

- Can do better
 - 9 unique product terms (instead of 15)
 - share terms among outputs
 - each output not necessarily in minimized form

	A			
C2	1	1	X	1
	1	1	X	1
C	1	1	X	X
	0	1	X	X
	B			


$$\begin{aligned}
 C0 &= A + BD + C + B'D' \\
 C1 &= C'D' + CD + B' \\
 C2 &= B + C' + D \\
 C3 &= B'D' + C'D' + BC'D + B'C \\
 C4 &= B'D' + C'D' \\
 C5 &= A + C'D' + BD' + BC' \\
 C6 &= A + C'D' + BC' + B'C
 \end{aligned}$$

	A			
C2	1	1	X	1
	1	1	X	1
C	1	1	X	X
	0	1	X	X
	B			

$$\begin{aligned}
 C0 &= BC'D + CD + B'D' + BCD' + A \\
 C1 &= B'D + C'D' + CD + B'D' \\
 C2 &= B'D + BC'D + C'D' + CD + BCD' \\
 C3 &= BC'D + B'D + B'D' + BCD' \\
 C4 &= B'D' + BCD' \\
 C5 &= BC'D + C'D' + A + BCD' \\
 C6 &= B'C + BC' + BCD' + A
 \end{aligned}$$

CSE 370 - Spring 2000 - Combinational Examples - 9

PLA implementation

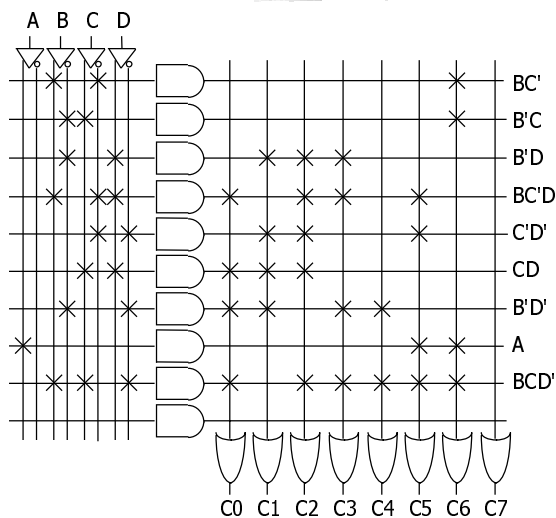

CSE 370 - Spring 2000 - Combinational Examples - 10

PAL implementation

- Limit of 4 product terms per output
 - decomposition of functions with larger number of terms
 - do not share terms in PAL anyway (although there are some with some shared terms)

$$C2 = B + C' + D$$

$$C2 = B' D + B C' D + C' D' + C D + B C D'$$

$$C2 = B' D + B C' D + C' D' + W$$

$$W = C D + B C D'$$

← need another input and another output
- decompose into multi-level logic (hopefully with CAD support)
 - find common sub-expressions among functions

$$C0 = C3 + A' B X' + A D Y$$

$$C1 = Y + A' C5' + C' D' C6$$

$$C2 = C5 + A' B' D + A' C D$$

$$C3 = C4 + B D C5 + A' B' X'$$

$$C4 = D' Y + A' C D'$$

$$C5 = C' C4 + A Y + A' B X$$

$$C6 = A C4 + C C5 + C4' C5 + A' B' C$$

$$X = C' + D'$$

$$Y = B' C'$$

CSE 370 - Spring 2000 - Combinational Examples - 11


Production line control

- Rods of varying length (+/-10%) travel on conveyor belt
 - mechanical arm pushes rods within spec (+/-5%) to one side
 - second arm pushes rods too long to other side
 - rods that are too short stay on belt
 - 3 light barriers (light source + photocell) as sensors
 - design combinational logic to activate the arms
- Understanding the problem
 - inputs are three sensors
 - outputs are two arm control signals
 - assume sensor reads "1" when tripped, "0" otherwise
 - call sensors A, B, C

CSE 370 - Spring 2000 - Combinational Examples - 12

Sketch of problem

- Position of sensors
 - A to B distance = specification - 5%
 - A to C distance = specification + 5%

 

CSE 370 - Spring 2000 - Combinational Examples - 13

Formalize the problem

- Truth table
 - show don't cares

A	B	C	Function	
0	0	0	do nothing	logic implementation now straightforward just use three 3-input AND gates
0	0	1	do nothing	
0	1	0	do nothing	"too short" = $AB'C$
0	1	1	do nothing	(only first sensor tripped)
1	0	0	too short	"in spec" = $AB C'$
1	0	1	don't care	
1	1	0	in spec	"too long" = ABC
1	1	1	too long	

CSE 370 - Spring 2000 - Combinational Examples - 14

Logical function unit

- Multi-purpose function block
 - 3 control inputs to specify operation to perform on operands
 - 2 data inputs for operands
 - 1 output of the same bit-width as operands

C0	C1	C2	Function	Comments
0	0	0	1	always 1
0	0	1	$A + B$	logical OR
0	1	0	$(A \cdot B)'$	logical NAND
0	1	1	$A \text{ xor } B$	logical xor
1	0	0	$A \text{ xnor } B$	logical xnor
1	0	1	$A \cdot B$	logical AND
1	1	0	$(A + B)'$	logical NOR
1	1	1	0	always 0


3 control inputs: C0, C1, C2
2 data inputs: A, B
1 output: F

CSE 370 - Spring 2000 - Combinational Examples - 15

Formalize the problem

C0	C1	C2	A	B	F
0	0	0	0	0	1
0	0	0	0	1	1
0	0	0	1	0	1
0	0	0	1	1	1
0	0	1	0	0	0
0	0	1	0	1	1
0	0	1	1	0	1
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	0	1	1
0	1	0	1	0	1
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	0	1	1
0	1	1	1	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	0	0	1	0
1	0	0	1	0	0
1	0	0	1	1	1
1	0	1	0	0	0
1	0	1	0	1	0
1	0	1	1	0	0
1	0	1	1	1	1
1	1	0	0	0	1
1	1	0	0	1	0
1	1	0	1	0	0
1	1	0	1	1	0
1	1	1	0	0	0
1	1	1	0	1	0
1	1	1	1	0	0
1	1	1	1	1	0

choose implementation technology
5-variable K-map to discrete gates
multiplexor implementation

 

CSE 370 - Spring 2000 - Combinational Examples - 16

Arithmetic circuits


- Excellent examples of combinational logic design
- Time vs. space trade-offs
 - ┆ doing things fast may require more logic and thus more space
 - ┆ example: carry lookahead logic
- Arithmetic and logic units
 - ┆ general-purpose building blocks
 - ┆ critical components of processor datapaths
 - ┆ used within most computer instructions

Number systems

- Representation of positive numbers is the same in most systems
- Major differences are in how negative numbers are represented
- Representation of negative numbers come in three major schemes
 - ┆ sign and magnitude
 - ┆ 1s complement
 - ┆ 2s complement
- Assumptions
 - ┆ we'll assume a 4 bit machine word
 - ┆ 16 different values can be represented
 - ┆ roughly half are positive, half are negative

Sign and magnitude

- One bit dedicate to sign (positive or negative)
 - ▮ sign: 0 = positive (or zero), 1 = negative 0 100 = + 4
- Rest represent the absolute value or magnitude 1 100 = - 4
 - ▮ three low order bits: 0 (000) thru 7 (111)
- Range for n bits
 - ▮ +/- $2^{n-1} - 1$ (two representations for 0)
- Cumbersome addition/subtraction
 - ▮ must compare magnitudes to determine sign of result

 

CSE 370 - Spring 2000 - Combinational Examples - 19

1s complement

- If N is a positive number, then the negative of N (its 1s complement or N') is $N' = (2^n - 1) - N$
 - ▮ example: 1s complement of 7

$$\begin{array}{rcl}
 2^4 & = & 10000 \\
 1 & = & \underline{00001} \\
 2^4 - 1 & = & 1111 \\
 7 & = & \underline{0111} \\
 & & 1000 = -7 \text{ in 1s complement form}
 \end{array}$$

- ▮ shortcut: simply compute bit-wise complement (0111 -> 1000)


CSE 370 - Spring 2000 - Combinational Examples - 20

1s complement (cont'd)

- Subtraction implemented by 1s complement and then addition
- Two representations of 0
 - causes some complexities in addition
- High-order bit can act as sign bit

$$0\ 100 = +4$$

$$1\ 011 = -4$$

 


CSE 370 - Spring 2000 - Combinational Examples - 21

2s complement

- 1s complement with negative numbers shifted one position clockwise
 - only one representation for 0
 - one more negative number than positive number
 - high-order bit can act as sign bit

$$0\ 100 = +4$$

$$1\ 100 = -4$$

 

CSE 370 - Spring 2000 - Combinational Examples - 22

2s complement (cont'd)

- If N is a positive number, then the negative of N (its 2s complement or N^*) is $N^* = 2n - N$

- example: 2s complement of 7

$$\begin{array}{r}
 2^4 = 10000 \\
 \text{subtract } 7 = \underline{0111} \\
 \hline
 1001 = \text{repr. of } -7
 \end{array}$$

- example: 2s complement of -7

$$\begin{array}{r}
 2^4 = 10000 \\
 \text{subtract } -7 = \underline{1001} \\
 \hline
 0111 = \text{repr. of } 7
 \end{array}$$

- shortcut: 2s complement = bit-wise complement + 1
 - | 0111 -> 1000 + 1 -> 1001 (representation of -7)
 - | 1001 -> 0110 + 1 -> 0111 (representation of 7)

2s complement addition and subtraction

- Simple addition and subtraction
 - simple scheme makes 2s complement the virtually unanimous choice for integer number systems in computers

$$\begin{array}{r}
 4 \quad 0100 \\
 + 3 \quad 0011 \\
 \hline
 7 \quad 0111
 \end{array}
 \qquad
 \begin{array}{r}
 -4 \quad 1100 \\
 + (-3) \quad 1101 \\
 \hline
 -7 \quad 11001
 \end{array}$$

$$\begin{array}{r}
 4 \quad 0100 \\
 - 3 \quad 1101 \\
 \hline
 1 \quad 10001
 \end{array}
 \qquad
 \begin{array}{r}
 -4 \quad 1100 \\
 + 3 \quad 0011 \\
 \hline
 -1 \quad 1111
 \end{array}$$

Why can the carry-out be ignored?

- Can't ignore it completely
 - needed to check for overflow (see next two slides)
- When there is no overflow, carry-out may be true but can be ignored

– $M + N$ when $N > M$:

$$M^* + N = (2n - M) + N = \underline{2n} + (N - M)$$

ignoring carry-out is just like subtracting $2n$


– $M + -N$ where $N + M \leq 2n-1$

$$(-M) + (-N) = M^* + N^* = (2n - M) + (2n - N) = 2n - (M + N) + \underline{2n}$$

ignoring the carry, it is just the 2s complement representation for $-(M + N)$

Overflow in 2s complement addition/subtraction

 - Overflow conditions
 - add two positive numbers to get a negative number
 - add two negative numbers to get a positive number



Overflow conditions

- Overflow when carry into sign bit position is not equal to carry-out

$ \begin{array}{r} 5 \\ \underline{-3} \\ -8 \end{array} $	$ \begin{array}{r} 0111 \\ 0101 \\ \underline{0011} \\ 1000 \end{array} $	$ \begin{array}{r} -7 \\ \underline{-2} \\ 7 \end{array} $	$ \begin{array}{r} 1000 \\ 1001 \\ \underline{1110} \\ 10111 \end{array} $
overflow		overflow	

$ \begin{array}{r} 5 \\ \underline{2} \\ 7 \end{array} $	$ \begin{array}{r} 0000 \\ 0101 \\ \underline{0010} \\ 0111 \end{array} $	$ \begin{array}{r} -3 \\ \underline{-5} \\ -8 \end{array} $	$ \begin{array}{r} 1111 \\ 1101 \\ \underline{1011} \\ 11000 \end{array} $
no overflow		no overflow	


Circuits for binary addition

- Half adder (add 2 1-bit numbers)
 - Sum = $A_i' B_i + A_i B_i' = A_i \text{ xor } B_i$
 - Cout = $A_i B_i$
- Full adder (carry-in to cascade for multi-bit adders)
 - Sum = $C_i \text{ xor } A \text{ xor } B$
 - Cout = $B C_i + A C_i + A B = C_i (A + B) + A B$

Ai	Bi	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


Full adder implementations

 - Standard approach
 - 6 gates
 - 2 XORs, 2 ANDs, 2 ORs




- Alternative implementation
 - 5 gates
 - half adder is an XOR gate and AND gate
 - 2 XORs, 2 ANDs, 1 OR
 
$$C_{out} = A \cdot B + C_{in} \cdot (A \oplus B) = A \cdot B + B \cdot C_{in} + A \cdot C_{in}$$



Adder/subtractor

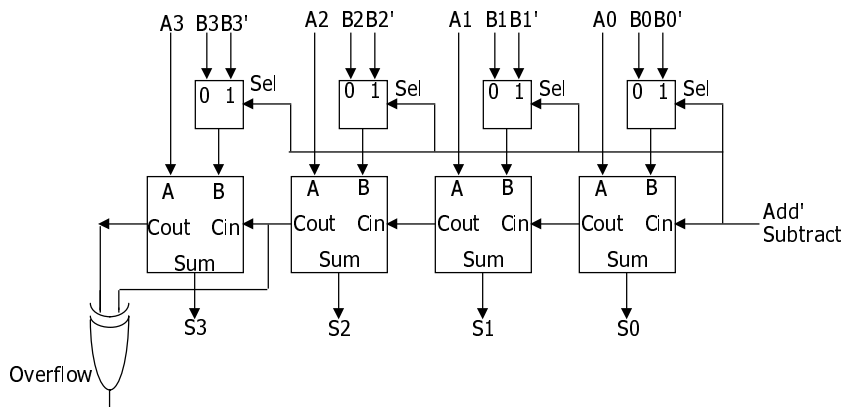
- Use an adder to do subtraction thanks to 2s complement representation
 - $A - B = A + (-B) = A + B' + 1$
 - control signal selects B or 2s complement of B



Ripple-carry adders

- Critical delay

- the propagation of carry from low to high order stages

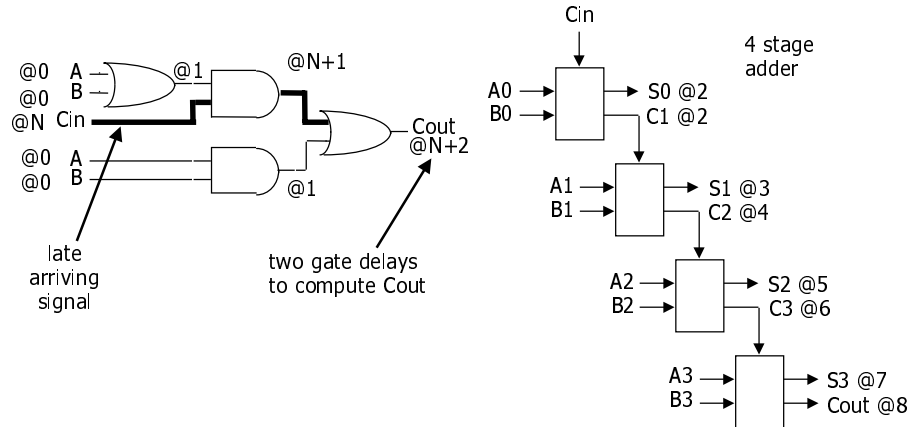


CSE 370 - Spring 2000 - Combinational Examples - 31

Ripple-carry adders (cont'd)

- Critical delay

- the propagation of carry from low to high order stages
 - 1111 + 0001 is the worst case addition
 - carry must propagate through all bits

 

CSE 370 - Spring 2000 - Combinational Examples - 32

Carry-lookahead logic


- Carry generate: $G_i = A_i B_i$
 - ┆ must generate carry when $A = B = 1$
- Carry propagate: $P_i = A_i \text{ xor } B_i$
 - ┆ carry-in will equal carry-out here
- Sum and Cout can be re-expressed in terms of generate/propagate:
 - ┆ $S_i = A_i \text{ xor } B_i \text{ xor } C_i$
= $P_i \text{ xor } C_i$
 - ┆ $C_{i+1} = A_i B_i + A_i C_i + B_i C_i$
= $A_i B_i + C_i (A_i + B_i)$
= $A_i B_i + C_i (A_i \text{ xor } B_i)$
= $G_i + C_i P_i$

Carry-lookahead logic (cont'd)

- Re-express the carry logic as follows:
 - ┆ $C_1 = G_0 + P_0 C_0$
 - ┆ $C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0$
 - ┆ $C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$
 - ┆ $C_4 = G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0$
+ $P_3 P_2 P_1 P_0 C_0$
- Each of the carry equations can be implemented with two-level logic
 - ┆ all inputs are now directly derived from data inputs and not from intermediate carries
 - ┆ this allows computation of all sum outputs to proceed in parallel

Carry-lookahead implementation

■ Adder with propagate and generate outputs

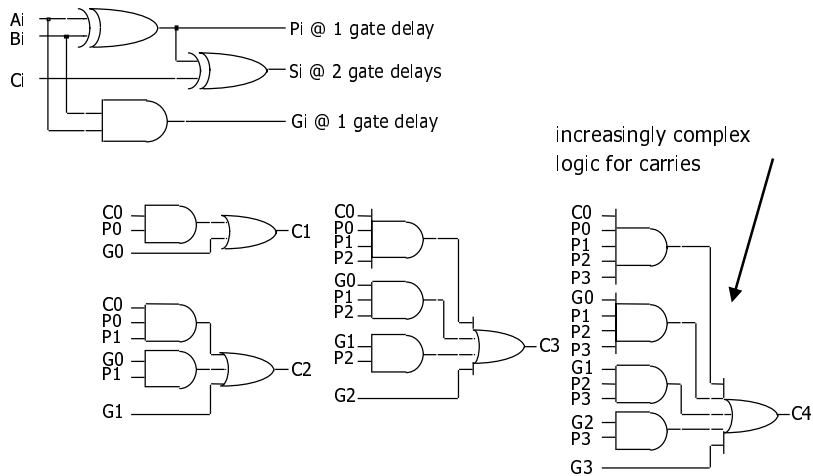


CSE 370 - Spring 2000 - Combinational Examples - 35

Carry-lookahead implementation (cont'd)

■ Carry-lookahead logic generates individual carries


- sums computed much more quickly in parallel
- however, cost of carry logic increases with more stages

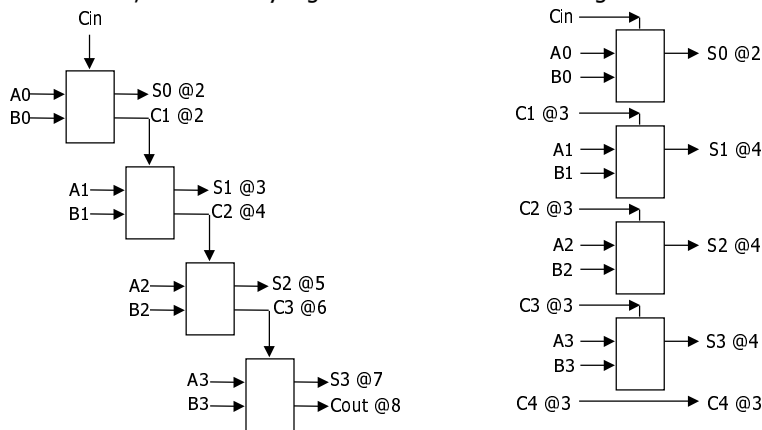

CSE 370 - Spring 2000 - Combinational Examples - 36

Carry-lookahead adder with cascaded carry-lookahead logic


- Carry-lookahead adder
 - ▮ 4 four-bit adders with internal carry lookahead
 - ▮ second level carry lookahead unit extends lookahead to 16 bits

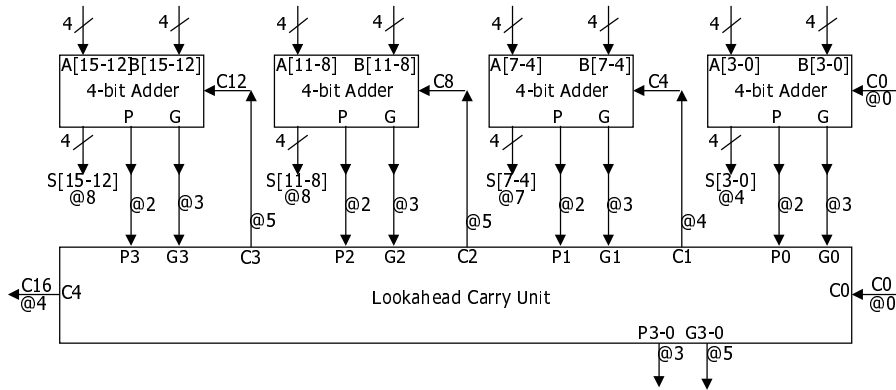

CSE 370 - Spring 2000 - Combinational Examples - 37

Carry-select adder

- Redundant hardware to make carry calculation go faster
 - ▮ compute two high-order sums in parallel while waiting for carry-in
 - ▮ one assuming carry-in is 0 and another assuming carry-in is 1
 - ▮ select correct result once carry-in is finally computed

 

CSE 370 - Spring 2000 - Combinational Examples - 38

Arithmetic logic unit design specification

M = 0, logical bitwise operations

S1	S0	Function	Comment
0	0	$F_i = A_i$	input A_i transferred to output
0	1	$F_i = \text{not } A_i$	complement of A_i transferred to output
1	0	$F_i = A_i \text{ xor } B_i$	compute XOR of A_i, B_i
1	1	$F_i = A_i \text{ xnor } B_i$	compute XNOR of A_i, B_i

M = 1, C0 = 0, arithmetic operations

0	0	$F = A$	input A passed to output
0	1	$F = \text{not } A$	complement of A passed to output
1	0	$F = A \text{ plus } B$	sum of A and B
1	1	$F = (\text{not } A) \text{ plus } B$	sum of B and complement of A

M = 1, C0 = 1, arithmetic operations

0	0	$F = A \text{ plus } 1$	increment A
0	1	$F = (\text{not } A) \text{ plus } 1$	twos complement of A
1	0	$F = A \text{ plus } B \text{ plus } 1$	increment sum of A and B
1	1	$F = (\text{not } A) \text{ plus } B \text{ plus } 1$	B minus A

logical and arithmetic operations
not all operations appear useful, but "fall out" of internal logic

CSE 370 - Spring 2000 - Combinational Examples - 39

Arithmetic logic unit design (cont'd)


■ Sample ALU – truth table

M	S1	S0	Ci	Ai	Bi	Fi	Ci+1
0	0	0	X	0	X	0	X
			X	1	X	1	X
	0	1	X	0	X	1	X
			X	1	X	0	X
	1	0	X	0	0	0	X
			X	0	1	1	X
			X	1	0	1	X
	1	1	X	0	1	1	X
			X	1	0	0	X
			X	1	1	1	X
1	0	0	0	0	X	0	X
			0	1	X	1	X
	0	1	0	0	X	1	X
			0	1	X	0	X
	1	0	0	0	0	0	0
			0	0	1	1	0
			0	1	0	1	0
	1	1	0	0	1	1	0
			0	0	0	1	0
			0	1	0	0	0
			0	1	1	1	0
1	0	0	1	0	X	1	0
			1	1	X	0	1
	0	1	1	0	X	0	1
			1	1	X	1	0
	1	0	1	0	0	1	0
			1	0	1	0	1
			1	1	0	1	1
	1	1	1	0	1	0	1
			1	0	0	1	0
			1	1	0	1	0
			1	1	1	1	0
			1	1	1	1	1

CSE 370 - Spring 2000 - Combinational Examples - 40

Arithmetic logic unit design (cont'd)


Sample ALU – multi-level discrete gate logic implementation

 

CSE 370 - Spring 2000 - Combinational Examples - 41

Arithmetic logic unit design (cont'd)

Sample ALU – clever multi-level implementation

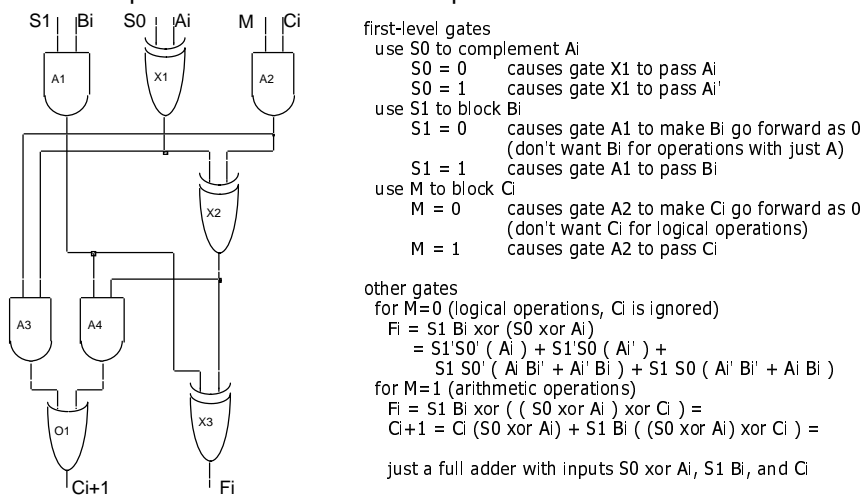

CSE 370 - Spring 2000 - Combinational Examples - 42

Summary for examples of combinational logic

- Combinational logic design process
 - ┆ formalize problem: encodings, truth-table, equations
 - ┆ choose implementation technology (ROM, PAL, PLA, discrete gates)
 - ┆ implement by following the design procedure for that technology
- Binary number representation
 - ┆ positive numbers the same
 - ┆ difference is in how negative numbers are represented
 - ┆ 2s complement easiest to handle: one representation for zero, slightly complicated complementation, simple addition
- Circuits for binary addition
 - ┆ basic half-adder and full-adder
 - ┆ carry lookahead logic
 - ┆ carry-select
- ALU Design
 - ┆ specification, implementation