

Today

- K-maps
- Reverse Engineering Example
- Max block example

Thursday, May 11,
2000

1

CSE-370 Section

Karnaugh Maps

- What was the idea in doing simplification? Well, one of the ideas was to try to apply the unification theorem ($AB + AB' = A$).
- What we're looking for then are terms that differ only in one variable.
- This can be difficult to do when there are many terms and many variables. K-maps are just a graphical method that makes it easier.


Thursday, May 11,
2000

2

CSE-370 Section

Cube Representation.

- Draw a cube: each vertex is a possible term, AND two adjacent vertices only differ in one variable.
- Now, draw a dot for each term from our boolean expression, and group dots that are connected.
- An edge that connects two dots means that we can apply the unification theorem to merge those two terms. The variable that differs is dropped.
- By applying the unification theorem twice, we can merge 4 vertices that are fully connected.

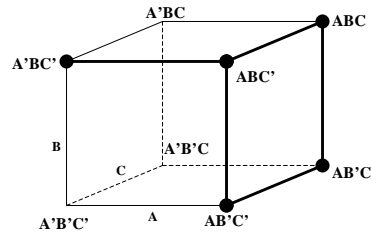



The above cube shows the expression $A'BC + ABC' + ABC + AB'C + AB'C'$.
It simplifies to:
 $A + BC'$

Thursday, May 11, 2000

3

CSE-370 Section

Karnaugh Maps (cont'd)

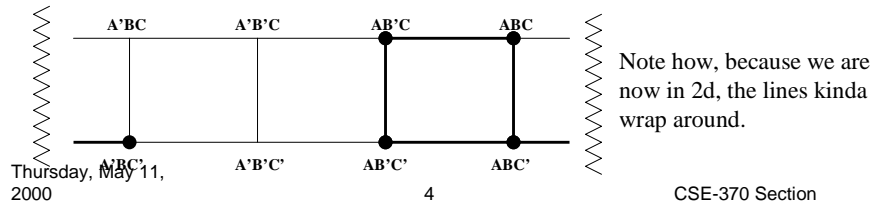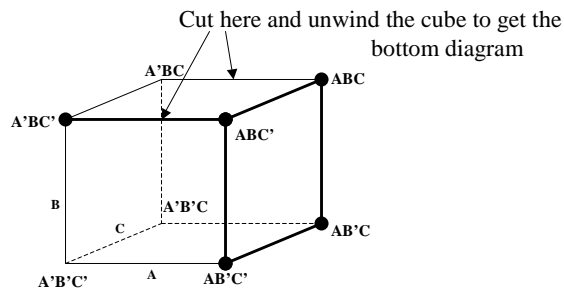


Thursday, May 11, 2000

4

CSE-370 Section

Karnaugh Maps (cont'd)

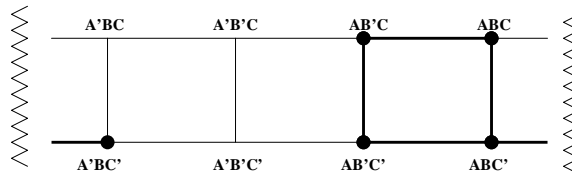

A simpler drawing of this is given below. We call this kind of table a Karnaugh map.

AB	01	00	10	11
C				
1	0	0	1	1
0	1	0	1	1

Thursday, May 11,
2000

5

CSE-370 Section

Implicants

- **Implicant:** A product term whose "oneness" *implies* the functions "oneness".
- **Prime Implicant:** Implicant that cannot be combined with another implicant.
- **Essential Prime Implicant:** Implicant that covers an element of the on-set which is not covered by any other implicant.

Thursday, May 11,
2000

6

CSE-370 Section

Example of Implicants

- Implicants
- Six Prime Implicants:
 $A'B'D$, BC' , AC , $A'C'D$,
 AB , $B'CD$
- Essential PI: AC, BC'
- $F = A'B'D + BC' + AC$

AB	00	01	11	10
CD				
00	0	1	1	0
01	1	1	1	0
11	1	0	1	1
10	0	0	1	1

Thursday, May 11,
2000

7

CSE-370 Section

K-map: SoP and PoS

- SoP:
 $A'BC'D' + A'B'C'D + ABC'D + AB'C'D + A'B'CD + AB'CD$
- Minimized Exp
 $A'BC'D' + B'D + AC'D$
- PoS:
 $(A+B+C+D)(A'+B'+C+D)(A'+B+C+D)(A+B'+C+D)$

- Minimized PoS
 $(B+D)(A'+D)(B'+C')(A+B'+D')$

AB	00	01	11	10
CD				
00	0	1	0	0
01	1	0	1	1
11	1	0	0	1
10	0	0	0	0


Thursday, May 11,
2000

8

CSE-370 Section

Reverse Engineering Example

- Write down the Boolean expression:

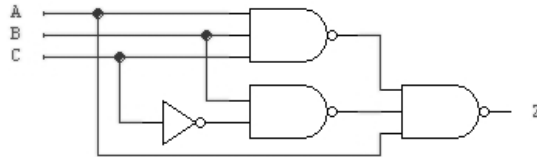

$$f(A, B, C) = \overline{ABC} \cdot \overline{BC} \cdot A$$

Thursday, May 11,
2000

9

CSE-370 Section

Reverse Engineering Ex (cont.)

- Write the complete truth table for the circuit.

A	B	C	Z
0	0	0	1
	0	1	1
	1	0	1
	1	1	1
1	0	0	0
	0	1	0
	1	0	1
	1	1	1

Thursday, May 11,
2000

10

CSE-370 Section

Reverse Engineering Ex (cont.)

- Do a k-map:

Thursday, May 11,
2000

11

CSE-370 Section

Reverse Engineering Ex (cont.)

- Re-implement the better design.

Thursday, May 11,
2000

12

CSE-370 Section

Max function

- The max block has 4 inputs (X1, X0, Y1, Y0), and 2 outputs (M1, M0)
- X1, X0 is a 2 bit 2's complement number, and so is Y1, Y0
- M1, M0 is the maximum between the two input numbers

Thursday, May 11,
2000

13

CSE-370 Section

Truth Table

X1	X0	Y1	Y0	M1	M0
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	0	0
0	0	1	1	0	0
0	1	0	0	0	1
0	1	0	1	0	1
0	1	1	0	0	1
0	1	1	1	0	1
1	0	0	0	0	0
1	0	0	1	0	1
1	0	1	0	1	0
1	0	1	1	1	1
1	1	0	0	0	0
1	1	0	1	1	1
1	1	1	0	1	1
1	1	1	1	1	1

Thursday, May 11,
2000

14

CSE-370 Section

K-map

		X1		
	0	0	0	0
	0	0	1	0
Y1	0	0	1	1
	0	0	1	1
		X0		

$$M_1 = X_1 Y_1 + X_1 X_0 Y_0$$

		X1		
	0	1	0	0
	1	1	1	1
Y1	0	1	1	1
	0	1	1	0
		X0		

$$M_0 = Y_1' Y_0 + X_1' X_0 + X_1 Y_0 + X_0 Y_1$$

Thursday, May 11,
2000

15

CSE-370 Section