

## Sequential Logic : A Review

- ⌘ State Minimization (Implication Chart vs Row Matching)
- ⌘ DataPath vs Control Path
- ⌘ Reverse Engineering FSM
- ⌘ FSMs: Mealy vs Moore
- ⌘ FFs converting one from another and using them to implement


## Algorithmic approach to state minimization

- ⌘ Goal – identify and combine states that have equivalent behavior
- ⌘ Equivalent states:
  - ☒ same output
  - ☒ for all input combinations, states transition to same or equivalent states
- ⌘ Algorithm sketch
  - ☒ 1. place all states in one set
  - ☒ 2. initially partition set based on output behavior
  - ☒ 3. successively partition resulting subsets based on next state transitions
  - ☒ 4. repeat (3) until no further partitioning is required
    - ☒ states left in the same set are equivalent
  - ☒ polynomial time procedure

## State minimization example

⌘ Sequence detector for 010 or 110

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S0	S1	S2	0	0
0	S1	S3	S4	0	0
1	S2	S5	S6	0	0
00	S3	S0	S0	0	0
01	S4	S0	S0	1	0
10	S5	S0	S0	0	0
11	S6	S0	S0	1	0

 

CSE 370 – Spring 2001 - Combinational Logic - 3

## Method of successive partitions

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S0	S1	S2	0	0
0	S1	S3	S4	0	0
1	S2	S5	S6	0	0
00	S3	S0	S0	0	0
01	S4	S0	S0	1	0
10	S5	S0	S0	0	0
11	S6	S0	S0	1	0

( S0 S1 S2 S3 S4 S5 S6 )

S1 is equivalent to S2

( S0 S1 S2 S3 S5 ) ( S4 S6 )

S3 is equivalent to S5

( S0 S3 S5 ) ( S1 S2 ) ( S4 S6 )

S4 is equivalent to S6


( S0 ) ( S3 S5 ) ( S1 S2 ) ( S4 S6 )

CSE 370 – Spring 2001 - Combinational Logic - 4

## Minimized FSM

⌘ State minimized sequence detector for 010 or 110


Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S0	S1'	S1'	0	0
0 + 1	S1'	S3'	S4'	0	0
X0	S3'	S0	S0	0	0
X1	S4'	S0	S0	1	0

 

CSE 370 – Spring 2001 - Combinational Logic - 5

## More complex state minimization

⌘ Multiple input example

 

inputs here

present state	next state				output
	00	01	10	11	
S0	S0	S1	S2	S3	1
S1	S0	S3	S1	S4	0
S2	S1	S3	S2	S4	1
S3	S1	S0	S4	S5	0
S4	S0	S1	S2	S5	1
S5	S1	S4	S0	S5	0

symbolic state transition table


CSE 370 – Spring 2001 - Combinational Logic - 6

## Minimized FSM

⌘ Implication chart method

☒ cross out incompatible states based on outputs

 ☒ then cross out more cells if indexed chart entries are already crossed out



present state	next state				output
	00	01	10	11	
S0'	S0'	S1	S2	S3'	1
S1	S0'	S3'	S1	S3'	0
S2	S1	S3'	S2	S0'	1
S3'	S1	S0'	S0'	S3'	0

minimized state table  
(S0==S4) (S3==S5)

## Minimizing incompletely specified FSMs

⌘ Equivalence of states is transitive when machine is fully specified


⌘ But its not transitive when don't cares are present

e.g.,	state	output	
	S0	– 0	S1 is compatible with both S0 and S2
	S1	1 –	but S0 and S2 are incompatible
	S2	– 1	

⌘ No polynomial time algorithm exists for determining best grouping of states into equivalent sets that will yield the smallest number of final states

## Data-path and control


- ⌘ Digital hardware systems = data-path + control
  - ☒ datapath: registers, counters, combinational functional units (e.g., ALU), communication (e.g., busses)
  - ☒ control: FSM generating sequences of control signals that instructs datapath what to do next

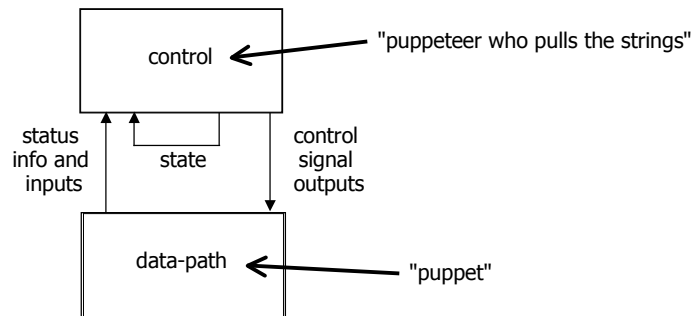

CSE 370 – Spring 2001 - Combinational Logic - 9

## Comparison of Mealy and Moore machines

- ⌘ Mealy machines tend to have less states
  - ☒ different outputs on arcs ( $n^2$ ) rather than states ( $n$ )
- ⌘ Moore machines are safer to use
  - ☒ outputs change at clock edge (always one cycle later)
  - ☒ in Mealy machines, input change can cause output change as soon as logic is done – a big problem when two machines are interconnected – asynchronous feedback
- ⌘ Mealy machines react faster to inputs
  - ☒ react in same cycle – don't need to wait for clock
  - ☒ in Moore machines, more logic may be necessary to decode state into outputs – more gate delays after

 

CSE 370 – Spring 2001 - Combinational Logic - 10