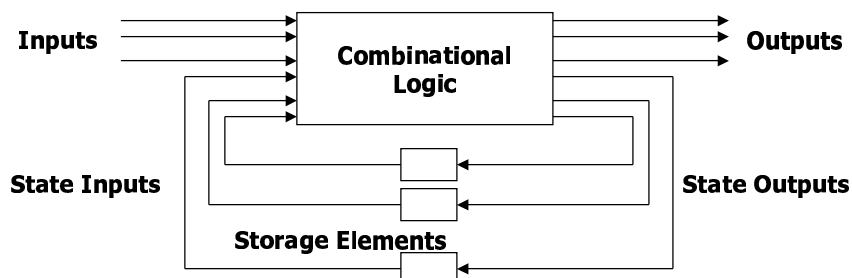


Finite State Machines

- ⌘ Sequential circuits
 - ☒ primitive sequential elements
 - ☒ combinational logic
- ⌘ Models for representing sequential circuits
 - ☒ finite-state machines (Moore and Mealy)
- ⌘ Basic sequential circuits revisited
 - ☒ shift registers
 - ☒ counters
- ⌘ Design procedure
 - ☒ state diagrams
 - ☒ state transition table
 - ☒ next state functions
- ⌘ Hardware description languages


Abstraction of state elements

- ⌘ Divide circuit into combinational logic and state
- ⌘ Localize the feedback loops and make it easy to break cycles
- ⌘ Implementation of storage elements leads to various forms of sequential logic




Forms of sequential logic

 - ⌘ Asynchronous sequential logic – state changes occur whenever state inputs change (elements may be simple wires or delay elements)
- ⌘ Synchronous sequential logic – state changes occur in lock step across all storage elements (using a periodic waveform - the clock)



Finite state machine representations

 
- ⌘ States: determined by possible values in sequential storage elements
- ⌘ Transitions: change of state
- ⌘ Clock: controls when state can change by controlling storage elements
- ⌘ Sequential logic
 - ☒ sequences through a series of states
 - ☒ based on sequence of values on input signals
 - ☒ clock period defines elements of sequence



 Example finite state machine diagram

⌘ Combination lock from introduction to course



- ☒ 5 states
- ☒ 5 self-transitions + 1 reset to state S1
- ☒ 6 transitions + 4 resets



Can any sequential system be represented with a state diagram?

⌘ Shift register

  - ☒ input value shown on transition arcs
- ☒ output values shown within state node



Counters are simple finite state machines


⌘ Counters

☒ proceed through well-defined sequence of states in response to enable

⌘ Many types of counters: binary, BCD, Gray-code

☒ 3-bit up-counter: 000, 001, 010, 011, 100, 101, 110, 111, 000, ...

 ☒ 3-bit down-counter: 111, 110, 101, 100, 011, 010, 001, 000, 111, ...



How do we turn a state diagram into logic?

⌘ Counter


☒ 3 flip-flops to hold state

☒ logic to compute next state

☒ clock signal controls when flip-flop memory can change

☒ wait long enough for combinational logic to compute new value

 ☒ don't wait too long as that is low performance



FSM design procedure

- ⌘ Start with counters
 - ☒ simple because output is just state
 - ☒ simple because no choice of next state based on input


- ⌘ State diagram to state transition table
 - ☒ tabular form of state diagram
 - ☒ like a truth-table

- ⌘ State encoding
 - ☒ decide on representation of states
 - ☒ for counters it is simple: just its value

- ⌘ Implementation
 - ☒ flip-flop for each state bit
 - ☒ combinational logic based on encoding

FSM design procedure: state diagram to encoded state transition table

 - ⌘ Tabular form of state diagram
- ⌘ Like a truth-table (specify output for all input combinations)
- ⌘ Encoding of states: easy for counters – just use value



	current state	next state	
0	000	001	1
1	001	010	2
2	010	011	3
3	011	100	4
4	100	101	5
5	101	110	6
6	110	111	7
7	111	000	0

Implementation




- ⌘ D flip-flop for each state bit
- ⌘ Combinational logic based on encoding

C3	C2	C1	N3	N2	N1
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

Verilog notation to show function represents an input to D-FF

```

N1 <= C1'
N2 <= C1C2' + C1'C2
    <= C1 xor C2
N3 <= C1C2C3' + C1'C3 + C2'C3
    <= (C1C2)C3' + (C1' + C2')C3
    <= (C1C2)C3' + (C1C2)'C3
    <= (C1C2) xor C3
    
```

   

Winter 2001


CSE370 - VII - Finite State Machines

11

Back to the shift register


- ⌘ Input determines next state

In	C1	C2	C3	N1	N2	N3
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	0	1	0
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	0	1	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	1	0	1
1	0	1	1	1	0	1
1	1	0	0	1	1	0
1	1	0	1	1	1	0
1	1	1	0	1	1	1
1	1	1	1	1	1	1

 

```

N1 <= In
N2 <= C1
N3 <= C2
    
```

 

Winter 2001

CSE370 - VII - Finite State Machines

12

More complex counter example


⌘ Complex counter

- ☒ repeats 5 states in sequence
- ☒ not a binary number representation

⌘ Step 1: derive the state transition diagram

- ☒ count sequence: 000, 010, 011, 101, 110

 ⌘ Step 2: derive the state transition table from the state transition diagram



Present State			Next State		
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	-	-	-
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	-	-	-
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	-	-	-

note the don't care conditions that arise from the unused state codes

More complex counter example (cont'd)

⌘ Step 3: K-maps for next state functions

		C			
		0	0	0	X
A	0	X	1	X	1
	1				

B

		C			
		1	1	0	X
A	0	1	1	0	X
	1	X	0	X	1

B

		C			
		0	1	0	X
A	0	0	1	0	X
	1	X	1	X	0

B

$$C+ \leq A$$

$$B+ \leq B' + A'C'$$

$$A+ \leq BC'$$

Self-starting counters (cont'd)


⌘ Re-deriving state transition table from don't care assignment

		C			
C+		0	0	0	0
A		1	1	1	1
		B			

		C			
B+		1	1	0	1
A		1	0	0	1
		B			

		C			
A+		0	1	0	0
A		0	1	0	0
		B			

Present State			Next State		
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	1	1	0
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	1	0	0

 


Self-starting counters

⌘ Start-up states

- ☒ at power-up, counter may be in an unused or invalid state
- ☒ designer must guarantee that it (eventually) enters a valid state

⌘ Self-starting solution

 - ☒ design counter so that invalid states eventually transition to a valid state
- ☒ may limit exploitation of don't cares



Activity

⌘ 2-bit up-down counter (2 inputs)


direction: D = 0 for up, D = 1 for down

count: C = 0 for hold, C = 1 for count

Activity (cont'd)


Counter/shift-register model

 - ⌘ Values stored in registers represent the state of the circuit
- ⌘ Combinational logic computes:
 - ☒ next state
 - ☒ function of current state and inputs
 - ☒ outputs
 - ☒ values of flip-flops





General state machine model

 - ⌘ Values stored in registers represent the state of the circuit
- ⌘ Combinational logic computes:
 - ☒ next state
 - ☒ function of current state and inputs
 - ☒ outputs
 - ☒ function of current state and inputs (Mealy machine)
 - ☒ function of current state only (Moore machine)




State machine model (cont'd)

  - ⌘ States: S_1, S_2, \dots, S_k
- ⌘ Inputs: I_1, I_2, \dots, I_m
- ⌘ Outputs: O_1, O_2, \dots, O_n
- ⌘ Transition function: $F_s(S_i, I_j)$
- ⌘ Output function: $F_o(S_i)$ or $F_o(S_i, I_j)$




 Example: ant brain (Ward, MIT)

- ⌘ Sensors: L and R antennae, 1 if in touching wall
- ⌘ Actuators: F - forward step, TL/TR - turn left/right slightly
- ⌘ Goal: find way out of maze
- ⌘ Strategy: keep the wall on the right



Ant behavior

 


Winter 2001

CSE370 - VII - Finite State Machines

23

Designing an ant brain

⌘ State diagram

 

Winter 2001

CSE370 - VII - Finite State Machines


24

Synthesizing the ant brain circuit

- ⌘ Encode states using a set of state variables
 - ☒ arbitrary choice - may affect cost, speed
- ⌘ Use transition truth table
 - ☒ define next state function for each state variable
 - ☒ define output function for each output
- ⌘ Implement next state and output functions using combinational logic
 - ☒ 2-level logic (ROM/PLA/PAL)
 - ☒ multi-level logic
 - ☒ next state and output functions can be optimized together

Transition truth table

- ⌘ Using symbolic states and outputs

 

state	L	R	next state	outputs
LOST	0	0	LOST	F
LOST	-	1	E/G	F
LOST	1	-	E/G	F
A	0	0	B	TL, F
A	0	1	A	TL, F
A	1	-	E/G	TL, F
B	-	0	C	TR, F
B	-	1	A	TR, F
...

Synthesis

- ⌘ 5 states : at least 3 state variables required (X, Y, Z)
- ☒ state assignment (in this case, arbitrarily chosen)

LOST - 000
 E/G - 001
 A - 010
 B - 011
 C - 100

state X,Y,Z	L R	next state X ⁺ , Y ⁺ , Z ⁺	outputs F TR TL
000	00	000	1 0 0
000	01	001	1 0 0
...
010	00	011	1 0 1
010	01	010	1 0 1
010	10	001	1 0 1
010	11	001	1 0 1
011	00	100	1 1 0
011	01	010	1 1 0
...

it now remains
to synthesize
these 6 functions

Synthesis of next state and output functions

state X,Y,Z	inputs L R	next state X ⁺ , Y ⁺ , Z ⁺	outputs F TR TL
000	00	000	1 0 0
000	- 1	001	1 0 0
000	1 -	001	1 0 0
001	00	011	0 0 1
001	- 1	010	0 0 1
001	1 -	010	0 0 1
010	00	011	1 0 1
010	01	010	1 0 1
010	1 -	001	1 0 1
011	- 0	100	1 1 0
011	- 1	010	1 1 0
100	- 0	100	1 1 0
100	- 1	010	1 1 0


e.g.

$$TR = X + YZ$$

$$X^+ = X R' + YZ R' = R' TR$$


Circuit implementation

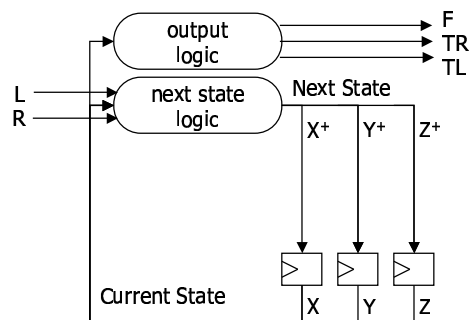⌘ Outputs are a function of the current state only - Moore machine



Don't cares in FSM synthesis

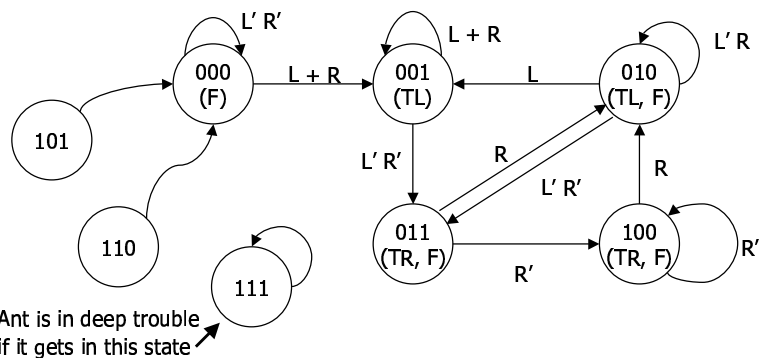- ⌘ What happens to the "unused" states (101, 110, 111)?
- ⌘ They were exploited as don't cares to minimize the logic
 - ☒ if the states can't happen, then we don't care what the functions do
 - ☒ if states do happen, we may be in trouble




State minimization

- ⌘ Fewer states may mean fewer state variables
- ⌘ High-level synthesis may generate many redundant states
- ⌘ Two states are equivalent if they are impossible to distinguish from the outputs of the FSM, i. e., for any input sequence the outputs are the same
- ⌘ Two conditions for two states to be equivalent:
 - ☒ 1) output must be the same in both states
 - ☒ 2) must transition to equivalent states for all input combinations


Ant brain revisited

- ⌘ Any equivalent states?

 



New improved brain

 - ⌘ Merge equivalent B and C states
- ⌘ Behavior is exactly the same as the 5-state brain
- ⌘ We now need only 2 state variables rather than 3




New brain implementation

state	inputs	next state	outputs
X, Y	L R	X^+, Y^+	F TR TL
00	00	00	1 0 0
00	- 1	01	1 0 0
00	1 -	01	1 0 0
01	00	11	0 0 1
01	- 1	01	0 0 1
01	1 -	01	0 0 1
10	00	11	1 0 1
10	0 1	10	1 0 1
10	1 -	01	1 0 1
11	- 0	11	1 1 0
11	- 1	10	1 1 0

  


Mealy vs. Moore machines

 - ⌘ Moore: outputs depend on current state only
- ⌘ Mealy: outputs may depend on current state and current inputs
- ⌘ Our ant brain is a Moore machine
 - ☒ output does not react immediately to input change
- ⌘ We could have specified a Mealy FSM
 - ☒ outputs have immediate reaction to inputs
 - ☒ as inputs change, so does next state, doesn't commit until clocking event



Specifying outputs for a Moore machine

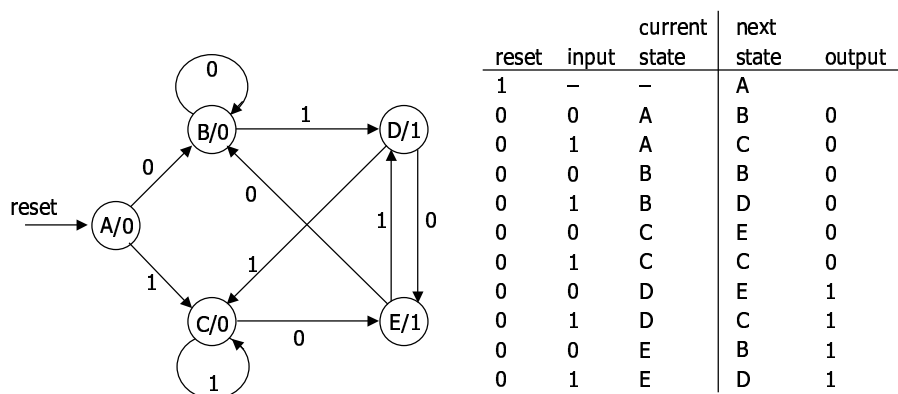- ⌘ Output is only function of state
 - ☒ specify in state bubble in state diagram
 - ☒ example: sequence detector for 01 or 10




Specifying outputs for a Mealy machine

⌘ Output is function of state and inputs

☒ specify output on transition arc between states

 ☒ example: sequence detector for 01 or 10



reset	input	current state	next state	output
1	-	-	A	0
0	0	A	B	0
0	1	A	C	0
0	0	B	B	0
0	1	B	C	1
0	0	C	B	1
0	1	C	C	0

Comparison of Mealy and Moore machines

⌘ Mealy machines tend to have less states

☒ different outputs on arcs (n^2) rather than states (n)

⌘ Moore machines are safer to use



☒ outputs change at clock edge (always one cycle later)

☒ in Mealy machines, input change can cause output change as soon as logic is done – a big problem when two machines are interconnected – asynchronous feedback

⌘ Mealy machines react faster to inputs

☒ react in same cycle – don't need to wait for clock

 
 
☒ in Moore machines, more logic may be necessary to decode state into outputs – more gate delays after



Mealy and Moore examples

⌘ Recognize $A, B = 0, 1$



☒ Mealy or Moore?

  

Mealy and Moore examples (cont'd)

⌘ Recognize $A, B = 1, 0$ then $0, 1$

☒ Mealy or Moore?

  


Registered Mealy machine (really Moore)

⌘ Synchronous (or registered) Mealy machine

- ☒ registered state AND outputs
- ☒ avoids 'glitchy' outputs
- ☒ easy to implement in PLDs

⌘ Moore machine with no output decoding

 - ☒ outputs computed on transition to next state rather than after entering
- ☒ view outputs as expanded state vector



Hardware Description Languages and Sequential Logic

⌘ Flip-flops

- ☒ representation of clocks - timing of state changes
- ☒ asynchronous vs. synchronous

⌘ FSMs


- ☒ structural view (FFs separate from combinational logic)
- ☒ behavioral view (synthesis of sequencers – not in this course)

⌘ Data-paths = data computation (e.g., ALUs, comparators) + registers

- ☒ use of arithmetic/logical operators
- ☒ control of storage elements

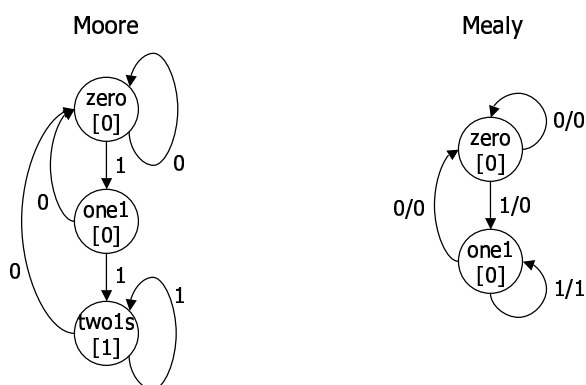Example: reduce-1-string-by-1

⌘ Remove one 1 from every string of 1s on the input



Verilog FSM - Reduce 1s example

⌘ Moore machine


```

`define zero 0
`define one1 1 ← state assignment
`define two1s 2

module reduce (clk, reset, in, out);
  input clk, reset, in;
  output out;
  reg out;
  reg [2:1] state; // state variables
  reg [2:1] next_state;

  always @(posedge clk)
    if (reset) state = `zero;
    else state = next_state;

```

 

Moore Verilog FSM (cont'd)

```

always @(in or state)
    case (state)
    `zero:
    // last input was a zero
    begin
        if (in) next_state = `one1;
        else next_state = `zero;
    end
    `one1:
    // we've seen one 1
    begin
        if (in) next_state = `twos;
        else next_state = `zero;
    end
    `twos:
    // we've seen at least 2 ones
    begin
        if (in) next_state = `twos;
        else next_state = `zero;
    end
    endcase
endmodule

```

crucial to include
all signals that are
input to state determination

note that output
depends only on state

```

always @(state)
    case (state)
    `zero: out = 0;
    `one1: out = 0;
    `twos: out = 1;
    endcase
endmodule

```

Mealy Verilog FSM


```

module reduce (clk, reset, in, out);
    input clk, reset, in;
    output out;
    reg out;
    reg state; // state variables
    reg next_state;

    always @(posedge clk)
        if (reset) state = `zero;
        else state = next_state;

    always @(in or state)
        case (state)
        `zero: // last input was a zero
        begin
            out = 0;
            if (in) next_state = `one;
            else next_state = `zero;
        end
        `one: // we've seen one 1
        if (in) begin
            next_state = `one; out = 1;
        end else begin
            next_state = `zero; out = 0;
        end
        endcase
endmodule

```

 

Synchronous Mealy Machine

```
module reduce (clk, reset, in, out);
  input clk, reset, in;
  output out;
  reg out;
  reg state; // state variables

  always @(posedge clk)
    if (reset) state = `zero;
    else
      case (state)
        `zero: // last input was a zero
          begin
            out = 0;
            if (in) state = `one;
            else state = `zero;
          end
        `one: // we've seen one 1
          if (in) begin
            state = `one; out = 1;
          end else begin
            state = `zero; out = 0;
          end
      endcase
endmodule
```

Sequential logic implementation summary

- ⌘ Models for representing sequential circuits
 - ☒ abstraction of sequential elements
 - ☒ finite state machines and their state diagrams
 - ☒ inputs/outputs
 - ☒ Mealy, Moore, and synchronous Mealy machines
- ⌘ Finite state machine design procedure
 - ☒ deriving state diagram
 - ☒ deriving state transition table
 - ☒ determining next state and output functions
 - ☒ implementing combinational logic
- ⌘ Hardware description languages