

## Overview


- ◆ Last lecture
  - Introduction to finite-state machines
    - ↳ Example: A sequence detector FSM
    - ↳ Example: A vending machine FSM
- ◆ Today
  - A bigger example
    - ↳ Ant-brain FSM

CSE370, Lecture 22

1

## Example: ant brain (special case 1)

- ◆ Left (L) Antenna touching the wall

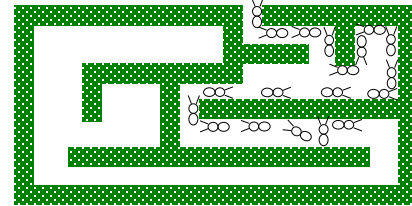


CSE370, Lecture 22

4
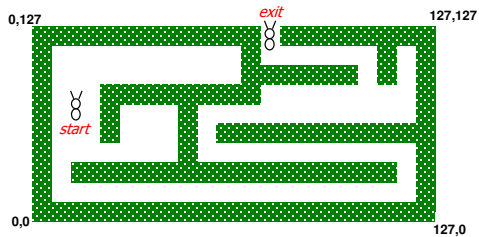
## Ant in a maze

- ◆ Electronic ant, electronic maze
  - Design the ant




CSE370, Lecture 22

2

## Example: ant brain (special case 2)

- ◆ Ant Lost

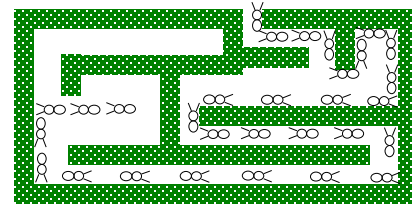


CSE370, Lecture 22

5
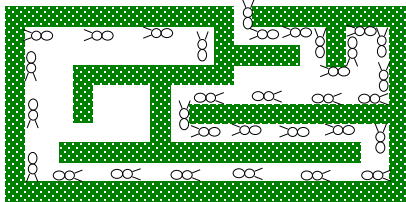
## Example: ant brain (Ward, MIT)

- ◆ Sensors: L and R antennae, 1 if in touching wall
- ◆ Actuators: F - forward step, TL/TR - turn left/right slightly
- ◆ Goal: find way out of maze
- ◆ Strategy: keep the wall on the right




CSE370, Lecture 22

3



## Example: ant brain (special case 2)

- ◆ Ant Lost (another example)

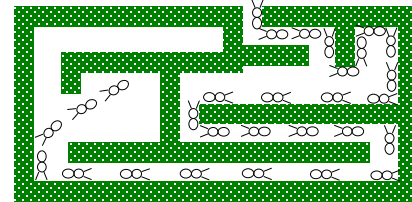

CSE370, Lecture 22

6

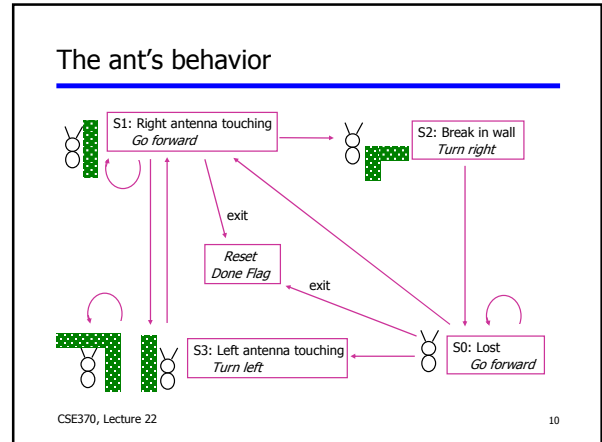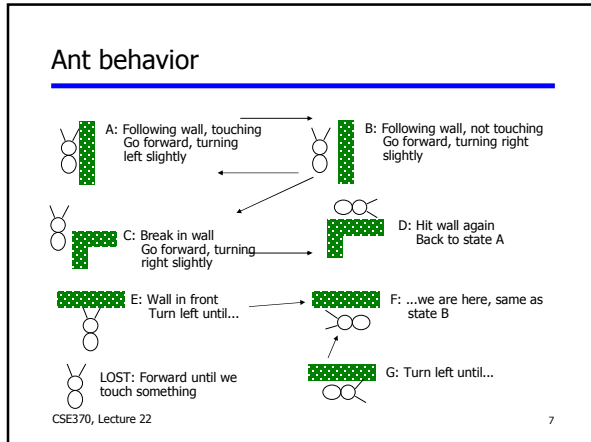

- ### Goal: Find a way out of maze
- ◆ Sensors on L and R antennae
    - Sensor = "1" if touching wall; "0" if not touching wall
      - ☒ L'R' = no wall
      - ☒ L'R = wall on right
      - ☒ LR' = wall on left
      - ☒ LR = wall in front
      - ☒ \*\*\* = exit
  - ◆ Movement:
    - F = forward one step
    - TL = turn left 90 degrees
    - TR = turn right 90 degrees
- CSE370, Lecture 22 8

- ### The maze
- ◆ Virtual maze
    - 128 × 128 grid
      - ☒ Stored in memory
      - ☒ 16384 8-bit words
    - XY is maze addresses
      - ☒ X is the ant's horizontal position (7 bits)
      - ☒ Y is the ant's vertical position (7 bits)
    - Each memory location says
      - ☒ 00000001 = No wall
      - ☒ 00000010 = North wall
      - ☒ 00000100 = West wall
      - ☒ 00001000 = South wall
      - ☒ 00010000 = East wall
      - ☒ 00100000 = Exit
- Can have multiple walls  
Example: 00001100  
⇒ Walls on South and East
- CSE370, Lecture 22 11

- ### Notes & strategy
- ◆ Notes
    - Maze has no islands
    - Corridors are wider than ant
    - Don't worry about startup
    - Assume a Moore machine
    - Assume D flip-flops
  - ◆ Strategy
    - Partition your design into datapath and control
    - Keep the wall on the right
- CSE370, Lecture 22 9

### Where do you start???

# Don't look ahead

CSE370, Lecture 22 12

## What you need

- ◆ An FSM for the ant
  - 3 outputs
    - ↳ Go forward
    - ↳ Turn left
    - ↳ Turn right
- ◆ Two 7-bit registers for  $X$  and  $Y$ 
  - With preload, increment, decrement
- ◆ A register to hold the ant's heading
- ◆ Logic to convert memory data to antennae info

CSE370, Lecture 22

13

## Design the ant-brain FSM

1. State diagram and state-transition table
2. State minimization
3. State assignment (or state encoding)
4. Minimize next-state logic
5. Implement the design

CSE370, Lecture 22

16


## Recommendations

- ◆ 7-bit counters for  $X, Y$ 
  - Move horizontally: Increment or decrement  $X$
  - Move vertically: Increment or decrement  $Y$
- ◆ Shift register for heading
  - N: 0001
  - W: 0010
  - S: 0100
  - E: 1000
  - Rotate right when ant turns right
  - Rotate left when ant turns left
- ◆ Combinational logic for antennae decoder

CSE370, Lecture 22

14


## Step 1a: State diagram

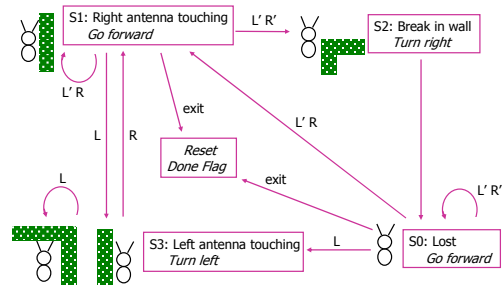

CSE370, Lecture 22

17

## Partition the design

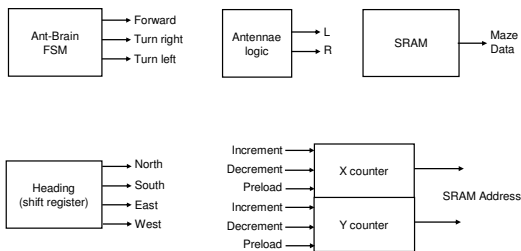

CSE370, Lecture 22

15

## Step 1b: State-transition table

Exit	State	L	R	Next State	Output
1	Reset				
0	S0	0 0	S0	F	
		0 1	S1	F	
		1 0	S3	F	
		1 1	S3	F	
0	S1	0 0	S2	F	
		0 1	S1	F	
		1 0	S3	F	
		1 1	S3	F	
0	S2	0 0	S0	TR	
		0 1	S0	TR	
		1 0	S0	TR	
		1 1	S0	TR	
0	S3	0 0	S1	TL	
		0 1	S1	TL	
		1 0	S3	TL	
		1 1	S3	TL	


CSE370, Lecture 22

18

## Step 2: State minimization

- Two states are equivalent if they cannot be distinguished at the outputs of the FSM
  - The outputs are the same for any input sequence
- Two conditions for two states to be equivalent
  - Outputs must be the same in both states
  - Machine must transition to equivalent states for all inputs
- Any equivalent states in our state diagram?

## Step 5: Implement the design

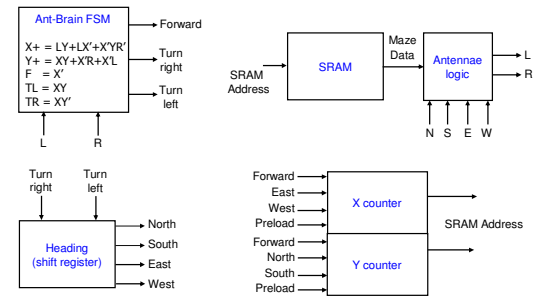


## Step 3: State encoding

Exit	XY	L R	X+ Y+	F TL TR	
1	Reset				
0	0 0	0 0	0 0	1 0 0	S0 ^ 00
	0 0	0 1	0 1	1 0 0	S1 ^ 00
	0 0	1 0	1 1	1 0 0	S2 ^ 10
	0 0	1 1	1 1	1 0 0	S3 ^ 11
0	0 1	0 0	1 0	1 0 0	
	0 1	0 1	0 1	1 0 0	
	0 1	1 0	1 1	1 0 0	
	0 1	1 1	1 1	1 0 0	
0	1 0	0 0	0 0	0 0 1	
	1 0	0 1	0 0	0 0 1	
	1 0	1 0	0 0	0 0 1	
	1 0	1 1	0 0	0 0 1	
0	1 1	0 0	0 1	0 1 0	
	1 1	0 1	0 1	0 1 0	
	1 1	1 0	1 1	0 1 0	
	1 1	1 1	1 1	0 1 0	

## Antennae logic

- Each memory location says
    - 00000001 = No wall
    - 00000010 = North wall (NW)
    - 00000100 = West wall (WW)
    - 00001000 = South wall (SW)
    - 00010000 = East wall (EW)
    - 00100000 = Exit
  - The ant can be heading
    - N: 0001
    - E: 0010
    - S: 0100
    - E: 1000
- Logic for right antennae
- $$R = NW(N + W) + WW(W + S) + SW(S + E) + EW(E + N)$$
- Logic for left antennae
- $$L = NW(N + E) + WW(W + N) + SW(S + W) + EW(E + S)$$
- Gate count:
- 4 2-input ORs
  - 8 2-input ANDs
  - 2 4-input ORs

## Step 4: Minimize the logic

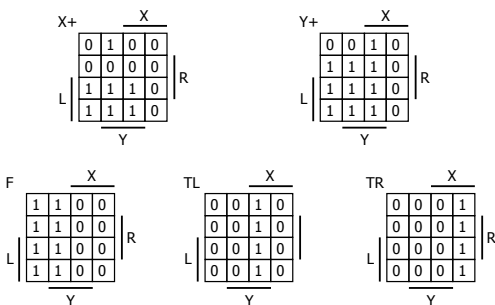

## What we left out...

- Crumbs in cell
  - Ant eats crumbs in every cell it visits
  - Writes crumb file back to SRAM
  - Read crumb file, for future display on monitor
- Need a memory controller
  - A state machine to talk to the SRAM
- Need to deal with startup, exit states