 


## Sequential logic

- Sequential circuits
  - simple circuits with feedback
  - latches
  - edge-triggered flip-flops
- Timing methodologies
  - cascading flip-flops for proper operation
  - clock skew
- Asynchronous inputs
  - metastability and synchronization
- Basic registers
  - shift registers
  - simple counters
- Hardware description languages and sequential logic


## Sequential circuits

- Circuits with feedback
  - outputs =  $f(\text{inputs, past inputs, past outputs})$
  - basis for building "memory" into logic circuits
  - door combination lock is an example of a sequential circuit
    - state is memory
    - state is an "output" and an "input" to combinational logic
    - combination storage elements are also memory



 
## Circuits with feedback

- How to control feedback?
  - what stops values from cycling around endlessly



 
## Simplest circuits with feedback

- Two inverters form a static memory cell
  - will hold value as long as it has power applied



 
- How to get a new value into the memory cell?
  - selectively break feedback path
  - load new value into cell


 
## Memory with cross-coupled gates


- Cross-coupled NOR gates

- similar to inverter pair, with capability to force output to 0 (reset=1) or 1 (set=1)



- Cross-coupled NAND gates



- similar to inverter pair, with capability to force output to 0 (reset=0) or 1 (set=0)

 

CSE370 - VI - Sequential Logic

5


## Timing behavior

  

CSE370 - VI - Sequential Logic

6

## State behavior of R-S latch

 


- Truth table of R-S latch behavior

| S | R | Q        |
|---|---|----------|
| 0 | 0 | hold     |
| 0 | 1 | 0        |
| 1 | 0 | 1        |
| 1 | 1 | unstable |




## Theoretical R-S latch behavior

 


- State diagram
  - states: possible values
  - transitions: changes based on inputs

 
possible oscillation between states 00 and 11



## Observed R-S latch behavior

 

- Very difficult to observe R-S latch in the 1-1 state
  - one of R or S usually changes first
- Ambiguously returns to state 0-1 or 1-0
  - a so-called "race condition"
  - or non-deterministic transition


 


CSE370 - VI - Sequential Logic

9

## R-S latch analysis

- Break feedback path

  

| S | R | Q(t) | Q(t+Δ) |             |
|---|---|------|--------|-------------|
| 0 | 0 | 0    | 0      | hold        |
| 0 | 0 | 1    | 1      |             |
| 0 | 1 | 0    | 0      | reset       |
| 0 | 1 | 1    | 0      |             |
| 1 | 0 | 0    | 1      | set         |
| 1 | 0 | 1    | 1      |             |
| 1 | 1 | 0    | X      | not allowed |
| 1 | 1 | 1    | X      |             |


|      |   | S |   |
|------|---|---|---|
|      |   | 0 | 1 |
| Q(t) | 0 | 0 | X |
|      | 1 | 0 | X |

characteristic equation  
 $Q(t+\Delta) = S + R' Q(t)$

CSE370 - VI - Sequential Logic



10

## Activity: R-S latch using NAND gates

 

  
## Gated R-S latch

- Control when R and S inputs matter
  - otherwise, the slightest glitch on R or S while enable is low could cause change in value stored




 
## Clocks

- Used to keep time
  - wait long enough for inputs (R' and S') to settle
  - then allow to have effect on value stored
- Clocks are regular periodic signals
  - period (time between ticks)
  - duty-cycle (time clock is high between ticks - expressed as % of period)



  
## Clocks (cont'd)

- Controlling an R-S latch with a clock
  - can't let R and S change while clock is active (allowing R and S to pass)
  - only have half of clock period for signal changes to propagate
  - sig half of clock period



 
## Cascading latches

- Connect output of one latch to input of another
- How to stop changes from racing through chain?
  - need to be able to control flow of data from one latch to the next
  - move one latch per clock period
  - have to worry about logic between latches (arrows) that is too fast


 
## Master-slave structure


- Break flow by alternating clocks (like an air-lock)
  - use positive clock to latch inputs into one R-S latch
  - use negative clock to change outputs with another R-S latch
- View pair as one basic unit
  - master-slave flip-flop
  - twice as much logic
  - output changes a few gate delays after the falling edge of clock but does not affect any cascaded flip-flops





## The 1s catching problem

- In first R-S stage of master-slave FF
  - 0-1-0 glitch on R or S while clock is high is "caught" by master stage
  - leads to constraints on logic to be hazard-free

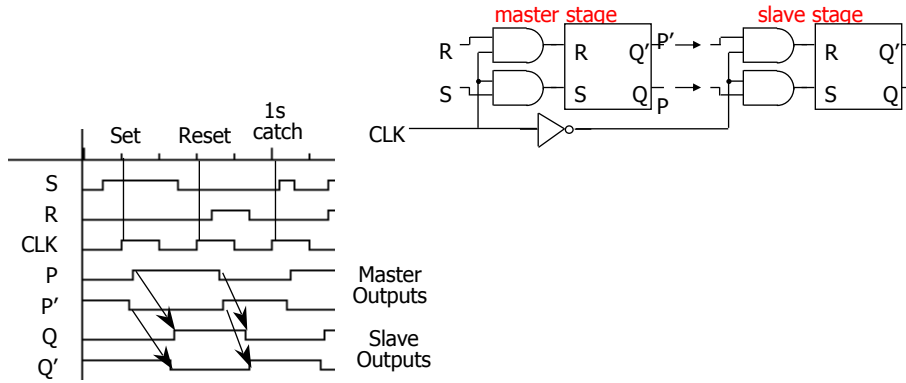


CSE370 - VI - Sequential Logic

17
 
## D flip-flop

- Make S and R complements of each other
  - eliminates 1s catching problem
  - can't just hold previous value (must have new value ready every clock period)
  - value of D just before clock goes low is what is stored in flip-flop
  - can make R-S flip-flop by adding logic to make  $D = S + R'Q$




10 gates

CSE370 - VI - Sequential Logic

18
 
## Edge-triggered flip-flops


- More efficient solution: only 6 gates
  - sensitive to inputs only near edge of clock signal (not while high)



negative edge-triggered D flip-flop (D-FF)

 4-5 gate delays


must respect setup and hold time constraints to successfully capture input



characteristic equation  
 $Q(t+1) = D$


## Edge-triggered flip-flops (cont'd)

- Step-by-step analysis

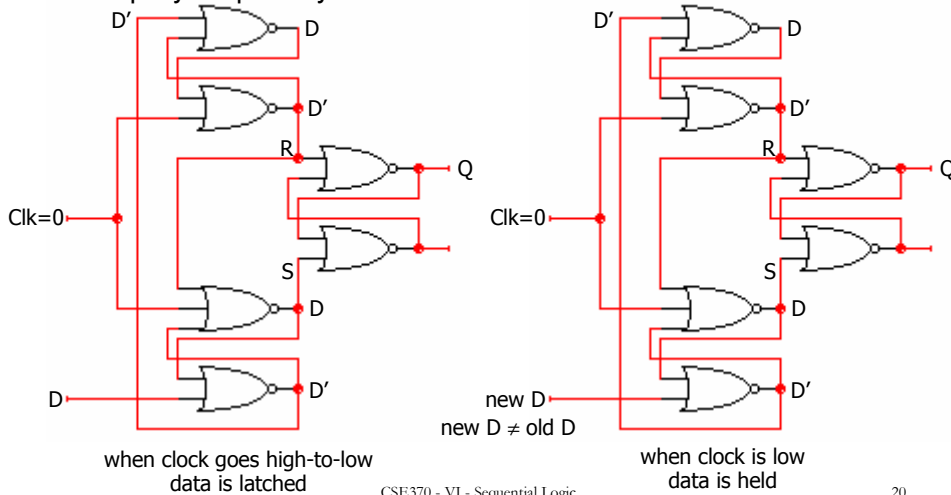
 
## Edge-triggered flip-flops (cont'd)

- Positive edge-triggered
  - inputs sampled on rising edge; outputs change after rising edge
- Negative edge-triggered flip-flops
  - inputs sampled on falling edge; outputs change after falling edge




## Timing methodologies

- Rules for interconnecting components and clocks
  - guarantee proper operation of system when strictly followed
- Approach depends on building blocks used for memory elements
  - we'll focus on systems with edge-triggered flip-flops
    - found in programmable logic devices
  - many custom integrated circuits focus on level-sensitive latches
- Basic rules for correct timing:
  - (1) correct inputs, with respect to time, are provided to the flip-flops
  - (2) no flip-flop changes state more than once per clocking event


## Timing methodologies (cont'd)
 
### ■ Definition of terms

- clock: periodic event, causes state of memory element to change can be rising edge or falling edge or high level or low level
- setup time: minimum time before the clocking event by which the input must be stable ( $T_{su}$ )
- hold time: minimum time after the clocking event until which the input must remain stable ( $T_h$ )






there is a timing "window" around the clocking event during which the input must remain stable and unchanged in order to be recognized

 

CSE370 - VI - Sequential Logic

23

## Comparison of latches and flip-flops

   

behavior is the same unless input changes while the clock is high

CSE370 - VI - Sequential Logic


24

## Comparison of latches and flip-flops (cont'd)

| Type                              | When inputs are sampled   | When output is valid   |
|-----------------------------------|---|--|
| unclocked latch                   | always  | propagation delay from input change                                    |
| level-sensitive latch             | clock high (Tsu/Th around falling edge of clock)                | propagation delay from input change or clock edge (whichever is later) |
| master-slave flip-flop            | clock high (Tsu/Th around falling edge of clock)                | propagation delay from falling edge of clock                           |
| negative edge-triggered flip-flop | clock hi-to-lo transition (Tsu/Th around falling edge of clock) | propagation delay from falling edge of clock                           |
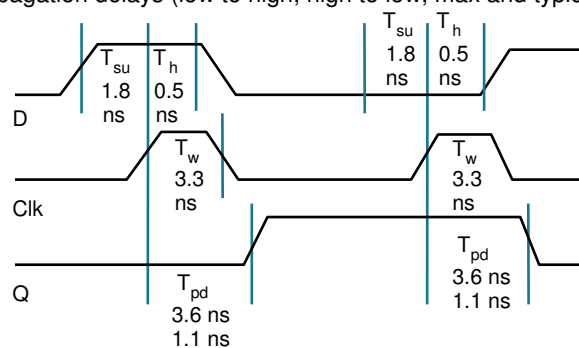
## Typical timing specifications


- Positive edge-triggered D flip-flop
  - setup and hold times
  - minimum clock width
  - propagation delays (low to high, high to low, max and typical)



all measurements are made from the clocking event (the rising edge of the clock)

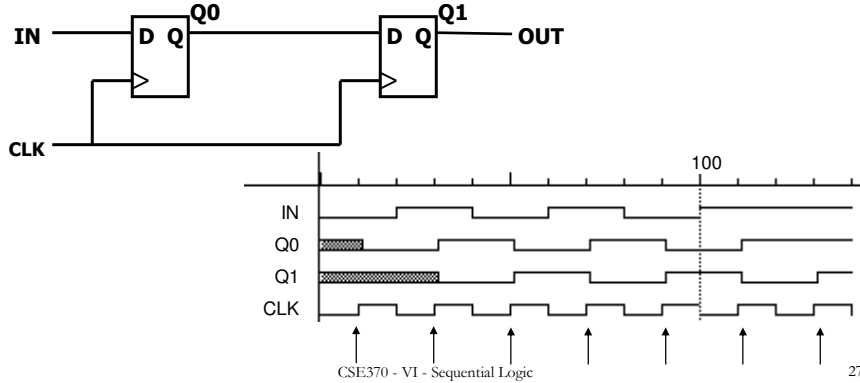
## Cascading edge-triggered flip-flops

- Shift register
  - new value goes into first stage
  - while previous value of first stage goes into second stage
  - consider setup/hold/propagation delays (prop must be > hold)


 
## Cascading edge-triggered flip-flops (cont'd)

- Why this works
  - propagation delays exceed hold times
  - clock width constraint exceeds setup time
  - this guarantees following stage will latch current value before it changes to new value




timing constraints  
guarantee proper  
operation of  
cascaded components

assumes infinitely fast  
distribution of the clock
 
## Clock skew

- The problem
  - correct behavior assumes next state of all storage elements determined by all storage elements at the same time
  - this is difficult in high-performance systems because time for clock to arrive at flip-flop is comparable to delays through logic
  - effect of skew on cascaded flip-flops:



original state:  $IN = 0, Q0 = 1, Q1 = 1$   
due to skew, next state becomes:  $Q0 = 0, Q1 = 0$ , and not  $Q0 = 0, Q1 = 1$

## Summary of latches and flip-flops


- Development of D-FF
  - level-sensitive used in custom integrated circuits
    - can be made with 4 switches
  - edge-triggered used in programmable logic devices
  - good choice for data storage register
- Historically J-K FF was popular but now never used
  - similar to R-S but with 1-1 being used to toggle output (complement state)
  - good in days of TTL/SSI (more complex input function:  $D = J Q' + K' Q$ )
  - not a good choice for PALs/PLAs as it requires 2 inputs
  - can always be implemented using D-FF
- Preset and clear inputs are highly desirable on flip-flops
  - used at start-up or to reset system to a known state

## Metastability and asynchronous inputs


- Clocked synchronous circuits
  - inputs, state, and outputs sampled or changed in relation to a common reference signal (called the clock)
  - e.g., master/slave, edge-triggered
- Asynchronous circuits
  - inputs, state, and outputs sampled or changed independently of a common reference signal (glitches/hazards a major concern)
  - e.g., R-S latch
- Asynchronous inputs to synchronous circuits
  - inputs can change at any time, will not meet setup/hold times
  - dangerous, synchronous inputs are greatly preferred
  - cannot be avoided (e.g., reset signal, memory wait, user input)
 
## Synchronization failure

- Occurs when FF input changes close to clock edge
  - the FF may enter a metastable state – neither a logic 0 nor 1 –
  - it may stay in this state an indefinite amount of time
  - this is not likely in practice but has some probability



 small, but non-zero probability  
that the FF output will get stuck  
in an in-between state




oscilloscope traces demonstrating  
synchronizer failure and eventual  
decay to steady state



 
## Dealing with synchronization failure

- Probability of failure can never be reduced to 0, but it can be reduced
  - (1) slow down the system clock  
this gives the synchronizer more time to decay into a steady state;  
synchronizer failure becomes a big problem for very high speed systems
  - (2) use fastest possible logic technology in the synchronizer  
this makes for a very sharp "peak" upon which to balance
  - (3) cascade two synchronizers  
this effectively synchronizes twice (both would have to fail)



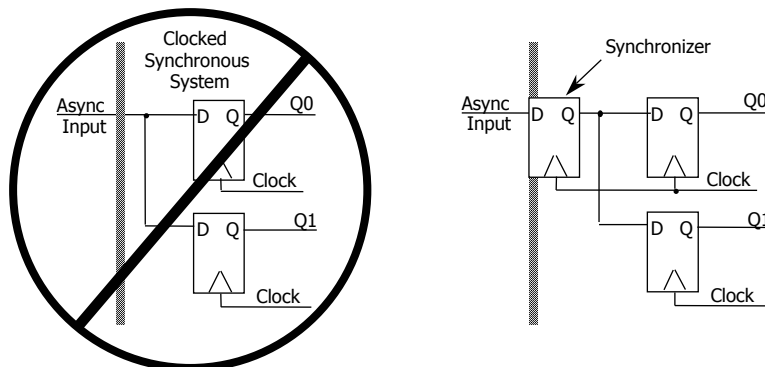
## Handling asynchronous inputs

- Never allow asynchronous inputs to fan-out to more than one flip-flop
  - synchronize as soon as possible and then treat as synchronous signal


 
## Handling asynchronous inputs (cont'd)

- What can go wrong?
  - input changes too close to clock edge (violating setup time constraint)




## Flip-flop features

- Reset (set state to 0) – R
  - synchronous:  $D_{new} = R' \cdot D_{old}$  (when next clock edge arrives)
  - asynchronous: doesn't wait for clock, quick but dangerous
- Preset or set (set state to 1) – S (or sometimes P)
  - synchronous:  $D_{new} = D_{old} + S$  (when next clock edge arrives)
  - asynchronous: doesn't wait for clock, quick but dangerous
- Both reset and preset
  - $D_{new} = R' \cdot D_{old} + S$  (set-dominant)
  - $D_{new} = R' \cdot D_{old} + R'S$  (reset-dominant)
- Selective input capability (input enable or load) – LD or EN
  - multiplexor at input:  $D_{new} = LD' \cdot Q + LD \cdot D_{old}$
  - load may or may not override reset/set (usually R/S have priority)
- Complementary outputs – Q and Q'

 
## Registers

- Collections of flip-flops with similar controls and logic
  - stored values somehow related (for example, form binary value)
  - share clock, reset, and set lines
  - similar logic at each stage
- Examples
  - shift registers
  - counters



 
## Shift register

- Holds samples of input
  - store last 4 input values in sequence
  - 4-bit shift register:


 
## Universal shift register

- Holds 4 values
  - serial or parallel inputs
  - serial or parallel outputs
  - permits shift left or right
  - shift in new values from left or right



clear sets the register contents and output to 0


s1 and s0 determine the shift function

| s0 | s1 | function       |
|----|----|----------------|
| 0  | 0  | hold state     |
| 0  | 1  | shift right    |
| 1  | 0  | shift left     |
| 1  | 1  | load new input |

## Design of universal shift register


- Consider one of the four flip-flops
  - new value at next clock cycle:

| clear | s0 | s1 | new value                                |
|-------|----|----|--|
| 1     | -  | -  | 0  |
| 0     | 0  | 0  | output                                   |
| 0     | 0  | 1  | output value of FF to left (shift right) |
| 0     | 1  | 0  | output value of FF to right (shift left) |
| 0     | 1  | 1  | input                                    |

 

 
## Shift register application

- Parallel-to-serial conversion for serial transmission



 
## Pattern recognizer

- Combinational function of input samples
  - in this case, recognizing the pattern 1001 on the single input signal



 
## Counters

- Sequences through a fixed set of patterns
  - in this case, 1000, 0100, 0010, 0001
  - if one of the patterns is its initial state (by loading or set/reset)




## Activity

- How does this counter work?

 

## Binary counter

- Logic between registers (not just multiplexer)
  - XOR decides when bit should be toggled
  - always for low-order bit,
  - only when first bit is true for second bit,
  - and so on


 


CSE370 - VI - Sequential Logic

45
  
## Four-bit binary synchronous up-counter

- Standard component with many applications
  - positive edge-triggered FFs w/ synchronous load and clear inputs
  - parallel load data from D, C, B, A
  - enable inputs: must be asserted to enable counting
  - RCO: ripple-carry out used for cascading counters
    - high when counter is in its highest state 1111
    - implemented using an AND gate




Sequential Logic

46
 
## Offset counters


- Starting offset counters – use of synchronous load

- e.g., 0110, 0111, 1000, 1001, 1010, 1011, 1100, 1101, 1111, 0110, . . .



- Ending offset counter – comparator for ending value

 - e.g., 0000, 0001, 0010, ..., 1100, 1101, 0000



- Combinations of the above (start and stop value)

## Hardware Description Languages and Sequential Logic

- Flip-flops
  - representation of clocks - timing of state changes
  - asynchronous vs. synchronous
- Shift registers
- Simple counters



## Flip-flop in Verilog

- Use always block's sensitivity list to wait for clock edge

```
module dff (clk, d, q);  
  
    input  clk, d;  
    output q;  
    reg   q;  
  
    always @(posedge clk)  
        q = d;  
  
endmodule
```

## More Flip-flops

- Synchronous/asynchronous reset/set
  - single thread that waits for the clock
  - three parallel threads – only one of which waits for the clock

### Synchronous

```
module dff (clk, s, r, d, q);  
    input clk, s, r, d;  
    output q;  
    reg q;  
  
    always @(posedge clk)  
        if (r)    q = 1'b0;  
        else if (s) q = 1'b1;  
        else     q = d;  
  
endmodule
```

### Asynchronous

```
module dff (clk, s, r, d, q);  
    input clk, s, r, d;  
    output q;  
    reg q;  
  
    always @(posedge r)  
        q = 1'b0;  
    always @(posedge s)  
        q = 1'b1;  
    always @(posedge clk)  
        q = d;  
  
endmodule
```

## Incorrect Flip-flop in Verilog

- Use always block's sensitivity list to wait for clock to change

```
module dff (clk, d, q);  
    input  clk, d;  
    output q;  
    reg   q;  
  
    always @(clk)  
        q = d;  
  
endmodule
```

Not correct! Q will change whenever the clock changes, not just on an edge.

## Blocking and Non-Blocking Assignments

- Blocking assignments ( $X=A$ )
  - completes the assignment before continuing on to next statement
- Non-blocking assignments ( $X<=A$ )
  - completes in zero time and doesn't change the value of the target until a blocking point (delay/wait) is encountered
- Example: swap

```
always @(posedge CLK)  
begin  
    temp = B;  
    B = A;  
    A = temp;  
end
```

```
always @(posedge CLK)  
begin  
    A <= B;  
    B <= A;  
end
```

## Register-transfer-level (RTL) Assignment

- Non-blocking assignment is also known as an RTL assignment
  - if used in an always block triggered by a clock edge
  - all flip-flops change together

```
// B,C,D all get the value of A
always @(posedge clk)
begin
    B = A;
    C = B;
    D = C;
end
```

```
// implements a shift register too
always @(posedge clk)
begin
    B <= A;
    C <= B;
    D <= C;
end
```

## Mobius Counter in Verilog

```
initial
begin
    A = 1'b0;
    B = 1'b0;
    C = 1'b0;
    D = 1'b0;
end

always @(posedge clk)
begin
    A <= ~D;
    B <= A;
    C <= B;
    D <= C;
end
```

## Binary Counter in Verilog

```
module binary_counter (clk, c8, c4, c2, c1);  
    input clk;  
    output c8, c4, c2, c1;  
  
    reg [3:0] count;  
  
    initial begin  
        count = 0;  
    end  
  
    always @(posedge clk) begin  
        count = count + 4'b0001;  
    end  
  
    assign c8 = count[3];  
    assign c4 = count[2];  
    assign c2 = count[1];  
    assign c1 = count[0];  
  
endmodule
```

```
module binary_counter (clk, c8, c4, c2, c1, rco);  
    input clk;  
    output c8, c4, c2, c1, rco;  
  
    reg [3:0] count;  
    reg rco;  
  
    initial begin . . . end  
  
    always @(posedge clk) begin . . . end  
  
    assign c8 = count[3];  
    assign c4 = count[2];  
    assign c2 = count[1];  
    assign c1 = count[0];  
    assign rco = (count == 4b'1111);  
  
endmodule
```

## Sequential logic summary

- Fundamental building block of circuits with state
  - latch and flip-flop
  - R-S latch, R-S master/slave, D master/slave, edge-triggered D flip-flop
- Timing methodologies
  - use of clocks
  - cascaded FFs work because propagation delays exceed hold times
  - beware of clock skew
- Asynchronous inputs and their dangers
  - synchronizer failure: what it is and how to minimize its impact
- Basic registers
  - shift registers
  - counters
- Hardware description languages and sequential logic