

## Finite state machine optimization

- State minimization
  - fewer states require fewer state bits
  - fewer bits require fewer logic equations
- Encodings: state, inputs, outputs
  - state encoding with fewer bits has fewer equations to implement
    - however, each may be more complex
  - state encoding with more bits (e.g., one-hot) has simpler equations
    - complexity directly related to complexity of state diagram
  - input/output encoding may or may not be under designer control


## Algorithmic approach to state minimization

- Goal – identify and combine states that have equivalent behavior
- Equivalent states:
  - same output
  - for all input combinations, states transition to same or equivalent states
- Algorithm sketch
  - 1. place all states in one set
  - 2. initially partition set based on output behavior
  - 3. successively partition resulting subsets based on next state transitions
  - 4. repeat (3) until no further partitioning is required
    - states left in the same set are equivalent
  - polynomial time procedure

## State minimization example

- Sequence detector for 010 or 110

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S0	S1	S2	0	0
0	S1	S3	S4	0	0
1	S2	S5	S6	0	0
00	S3	S0	S0	0	0
01	S4	S0	S0	1	0
10	S5	S0	S0	0	0
11	S6	S0	S0	1	0

 

Winter 2005

CSE370 - X - Working with Sequential Logic

3

## Method of successive partitions

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S0	S1	S2	0	0
0	S1	S3	S4	0	0
1	S2	S5	S6	0	0
00	S3	S0	S0	0	0
01	S4	S0	S0	1	0
10	S5	S0	S0	0	0
11	S6	S0	S0	1	0

( S0 S1 S2 S3 S4 S5 S6 )

S1 is equivalent to S2

( S0 S1 S2 S3 S5 ) ( S4 S6 )

S3 is equivalent to S5

( S0 S3 S5 ) ( S1 S2 ) ( S4 S6 )

S4 is equivalent to S6

( S0 ) ( S3 S5 ) ( S1 S2 ) ( S4 S6 )

Winter 2005


CSE370 - X - Working with Sequential Logic

4

## Minimized FSM


- State minimized sequence detector for 010 or 110

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S0	S1'	S1'	0	0
0 + 1	S1'	S3'	S4'	0	0
X0	S3'	S0	S0	0	0
X1	S4'	S0	S0	1	0

 

## More complex state minimization

- Multiple input example

 


inputs here

present state	next state				output
	00	01	10	11	
S0	S0	S1	S2	S3	1
S1	S0	S3	S1	S4	0
S2	S1	S3	S2	S4	1
S3	S1	S0	S4	S5	0
S4	S0	S1	S2	S5	1
S5	S1	S4	S0	S5	0

symbolic state transition table
 
## Minimized FSM

- Implication chart method
  - cross out incompatible states based on outputs
  - then cross out more cells if indexed chart entries are already crossed out



present state	next state				output
	00	01	10	11	
S0'	S0'	S1	S2	S3'	1
S1	S0'	S3'	S1	S3'	0
S2	S1	S3'	S2	S0'	1
S3'	S1	S0'	S0'	S3'	0

minimized state table  
(S0==S4) (S3==S5)

## Minimizing incompletely specified FSMs


- Equivalence of states is transitive when machine is fully specified
- But its not transitive when don't cares are present

e.g.,	state	output	
	S0	- 0	S1 is compatible with both S0 and S2
	S1	1 -	but S0 and S2 are incompatible
	S2	- 1	

- No polynomial time algorithm exists for determining best grouping of states into equivalent sets that will yield the smallest number of final states

## Minimizing states may not yield best circuit

 - Example: edge detector - outputs 1 when input goes from 0 to 1





X	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>1</sub> <sup>+</sup>	Q <sub>0</sub> <sup>+</sup>
0	0	0	0	0
0	0	1	0	0
0	1	1	0	0
1	0	0	0	1
1	0	1	1	1
1	1	1	1	1
-	1	0	0	0

$$Q_1^+ = X (Q_1 \text{ xor } Q_0)$$

$$Q_0^+ = X Q_1' Q_0'$$
  
## Another implementation of edge detector

- "Ad hoc" solution - not minimal but cheap and fast



## State assignment

- Choose bit vectors to assign to each “symbolic” state
  - with  $n$  state bits for  $m$  states there are  $2^n! / (2^n - m)!$   
[ $\log n \leq m \leq 2^n$ ]
  - $2^n$  codes possible for 1st state,  $2^n - 1$  for 2nd,  $2^n - 2$  for 3rd, ...
  - huge number even for small values of  $n$  and  $m$ 
    - intractable for state machines of any size
    - heuristics are necessary for practical solutions
  - optimize some metric for the combinational logic
    - size (amount of logic and number of FFs)
    - speed (depth of logic and fanout)
    - dependencies (decomposition)

## State assignment strategies

- Possible strategies
  - sequential – just number states as they appear in the state table
  - random – pick random codes
  - one-hot – use as many state bits as there are states (bit=1 → state)
  - output – use outputs to help encode states
  - heuristic – rules of thumb that seem to work in most cases
- No guarantee of optimality – another intractable problem

## One-hot state assignment

- Simple
  - easy to encode
  - easy to debug
- Small logic functions
  - each state function requires only predecessor state bits as input
- Good for programmable devices
  - lots of flip-flops readily available
  - simple functions with small support (signals its dependent upon)
- Impractical for large machines
  - too many states require too many flip-flops
  - decompose FSMs into smaller pieces that can be one-hot encoded
- Many slight variations to one-hot
  - one-hot + all-0


## Heuristics for state assignment

- Adjacent codes to states that share a common next state

- group 1's in next state map

I	Q	Q <sup>+</sup>	O
i	a	c	j
i	b	c	k

$$c = i * a + i * b$$

 


- Adjacent codes to states that share a common ancestor state

- group 1's in next state map

I	Q	Q <sup>+</sup>	O
i	a	b	j
k	a	c	l

$$b = i * a$$

$$c = k * a$$

 

- Adjacent codes to states that have a common output behavior


- group 1's in output map

I	Q	Q <sup>+</sup>	O
i	a	b	j
i	c	d	j

$$j = i * a + i * c$$

$$b = i * a$$

$$d = i * c$$

 

## General approach to heuristic state assignment

- All current methods are variants of this
  - 1) determine which states “attract” each other (weighted pairs)
  - 2) generate constraints on codes (which should be in same cube)
  - 3) place codes on Boolean cube so as to maximize constraints satisfied (weighted sum)
- Different weights make sense depending on whether we are optimizing for two-level or multi-level forms
- Can't consider all possible embeddings of state clusters in Boolean cube
  - heuristics for ordering embedding
  - to prune search for best embedding
  - expand cube (more state bits) to satisfy more constraints

## Output-based encoding

- Reuse outputs as state bits - use outputs to help distinguish states
  - why create new functions for state bits when output can serve as well
  - fits in nicely with synchronous Mealy implementations

Inputs			Present State	Next State	Outputs		
C	TL	TS			ST	H	F
0	-	-	HG	HG	0	00	10
-	0	-	HG	HG	0	00	10
1	1	-	HG	HY	1	00	10
-	-	0	HY	HY	0	01	10
-	-	1	HY	FG	1	01	10
1	0	-	FG	FG	0	10	00
0	-	-	FG	FY	1	10	00
-	1	-	FG	FY	1	10	00
-	-	0	FY	FY	0	10	01
-	-	1	FY	HG	1	10	01

$$\begin{aligned}
 HG &= ST' H1' H0' F1 F0' + ST H1 H0' F1' F0 \\
 HY &= ST H1' H0' F1 F0' + ST' H1' H0 F1 F0' \\
 FG &= ST H1' H0 F1 F0' + ST' H1 H0' F1' F0' \\
 FY &= ST H1 H0' F1' F0' + ST' H1 H0' F1' F0
 \end{aligned}$$

Output patterns are unique to states, we do not need ANY state bits – implement 5 functions (one for each output) instead of 7 (outputs plus 2 state bits)




## Current state assignment approaches

- For tight encodings using close to the minimum number of state bits
  - best of 10 random seems to be adequate (averages as well as heuristics)
  - heuristic approaches are not even close to optimality
  - used in custom chip design
- One-hot encoding
  - easy for small state machines
  - generates small equations with easy to estimate complexity
  - common in FPGAs and other programmable logic
- Output-based encoding
  - ad hoc - no tools
  - most common approach taken by human designers
  - yields very small circuits for most FSMs

## State machines and PLDs

- Moore and synchronous Mealy most common
- Output-directed state assignment
  - All outputs already have FFs and are fed back in as input to logic array
  - Use these as part of the state register
  - Add only as many extra states bits as needed to make all state codes unique

Functional Logic Diagram for PALC22V10D

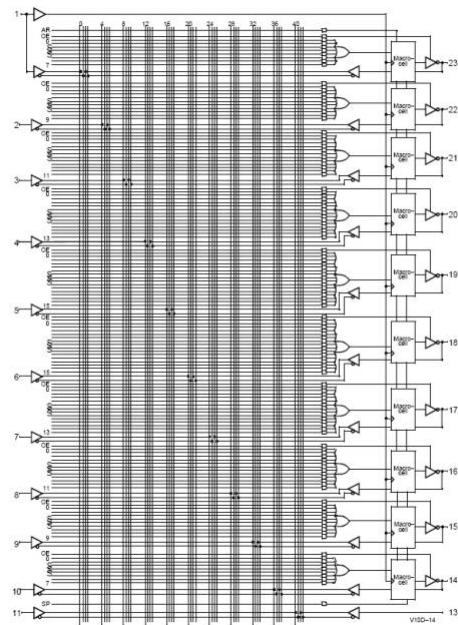

## State assignment in processors

- Instruction register can be viewed as part of state register
- Basic cycle
  - Fetch, decode, execute
- Consider concatenation of IR and controller state
  - {controller\_state, IR[31:26]}
  - Controller\_state = fetch, decode, execute1, execute2, ...
  - Fetch and decode states don't care about IR[31:26]
    - {fetch, 6'bxxxxxx}
    - {decode, 6'bxxxxxx}
  - Full state is op\_code in execute1, execute2, ...
    - {execute1, ALU}
    - {execute1, LW}
    - {execute2, LW}
    - {execute3, LW}

## Sequential logic optimization summary

- State minimization
  - straightforward in fully-specified machines
  - computationally intractable, in general (with don't cares)
- State assignment
  - many heuristics
  - best-of-10-random just as good or better for most machines
  - output encoding can be attractive (especially for PAL implementations)