 


# CSE 370 Spring 2006 Introduction to Digital Design

## Lecture 12: Adders



### Last Lecture

- PLAs and PALs

### Today


- Adders

## Binary full adder

### 1-bit full adder

- Computes sum, carry-out
  - Carry-in allows cascaded adders
- Sum = Cin xor A xor B
- Cout = ACin + BCin + AB

A	B	C <sub>in</sub>	S	C <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

## Full adder: Alternative Implementation


### Multilevel logic

- Slower
- Less gates
  - 2 XORs, 2 ANDs, 1 OR


$$\text{Sum} = (A \oplus B) \oplus \text{Cin}$$

$$\begin{aligned} \text{Cout} &= AC_{in} + BC_{in} + AB \\ &= (A \oplus B)C_{in} + AB \end{aligned}$$

A	B	C <sub>in</sub>	S	C <sub>out</sub>	C <sub>out</sub>
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	0	1	1
1	0	0	1	0	0
1	0	1	0	1	1
1	1	0	0	1	1
1	1	1	1	1	1

 


## 2-bit ripple-carry adder

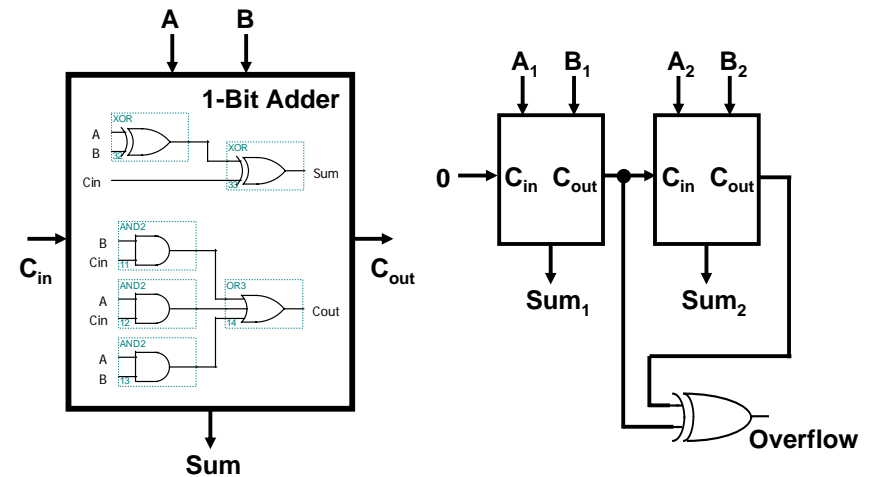
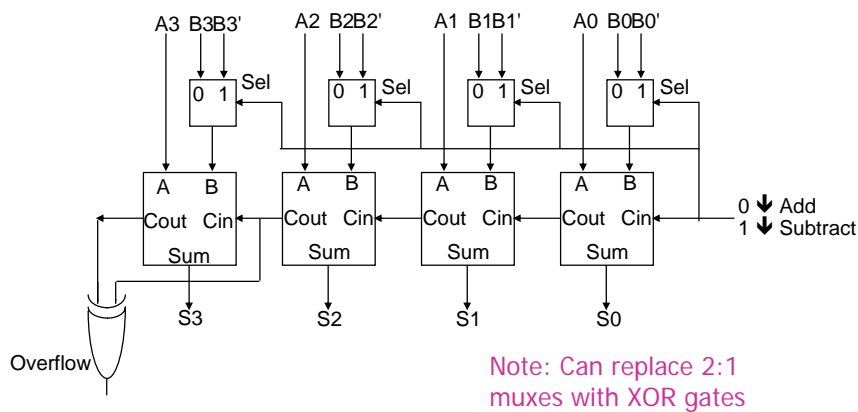
# 4-bit ripple-carry adder/subtractor


- Circuit adds or subtracts

- 2s complement:  $A - B = A + (-B) = A + B' + 1$



# Problem: Ripple-carry delay

- Carry propagation limits adder speed

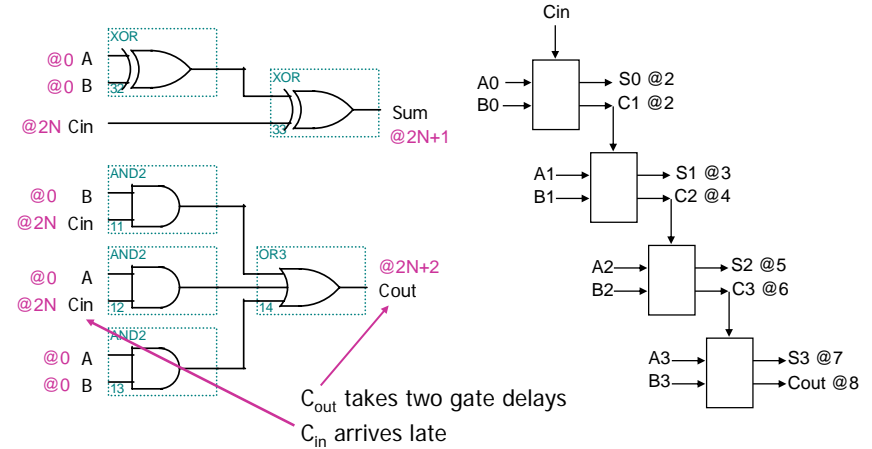


# Ripple-carry adder timing diagram

- Critical delay

- Carry propagation

- 1111 + 0001 = 10000 is worst case

 

# One solution: Carry lookahead logic

- Compute all the carries in parallel

- Derive carries from the data inputs

- Not from intermediate carries

- Use two-level logic

- Compute all sums in parallel

- Cascade simple adders to make large adders


- Speed improvement

- 16-bit ripple-carry: ~32 gate delays


- 16-bit carry-lookahead: ~8 gate delays

- Issues

- Complex combinational logic

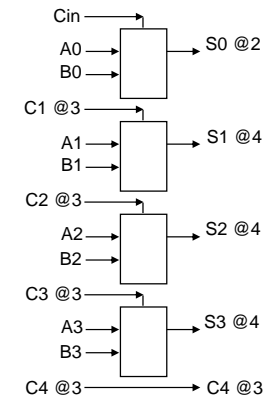

## Full adder again

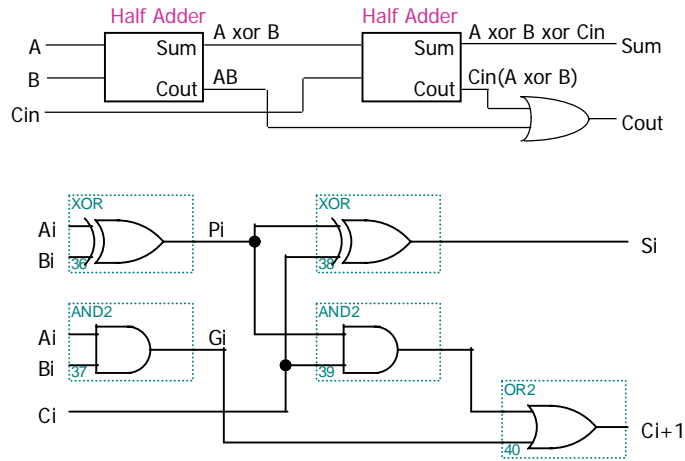

## Carry-lookahead logic

- Carry **generate**:  $G_i = A_i B_i$ 
  - Generate carry when  $A = B = 1$
- Carry **propagate**:  $P_i = A_i \text{ xor } B_i$ 
  - Propagate carry-in to carry-out when  $(A \text{ xor } B) = 1$
- Sum and Cout in terms of generate/propagate:


$$\begin{aligned} \blacksquare S_i &= A_i \text{ xor } B_i \text{ xor } C_i \\ &= P_i \text{ xor } C_i \end{aligned}$$

$$\begin{aligned} \blacksquare C_{i+1} &= A_i B_i + C_i (A_i \text{ xor } B_i) \\ &= G_i + C_i P_i \end{aligned}$$


## Carry-lookahead logic (cont'd)

- Re-express the carry logic in terms of G and P
  - $C_1 = G_0 + P_0 C_0$
  - $C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0$
  - $C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$
  - $C_4 = G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$
- Implement each carry equation with two-level logic
  - Derive intermediate results directly from inputs
    - Rather than from carries
  - Allows "sum" computations to proceed in parallel
 
## Implementing the carry-lookahead logic




 Logic complexity increases with adder size



 
# Cascaded carry-lookahead adder

- 4 four-bit adders with internal carry lookahead
- Second level lookahead extends adder to 16 bits


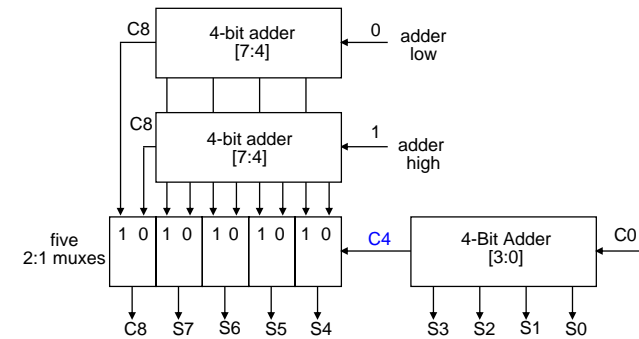
# Another solution: Carry-select adder


- Redundant hardware speeds carry calculation
- Compute two high-order sums while waiting for carry-in (C4)
- Select correct high-order sum after receiving C4



# We've finished combinational logic...

- What you should know
  - Two's complement arithmetic
  - Truth tables
  - Basic logic gates
  - Schematic diagrams
  - Timing diagrams
  - Minterm and maxterm expansions (canonical, minimized)
  - de Morgan's theorem
  - AND/OR to NAND/NOR logic conversion
  - K-maps, logic minimization, don't cares
  - Multiplexers/demultiplexers
  - PLAs/PALs
  - ROMs
  - Adders

# Sequential versus combinational

 

Apply fixed inputs A, B  
 Wait for clock edge  
 Observe C  
 Wait for another clock edge  
 Observe C again


Combinational: C will stay the same  
 Sequential: C may be different

# Sequential logic


- Two types
  - Synchronous = clocked
  - Asynchronous = self-timed
- Has state
  - State = memory
- Employs feedback
- Assumes steady-state signals
  - Signals are valid after they have settled
  - State elements hold their settled output values
 
# Sequential versus combinational (again)

- Combinational systems are memoryless
  - Outputs depend only on the present inputs




 - Sequential systems have memory
  - Outputs depend on the present and the previous inputs



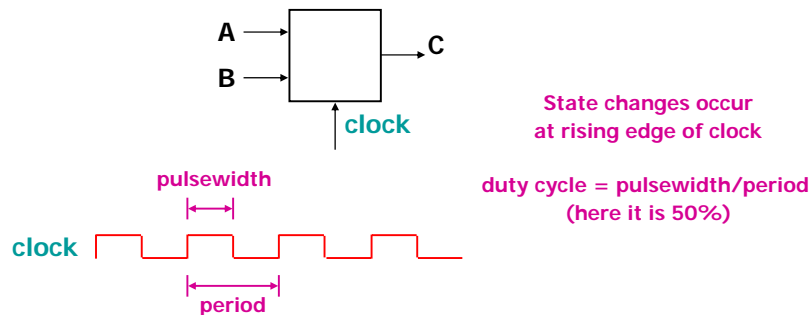
# Synchronous sequential systems

- Memory holds a system's state
  - Changes in state occur at specific times
  - A periodic signal times or clocks the state changes
  - The clock period is the time between state changes


 
# Steady-state abstraction

- Outputs retain their settled values
  - The clock period must be long enough for all voltages to settle to a steady state before the next state change



## Example: A sequential system

- Door combination lock
  - Enter 3 numbers in sequence and the door opens
  - If there is an error the lock must be reset
  - After the door opens the lock must be reset
  - Inputs: Sequence of numbers, reset
  - Outputs: Door open/close
  - Memory: Must remember the combination