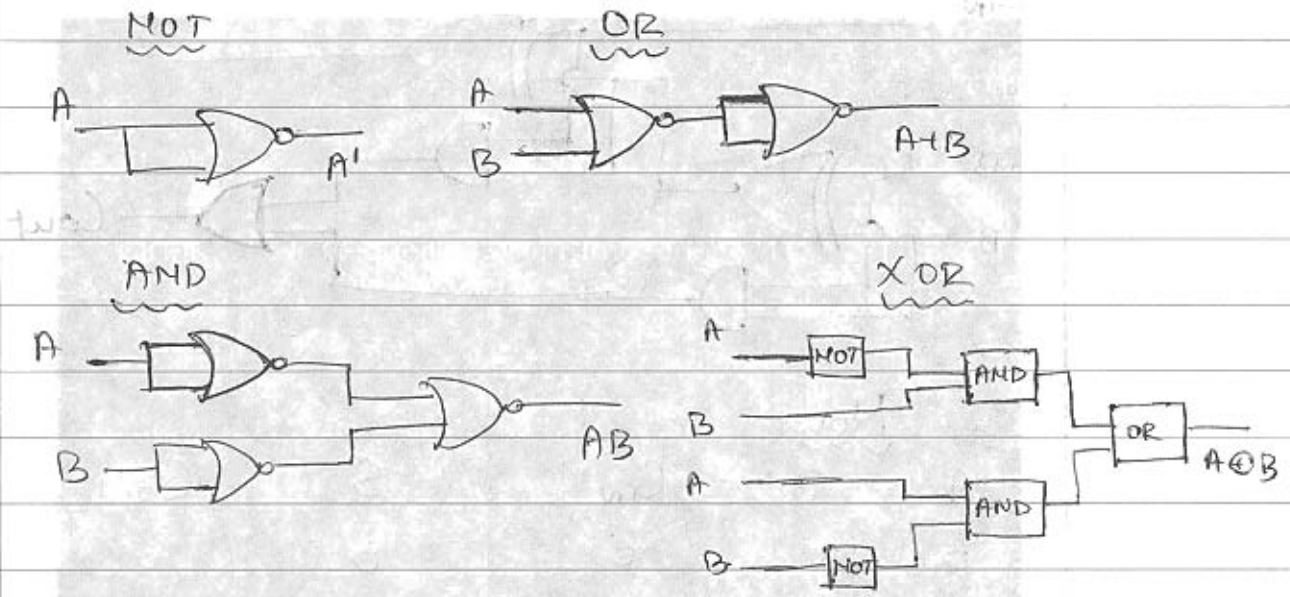


HOMEWORK 2 - DUE DATE OCT 10

415


SOLUTIONS

2.13) (I) NOR Gate:



XOR Gate is not UNIVERSAL GATE since it cannot be used to implement all basic gates like NOT, AND, OR


(II) NAND Gate:

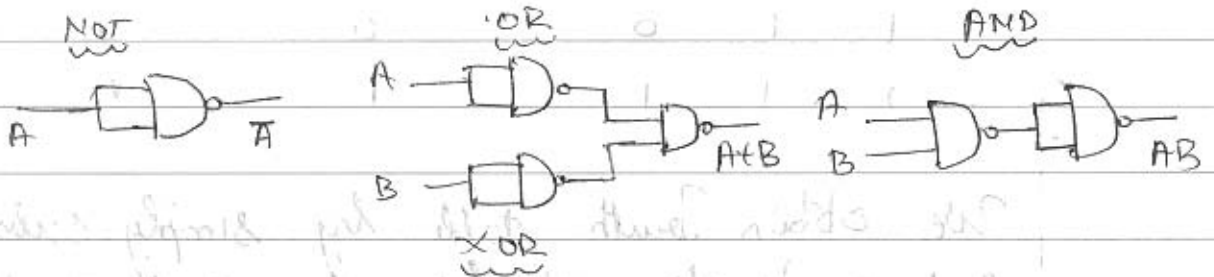

Can be constructed with above blocks as done for NOR Gate.

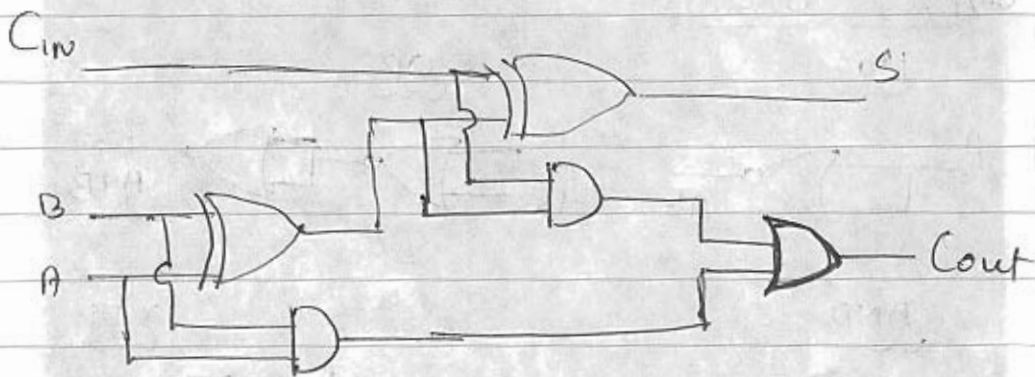2.14)

Convert the block diagram in book in terms of gate. Let the 3rd i/p be named as C_{in} .



Now

A	B	C_{in}	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

We obtain truth table by simply substituting each combination of bit values and walking through circuit to find o/p.
Thus it is same as a FULL ADDER

2.15)

No. $[C(A+B) + B(A+C)]$ (2) (3)
 In two level implementation we get a Max. delay of 3 units to get sum o/p.

whereas in cascaded HALF adder implementation we get

2 unit delay to get sum o/p

[NOTE: Assuming 1 unit delay for each gate]

2.17) (c)

$$\begin{aligned}
 f &= Y'Z + X'YZ + XYZ \\
 &= Y'Z + YZ(X+X') \\
 &= Y'Z + YZ \quad [X+X'=1] \\
 &= Z(Y+Y') \\
 &= Z \quad [Y+Y'=1]
 \end{aligned}$$

(e)

$$\begin{aligned}
 f &= X + XYZ + X'YZ + X'Y + WX + WX' \\
 &= X + YZ(X+X') + X'Y + W(X+X') \quad [X+X'=1] \\
 f &= X + YZ + X'Y + W
 \end{aligned}$$

$(A+B)(A+C) = A^2 + AB + AC + BC = A + AB + AC + BC$

(a, b, c, d, e, f, g, h, i, j, k, l, m, n, o, p, q, r, s, t, u, v, w, x, y, z)

(A, B, C, D, E, F, G, H, I, J, K, L, M, N, O, P, Q, R, S, T, U, V, W, X, Y, Z)


(A+B)(A+C) = A^2 + AB + AC + BC = A + AB + AC + BC

(A+B)(A+C) = A^2 + AB + AC + BC = A + AB + AC + BC

2.18)

$$f = (AD + A'C) [B'(C+BD)']$$


(a)

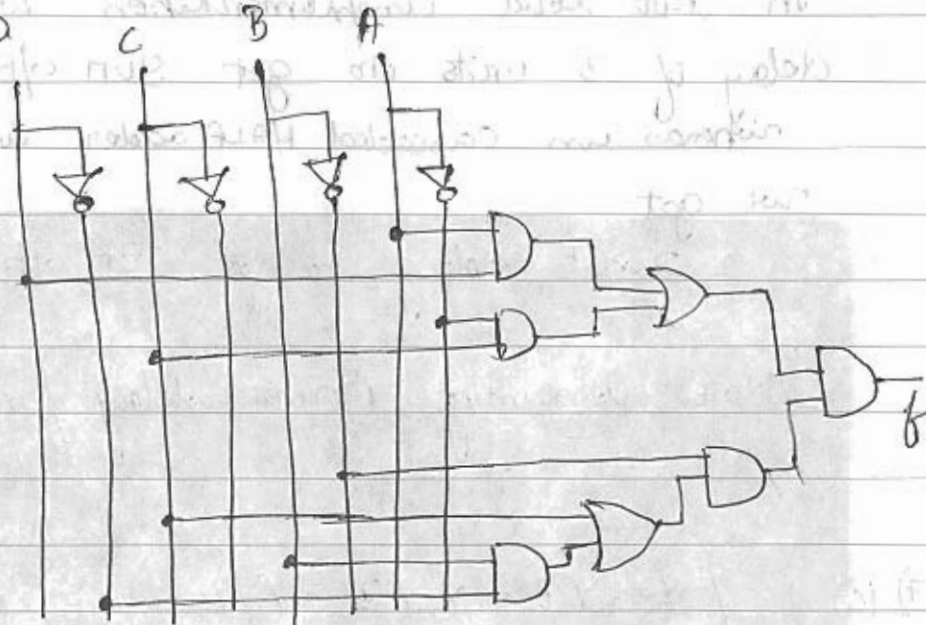

(b)

$$f = (AD + A'C) B'C$$

$$f = AB'CD + A'B'C$$

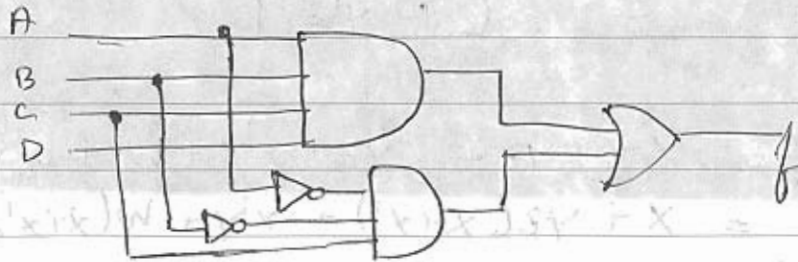

2.19) (a)

$$F = A'B'C'D' + A'B'C'D + A'B'CD' + A'B'CD + AB'C'D' + AB'C'D + AB'CD' + ABCD$$

(b)

$$F = \sum m(0, 1, 2, 7, 8, 9, 10, 15)$$

$$= \prod M(3, 4, 5, 6, 11, 12, 13, 14)$$

$$= (A+B+C+D')(A+B'+C+D)(A+B'+C+D')(A+B'+C+D)$$

$$(A'+B+C+D')(A'+B'+C+D)(A'+B'+C+D)$$

(c) \bar{F} = Take complement of F in Max terms to get \bar{F} as MIN terms and apply DeMORGAN'S LAW

$$\bar{F} = A'B'CD + A'BC'D + A'BC'D + A'BCD' + AB'CD + ABC'D + ABC'D + ABCD'$$

$$\bar{F} = \sum m(3, 4, 5, 6, 11, 12, 13, 14)$$

(d) \bar{F} = Take complement of F in Min term to get \bar{F} as Max Term and use DeMORGAN'S LAW.

$$\bar{F} = (A+B+C+D)(A+B+C+D')(A+B+C'+D)(A+B'+C'+D')(A'+B+C+D)(A'+B+C+D')(A'+B'+C'+D)(A'+B'+C'+D')$$

2.21) $f = AB + B'C' + AC'$

(a) $= AB(C+C') + B'C'(A+A') + AC'(B+B')$

$\therefore f = ABC + ABC' + AB'C' + A'B'C'$

$f = \sum m(0, 4, 6, 7)$

(b) $\bar{F} = (A'+B'+C')(A'+B'+C)(A'+B+C)(A+BC)$
 $= \prod M(0, 4, 6, 7)$

2.22) Simplify $F = A'B'C + AD + AC$ (2)

(a) $F = A'B'C(D+D') + AD(B+B') + AC(B+B')$

$= A'B'CD + A'B'CD' + ADB + ADB' + ACB + ACB'$

$= A'B'CD + A'B'CD' + ADB(C+C') + ADB'(C+C') + ACB(D+D') + ACB'(D+D')$

$F = A'BCD + A'B'CD' + ABC'D + AB'CD + AB'C'D + ABCD' + AB'CD'$


Simplify $F = \sum m(6, 9, 10, 11, 13, 14, 15)$

$F = \sum m(6, 9, 10, 11, 13, 14, 15)$


(b) $F' = [A'B'C + AD + AC]$

$F' = (A+B'+C')(A'+D')(A'+C')$

F as NAND

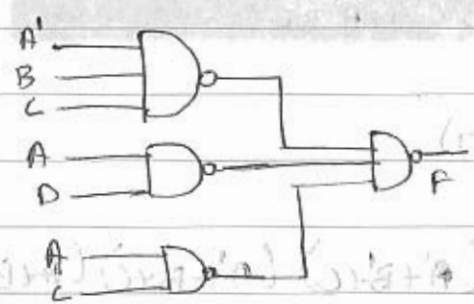


F as NOR

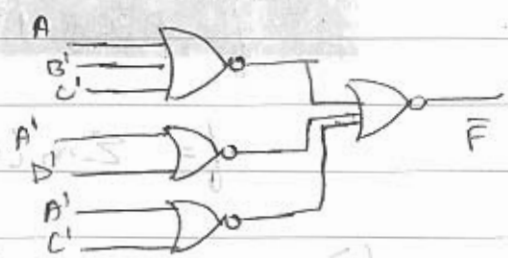

BOOLEAN CUBE

$$f = \sum m (1, 2, 4, 5)$$

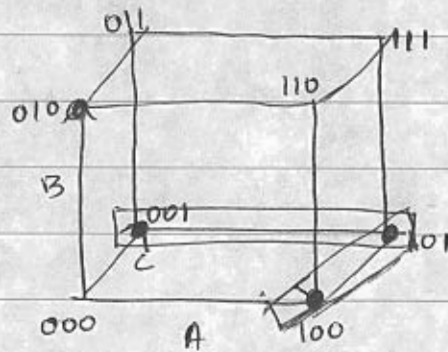

$$f = AB' + B'C + A'BC'$$