

# Lecture 5: 2-Level Logic and Canonical Forms


CSE 370, Autumn 2007  
Benjamin Ylvisaker

## Where We Are

- Last lecture: Truth tables and more functions
- This lecture: 2-level implementations and canonical forms
- Next lecture: Boolean cubes
- Homework 1 in the grading pipeline; start 2
- How was lab 2?
  - Start looking at lab 3
- Tutoring available


## Every Function Can Be Implemented in 2 Levels

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

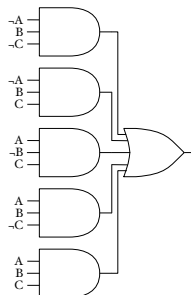


## But We Can Be More Clever

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

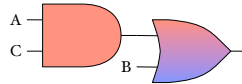


## We Can Also Look At the 0's

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

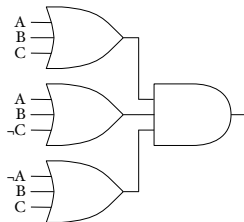

## Again With the Cleverness

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

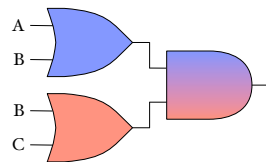

# There Are Lots of Ways to Implement a Function

- ... even if we only consider circuits of the 2 level style
- Sometimes we only want one possible representation for a given function
  - Makes it easy to decide when two people (or programs) have the same function
- Canonical forms to the rescue!

## Minterms and Maxterms

Row#	A	B	$\overline{A}B$	$A\overline{B}$	$\overline{\overline{A}B}$	$\overline{A+B}$	$A\oplus B$	$\overline{A\oplus B}$
0	0	0	0	0	1	1	0	1
1	0	1	0	1	1	0	1	0
2	1	0	0	1	1	0	1	0
3	1	1	1	1	0	0	0	1

- $AB = \Sigma m(3) = \Pi M(0,1,2)$
- $A+B = \Sigma m(1,2,3) = \Pi M(0)$
- $\overline{(AB)} = \Sigma m(0,1,2) = \Pi M(3)$
- $A\oplus B = \Sigma m(1,2) = \Pi M(0,3)$

## Gray Code

- In the coming examples we will use a system called gray code
  - Successive numbers differ in exactly 1 bit position
- 0 = 000
  - 1 = 001
  - 2 = 011
  - 3 = 010
  - 4 = 110
  - 5 = 111
  - 6 = 101
  - 7 = 100

# Gray Code Successor Function

- **Input:**      **Output:**  
 000      001  
 001      011  
 011      010  
 010      110  
 110      111  
 111      101  
 101      100  
 100      000

- We can treat each bit (each column) of the output as its own 3-variable Boolean function
- The three functions taken together give us the complete successor

# Gray Code Successor Function Truth Table

- **Input:**      **Output:**

A	B	C	D	E	F
0	0	0	0	0	1
0	0	1	0	1	1
0	1	0	1	1	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	1	0	0
1	1	0	1	1	1
1	1	1	1	0	1

# Gray Code Successor Function(s) in Minterm Notation

A	B	C	D	E	F
0	0	0	0	0	1
0	0	1	0	1	1
0	1	0	1	1	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	1	0	0
1	1	0	1	1	1
1	1	1	1	0	1

$D(A,B,C) = \sum m(2,5,6,7)$   
 $E(A,B,C) = \sum m(1,2,3,6)$   
 $F(A,B,C) = \sum m(0,1,6,7)$

Order of the variables matters!

$D(A,C,B) = \sum m(1,5,6,7)$   
 $E(A,C,B) = \sum m(1,2,3,5)$   
 $F(A,C,B) = \sum m(0,2,5,7)$

## Now in Maxterm Notation

• A	B	C	D	E	F	D(A,B,C) = ΠM(0,1,3,4)
0	0	0	0	0	1	E(A,B,C) = ΠM(0,4,5,7)
0	0	1	0	1	1	F(A,B,C) = ΠM(2,3,4,5)
0	1	0	1	1	0	
0	1	1	0	1	0	Order of the variables matters!
1	0	0	0	0	0	
1	0	1	1	0	0	D(B,A,C) = ΠM(0,1,2,5)
1	1	0	1	1	1	E(B,A,C) = ΠM(0,2,3,7)
1	1	1	1	0	1	F(B,A,C) = ΠM(2,3,4,5)

## Binary-Coded Decimal (BCD)

- BCD is an encoding for more directly representing decimal numbers with binary digits
  - Each 4 bits represents 1 decimal digit
  - Useful in some numerical programs
- |            |          |
|------------|----------|
| • 0 = 0000 | 5 = 0101 |
| 1 = 0001   | 6 = 0110 |
| 2 = 0010   | 7 = 0111 |
| 3 = 0011   | 8 = 1000 |
| 4 = 0100   | 9 = 1001 |

## BCD to Gray Code Converter

• A	B	C	D	E	F	G	H	A	B	C	D	E	F	G	H
0	0	0	0	0	0	0	0	1	0	0	0	1	1	0	0
0	0	0	1	0	0	0	1	1	0	0	1	1	1	0	1
0	0	1	0	0	0	1	1	1	0	1	0	X	X	X	X
0	0	1	1	0	0	1	0	1	0	1	1	X	X	X	X
0	1	0	0	0	1	1	0	1	1	0	0	X	X	X	X
0	1	0	1	0	1	1	1	1	1	0	1	X	X	X	X
0	1	1	0	0	1	0	1	1	1	0	X	X	X	X	X
0	1	1	1	0	1	0	0	1	1	1	1	X	X	X	X

## We Can Compact the Table

A	B	C	D	E	F	G	H	A	B	C	D	E	F	G	H
0	0	0	0	0	0	0	0	1	0	0	0	1	1	0	0
0	0	0	1	0	0	0	1	1	0	0	1	1	1	0	1
0	0	1	0	0	0	1	1	1	0	1	X	X	X	X	X
0	0	1	1	0	0	1	0	1	1	X	X	X	X	X	X
0	1	0	0	0	1	1	0								
0	1	0	1	0	1	1	1								
0	1	1	0	0	1	0	1								
0	1	1	1	0	1	0	0								

## We Can Compact the Table

A	B	C	D	E	F	G	H	A	B	C	D	E	F	G	H
0	0	0	0	0	0	0	0	1	0	0	0	1	1	0	0
0	0	0	1	0	0	0	1	1	0	0	1	1	1	0	1
0	0	1	0	0	0	1	1	1	0	1	X	X	X	X	X
0	0	1	1	0	0	1	0	1	1	X	X	X	X	X	X
0	1	0	0	0	1	1	0								
0	1	0	1	0	1	1	1								
0	1	1	0	0	1	0	1								
0	1	1	1	0	1	0	0								

$E(A,B,C,D) = \Sigma m(8,9) + \Sigma d(10-15)$   
 $E(A,B,C,D) = \Pi M(0-7) \Pi D(10-15)$

## We Can Compact the Table

A	B	C	D	E	F	G	H	A	B	C	D	E	F	G	H
0	0	0	0	0	0	0	0	1	0	0	0	1	1	0	0
0	0	0	1	0	0	0	1	1	0	0	1	1	1	0	1
0	0	1	0	0	0	1	1	1	0	1	X	X	X	X	X
0	0	1	1	0	0	1	0	1	1	X	X	X	X	X	X
0	1	0	0	0	1	1	0								
0	1	0	1	0	1	1	1								
0	1	1	0	0	1	0	1								
0	1	1	1	0	1	0	0								

$F(A,B,C,D) = \Sigma m(4-9) + \Sigma d(10-15)$   
 $F(A,B,C,D) = \Pi M(0-3) \Pi D(10-15)$

## We Can Compact the Table

A	B	C	D	E	F	G	H	A	B	C	D	E	F	G	H
0	0	0	0	0	0	0	0	1	0	0	0	1	1	0	0
0	0	0	1	0	0	0	1	1	0	0	1	1	1	0	1
0	0	1	0	0	0	1	1	1	0	1	X	X	X	X	X
0	0	1	1	0	0	1	0	1	1	X	X	X	X	X	X
0	1	0	0	0	1	1	0								
0	1	0	1	0	1	1	1	$G(A,B,C,D) = \Sigma m(2,5) + \Sigma d(10-15)$							
0	1	1	0	0	1	0	1	$G(A,B,C,D) = \Pi M(0,1,6-9)\Pi D(10-15)$							
0	1	1	1	0	1	0	0								

## We Can Compact the Table

A	B	C	D	E	F	G	H	A	B	C	D	E	F	G	H
0	0	0	0	0	0	0	0	1	0	0	0	1	1	0	0
0	0	0	1	0	0	0	1	1	0	0	1	1	1	0	1
0	0	1	0	0	0	1	1	1	0	1	X	X	X	X	X
0	0	1	1	0	0	1	0	1	1	X	X	X	X	X	X
0	1	0	0	0	1	1	0								
0	1	0	1	0	1	1	1	$H(A,B,C,D) = \Sigma m(1,2,5,6,9) + \Sigma d(10-15)$							
0	1	1	0	0	1	0	1	$H(A,B,C,D) = \Pi M(0,3,4,7,8)\Pi D(10-15)$							
0	1	1	1	0	1	0	0								

## Lots of Representations

- Boolean algebra expressions/functions
- Digital circuit diagrams
- Truth tables
- Minterm and maxterm notation
- Next time: Boolean cubes & Karnaugh maps
- BDDs: {Boolean/Binary} Decision Diagrams
  - Not discussed in 370

## Thank You for Your Attention

- Collect your quizzes
- Continue work on homework 2
- Start looking at lab 2
- Continue reading the book