

Lecture 25

- ◆ Logistics
 - HW8 posted today, due 12/5
 - Lab9 this week
 - No Class for the rest of the week!
- ◆ Last lecture
 - Robot ant in maze
 - Started on FSM simplification a little bit
- ◆ Today
 - More on FSM simplification

The “WHY” slide


- ◆ FSM minimization
 - It is best to minimize FSM before expressing it as a logic circuit. As you saw in the ant robot example, minimization step is about looking for some patterns and merging states. There are systematic ways to do this (rather than the way we'd done it for the ant example) and we will learn them here.

Two Methods for FSM Minimization

- ◆ Row matching
 - Easier to do by hand
 - Misses minimization opportunities
- ◆ Implication table
 - Guaranteed to find the most reduced FSM
 - More complicated algorithm (but still relatively easy to write a program to do it)


Simple row matching does not guarantee most reduced state machine

Present State	Next State		Output
	X=0	X=1	
S_0	S_0	S_1	0
S_1	S_1	S_2	1
S_2	S_2	S_1	0

 

The Implication chart method

 
- ◆ Here's a slightly funkier FSM as an example



CSE370, Lecture 25

5

Step 1: Draw the table

 


s_0	s_1	s_2	s_3	s_4	s_5
s_0					
s_1					
s_2					
s_3					
s_4					
s_5					


CSE370, Lecture 25

6


Step 2: Consider the outputs

 

Step 3: Add transition pairs

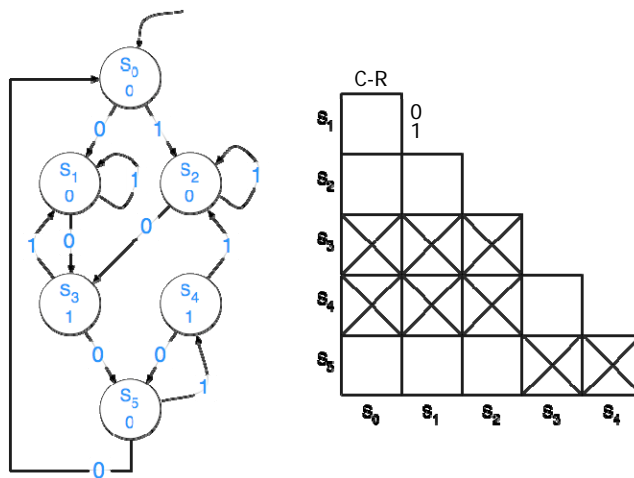

Step 3: Add transition pairs

 


C-R

s_1	s_1-s_3 s_2-s_1	0 1			
s_2	s_1-s_3 s_2-s_2	s_4-s_3 s_1-s_2			
s_3					
s_4				s_5-s_4 s_1-s_2	
s_5	s_1-s_1 s_2-s_4	s_3-s_1 s_1-s_4	s_3-s_1 s_2-s_4		
	s_0	s_1	s_2	s_3	s_4


Implied State Pairs

Step 4 (repeated): Consider transitions

 


s_1	s_1-s_3 s_2-s_1	0 1			
s_2	s_1-s_3 s_2-s_2	s_4-s_3 s_1-s_2			
s_3					
s_4				s_5-s_4 s_1-s_2	
s_5	s_1-s_1 s_2-s_4	s_3-s_1 s_1-s_4	s_3-s_1 s_2-s_4		
	s_0	s_1	s_2	s_3	s_4


Final reduced FSM

 

Odd parity checker revisited

 


Present State	Next State		Output
	X=0	X=1	
S_0	S_0	S_1	0
S_1	S_1	S_2	1
S_2	S_2	S_1	0

 

More complex state minimization

◆ Multiple input example

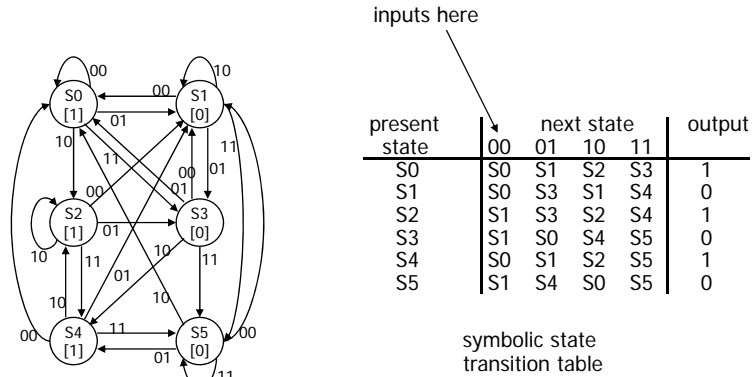


Minimized FSM


◆ Implication chart method

- cross out incompatible states based on outputs
- then cross out more cells if indexed chart entries are already crossed out

present state	next state				output
	00	01	10	11	
S0	S0	S1	S2	S3	1
S1	S0	S3	S1	S4	0
S2	S1	S3	S2	S4	1
S3	S1	S0	S4	S5	0
S4	S0	S1	S2	S5	1
S5	S1	S4	S0	S5	0

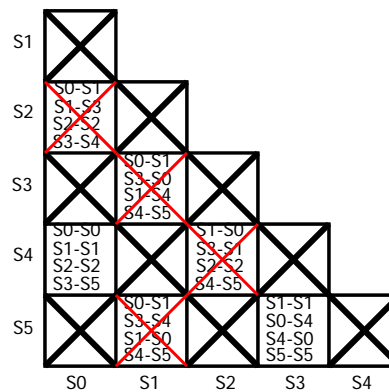

Minimized FSM

 

present state	next state				output
	00	01	10	11	
S0	S0	S1	S2	S3	1
S1	S0	S3	S1	S4	0
S2	S1	S3	S2	S4	1
S3	S1	S0	S4	S5	0
S4	S0	S1	S2	S5	1
S5	S1	S4	S0	S5	0

present state	next state				output
	00	01	10	11	
S0'	S0'	S1	S2	S3'	1
S1	S0'	S3'	S1	S3'	0
S2	S1	S3'	S2	S0'	1
S3'	S1	S0'	S0'	S3'	0

minimized state table
(S0'=S4) (S3'=S5)

Minimizing incompletely specified FSMs

- ◆ Equivalence of states is transitive when machine is fully specified
- ◆ But its not transitive when don't cares are present


e.g., state output

S0	X 0	S1 is compatible with both S0 and S2
S1	1 X	but S0 and S2 are incompatible
S2	X 1	

- ◆ Hard to determining best grouping of states to yield the smallest number of final states

Minimizing FSMs isn't always good


- ◆ Two FSMs for 0->1 edge detection

 

CSE370, Lecture 25

17

 Minimal state diagram -> not necessarily best circuit



In	Q_1	Q_0	Q_1^+	Q_0^+
0	0	0	0	0
0	0	1	0	0
0	1	1	0	0
1	0	0	0	1
1	0	1	1	1
1	1	1	1	1
-	1	0	0	0

$$Q_1^+ = \text{In} \cdot (Q_1 \text{ xor } Q_0)$$


$$Q_0^+ = \text{In} \cdot Q_1' \cdot Q_0'$$

$$\text{Out} = Q_1' \cdot Q_0$$

CSE370, Lecture 25

18

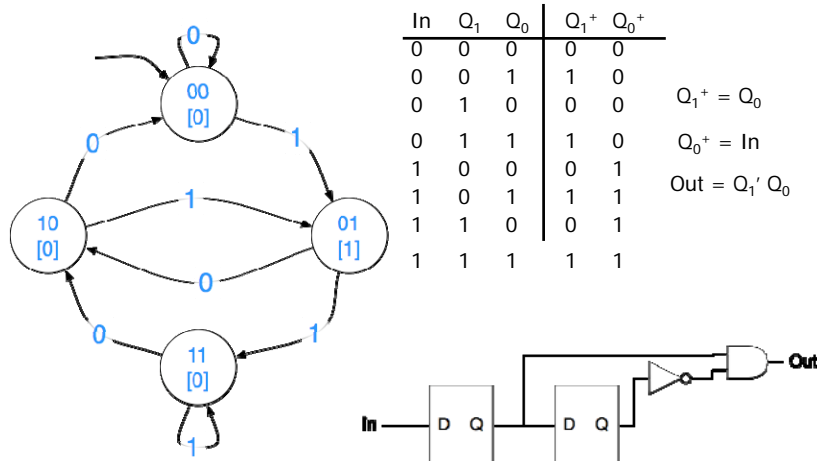Minimal state diagram -> not necessarily best circuit



A little perspective

- ◆ These kinds of optimizations are what CAD(Computer Aided Design)/EDA(Electronic Design Automation) is all about
- ◆ The interesting problems are almost always computationally intractable to solve optimally
- ◆ People **really** care about the automation of the design of billion-transistor chips