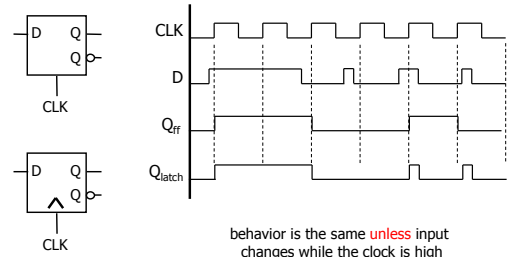



## Overview

- ◆ Last lecture
  - Sequential Verilog
- ◆ Today
  - Review of D latches and flip-flops
  - T flip-flops and SR latches
  - State diagrams
  - Asynchronous inputs

## Latches versus flip-flops




## The master-slave D

 

 
## How do we make a latch?

- ◆ Two inverters hold a bit
  - As long as power is applied




 - ◆ Storing a new memory
  - Temporarily break the feedback path



 
## How do we make a D F/F?

- ◆ Edge triggering is difficult
  - Label the internal nodes
  - Draw a timing diagram
  - Start with  $Clk=1$


 
## T flip-flop

- ◆ Full name: Toggle flip-flop
- ◆ Output toggles when input is asserted
  - If  $T=1$ , then  $Q \rightarrow Q'$  when  $CLK \uparrow$
  - If  $T=0$ , then  $Q \rightarrow Q$  when  $CLK \uparrow$




Input( $t$ )	$Q(t)$	$Q(t + \Delta t)$
0	0	0
0	1	1
1	0	1
1	1	0

## The SR latch

 
### ◆ Cross-coupled NOR gates

- Can set ( $S=1, R=0$ ) or reset ( $R=1, S=0$ ) the output




 
### ◆ Cross-coupled NAND gates

- Can set ( $S=1, R=0$ ) or reset ( $R=1, S=0$ ) the output



## SR latch behavior


### ◆ Truth table and timing

  

## SR latch is glitch sensitive
 
### ◆ Static 0 hazards can set/reset latch

- Glitch on S input sets latch
- Glitch on R input resets latch



## Clear and preset in flip-flops

### ◆ Clear and Preset set flip-flop to a known state

- Used at startup, reset

### ◆ Clear or Reset to a logic 0

- Synchronous:  $Q=0$  when next clock edge arrives
- Asynchronous:  $Q=0$  when reset is asserted
  - Doesn't wait for clock
  - Quick but dangerous

### ◆ Preset or Set the state to logic 1

- Synchronous:  $Q=1$  when next clock edge arrives
- Asynchronous:  $Q=1$  when preset is asserted
  - Doesn't wait for clock
  - Quick but dangerous

## State diagrams

### ◆ How do we characterize logic circuits?

- Combinational circuits: Truth tables
- Sequential circuits: State diagrams

### ◆ First draw the states

- States = Unique circuit configurations


### ◆ Second draw the transitions between states

- Transitions = Changes in state caused by inputs

## Example: SR latch
 
### ◆ Begin by drawing the states


- States = Unique circuit configurations
- Possible values for feedback ( $Q, Q'$ )




## Example: SR latch

- ◆ Now draw the state transitions

- Labeling inputs

 


 
possible oscillation  
between states 00 and 11


  
## Observed SR latch behavior

- ◆ The 1–1 state is transitory

- Either R or S "gets ahead"
- Latch settles to 0–1 or 1–0 state ambiguously
- Race condition → non-deterministic transition
  - ↳ Disallow  $(R,S) = (1,1)$



## System considerations


- ◆ Use edge-triggered flip-flops wherever possible
  - Avoid latches
  - Most common: Master-slave D
- ◆ Basic rules for correct timing
  - Clock flip-flops synchronously (all at the same time)
    - ↳ No flip-flop changes state more than once per clock cycle
    - ↳ FF propagation delay > hold time
  - Avoid mixing positive-edge triggered and negative-edge triggered flip-flops in the same circuit

## Asynchronous inputs

- ◆ Clocked circuits are **synchronous**
  - Circuit changes state only at clock edges
  - Signals (voltages) settle in-between clock edges
- ◆ Unclocked circuits or signals are **asynchronous**
  - No master clock
  - Real-world inputs (e.g. a keypress) are asynchronous
- ◆ Synchronous circuits have asynchronous inputs
  - Reset signal, memory wait, user input, etc.
  - Inputs "bounce"
  - Inputs can change at any time
    - ↳ We must **synchronize the input** to our clock
    - ↳ Inputs will violate flip-flop setup/hold times

 
## Debouncing

- ◆ Switch inputs bounce
  - i. e. don't make clean transitions
- ◆ Can use SR latch for debouncing
  - Eliminates dynamic hazards
  - "Cleans-up" inputs



 
## Synchronizer failure

- ◆ Occurs when FF input changes near clock edge
  - Input is neither 1 or 0 when clock goes high
  - Output may be neither 0 or 1
    - ↳ May stay undefined for a long time
  - Undefined state is called **metastability**


 
## Minimizing synchronizer failures

- ◆ Failure probability can never be 0
  - Can make it small
  - Cascade two (or more) flip-flops
    - ✦ Effectively synchronizes twice
    - ✦ Both would have to fail for system to fail



## Handling asynchronous inputs

- ◆ Never fan-out asynchronous inputs
  - Synchronize at circuit boundary
  - Fan-out synchronized signal

