

Lecture 15

- Registers
- Counters
- Finite State Machine (FSM) design

1


Registers

- Group of storage elements read/written as a unit
 - Store related values (e.g. a binary word)
- Collection of flip-flops with common control
 - Share clock, reset, set lines
- Example:
 - Storage registers
 - Shift registers
 - Counters

2

Storage registers

 
- Basic storage registers use flip-flops
- Example: 4 bit storage register



3

Shift registers

 
- Hold successively sampled input values
 - Delays values in time
- Example: 4-bit shift register
 - Stores 4 input values in sequence




4

Shift register applications

 - Parallel-to-serial conversion for signal transmission



 
- Pattern recognition (circuit recognizes 1001)



5

Counters: Ring counter

 
- Ring counter: Sequence is 1000, 0100, 0010, 0001
 - Assuming one of these patterns is the starting state



6

Counters: Johnson counter

 
- Johnson counter: Sequence is 1000, 1100, 1110, 1111, 0111, 0011, 0001, 0000



7

Counters: Binary counter


- Has logic between flip-flops

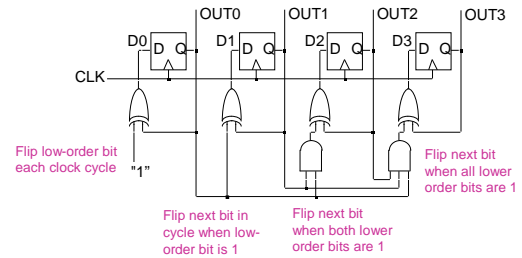

8

Storing "states" for FSMs

 - Combinational logic and storage elements
 - Localized feedback loops
 - Choice of storage elements alters the logic



9

Finite-state machines (FSMs)

- States: Possible storage-element values
 - Clock synchronizes the state changes
- Transitions: Changes in state
 - Clock synchronizes the state changes
- Sequential logic
 - Sequences through a series of states
 - Based on inputs and present state


10

FSM design example: Counters

- Draw a state diagram
- Draw a state-transition table
- Encode the next-state functions
 - Minimize the logic using k-maps
- Implement the design

11

1. Draw a state diagram

 

12

2. Draw a state-transition table

- Like a truth-table
 - State encoding is easy for counters → Use count value

current state	next state
0 000	001 1
1 001	010 2
2 010	011 3
3 011	100 4
4 100	101 5
5 101	110 6
6 110	111 7
7 111	000 0

13

3. Encode next state functions

- Assume D flip-flops as state elements

C3	C2	C1	N3	N2	N1
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

N1		C3	
1	1	1	1
0	0	0	0

N2		C3	
0	1	1	0
1	0	0	1


N3		C3	
0	0	1	1
0	1	0	1

$N1 := C1'$
 $N2 := C1C2' + C1'C2$
 $:= C1 \text{ xor } C2$
 $N3 := C1C2C3' + C1'C3 + C2C3$
 $:= C1C2C3' + (C1' + C2')C3$
 $:= (C1C2) \text{ xor } C3$

14

 4. Implement the design

- 3 flip-flops hold state
 - Counter is synchronously clocked
- Minimized logic computes next state



15

What if we use T flip-flops?

T flip-flops

$T_i = 1$ iff $N_i \neq C_i$

$T_0 := 1$

$T_1 := C_0$

$T_2 := C_0 C_1$



C2	C1	C0	N2	N1	N0	T2	T1	T0
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1


T0		C2	
1	1	1	1
1	1	1	1

T1		C2	
0	0	0	0
1	1	1	1

T2		C2	
0	0	0	0
0	1	1	0

16

4. Implement the design

 


17

Example: 5-state counter

- Counter repeats 5 states in sequence
 - Sequence is 000, 010, 011, 101, 110, 000

Step 1: State diagram

 


Step 2: State transition table

Assume D flip-flops

Present State			Next State		
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	X	X	X
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	X	X	X
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	X	X	X


18

3. Encode next state functions

 

19

4. Implement the design

 


Recall that a D flip flop also produces Q' so A', B', and C' would all be available without any extra inverters

20

Is our design robust?

 - What if the counter starts in a 111 state?



Does our counter get stuck in invalid states???

21

5-state counter


- Back-annotate our design to check it

Fill in state transition table

Present State			Next State		
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	1	1	0
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	1	0	0

$A+ = BC'$
 $B+ = B' + A'C'$
 $C+ = A$

Draw state diagram

 

The proper methodology is to *design* your counter to be self-starting

22

Self-starting counters

- Invalid states should **always** transition to valid states
 - Assures startup
 - Assures bit-error tolerance
- Design your counters to be self-starting
 - Draw **all** states in the state diagram
 - Fill in the **entire** state-transition table
 - May limit your ability to exploit don't cares
 - Choose startup transitions that minimize the logic

23