

Lecture 17

- General finite state machine (FSM) design
- Moore/Mealy machines

1

Finite state machines

- FSM: A system that visits a **finite** number of logically distinct states
- Counters are simple FSMs
 - Outputs and states are identical
 - Visit states in a fixed sequence without inputs

2

More than counters

- FSMs are typically more complex than counters
 - Outputs can depend on current state and on inputs
 - State sequencing depends on current state and on inputs

3


FSM design

- Counter design procedure
 1. State diagram
 2. State-transition table
 3. Next-state logic minimization
 4. Implement the design
- FSM design procedure
 1. State diagram
 2. State-transition table
 3. State minimization
 4. State encoding
 5. Next-state logic minimization
 6. Implement the design

4

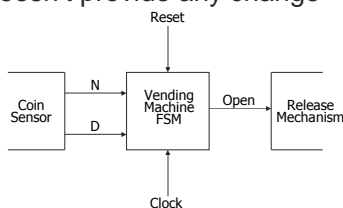
Example: Vending machine

- 15 cents for a cup of coffee
- Doesn't take pennies or quarters
- Doesn't provide any change



5

1. State diagram

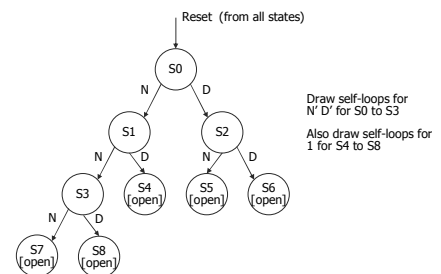


6

2. State transition table

present state	inputs D N	next state	output open
S0	0 0	S0	0
	0 1	S1	0
	1 0	S2	0
	1 1	X	X
S1	0 0	S1	0
	0 1	S3	0
	1 0	S4	0
	1 1	X	X
S2	0 0	S2	0
	0 1	S5	0
	1 0	S6	0
	1 1	X	X
S3	0 0	S3	0
	0 1	S7	0
	1 0	S8	0
	1 1	X	X
S4	X X	S4	1
S5	X X	S5	1
S6	X X	S6	1
S7	X X	S7	1
S8	X X	S8	1

7

3. State minimization

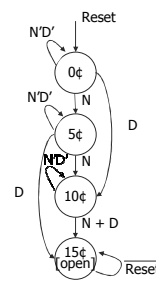

present state	inputs D N	next state	output open
0¢	0 0	0¢	0
	0 1	5¢	0
	1 0	10¢	0
	1 1	-	-
5¢	0 0	5¢	0
	0 1	10¢	0
	1 0	15¢	0
	1 1	-	-
10¢	0 0	10¢	0
	0 1	15¢	0
	1 0	15¢	0
	1 1	-	-
15¢	-	15¢	1

symbolic state table


8

4. State encoding

present state	inputs D N	next state	output open
Q1 Q0		D1 D0	
0 0	0 0	0 0	0
	0 1	0 1	0
	1 0	1 0	0
	1 1	-	-
0 1	0 0	0 1	0
	0 1	1 0	0
	1 0	1 1	0
	1 1	-	-
1 0	0 0	1 0	0
	0 1	1 1	0
	1 0	1 1	0
	1 1	-	-
1 1	-	1 1	1

9

5. Next-state logic minimization

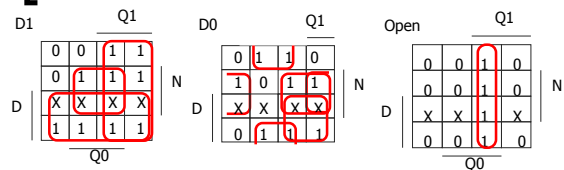


$$D1 = Q1 + D + Q0 N$$

$$D0 = Q0' N + Q0 N' + Q1 N + Q1 D$$

$$OPEN = Q1 Q0$$

10


6. Implement the design

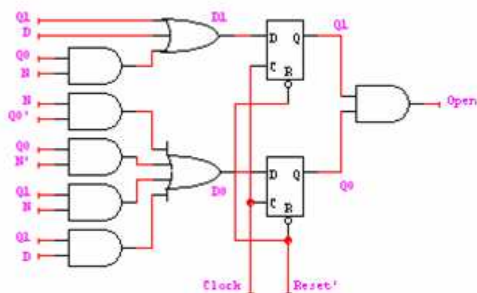

11


Generalized FSM model

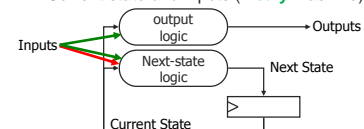- Combinational logic computes next state and outputs
 - Next state is a function of current state and inputs
 - Outputs are functions of
 - Current state (Moore machine)
 - Current state and inputs (Mealy machine)




12

Moore vs. Mealy machines

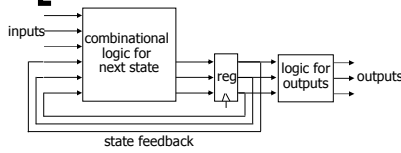

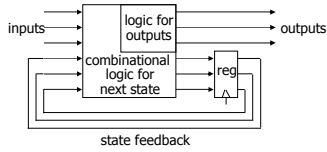Moore machine
 Outputs are a function of current state
 Outputs change synchronously with state changes




Mealy machine
 Outputs depend on state and on inputs
 Input changes can cause immediate output changes (**asynchronous**)

State diagrams

- Moore machine
 - Each *state* is labeled by a state-name/output pair.
- Mealy machine
 - Each *transition arc* is labeled by an input-condition/output pair.

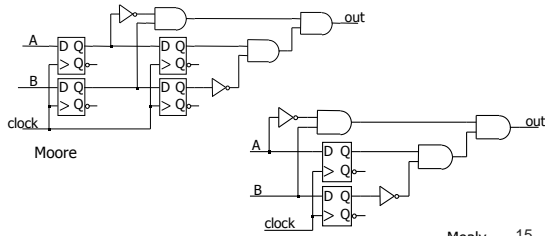
Example: 10 → 01

- Circuits recognize AB=10 followed by AB=01
 - What kinds of machines are they?



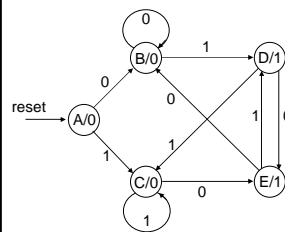Example: "01" or "10" detector


- Moore: Output is a function of state only
 - Specify output in the state bubble



reset	input	current state	next state	current output
1	-	-	A	0
0	0	A	B	0
0	1	A	C	0
0	0	B	B	0
0	1	B	D	0
0	0	C	E	0
0	1	C	C	0
0	0	D	E	1
0	1	D	C	1
0	0	E	B	1
0	1	E	D	116

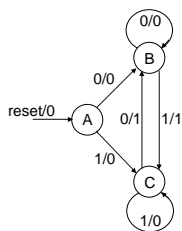Example: "01" or "10" detector

- Mealy: Output is a function of state and inputs
 - Specify outputs on transition arcs



reset	input	current state	next state	current output
1	-	-	A	0
0	0	A	B	0
0	1	A	C	0
0	0	B	B	0
0	1	B	C	1
0	0	C	B	1
0	1	C	C	0

Moore vs. Mealy

- Moore machines
 - + Safer to use because outputs change at clock edge
 - May take additional logic to decode state into outputs
- Mealy machines
 - + Typically have fewer states
 - + React faster to inputs — don't wait for clock
 - Asynchronous outputs can be dangerous


[Synchronous Mealy machines]

- We often design synchronous Mealy machines
 - Design a Mealy machine
 - Then register the outputs

19

[Synchronous Mealy machines]

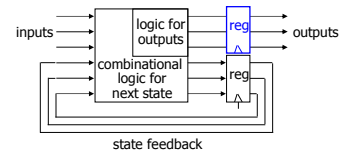- Registered state and registered outputs
 - No glitches on outputs
 - No race conditions between communicating machines




20

[Example: "==" 01?]

- Recognize $AB = 01$
 - Mealy or Moore?



Synchronous Mealy
(Moore)

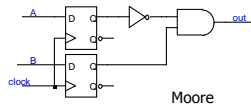

Moore

21