

Lecture 23

- Design example: Traffic light controller

1


FSM design process

1. Understand the problem
 - State diagram and state-transition table
2. Determine the machine's states
 - Consider missing transitions: Will the machine start?
 - Minimize the state diagram: Reuse states where possible
3. Encode the states
 - Encode states, outputs with a reasonable encoding choice
 - Consider the implementation target
4. Design the next-state logic
 - Minimize the combinational logic
 - Choices made in steps 2 & 3 affect the logic complexity
5. Implement the FSM

2

Example: Traffic light controller

- Highway/farm road intersection

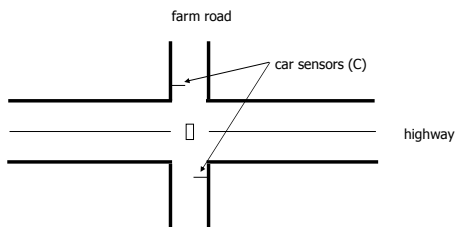

3

Example: Traffic light controller

- A busy highway is intersected by a little used farm road
- Detectors C sense the presence of cars on the farm road
 - With no car on farm road, lights remain Green in highway direction
 - If vehicle on farm road, highway lights go from Green to Yellow to Red, allowing the farm road lights to become Green
 - These stay Green only as long as a farm road car is detected but never longer than a set interval (say, 20 time units)
 - When these are met, farm lights transition from Green to Yellow to Red, allowing highway to return to Green
 - Even if farm road vehicles are waiting, highway gets at least a set interval as Green (say, 20 time units)

4

What are inputs and outputs?

- Inputs
 - Reset
 - C (farm road car detector)
- Outputs
 - HG (highway green)
 - HY (highway yellow)
 - HR (highway red)
 - FG (farm road green)
 - FY (farm road yellow)
 - FR (farm road red)

5

What are the states?

- How about color of the lights?
 - HG (highway green)
 - HY (highway yellow)
 - HR (highway red)
 - FG (farm road green)
 - FY (farm road yellow)
 - FR (farm road red)

6


[Any redundancy?]

- If the highway light is green or yellow, the farm road light must be red.
- States
 - HG (highway green)
 - HY (highway yellow)
 - FG (farm road green)
 - FY (farm road yellow)

7

[Partial traffic light controller]

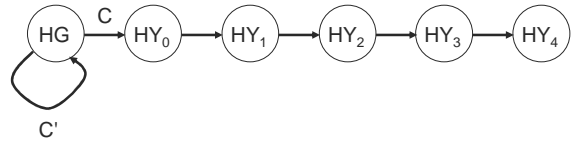- Useful to walk through typical execution sequence




- What's the problem?

8

[FSM can get very big!]

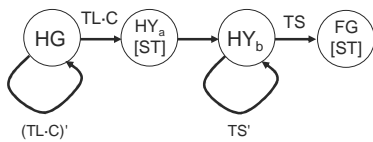
- Utilize external timer like a subroutine



9

[External timer]

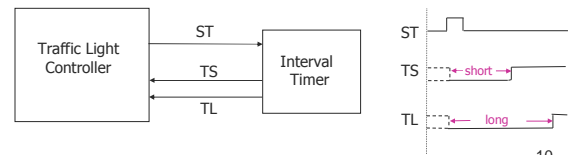- ST resets timer and starts counting
- Timer generates a short time pulse (TS) and a long time pulse (TL)
- TS is to be used for timing yellow lights and TL for green lights




10

[Revised FSM specification]

- **Inputs**
 - reset place FSM in initial state
 - C detect vehicle on the farm road
 - TS short time interval expired
 - TL long time interval expired
- **Outputs**
 - HG, HY, HR assert green/yellow/red highway lights
 - FG, FY, FR assert green/yellow/red farm road lights
 - ST start timing a short or long interval
- **State**
 - HG highway green (farm road red)
 - HY highway yellow (farm road red)
 - FG farm road green (highway red)
 - FY farm road yellow (highway red)


11

[Traffic light controller]

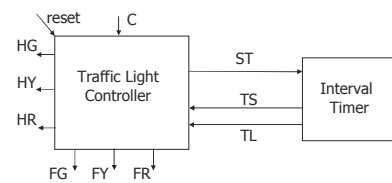

12

Moore/Mealy hybrid

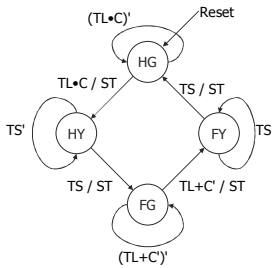

13

State encoding

- Let's use a one-hot encoding:
 - HG = 0001
 - HY = 0010
 - FG = 0100
 - FY = 1000

14

Next-state logic

- $P_3 = (C' \cdot Q_2) + (TL \cdot Q_2) + (TS' \cdot Q_3)$
- $P_2 = (TS \cdot Q_1) + (C \cdot TL' \cdot Q_2)$
- $P_1 = (C \cdot TL \cdot Q_0) + (TS' \cdot Q_1)$
- $P_0 = (C' \cdot Q_0) + (TL' \cdot Q_0) + (TS \cdot Q_3)$

- $ST = (C \cdot TL \cdot Q_0) + (TS \cdot Q_1) + (C' \cdot Q_2) + (TL \cdot Q_2) + (TS \cdot Q_3)$

15

Outputs


- Green = 00
- Yellow = 01
- Red = 10

- Two sets of outputs: H_1, H_0 and F_1, F_0

- $H_1 = Q_3 + Q_2$
- $H_0 = Q_1$
- $F_1 = Q_1 + Q_0$
- $F_0 = Q_3$


16

State partitioning

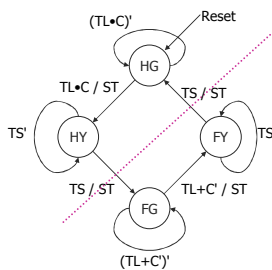

17

State partitioning

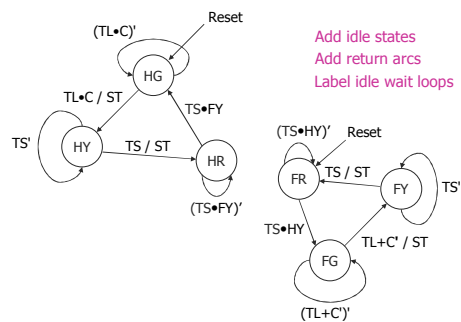

18