

## Lecture 12


- ◆ Logistics
  - HW4 due today
- ◆ Last lecture
  - Timing diagrams
  - Hazards
- ◆ Today
  - Time/space trade offs: Parallel prefix trees
  - Adders
  - The conclusion of combinational logic!!!

## The "WHY" slide

- ◆ Timing/space trade offs
  - In real life, complex logic circuits you will work on will not have one minimum circuit. You will have to learn to understand what parameters to optimize your design on, and be able to come up with "trade offs" suitable for your application or customer's needs.
- ◆ Adders
  - Arithmetic logic units (ALUs) such as adders and multipliers perform most computer instructions. Therefore, it is critical to know how they work, how they scale, and how they may be optimized for time/space.
 
## What do we mean by time/speed tradeoff?: Linear chains vs. trees


- ◆ Lets say we want to implement an 8-input OR function with only 2-input gates



Gates: 7  
Max delay: 7

## Linear chains vs. trees


- ◆ Now consider the tree version

 

Gates: 7  
Max delay: 3

 
## And now we change the problem slightly

- ◆ Build a circuit that takes 8 single bit inputs and calculates the OR of the first 2, the OR of the first 3, the OR of the first 4, and so on, up to the OR of all 8




Gates: 7  
Max delay: 7
 
## A parallel version of the prefix circuit



Gates: 12  
Max delay: 3

## The parallel prefix OR circuit

 

CSE370, Lecture 12


7

## Binary half adder

### 1-bit half adder

- Computes sum, carry-out
  - No carry-in
- Sum =  $A'B + AB' = A \oplus B$
- Cout =  $AB$

A	B	S	C <sub>out</sub>
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

CSE370, Lecture 12



8

## Binary full adder

### 1-bit full adder

- Computes sum, carry-out
  - Carry-in allows cascaded adders
- Sum =  $Cin \oplus A \oplus B$
- Cout =  $ACin + BCin + AB$

A	B	C <sub>in</sub>	S	C <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

  

CSE370, Lecture 12

9

## Full adder: using 2 half adders

### Multilevel logic


- Slower
- Fewer gates
  - 2 XORs, 2 ANDs, 1 OR

$$\text{Sum} = (A \oplus B) \oplus \text{Cin}$$

$$\text{Cout} = ACin + BCin + AB$$

$$= (A \oplus B)Cin + AB$$


A	B	C <sub>in</sub>	S	C <sub>out</sub>	C <sub>out</sub>
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	0	1	1
1	0	0	1	0	0
1	0	1	0	1	1
1	1	0	0	1	1
1	1	1	1	1	1

 

CSE370, Lecture 12

10
 
## 4-bit ripple-carry adder (also subtracts)




- Easy to convert to subtractor using twos complement
  - Twos complement:  $A - B = A + (-B) = A + B' + 1$

CSE370, Lecture 12

11

## Problem: Ripple-carry delay

### Carry propagation limits adder speed

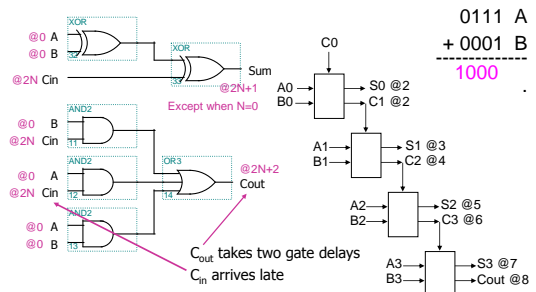


CSE370, Lecture 12

12

 
## Can we be clever and speed this up?

- ◆ Let's compute all the carries in parallel
  - Derive carries from the data inputs
    - ↳ Not from intermediate carries
    - ↳ Use two-level logic
  - Compute all sums in parallel
- How do we do that???



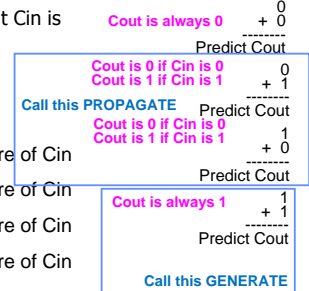
## Speeding up the adder

- ◆ Need to find a way to "predict" Cout for all bits
- ◆ Without knowing what Cin is



- ◆ Let's try all cases:
- ◆ A = 0, B = 0 but not sure of Cin
- ◆ A = 0, B = 1 but not sure of Cin
- ◆ A = 1, B = 0 but not sure of Cin
- ◆ A = 1, B = 1 but not sure of Cin
 
## Solution: Create a carry lookahead logic Step 1: Getting Pi and Gi




- ◆ Carry generate:  $G_i = A_i B_i$ 
  - Generate carry when A = B = 1
- ◆ Carry propagate:  $P_i = A_i \oplus B_i$ 
  - Propagate carry-in to carry-out when  $(A \oplus B) = 1$

## Solution: Carry-lookahead logic Step 2: Calculate Sum and Cout

- ◆ Sum and Cout in terms of generate/propagate:


$$S_i = A_i \oplus B_i \oplus C_i = P_i \oplus C_i$$
 
$$C_{i+1} = A_i B_i + C_i (A_i \oplus B_i) = G_i + C_i P_i$$



 
## Solution: Carry-lookahead logic Step 3: Express all carries in terms of C0


- ◆ Re-express the carry logic in terms of G and P
  - $C_1 = G_0 + P_0 C_0$
  - $C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0$
  - $C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$
  - $C_4 = G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$
- ◆ Implement each carry equation with two-level logic
  - Derive intermediate results directly from inputs
    - ↳ Rather than from carries
  - Allows "sum" computations to proceed in parallel


 
## Solution: carry-lookahead logic Step 4: implement with 2-level logic




 Logic complexity increases with adder size



## Solution: Carry lookahead logic
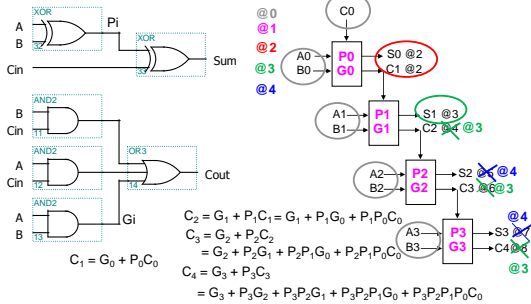
### ◆ Get Pi (propagate) and Gi (generate)



CSE370, Lecture 12

19

## Carry lookahead logic summary


### ◆ Compute all the carries in parallel

- Derive carries from the data inputs
  - ↳ Not from intermediate carries
  - ↳ Use two-level logic
- Compute all sums in parallel

### ◆ Cascade simple adders to make large adders

### ◆ Speed improvement

### ◆ Complex combinational logic

 

CSE370, Lecture 12

20

## We've finished combinational logic...

- Negative numbers in binary
- Truth tables
- Basic logic gates
- Schematic diagrams
- Minterm and maxterm expansions (canonical, minimized)
- de Morgan's theorem
- AND/OR to NAND/NOR logic conversion
- K-maps, logic minimization, don't cares
- Multiplexers/demultiplexers
- PLAs/PALs
- ROMs
- Multi-level logics
- Timing diagrams
- Hazards
- Adders

CSE370, Lecture 12

21