

Lecture 22


- ◆ Logistics
 - HW 8 posted today, due 3/11
 - Lab 9 this week
- ◆ Last lecture
 - Robot ant in maze
 - State matching for FSM simplification
- ◆ Today
 - General FSM minimization

Two Methods for FSM Minimization

- ◆ Row matching
 - Easier to do by hand
 - Misses minimization opportunities
- ◆ Implication table
 - Guaranteed to find the most reduced FSM
 - More complicated algorithm (but still relatively easy to write a program to do it)


Simple row matching does not guarantee most reduced state machine

Present State	Next State		Output
	X=0	X=1	
S_0	S_0	S_1	0
S_1	S_1	S_2	1
S_2	S_2	S_1	0

 

The Implication chart method

 
- ◆ Here's a slightly funkier FSM as an example




Implication Chart Method

- ◆ Basic Idea: assume that all states are grouped together and only split state pairs that must be split
- ◆ Algorithm
 1. Draw a table with a box for every pair of states
 2. Use output values to cross out boxes for pairs of states that cannot be combined
 3. Fill rest of table with transition pairs
 - For each box and possible input, list pairs of destination states, one per source state
 4. Repeatedly do:
 - If box (S_i, S_j) contains some transition pair $S_k \rightarrow S_l$ corresponding to an already crossed-out box then cross out box (S_i, S_j)
 - Until no more boxes can be crossed out
 5. Combine all pairs of states that are not crossed out

 
Step 1: Draw the table of pairs of states




Step 2: Consider the outputs

 

Step 3: Add transition pairs

 


Step 3: Add transition pairs

 


Transitivity:
if states are combined then successor states must be combined
⇒ if successor states cannot be combined then states cannot be combined


Step 4 (repeated): Consider transitions

 


Final reduced FSM

 

Odd parity checker revisited

 


Present State	Next State		Output
	X=0	X=1	
S_0	S_0	S_1	0
S_1	S_1	S_2	1
S_2	S_2	S_1	0

 

More complex state minimization

Multiple input example

 

inputs here

present state	00	01	10	11	output
S0	S0	S1	S2	S3	1
S1	S0	S3	S1	S4	0
S2	S1	S3	S2	S4	1
S3	S1	S0	S4	S5	0
S4	S0	S1	S2	S5	1
S5	S1	S4	S0	S5	0

symbolic state transition table

Minimized FSM

Implication chart method

- cross out incompatible states based on outputs
- then cross out more cells if indexed chart entries are already crossed out

present state	00	01	10	11	output
S0	S0	S1	S2	S3	1
S1	S0	S3	S1	S4	0
S2	S1	S3	S2	S4	1
S3	S1	S0	S4	S5	0
S4	S0	S1	S2	S5	1
S5	S1	S4	S0	S5	0

Minimized FSM

present state	00	01	10	11	output
S0	S0	S1	S2	S3	1
S1	S0	S3	S1	S4	0
S2	S1	S3	S2	S4	1
S3	S1	S0	S4	S5	0
S4	S0	S1	S2	S5	1
S5	S1	S4	S0	S5	0

present state	00	01	10	11	output
S0'	S0'	S1	S2	S3'	1
S1	S0'	S3'	S1	S3'	0
S2	S1	S3'	S2	S0'	1
S3'	S1	S0'	S0'	S3'	0

minimized state table
(S0'=S4) (S3'=S5)

Optimality and Moore vs Mealy


- Any two (Moore) FSMs with the same functionality lead to the same minimized FSM (up to state names) and this is best possible
 - Proof in CSE 322
- For Mealy FSMs need to do different marking for outputs in step 2
 - List pairs of outputs for each input value and cross out boxes with any pair of different outputs
 - Then erase these output pairs from the non-crossed-out boxes and continue as in Step 3 for the Moore FSM

Minimizing incompletely specified FSMs


- Equivalence of states is transitive when machine is fully specified
 - But its not transitive when don't cares are present
 - e.g., state output
- | | | |
|----|-----|--------------------------------------|
| S0 | X 0 | S1 is compatible with both S0 and S2 |
| S1 | 1 X | but S0 and S2 are incompatible |
| S2 | X 1 | |
- Hard to determine best grouping of states to yield the smallest number of final states

Minimizing FSMs isn't always good

- Two FSMs for 0 → 1 edge detection

 

 
Minimal state diagram: not necessarily best circuit



In	Q ₁	Q ₀	Q ₁ ⁺	Q ₀ ⁺
0	0	0	0	0
0	0	1	0	0
0	1	1	0	0
1	0	0	0	1
1	0	1	1	1
1	1	1	1	1
-	1	0	-	-


$Q_1^+ = \text{In} (Q_1 + Q_0)$
 $Q_0^+ = \text{In}$
 $\text{Out} = Q_1' Q_0$

 Minimal state diagram: not necessarily best circuit



In	Q ₁	Q ₀	Q ₁ ⁺	Q ₀ ⁺
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	1	0
1	0	0	0	1
1	0	1	1	1
1	1	0	0	1
1	1	1	1	1

 $Q_1^+ = Q_0$
 $Q_0^+ = \text{In}$
 $\text{Out} = Q_1' Q_0$



A little perspective

- ◆ These kinds of optimizations are what CAD(Computer Aided Design)/EDA(Electronic Design Automation) is all about
- ◆ The interesting problems are almost always computationally intractable to solve optimally
- ◆ People **really** care about the automation of the design of billion-transistor chips