

Lecture 15

◆ Logistics

- HW4 is due today
- HW5 posted today
- Exam questions: to me
- Class feedback

◆ Last lecture

- Adders

◆ Today




- More on Adder timing issues (hard!)
- Summary of Combinational Logic
- Introduction to Sequential Logic
 - ↳ The basic concepts
 - ↳ An example

Binary full adder

◆ 1-bit full adder


- Computes sum, carry-out
 - ↳ Carry-in allows cascaded adders
- $Sum = Cin \text{ xor } A \text{ xor } B$
- $Cout = ACin + BCin + AB$

A	B	C _{in}	S	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

   

Problem: Ripple-carry delay

- ◆ Carry propagation limits adder speed

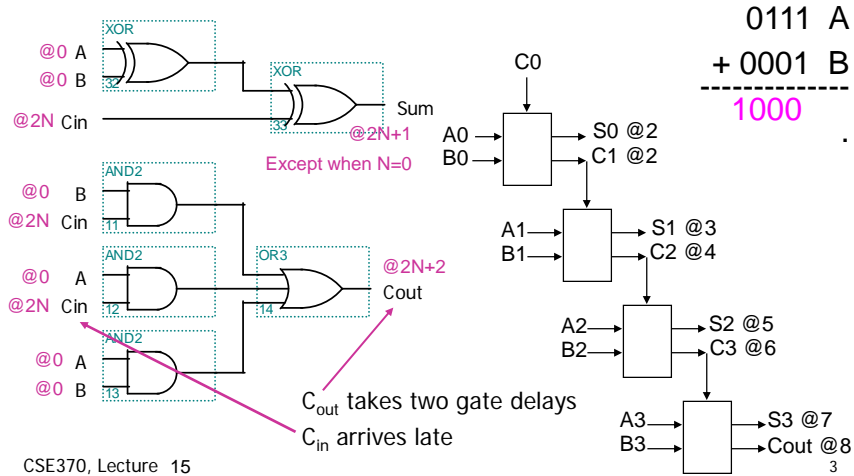

Speeding up the adder

- ◆ Need to find a way to "predict" Cout for all bits
- ◆ Without knowing what Cin is

Call this PROPAGATE

Cout is always 0

```

    0
  + 0
  -----
  Predict Cout
  0
  + 1
  -----
  Predict Cout
  1
  + 0
  -----
  Predict Cout
  1
  + 1
  -----
  Predict Cout
  
```


Cout is 0 if Cin is 0
Cout is 1 if Cin is 1

Cout is always 1

Call this GENERATE

- ◆ Let's try all cases:
- ◆ A = 0, B = 0 but not sure of Cin
- ◆ A = 0, B = 1 but not sure of Cin
- ◆ A = 1, B = 0 but not sure of Cin
- ◆ A = 1, B = 1 but not sure of Cin

 
Solution: Create a carry lookahead logic Getting Pi and Gi



- ◆ Carry **generate**: $G_i = A_i B_i$ for i-th bit
 - Generate Cout when $A = B = 1$
- ◆ Carry **propagate**: $P_i = A_i \text{ xor } B_i$ for i-th bit
 - Propagate Cin to Cout when $(A \text{ xor } B) = 1$
- ◆ So, $C_{out} = G + PC_{in}$ $C_{i+1} = G_i + P_i C_i$

One Solution: Carry lookahead logic

- ◆ Get Pi (propagate) and Gi (generate)

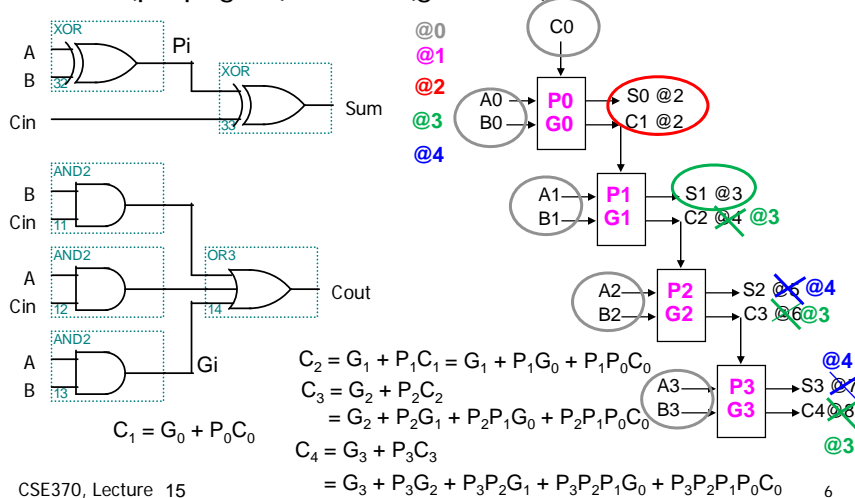

We've finished combinational logic...

- Negative numbers in binary
- Truth tables
- Basic logic gates
- Schematic diagrams
- Minterm and maxterm expansions (canonical, minimized)
- de Morgan's theorem
- AND/OR to NAND/NOR logic conversion
- K-maps, logic minimization, don't cares
- Multiplexers/demultiplexers
- PLAs/PALs
- ROMs
- Multi-level logics
- Timing diagrams
- Hazards
- Adders

We had no way to store memory:
When the input changed, the output changed

Next: Sequential logic can store memory...


Sequential Logic (next 5 weeks!)

- ◆ We learn the details
 - Latches, flip-flops, registers (**storage**)
 - Shift registers, counters (**we can count now!**)
 - State machines (**when we can store, we have states**)
 - Moore and Mealy machines (**types of state machines**)
 - Timing and timing diagrams
 - ✦ **timing more important than combinational logic**
 - Synchronous and asynchronous inputs
 - ✦ **Metastability (problem!)**

The “WHY” slide

- ◆ Learning sequential logic
 - Having the ability to hold memory is important. If you couldn't use your prior knowledge stored in the memory, you wouldn't be very smart (and same goes for a computer).

Sequential versus combinational

 


Apply fixed inputs A, B
When the clock ticks, the output becomes available
Observe C
Wait for another clock tick
Observe C again


Combinational: C will stay the same
Sequential: C may be different

Sequential versus combinational

 - ◆ Combinational systems are **memoryless**
 - Outputs depend only on the present inputs




 - ◆ Sequential systems have **memory**
 - Outputs depend on the present **and** the previous inputs




Synchronous sequential systems

 - ◆ **Memory** holds a system's **state**
 - Changes in state occur at specific times
 - A periodic signal times or **clocks** the state changes
 - The clock period is the time between state changes



 
State changes occur at rising edge of clock



duty cycle = pulsewidth/period
(here it is 50%)

Steady-state abstraction

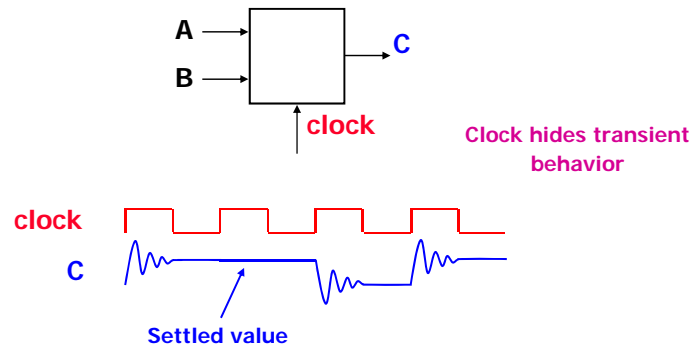- ◆ Outputs retain their *settled values*
 - The clock period must be long enough for all voltages to settle to a *steady state* before the next state change



What did I just say about sequential logic?

- ◆ Has clock
 - *Synchronous* = clocked
 - Exception: Asynchronous
- ◆ Has state
 - *State* = memory
- ◆ Employs *feedback*
- ◆ Assumes *steady-state* signals
 - Signals are valid after they have settled
 - State elements hold their settled output values

Example: A sequential system


- ◆ Door combination lock
 - Enter three numbers in sequence and the door opens
 - When one number is entered, press 'enter'
 - If there is an error the lock must be reset
 - After the door opens the lock must be reset
 - Inputs: Sequence of numbers, reset, enter
 - Outputs: Door open/close
 - Memory: Must remember the combination

We will go through the motion of designing a real system

We will teach details of “how” to do these steps
in the next few weeks

Understand the problem

 - ◆ Consider I/O and unknowns
 - How many bits per input?
 - How many inputs in sequence?
 - How do we know a new input is entered?
 - How do we represent the system states?




Implement using sequential logic

◆ Behavior

- Clock tells us when to look at inputs
 - ✦ After inputs have settled
- Sequential: Enter sequence of numbers
- Sequential: Remember if error occurred

◆ A diagram may be helpful

 - Assume synchronous inputs
- State sequence
 - ✦ Enter 3 numbers serially
 - ✦ Remember if error occurred
- All states have outputs
 - ✦ Lock open or closed



A diagram (called finite-state diagram)

◆ States: 5

- Each state has outputs


◆ Inputs: reset, new, results of comparisons

- Assume synchronous inputs

◆ Outputs: open/closed

We use state diagrams to represent sequential logic

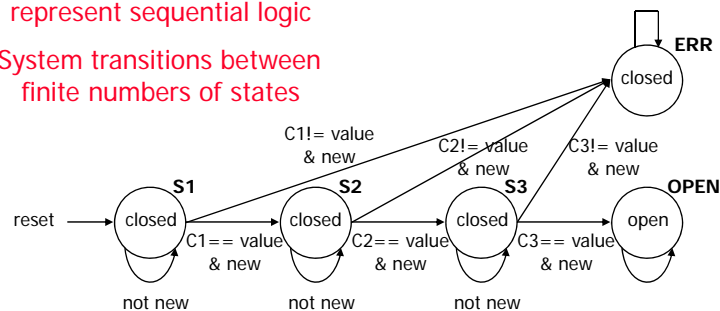System transitions between finite numbers of states




Separate data path and control

◆ Data path

- Stores combination
- Compares inputs with combination


◆ Control

 - Finite state-machine controller
- Control for data path
- State changes clocked



Refine diagram; generate state table

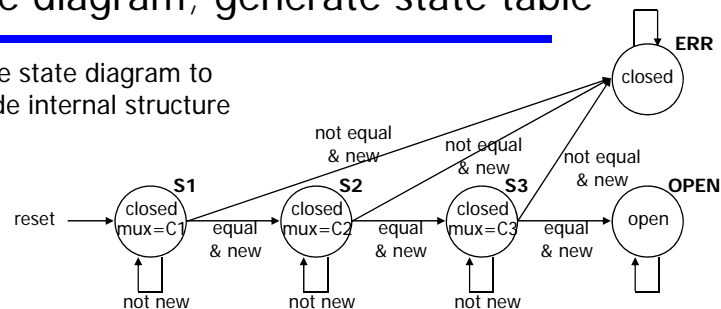- ◆ Refine state diagram to include internal structure



- ◆ Generate state table

reset	new	equal	state	next state	mux	open/closed
1	-	-	-	S1	C1	closed
0	0	-	S1	S1	C1	closed
0	1	0	S1	ERR	-	closed
0	1	1	S1	S2	C2	closed
...						
0	1	1	S3	OPEN	-	open
...						

Encode state table

- ◆ State can be: S1, S2, S3, OPEN, or ERR
 - Need at least 3 bits to encode: 000, 001, 010, 011, 100
 - Can use 5 bits: 00001, 00010, 00100, 01000, 10000
 - Choose 4 bits: 0001, 0010, 0100, 1000, 0000
- ◆ Output to mux can be: C1, C2, or C3
 - Need 2 or 3 bits to encode
 - Choose 3 bits: 001, 010, 100
- ◆ Output open/closed can be: Open or closed
 - Need 1 or 2 bits to encode
 - Choose 1 bit: 1, 0

Encode state table (con't)


- ◆ Good encoding choice!
 - Mux control is identical to last 3 state bits
 - Open/closed is identical to first state bit
 - Output encoding \Rightarrow the outputs and state bits are the same

reset	new	equal	state	next state	mux	open/closed
1	-	-	-	0001	001	0
0	0	-	0001	0001	001	0
0	1	0	0001	0000	-	0
0	1	1	0001	0010	010	0
...						
0	1	1	0100	1000	-	1
...						

Implementing the controller



- ◆ We will learn how to design the controller given the encoded state-transition table

 special circuit element, called a register, for storing inputs when told to by the clock




Designing the datapath

  - Four multiplexers
 - ↳ 2-input ANDs and 3-input OR
- Four single bit comparators
 - ↳ 2-input XNORs
- 4-input AND




Where did we use **memory**?

 - ◆ **Memory**: Stored combination, state (errors or successes in past inputs)



Where did we use **feedback**?

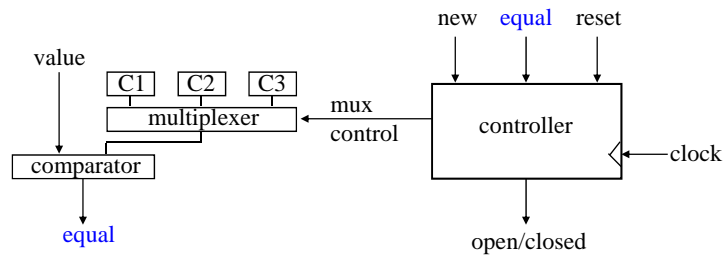- ◆ **Feedback**: Comparator output ("**equal**" signal)



Where did we use clock?

- ◆ Clock synchronizes the inputs
 - Accept inputs when clock goes high
- ◆ Controller is clocked
 - Mux-control and open/closed signals change on the clock edge

