

Lecture 22


- ◆ Logistics
 - HW7 is due on Friday
 - Lab 8 this week
- ◆ Last lecture
 - FSMs
 - Intro to Moore and Mealy machines
- ◆ Today
 - More Moore and Mealy machines

The “WHY” slide


- ◆ Moore/Mealy machines
 - There are two different ways to express the FSMs with respect to the output. Both have different advantages so it is good to know them.

Generalized FSM model: Moore and Mealy

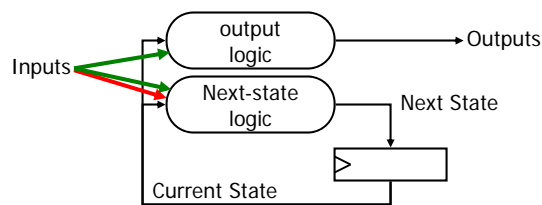- ◆ Combinational logic computes next state and outputs
 - Next state is a function of current state and inputs
 - Outputs are functions of
 - ☛ Current state (**Moore** machine)
 - ☛ Current state and inputs (**Mealy** machine)




Moore versus Mealy machines

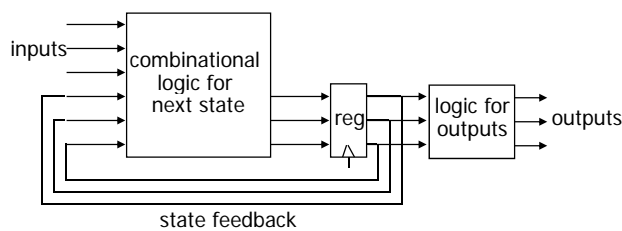

Moore machine

Outputs are a function of current state

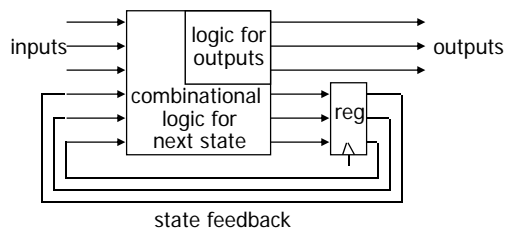Outputs change synchronously with state changes



Mealy machine

Outputs depend on state and on inputs


Input changes can cause immediate output changes (**asynchronous**)

Comparing Moore and Mealy machines

- ◆ Moore machines
 - + Safer to use because outputs change at clock edge
 - May take additional logic to decode state into outputs
- ◆ Mealy machines
 - + Typically have fewer states
 - + React faster to inputs — don't wait for clock
 - Asynchronous outputs can be dangerous
- ◆ We often design synchronous Mealy machines
 - Design a Mealy machine
 - Then register the outputs


Synchronous (registered) Mealy machine

- ◆ Registered state **and** registered outputs
 - No glitches on outputs

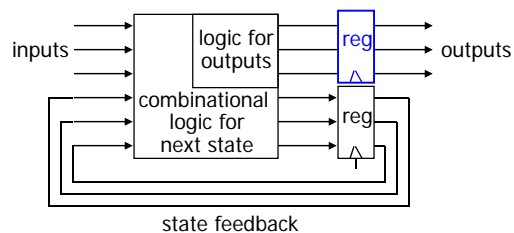


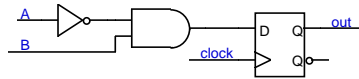Example 0 -> 1: Moore or Mealy?

- ◆ Recognize A,B = 0,1
 - Mealy or Moore?



Registered Mealy
(actually Moore)

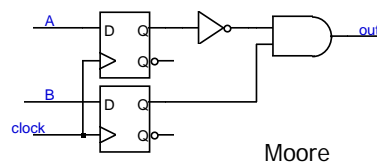

FSM design procedure reminder

- Counter-design procedure
 1. State diagram
 2. State-transition table
 3. Next-state logic minimization
 4. Implement the design
- FSM-design procedure
 1. State diagram
 2. state-transition table
 3. State minimization
 4. State encoding
 5. Next-state logic minimization
 6. Implement the design


Example: A parity checker

- ◆ Serial input string
 - OUT=1 if odd # of 1s in input
 - OUT=0 if even # of 1s in input
- ◆ Let's do this for Moore and Mealy


Example: A parity checker

1. State diagram

Moore

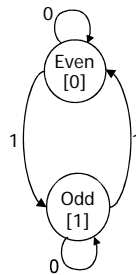

Mealy

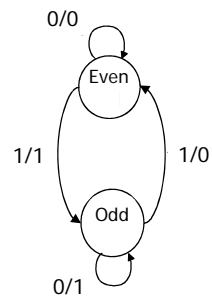

Example: A parity checker

1. State-transition table

Moore

Present State	Input	Next State	Present Output
Even	0	Even	0
Even	1	Odd	0
Odd	0	Odd	1
Odd	1	Even	1

Mealy

Present State	Input	Next State	Present Output
Even	0	Even	0
Even	1	Odd	1
Odd	0	Odd	1
Odd	1	Even	0

Example: A parity checker

3. State minimization: Already minimized

- Need both states (even and odd)
- Use one flip-flop

Example: A parity checker

4. State encoding

Moore

Assignment
Even 0
Odd 1

Present State	Input	Next State	Present Output
0	0	0	0
0	1	1	0
1	0	1	1
1	1	0	1

Mealy


Present State	Input	Next State	Present Output
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

Example: A parity checker

5. Next-state logic minimization

- Assume D flip-flops
- Next state = (present state) XOR (present input)

6. Implement the design

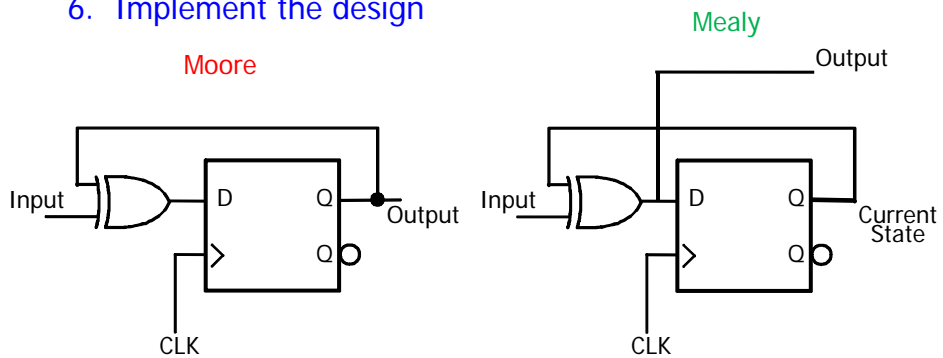


Example: A vending machine

- ◆ 15 cents for a cup of coffee
- ◆ Doesn't take pennies or quarters
- ◆ Doesn't provide any change


Last lecture

We had mix of

Moore and Mealy

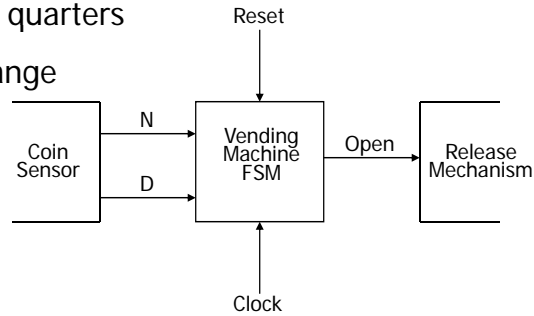


A vending machine: Moore machine

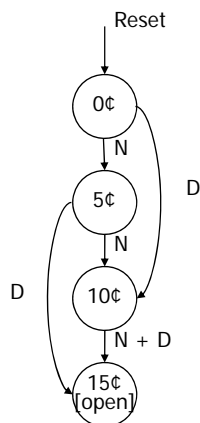

present state	inputs		next state	present output
	D	N		
0c	0	0	0c	0
	0	1	5c	0
	1	0	10c	0
	1	1	-	-
5c	0	0	5c	0
	0	1	10c	0
	1	0	15c	0
	1	1	-	-
10c	0	0	10c	0
	0	1	15c	0
	1	0	15c	0
	1	1	-	-
15c	-	-	15c	1

symbolic state table

A vending machine: Mealy machine

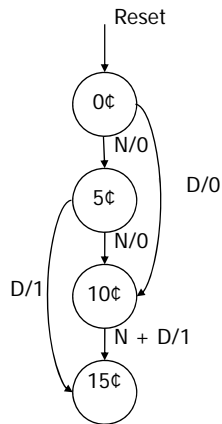

present state	inputs		next state	present output
	D	N		
0c	0	0	0c	0
	0	1	5c	0
	1	0	10c	0
	1	1	-	-
5c	0	0	5c	0
	0	1	10c	0
	1	0	15c	1
	1	1	-	-
10c	0	0	10c	0
	0	1	15c	1
	1	0	15c	1
	1	1	-	-
15c	-	-	15c	1

symbolic state table

A vending machine: State encoding


Moore

Mealy


present state		inputs		next state		present output	present state		inputs		next state		present output
Q1	Q0	D	N	D1	D0		Q1	Q0	D	N	D1	D0	
0	0	0	0	0	0	0	0	0	0	0	0	0	0
		0	1	0	1	0			0	1	0	1	0
		1	0	1	0	0			1	0	1	0	0
		1	1	-	-	-			-	-	-	-	-
0	1	0	0	0	1	0	0	1	0	0	0	1	0
		0	1	1	0	0			0	1	1	0	0
		1	0	1	1	0			1	0	1	1	1
		1	1	-	-	-			-	-	-	-	-
1	0	0	0	1	0	0	1	0	0	0	1	0	0
		0	1	1	1	0			0	1	1	1	1
		1	0	1	1	0			1	0	1	1	1
		1	1	-	-	-			-	-	-	-	-
1	1	-	-	1	1	1	1	-	-	1	1	1	

A vending machine: Logic minimization

Moore

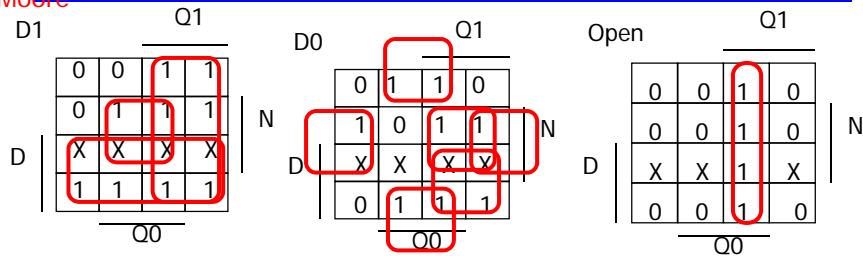


Mealy

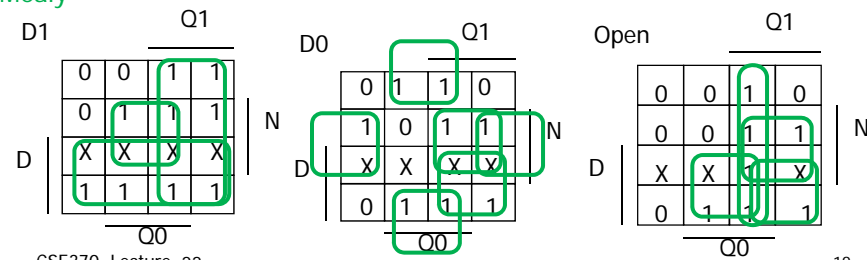

A vending machine: Implementation

Moore

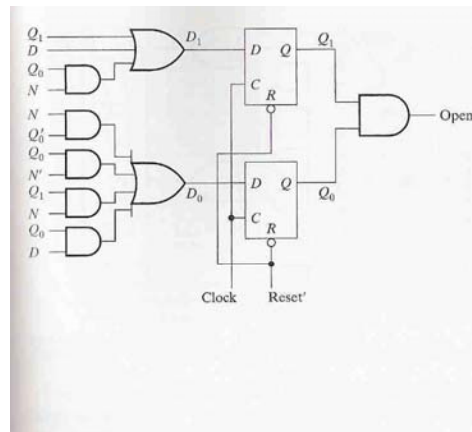

Mealy

