 


## Sequential logic

- Sequential circuits
  - simple circuits with feedback
  - latches
  - edge-triggered flip-flops
- Timing methodologies
  - cascading flip-flops for proper operation
  - clock skew
- Basic registers
  - shift registers
  - simple counters
- Hardware description languages and sequential logic


## Circuits with feedback

- How to control feedback?
  - what stops values from cycling around endlessly



 
## Simplest circuits with feedback

- Two inverters form a static memory cell
  - will hold value as long as it has power applied



- How to get a new value into the memory cell?
  - selectively break feedback path
  - load new value into cell

 



Autumn 2010

CSE370 - XIII - Sequential Logic



3
  
## Memory with cross-coupled gates

- Cross-coupled NOR gates
  - similar to inverter pair, with capability to force output to 0 (reset=1) or 1 (set=1)



- Cross-coupled NAND gates
  - similar to inverter pair, with capability to force output to 0 (reset=0) or 1 (set=0)

 
 


Autumn 2010


CSE370 - XIII - Sequential Logic

4

## Timing behavior

  

## State behavior of R-S latch

 


- Truth table of R-S latch behavior

S	R	Q
0	0	hold
0	1	0
1	0	1
1	1	unstable




## Theoretical R-S latch behavior

 

 
### State diagram

- states: possible values of outputs
- transitions: changes based on inputs




## Theoretical R-S latch behavior

 

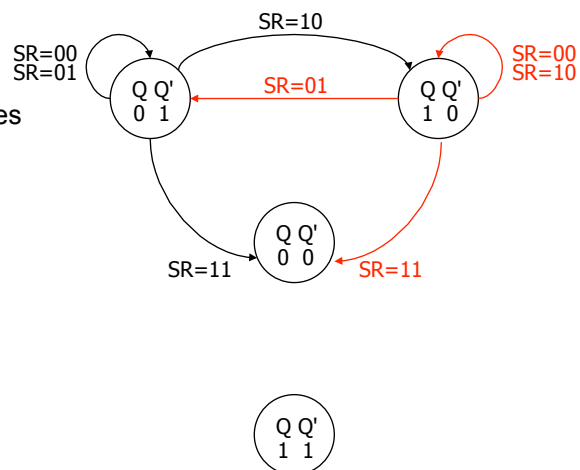
### State diagram

- states: possible values of outputs
- transitions: changes based on inputs




## Theoretical R-S latch behavior

 

 
### State diagram

- states: possible values of outputs
- transitions: changes based on inputs




## Theoretical R-S latch behavior

 

 
### State diagram

- states: possible values of outputs
- transitions: changes based on inputs


possible oscillation between states 00 and 11



## Observed R-S latch behavior


 


 - Very difficult to observe R-S latch in the 1-1 state
  - one of R or S usually changes first
- Ambiguously returns to state 0-1 or 1-0
  - a so-called "race condition"
  - or non-deterministic transition



## R-S latch analysis

- Break feedback path

  


S	R	Q(t)	Q(t+Δ)	
0	0	0	0	hold
0	0	1	1	
0	1	0	0	reset
0	1	1	0	
1	0	0	1	set
1	0	1	1	
1	1	0	X	not allowed
1	1	1	X	

		S	
Q(t)	0	0	1
	1	0	1
		R	

characteristic equation  
 $Q(t+\Delta) = S + R' Q(t)$

## R-S latch using NAND gates

 

S	R	S'	R'	Q(t)	Q(t+Δ)	
0	0	1	1	0	0	hold
0	0	1	1	1	1	
0	1	1	0	0	0	reset
0	1	1	0	1	0	
1	0	0	1	0	1	set
1	0	0	1	1	1	
1	1	0	0	0	X	not allowed
1	1	0	0	1	X	



		S	
Q(t)	0	0	1
	1	0	1
		R	

characteristic equation  
 $Q(t+\Delta) = S + R'Q(t)$
  
## Gated R-S latch


- Control when R and S inputs matter

- otherwise, the slightest glitch on R or S while enable is low could cause change in stored value




 
## Clocks

- Used to keep time
  - wait long enough for inputs (R' and S') to settle
  - then allow to have effect on value stored
- Clocks are regular periodic signals
  - period (time between clock ticks)
  - duty-cycle (clock pulse width - expressed as % of period)


  
## Clocks (cont'd)


- Controlling an R-S latch with a clock
  - R and S can't change while clock is active
  - only have half of clock period for signal changes to propagate
  - signals must be stable for the other half of clock period





 
## Cascading latches

- Connect output of one latch to input of another
- How to stop changes from racing through chain?
  - need to be able to control flow of data from one latch to the next
  - move one latch per clock period
  - have to worry about logic between latches (arrows) that is too fast



 
## Master-slave structure

- Break flow by alternating clocks (like an air-lock)
  - use positive clock to latch inputs into one R-S latch
  - use negative clock to change outputs with another R-S latch
- View pair as one basic unit
  - master-slave flip-flop
  - twice as much logic
  - output changes a few gate delays after the falling edge of clock but does not affect any cascaded flip-flops



## D flip-flop

- Make S and R complements of each other
  - eliminates 1s catching problem
  - can't just hold previous value
    - must have new value ready every clock period
  - value of D just before clock goes low is what is stored in flip-flop
  - can make R-S flip-flop by adding logic to make  $D = S + R'Q$

 


Autumn 2010

CSE370 - XIII - Sequential Logic

19
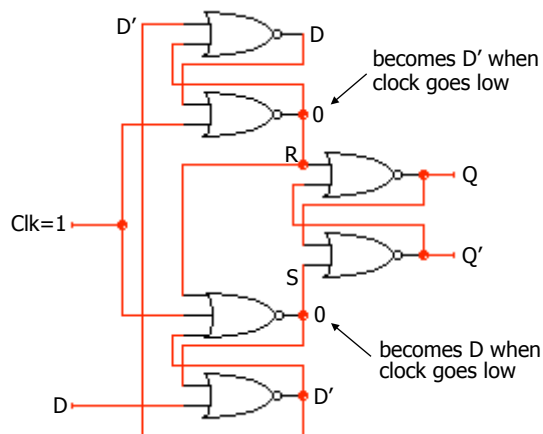
## Edge-triggered flip-flops using gates


- Only 6 gates
  - sensitive to inputs only near edge of clock signal (not while high)



negative edge-triggered D flip-flop (D-FF)

 4-5 gate delays

must respect setup and hold time constraints to successfully capture input



characteristic equation  
 $Q(t+1) = D$


Autumn 2010

CSE370 - XIII - Sequential Logic

20


## Edge-triggered flip-flops using transistors

- Only 8 transistors

 
 
## Edge-triggered flip-flops (cont'd)

- Positive edge-triggered
  - inputs sampled on rising edge; outputs change after rising edge
- Negative edge-triggered flip-flops
  - inputs sampled on falling edge; outputs change after falling edge




## Timing methodologies


- Rules for interconnecting components and clocks
  - guarantee proper operation of system when strictly followed
- Approach depends on building blocks used for memory elements
  - we'll focus on systems with edge-triggered flip-flops
    - found in programmable logic devices such as our FPGA
  - many custom integrated circuits focus on level-sensitive latches
    - they are much smaller (but need to be careful about timing)
- Basic rules for correct timing:
  - (1) correct inputs, with respect to clock, are provided to the flip-flops
  - (2) no flip-flop changes state more than once per clocking event
 
## Timing methodologies (cont'd)




- Definition of terms
  - Clock: periodic event, causes state of memory element to change can be rising edge or falling edge or high level or low level
  - Setup time: minimum time before the clocking event by which the input must be stable ( $T_{\text{setup}}$  or  $T_{\text{su}}$ )
  - Hold time: minimum time after the clocking event until which the input must remain stable ( $T_{\text{hold}}$  or  $T_{\text{h}}$ )



 there is a timing "window" around the clocking event during which the input must remain stable and unchanged in order to be recognized



## Comparison of latches and flip-flops

   


behavior is the same unless input changes  
while the clock is high

## Comparison of latches and flip-flops (cont'd)

Type	When inputs are sampled	When output is valid
unclocked latch	always	propagation delay from input change
level-sensitive latch	clock high ( $T_{su}/T_h$ around falling edge of clock)	propagation delay from input change or clock edge (whichever is later)
master-slave flip-flop	clock hi-to-lo transition ( $T_{su}/T_h$ around falling edge of clock)	propagation delay from falling edge of clock
negative edge-triggered flip-flop	clock hi-to-lo transition ( $T_{su}/T_h$ around falling edge of clock)	propagation delay from falling edge of clock
 
## Typical timing specifications


- Positive edge-triggered D flip-flop
  - setup and hold times
  - minimum clock width
  - propagation delays (low to high, high to low, max and typical)



all measurements are made from the clocking event (the rising edge of the clock)
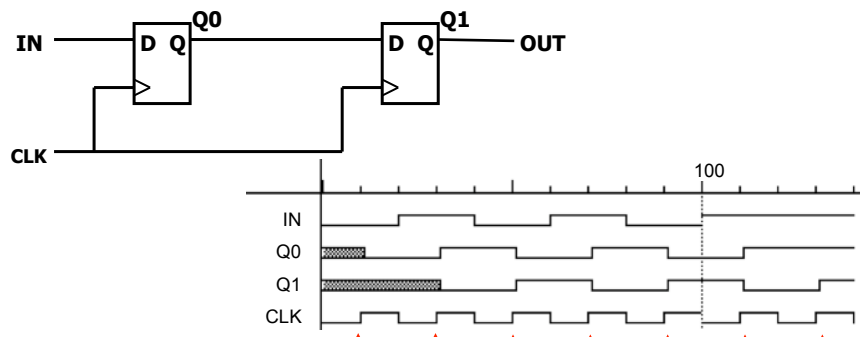
## Cascading edge-triggered flip-flops


- Shift register
  - new value goes into first stage
  - while previous value of first stage goes into second stage
  - consider setup/hold/propagation delays (prop must be > hold)


 
## Cascading edge-triggered flip-flops (cont'd)

- Why this works

- propagation delays exceed hold times
- clock width constraint exceeds setup time
- this guarantees following stage will latch current value before it changes to new value




timing constraints guarantee proper operation of cascaded components

assumes infinitely fast distribution of the clock
 
## Clock skew

- When it doesn't work

- correct behavior assumes next state of all storage elements determined by all storage elements at the same time
- this is difficult in high-performance systems because time for clock to arrive at flip-flop is comparable to delays through logic
- effect of skew on cascaded flip-flops:



original state: IN = 0, Q0 = 1, Q1 = 1      expected next state: Q0 = 0, Q1 = 1  
 due to skew, next state becomes: Q0 = 0, Q1 = 0 (0 races through two FFs instead of one)

## Summary of latches and flip-flops

- Development of D-FF
  - level-sensitive used in custom integrated circuits
    - can be made with 8 switches
  - edge-triggered used in modern programmable logic devices
  - good choice for data storage register
- Historically, JK-FF was popular but now never used
  - similar to RS but with 1-1 being used to toggle output
  - JK = 00 hold, 01 reset, 10 set, 11 toggle (complement state)
  - good in days of SSI (more complex input function:  $D = J Q' + K' Q$ )
  - can always be implemented using D-FF, if needed
- Preset and clear inputs are highly desirable on flip-flops
  - used at start-up or to reset system to a known state

## Flip-flop features

- Reset (set state to 0) – R
  - synchronous:  $D_{new} = R' \cdot D$  (when next clock edge arrives)
  - asynchronous: doesn't wait for clock, quick but dangerous
- Preset or set (set state to 1) – S (or sometimes P)
  - synchronous:  $D_{new} = D + S$  (when next clock edge arrives)
  - asynchronous: doesn't wait for clock, quick but dangerous
- Both reset and preset
  - $D_{new} = R' \cdot D + S$  (set-dominant)
  - $D_{new} = R' \cdot D + R'S$  (reset-dominant)
- Selective input capability (input enable or load) – LD or EN
  - multiplexor at input:  $D_{new} = LD' \cdot Q + LD \cdot D$
  - load may or may not override reset/set (usually R/S have priority)
- Complementary outputs – Q and Q'