

## Today

- Simplification
  - Practical use of DeMorgan's Theorem
  - Methodology
- Logic Gates
  - Equivalencies, Cost, and Notation
  - Multiple Input Semantics
- Effective Design Working

## DeMorgan and "Break the Bar"

- Motivation: Inversion of Entire Functions
- Heuristic: When simplifying, eliminate **multivariable negations** 1st
- Example: Simplify the following equation:

$$f(a,b) = \overline{ab}$$

$$f(a,b) = \overline{a} + \overline{b}$$

DeMorgan's Law

## "Break the Bar" Example 1

- Simplify the following equation:

$$f(x, y, z) = \overline{xy + xz}$$

$$f(x, y, z) = \overline{xy} \bullet \overline{xz}$$

DeMorgan's Law

$$f(x, y, z) = (\overline{x} + \overline{y})(\overline{x} + \overline{z})$$

DeMorgan's Law

$$f(x, y, z) = (\overline{x} + \overline{y})(x + \overline{z})$$

Involution

## "Break the Bar" Example 2

- Simplify the following equation:

$$f(x, y, z) = \overline{\overline{xy} + z} + x\overline{y}z + x\overline{y}\overline{z}$$

$$f(x, y, z) = \overline{\overline{xy}} \bullet \overline{z} + x\overline{y}z + x(\overline{y} + \overline{z})$$

DeMorgan's Law

$$f(x, y, z) = xy\overline{z} + x\overline{y}z + x(\overline{y} + \overline{z})$$

Involution

$$f(x, y, z) = xy\overline{z} + x\overline{y}z + x\overline{y} + x\overline{z}$$

Distributive

## Minimization "Cost"

- Dependant on target technology (CMOS)
- Possible Metrics: delay, integration, power, size, noise, \$\$, and driving capability
- Issues
  - "How do I minimize automatically?"
  - "How do I know something is minimized?"
- Better Algorithms
  - Boolean Cubes
  - Karnaugh Maps
  - Quine-McKlusky Algorithm

## Logic Gates

- Equivalencies and Notation
  - Understanding vs. Technology Mapping
  - Converting to NAND (or NOR) only circuits

$$f(a, b, c) = \overline{ab} + c$$

- Multiple Inputs
  - "Fan-in" (vs. "Fan-out")
  - Syntax and Semantics (AND, OR, XOR)

## Waveforms and Behavior

- Propagation Delay
  - Analog World
  - Scoped to many levels
- Highly Variable
  - Don't count on any particular behavior
  - Published Upper and Lower Bounds

## Effective DesignWorksing

- Draw a schematic for the following in DesignWorks:
  - Standard Wiring
  - Self-imposed regular structures

$$f(x, y, z) = \overline{\overline{x}}\overline{y} + xy + x\overline{y}$$