
 


Homework Set 6

DUE: Feb 19, 1999, 12:30 pm

Please show *all* of your work. Solutions not involving DesignWorks do not have to be typeset, but may be if desired. In any case, your solutions must be legible.

 - 1) Katz problem 6.12 (a), (b), (c), and (d) [True/False questions about latches and flipflops]. If your answer is FALSE, include a brief explanation of why.
- 2) Katz problem 6.11 (a), (b), and (c) [Timing diagram of D device].
- 3) Consider the following circuit and clock input as shown.
 - a) Draw the timing diagram for OUT. Assume that $OUT = 0$ at time $t = 0$. Describe the function the circuit performs.
 - b) In the waveform shown, the input clock is at a duty cycle of 20%. What would OUT's duty cycle be if the input clock's duty cycle were instead (a) 50% or (b) 80%?



- 4) Katz problem 6.22 [clocking issues].
- 5) You will now construct a fourth addition circuit to add to your growing library of adders developed for the homework assignments.
 - a) Construct a 4-bit adder as a Verilog module in Designworks. Use the Verilog "+" operator to implement addition. Refer back to the tutorial on the web page to the section on how to get going with Verilog. Make sure that your module includes a carry-out. Turn in your Verilog source code
 - b) Connect a keypad and probes to your adder block for testing. Verify that your adder works. Turn in printouts showing the following two tests:
 - i) "1111" + "0001"
 - ii) "1010" + "0101"