

Control Unit (single cycle implementation)

- Control unit sends control signals to data path and memory depending
 - on the opcode (and function field)
 - results in the ALU (for example for Zero test)
- These signals control
 - muxes; read/write enable for registers and memory etc.
- Some “control” comes directly from instruction
 - register names
- Some actions are performed at every instruction so no need for control (in this single cycle implementation)
 - incrementing PC by 4; reading instr. memory for fetching next

Building the control unit

- Decompose the problem into
 - Data path control (register transfers)
 - ALU control
- Setting of control lines by control unit totally specified in the ISA
 - for ALU by opcode + function bits if R-R format
 - for register names by instruction (including opcode)
 - for reading/writing memory and writing register by opcode
 - muxes by opcode
 - PC by opcode + result of ALU

Example

- Limit ourselves to:
 - R-R instructions: add, sub, and, or, slt –
 - OPcode = 0 but different function bits
 - Load-store: lw, sw
 - Branch: beq
- ALU control
 - Need to add for: add, lw, sw
 - Need to sub for: sub, beq
 - Need to and for :and
 - Need to or for :or
 - Need to set less than for : slt

ALU Control

- ALU control: combination of opcode and function bits
- Decoding of opcodes yields 3 possibilities hence 2 bits
 - AluOp1 and ALUOp2
- ALU control:
 - Input 2 ALUop bits and 6 function bits
 - Output one of 5 possible ALU functions
 - Of course, lots of don't care for this **very** limited implementation


Implementation of Overall Control Unit

- Input: opcode (and function bits for R-R instructions)
- Output: setting of control lines
- Can be done by logic equations
- If not too many, like in RISC machines
 - Use of PAL's (cf. CSE 370).
 - In RISC machines the control is “hardwired”
- If too large (too many states etc.)
 - Use of microprogramming (a microprogram is a hardwired program that interprets the ISA)
- Or use a combination of both techniques (Pentium)


Where are control signals needed (cf. Figure 5.13)

- Register file
 - **RegWrite** (Register write signal for R-type, Load)
 - **RegDst** (Register destination signal: rd for R-type, rt for Load)
- ALU
 - **ALUSrc** (What kind of second operand: register or immediate)
 - **ALUop** (What kind of function: ALU control for R-type)
- Data memory
 - **MemRead** (Load) or **MemWrite** (Store)
 - **MemtoReg** (Result register written from ALU or memory)
- Branch control
 - **PCSrc** (PC modification if branch is taken)


MIPS FloorPlan & Control lines

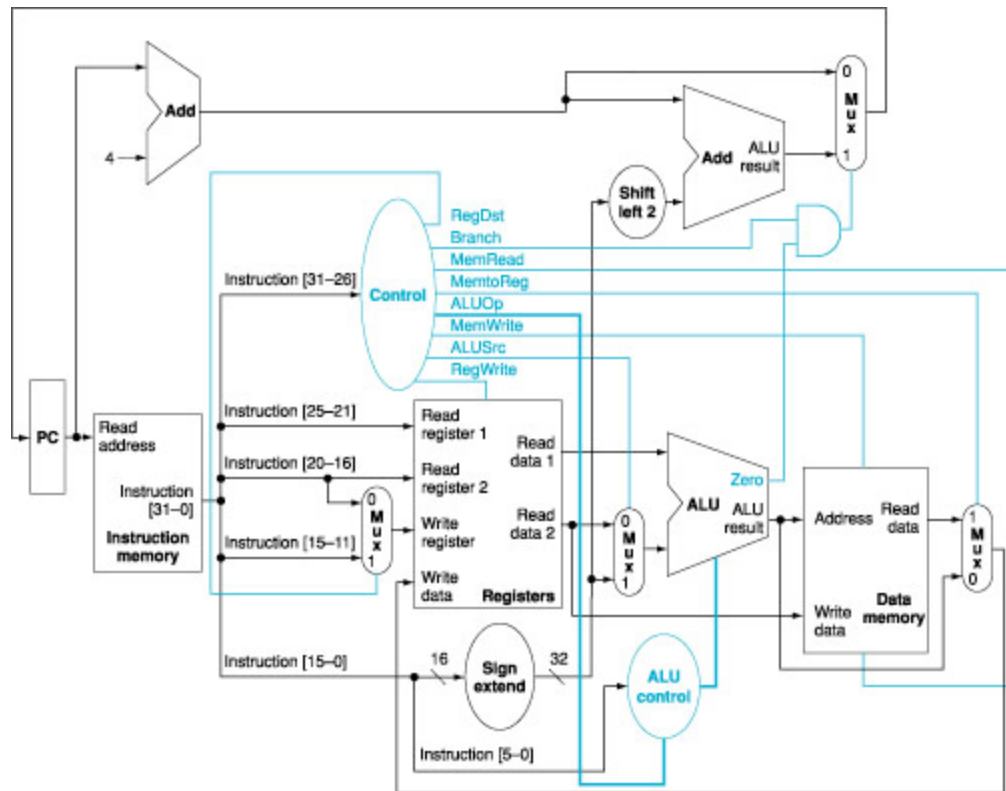


Basic 3 Operation 1-bit ALU

 



Chain Together 32 “3 Op 1-bit ALUs”

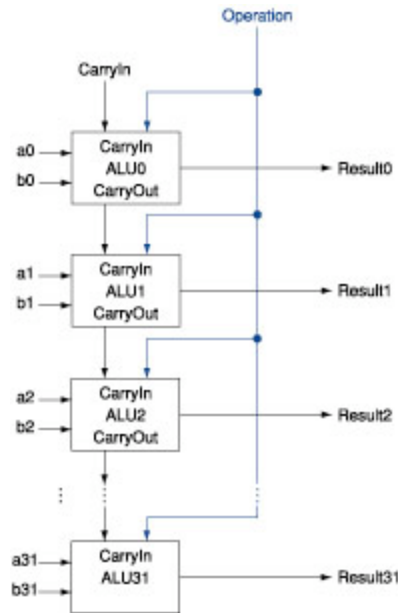


Basic 4 Operation 1-bit ALU

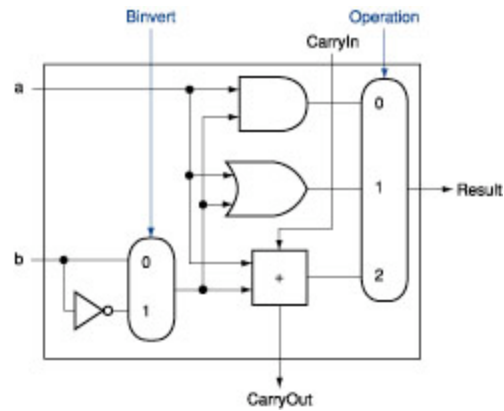

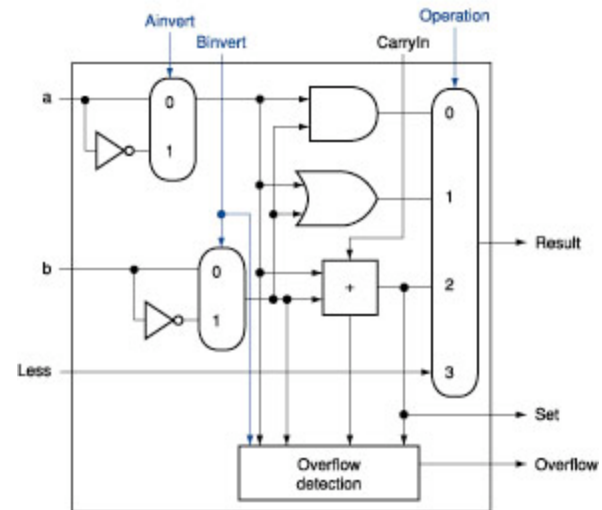
 
Adding SLT to 1-bit ALU & Detect Overflow




Chain Together 32 “1-bit ALUs”

 

ALU floorplan & Symbol

 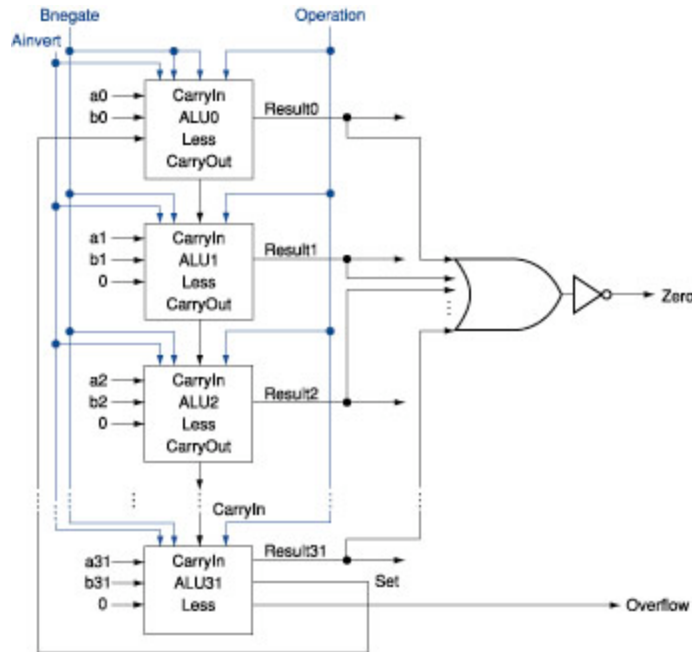

Control lines

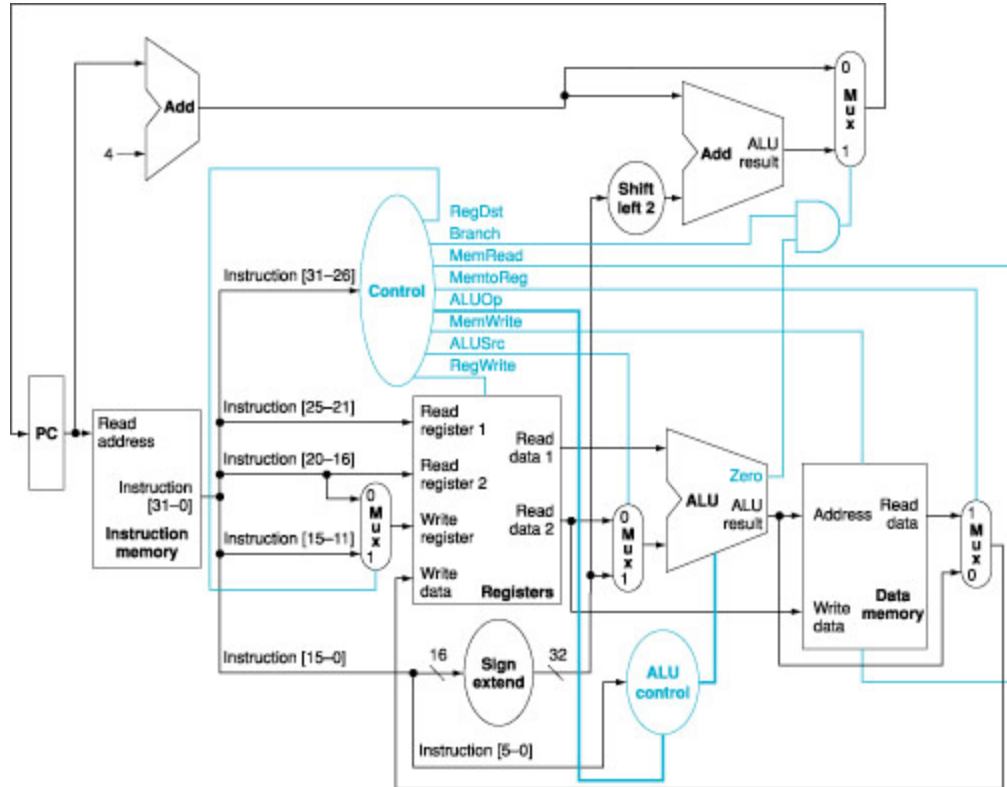


How are the control signals asserted

- Decoding of the opcode by control unit yields
 - Control of the 3 muxes (RegDst, ALUSrc, MemtoReg): 3 control lines
 - Signals for RegWrite, Memread, Memwrite: 3 control lines
 - Signals to activate ALU control (e.g., restrict ourselves to 2)
 - Signal for branch (1 control line)
 - decoding of opcode ANDed with ALU zero result
- Input Opcode: 6 bits
- Output 9 control lines


Control lines

Signal	R-type	lw	sw	beq
RegDest	1	0	X	X
ALUSrc	0	1	1	0
MemtoReg	0	1	X	X
RegWrite	1	1	0	0
MemRead	0	1	0	0
MemWrite	0	0	1	0
Branch	0	0	0	1
ALUOp1	1	0	0	0
ALUOp0	0	0	0	1

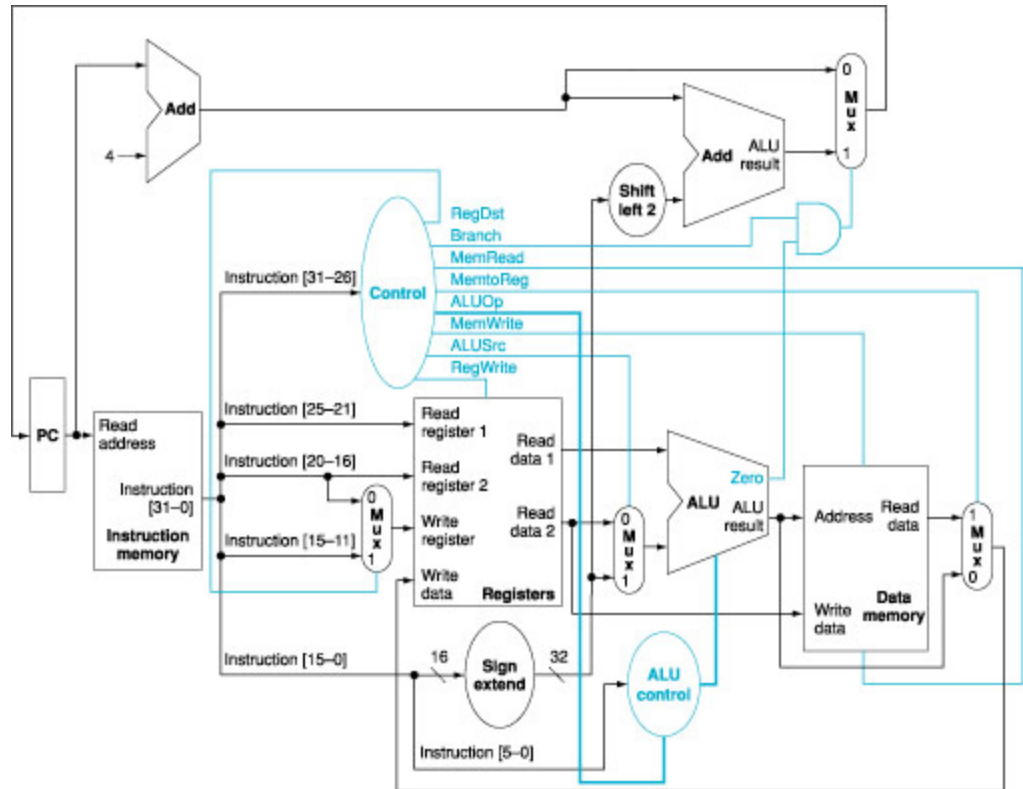

Computing the Control

Signal	R-type	lw	sw	beq
Op5	0	1	1	0
Op4	0	0	0	0
Op3	0	0	1	0
Op2	0	0	0	1
Op1	0	1	1	0
Op0	0	1	1	0
RegDest	1	0	X	X
ALUSrc	0	1	1	0
MemtoReg	0	1	X	X
RegWrite	1	1	0	0
MemRead	0	1	0	0
MemWrite	0	0	1	0
Branch	0	0	0	1
ALUOp1	1	0	0	0
ALUOp0	0	0	0	1

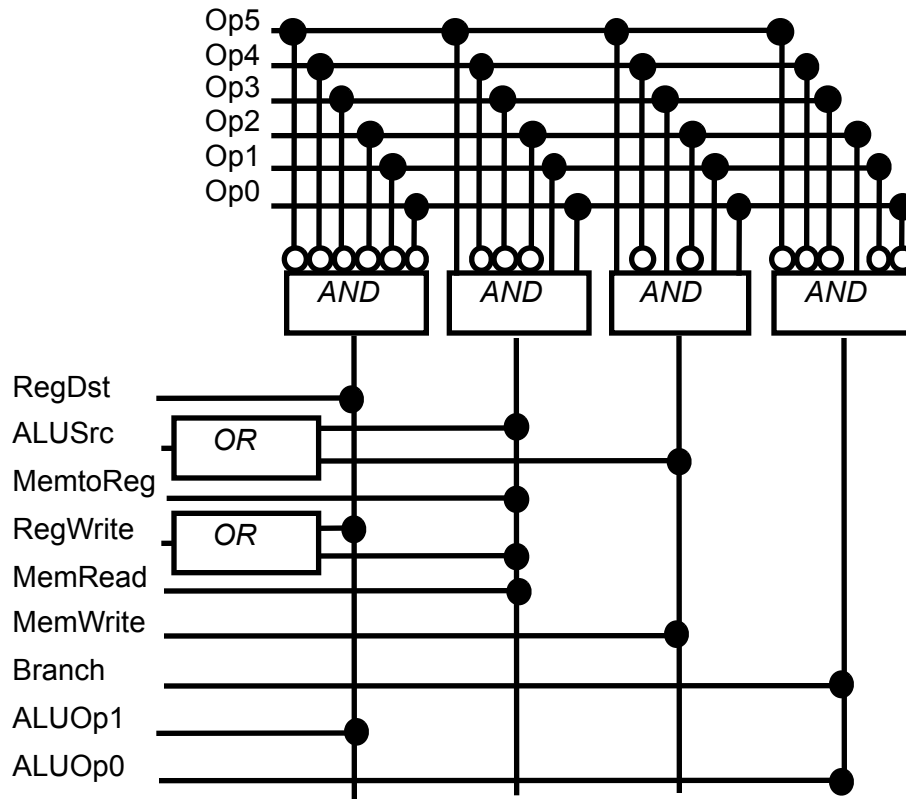

Computing the Cycle Time

Suppose the following times apply ...

Memory units: 10ns

ALU and adders: 10ns

Register file ref: 5ns

All other operations are 0ns.

Charges for instructions are ...

R-format: 30ns

Load inst: 40ns

Store inst: 35ns

Branch: 25ns

Jump: 10ns

Instruction Mix GCC	
22%	Load
11%	Store
49%	R-type
16%	Branch
2%	Jump