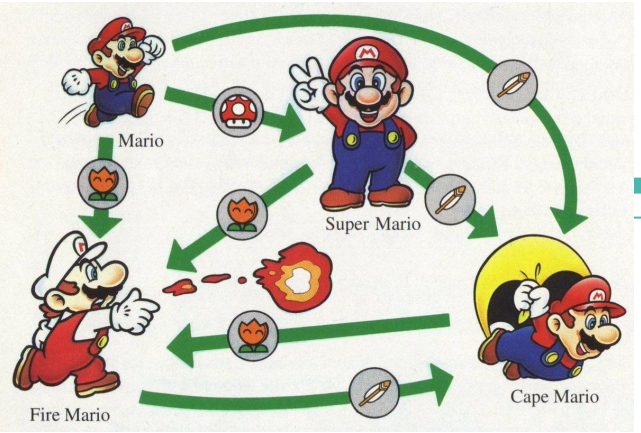



Section 5

Finite State Machines

Or “Fun” State Machines with Violet & Packard

Administrivia

- **Lab 5:** Report due next Thursday (11/12) @ 2:30 pm, no demos on Wednesday due to Veteran's day!
  - ⚠️ This lab is harder than previous labs ⚠️
  - Resource Utilization Extra Credit - moving on from gate level optimization to number of registers and adaptive logic units.
  - Resource Utilization Leaderboard - Extra credit will not be assigned based on the leaderboard, it is just a fun way to compare with peers.
- **Lab 6:** Report due 11/18
  - ⚠️ This lab is a LOT harder than Lab 5 ⚠️

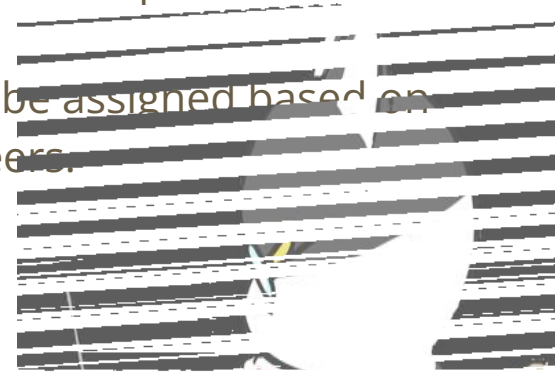

New SystemVerilog Commands

New SystemVerilog Commands (1/2)

- `enum` – create an enumerated type with a restricted set of named values.
  - Basic usage: `enum <original type> {<name_list>} <vars>;`
  - `<original type>` must be wide enough to support the length of `<name_list>`; if omitted, defaults to `int` type.
  - By default, names in the `<name_list>` are assigned consecutive values starting from `0`.
    - Can explicitly assign values using `name=<value>` syntax.
- Example: `enum logic [1:0] {S0, S1, S11=2'b11} ps, ns;`
  - `S0` assigned `2'b00`, `S1` assigned `2'b01`.
  - Two variables declared that can *only* take on the values `S0`, `S1`, and `S11` (no `2'b10`).


New SystemVerilog Commands (2/2)

- Ternary operator – shorthand for an `if-else` statement using the syntax `<cond> ? <then> : <else>` (same syntax as C).
  - Same syntax as C/C++.
  - Never necessary to use, just results in more compact code.
  - Very useful in combinational logic for next state and output logic
- Examples:
  - ```
    case (ps)
      S0:  ns = w ? S1  : S0;
      S1:  ns = w ? S11 : S0;
      S11: ns = w ? S11 : S0;
    endcase
    ```
  - ```
    assign HEX0 = SW[0] ? leds : 7'b1111111;
    ```

Finite State Machine Implementation

FSM Implementation Notes

- The **state diagram design** is *by far* the most important part! The SystemVerilog implementation process is fairly mechanical.
  - It is worth it to spend time on a good FSM drawing. It will help prevent a lot of debugging.
- Module design notes:
  - Must have a clock input (*e.g.*, `clk`, `clock`, `CLOCK_50`) for sequential elements.
  - Should have a reset input (*e.g.*, `rst`, `reset`) for "initialization."
  - Must have a present state (`ps`); recommended to also have a next state (`ns`).
    - Packard note: ALWAYS HAVE NS!!!

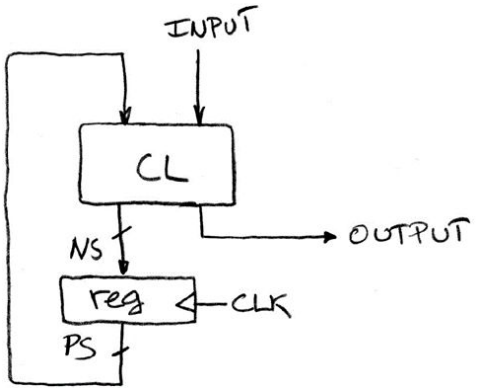


FSM Design Pattern

1) `// State Encodings and Variables`
   a) `enum` to define `ps` and `ns`
2) `// Next State Logic (ns)`
   a) `always_comb` or `assign` with *blocking* assignments (=)
3) `// Output Logic`
   a) `assign` or `always_comb` with *blocking* assignments (=)
   b) Mealy-type output example: `assign out = (ps == S1) & in;`
4) `// State Update Logic (ps) - including reset`
   a) `always_ff` with *non-blocking* assignments (<=)

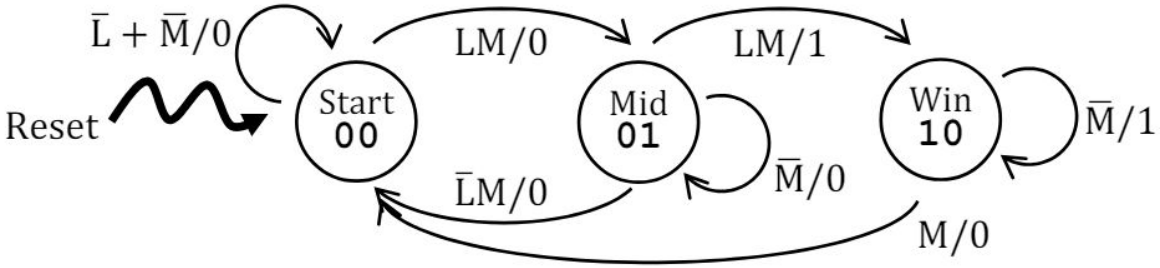
Exercise 1

- The following FSM represents a *Red Light, Green Light game*, where a player is only allowed to move forward (`M=1`) when the light is green (`L=1`). Here, the player wins (output `W=1`) after successfully moving twice; moving when the light is red (`L=0`) results in returning to the start



  - Implement this system in a module called **`light_game`**.

Exercise 1 (Solution) (1/5)

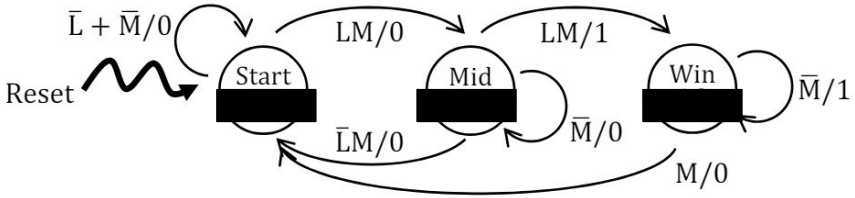

- Module outline

```
module light_game (input logic clk, reset, M, L, output logic W);










endmodule  // light_game
```

Exercise 1 (Solution) (2/5)

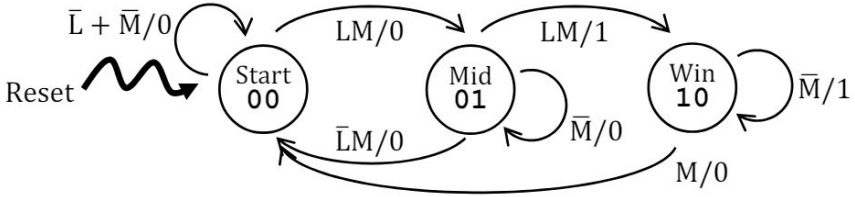

- State encodings and variables

```
module light_game (input logic clk, reset, M, L, output logic W);

  enum logic [1:0] {Start, Mid, Win} ps, ns;










endmodule  // light_game
```

Exercise 1 (Solution) (3/5)

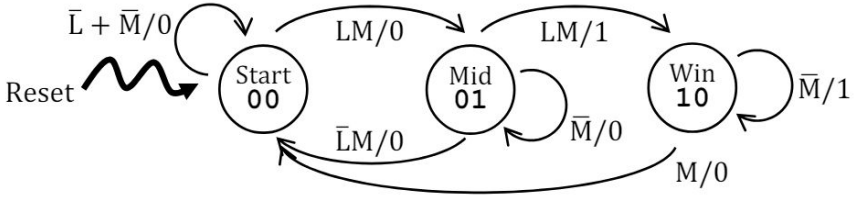

- Next state logic

```
module light_game (input logic clk, reset, M, L, output logic W);

  enum logic [1:0] {Start, Mid, Win} ps, ns;


  always_comb
    case (??)

    endcase



endmodule  // light_game
```

Exercise 1 (Solution) (3/5)

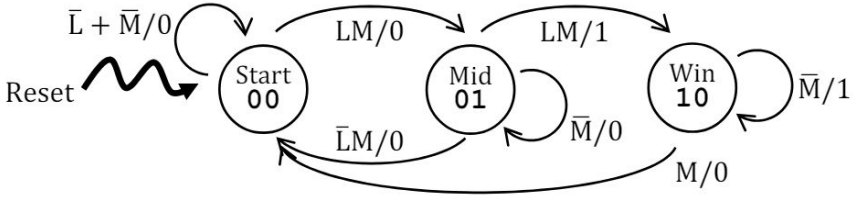

- Next state logic

```
module light_game (input logic clk, reset, M, L, output logic W);


  enum logic [1:0] {Start, Mid, Win} ps, ns;

  always_comb
    case (ps)
      Start: ns = (L & M) ? Mid : Start;
      Mid:   ns = (L & M) ? Win : (M ? Start : Mid);
      Win:   ns = M ? Start : Win;
    endcase



endmodule  // light_game
```

Exercise 1 (Solution) (4/5)

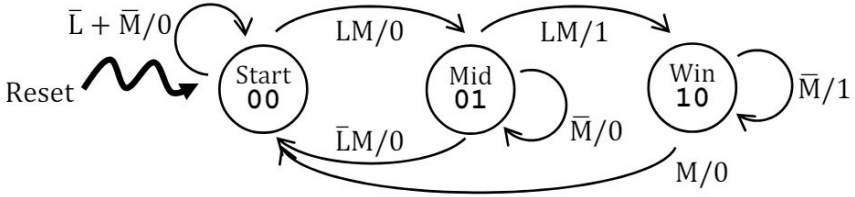

- Output logic


```
module light_game (input logic clk, reset, M, L, output logic W);

  enum logic [1:0] {Start, Mid, Win} ps, ns;

  always_comb
    case (ps)
      Start: ns = (L & M) ? Mid : Start;
      Mid:   ns = (L & M) ? Win : (M ? Start : Mid);
      Win:   ns = M ? Start : Win;
    endcase

  assign W = (ns == Win);  // alt: ((ps == Mid) & L & M) |
                           //      ((ps == Win) & ~M)
endmodule  // light_game
```

Exercise 1 (Solution) (5/5)

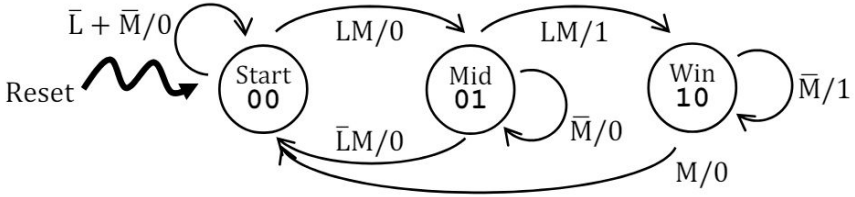

- State update logic

```
module light_game (input logic clk, reset, M, L, output logic W);

  enum logic [1:0] {Start, Mid, Win} ps, ns;


  ...  // next state logic
  ...  // output logic

  always_ff @(posedge clk)
    if (reset)
      ps <= Start;
    else
      ps <= ns;

endmodule  // light_game
```

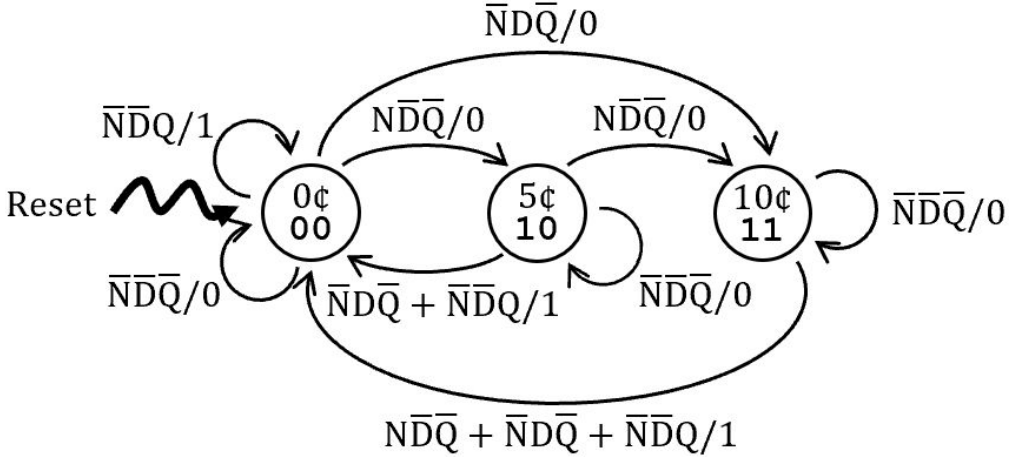
Exercise 2

- Below is an FSM for a modified vending machine with increased cost of 15¢ for gumballs that also accepting quarters (Q: 25¢); it still does not give change and can only take one coin at a time.



  - Implement this system in a module called **vend15**.

Exercise 2 (Solution) (1/5)

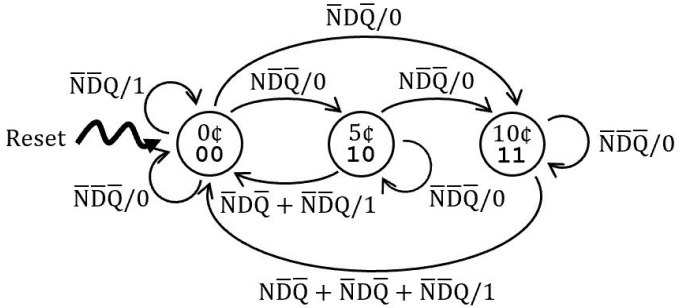

- Module outline

```
module vend15 (input logic clk, reset, N, D, Q, output logic Open);










endmodule  // vend15
```

Exercise 2 (Solution) (2/5)

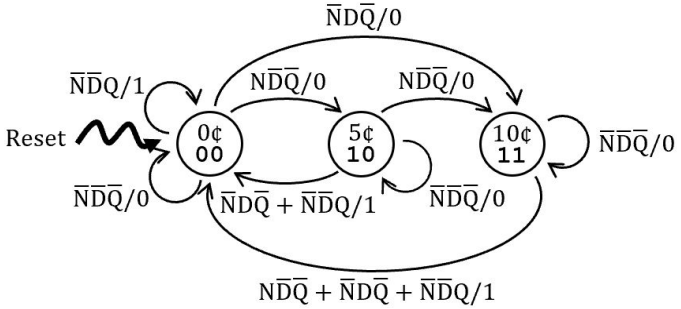

- State encodings and variables

```
module vend15 (input logic clk, reset, N, D, Q, output logic Open);
  enum logic [1:0] {Zero, Five=2'b10, Ten=2'b11} ps, ns;










endmodule  // vend15
```

Exercise 2 (Solution) (3/5)

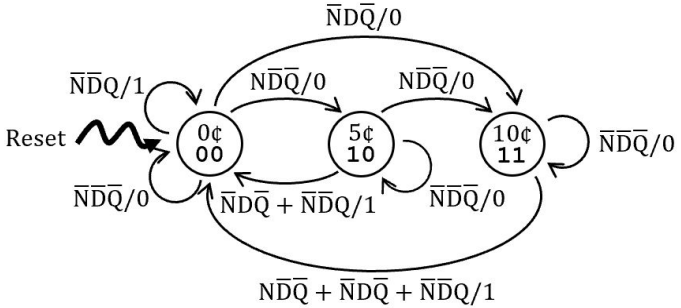


- Next state logic

```
module vend15 (input logic clk, reset, N, D, Q, output logic Open);
  enum logic [1:0] {Zero, Five=2'b10, Ten=2'b11} ps, ns;

  always_comb
    case (ps)
      Zero: case ({N, D, Q})
              3'b000: ns = Zero;
              3'b100: ns = Five;
              3'b010: ns = Ten;
              3'b001: ns = Zero;
              default: ns = ps;
            endcase
      ...  // Five and Ten defined similarly
    endcase
endmodule  // vend15
```

Exercise 2 (Solution) (4/5)

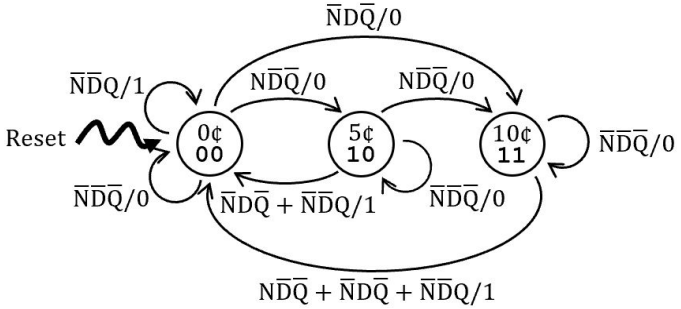

- Output logic

```
module vend15 (input logic clk, reset, N, D, Q, output logic Open);
  enum logic [1:0] {Zero, Five=2'b10, Ten=2'b11} ps, ns;

  ...  // next state logic

  assign Open = Q | ((ps != Zero) & D) | ((ps == Ten) & N);










endmodule  // vend15
```

Exercise 2 (Solution) (5/5)

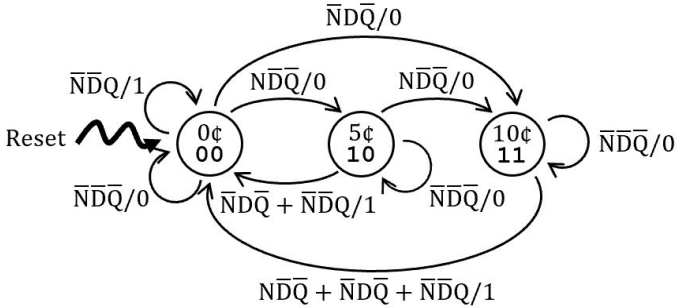

- State update logic

```
module vend15 (input logic clk, reset, N, D, Q, output logic Open);
  enum logic [1:0] {Zero, Five=2'b10, Ten=2'b11} ps, ns;

  ...  // next state logic

  assign Open = Q | ((ps != Zero) & D) | ((ps == Ten) & N);

  always_ff @(posedge clk)
    if (reset)
      ps <= Zero;
    else
      ps <= ns;

endmodule  // vend15
```

Finite State Machine Testing


FSM Test Bench Notes

- All notes about sequential test benches from last week still apply!
  - Generate a simulated clock (don't use `clock_divider`), start with a reset and define all inputs at `t=0`, add extra delay at end to see the effects of your last input changes.
- To thoroughly test your FSM, need to **take every transition that we care about** (can omit/ignore don't cares).
- Recommended test bench lines in `initial` block:

```
<input changes> @(posedge clk);  // current state: ???
```

- In ModelSim, you should at least add `ps` to waveforms.
  - Could also include `ns` or other signals involved in `ps`/`ns` computations.

FSM Test Bench Example (1/2)

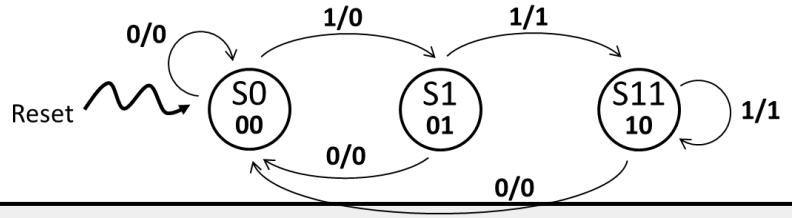


```
// generate test vectors
initial begin
  reset <= 1; w <= 0; @(posedge clk);  // reset
  reset <= 0;         @(posedge clk);  // curr state: S0










  $stop;  // pause the simulation
 end
```

FSM Test Bench Example (2/2)

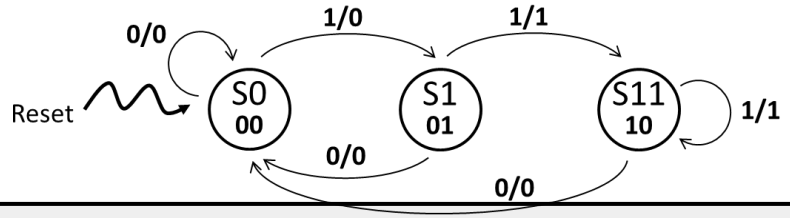


```
// generate test vectors
initial begin
  reset <= 1; w <= 0; @(posedge clk);  // reset
  reset <= 0;         @(posedge clk);  // curr state: S0
              w <= 1; @(posedge clk);  // curr state: S0
              w <= 0; @(posedge clk);  // curr state: S1
              w <= 1; @(posedge clk);  // curr state: S0
                      @(posedge clk);  // curr state: S1
                      @(posedge clk);  // curr state: S11
                      @(posedge clk);  // curr state: S11
              w <= 0; @(posedge clk);  // curr state: S11
                      @(posedge clk);  // curr state: S0 (extra cycle)
  $stop;  // pause the simulation
 end
```

Exercise 3

- Create a test bench for `vend15` and simulate it in ModelSim.
  - What's the minimum number of clock cycles required to thoroughly test it?

Exercise 3- Setup DUT (1/4)

- Create module, declare port connections, instantiate dut.

```
module vend15_tb ();
  logic clk, reset, N, D, Q, Open;

  vend15 dut (.*);









endmodule  // vend15_tb
```

Exercise 3- Setup DUT (2/4)

- Setup clock.

```
module vend15_tb ();
  ...  // signal declarations and dut instantiation

  parameter T = 100;
  initial
    clk = 1'b0;
  always begin
    #(T/2)  clk <= 1'b0;
    #(T/2)  clk <= 1'b1;
  end



endmodule  // vend15_tb
```

Exercise 3- Setup DUT (3/4)

- Define `initial` block and add `$stop` system task.

```
module vend15_tb ();
  ...  // signal declarations and dut instantiation
  ...  // clock generation

  initial begin

    $stop;
  end




endmodule  // vend15_tb
```

Exercise 3- Setup DUT (4/4)

- Start with a reset and initialize all inputs.

```
module vend15_tb ();
  ...  // signal declarations and dut instantiation
  ...  // clock generation

  initial begin
    {reset,N,D,Q} <= 4'b1000; @(posedge clk);  // reset


    $stop;
  end




endmodule  // vend15_tb
```


Exercise 3- Test Transitions (1/4)

- Map out a sequence of inputs that would allow us to test every transition.

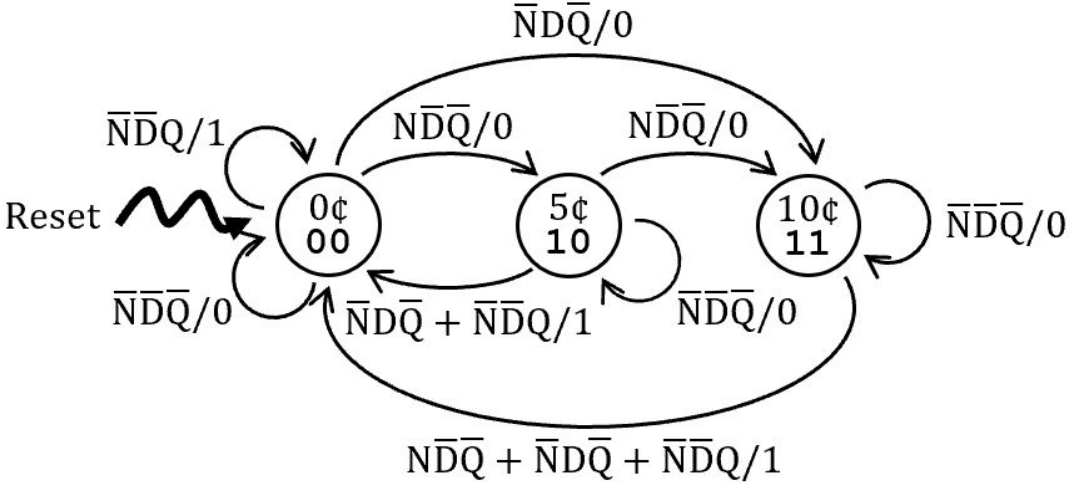


Exercise 3- Test Transitions (1/4)

- Map out a sequence of inputs that would allow us to test every transition.

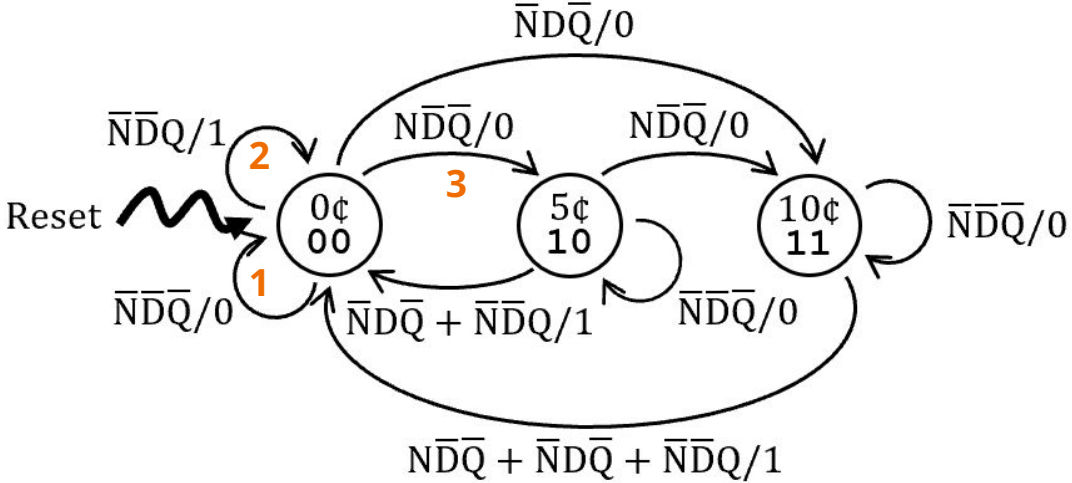


Exercise 3- Test Transitions (2/4)

- Map out a sequence of inputs that would allow us to test every transition.
  - This is just one of many possibilities!

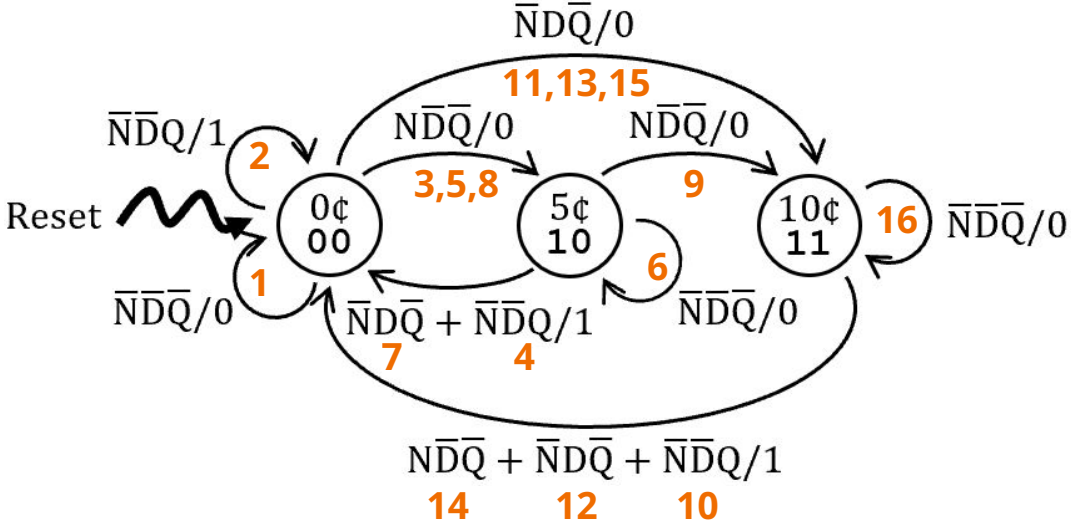

Exercise 3- Test Transitions (3/4)

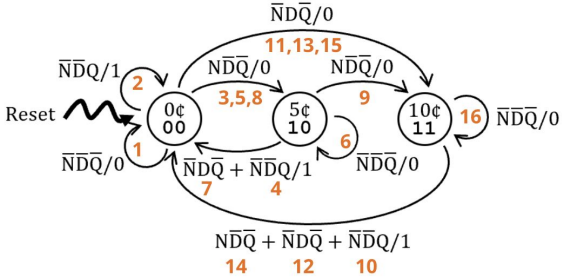

- Add the transitions we mapped out.

```
module vend15_tb ();
  ...  // signal declarations, dut instantiation, clock generation
  initial begin
    {reset,N,D,Q} <= 4'b1000; @(posedge clk);  // reset
    {reset,N,D,Q} <= 4'b0000; @(posedge clk);  // Zero (1)
          {N,D,Q} <= 3'b001;  @(posedge clk);  // Zero (2)
          {N,D,Q} <= 3'b100;  @(posedge clk);  // Zero (3)
          {N,D,Q} <= 3'b001;  @(posedge clk);  // Five (4)
          {N,D,Q} <= 3'b100;  @(posedge clk);  // Zero (5)
          {N,D,Q} <= 3'b000;  @(posedge clk);  // Five (6)
          {N,D,Q} <= 3'b010;  @(posedge clk);  // Five (7)
          {N,D,Q} <= 3'b100;  @(posedge clk);  // Zero (8)
                              @(posedge clk);  // Five (9)
    ...  // continued on next slide
```

Exercise 3- Test Transitions (4/4)


- Add the transitions we mapped out.


```
  ...  // signal declarations, dut instantiation, clock generation
  initial begin
    ...  // previous clock cycles
          {N,D,Q} <= 3'b001;  @(posedge clk);  // Ten  (10)
          {N,D,Q} <= 3'b010;  @(posedge clk);  // Zero (11)
                              @(posedge clk);  // Ten  (12)
                              @(posedge clk);  // Zero (13)
          {N,D,Q} <= 3'b100;  @(posedge clk);  // Ten  (14)
          {N,D,Q} <= 3'b010;  @(posedge clk);  // Zero (15)
          {N,D,Q} <= 3'b000;  @(posedge clk);  // Ten  (16)
                              @(posedge clk);  // extra
    $stop;
  end
endmodule  // vend15_tb
```

Exercise 3- Simulation Analysis (1/4)

Want to verify:

1. reset works
2. ALL the transitions between states as expected
3. our output matches what we expect

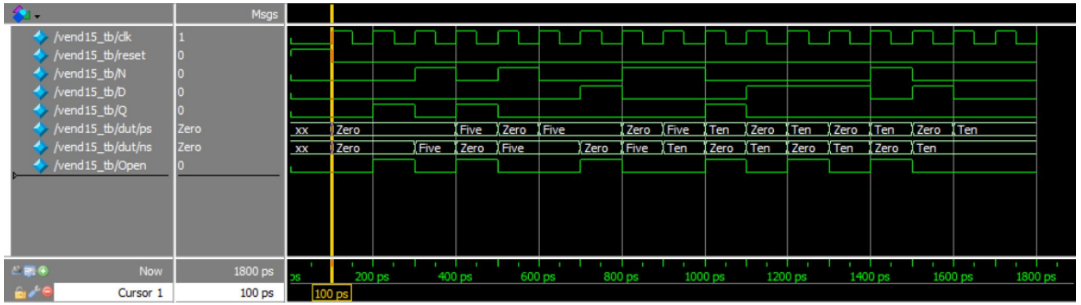

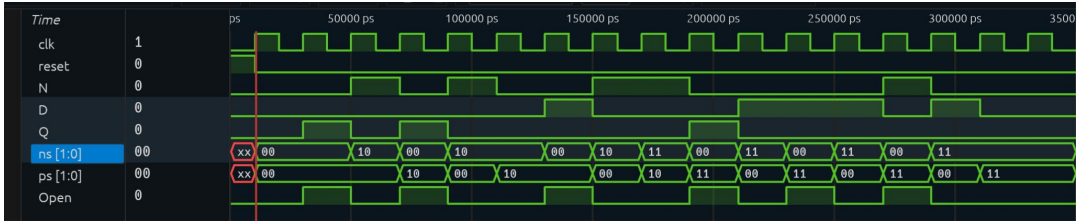

Exercise 3- Simulation Analysis (2/4)

- Step 1 - Verify the reset behavior.

```
module vend15 (...)
  ...
  always_ff @(posedge
clk)
    if (reset)
      ps <= Zero;
    else
      ps <= ns;
  ...
endmodule  // vend15
```


```
module vend15_tb ();
  ...  // signal declarations, dut instantiation, clock generation
  initial begin
    {reset,N,D,Q} <= 4'b1000; @(posedge clk);  // reset
    {reset,N,D,Q} <= 4'b0000; @(posedge clk);  // Zero (1)
    ...
```



Exercise 3- Simulation Analysis (3/4)


- Step 2 - Verifying every transition between states as expected.

```
...
initial begin
  {reset,N,D,Q} <= 4'b1000; @(posedge clk);  // reset
  {reset,N,D,Q} <= 4'b0000; @(posedge clk);  // Zero (1)
        {N,D,Q} <= 3'b001;  @(posedge clk);  // Zero (2)
        {N,D,Q} <= 3'b100;  @(posedge clk);  // Zero (3)
        {N,D,Q} <= 3'b001;  @(posedge clk);  // Five (4)
        {N,D,Q} <= 3'b100;  @(posedge clk);  // Zero (5)
        {N,D,Q} <= 3'b000;  @(posedge clk);  // Five (6)
        {N,D,Q} <= 3'b010;  @(posedge clk);  // Five (7)
        {N,D,Q} <= 3'b100;  @(posedge clk);  // Zero (8)
                            @(posedge clk);  // Five (9)
        {N,D,Q} <= 3'b001;  @(posedge clk);  // Ten  (10)
        {N,D,Q} <= 3'b010;  @(posedge clk);  // Zero (11)
                            @(posedge clk);  // Ten  (12)
                            @(posedge clk);  // Zero (13)
        {N,D,Q} <= 3'b100;  @(posedge clk);  // Ten  (14)
        {N,D,Q} <= 3'b010;  @(posedge clk);  // Zero (15)
        {N,D,Q} <= 3'b000;  @(posedge clk);  // Ten  (16)
                            @(posedge clk);  // extra
  ...
```

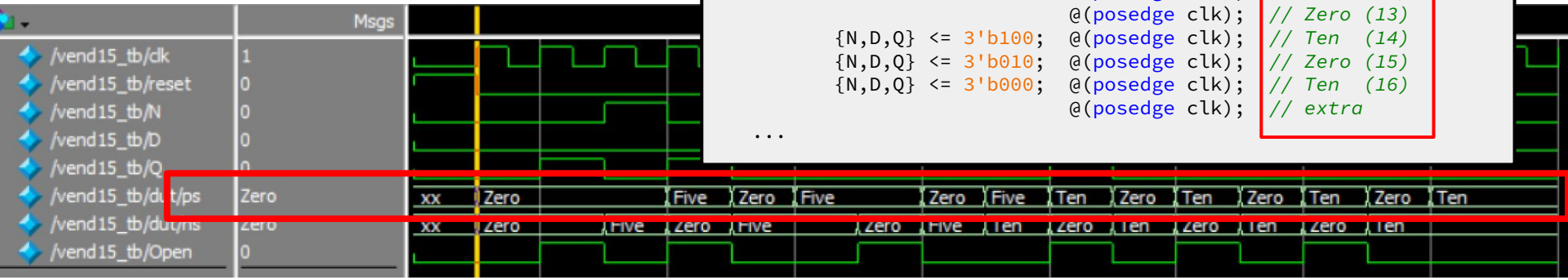


Exercise 3- Simulation Analysis (4/4)

Transitions that should output 1:

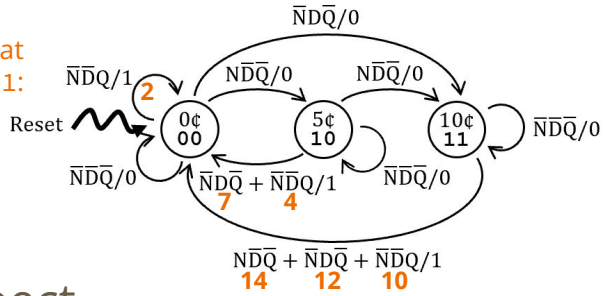

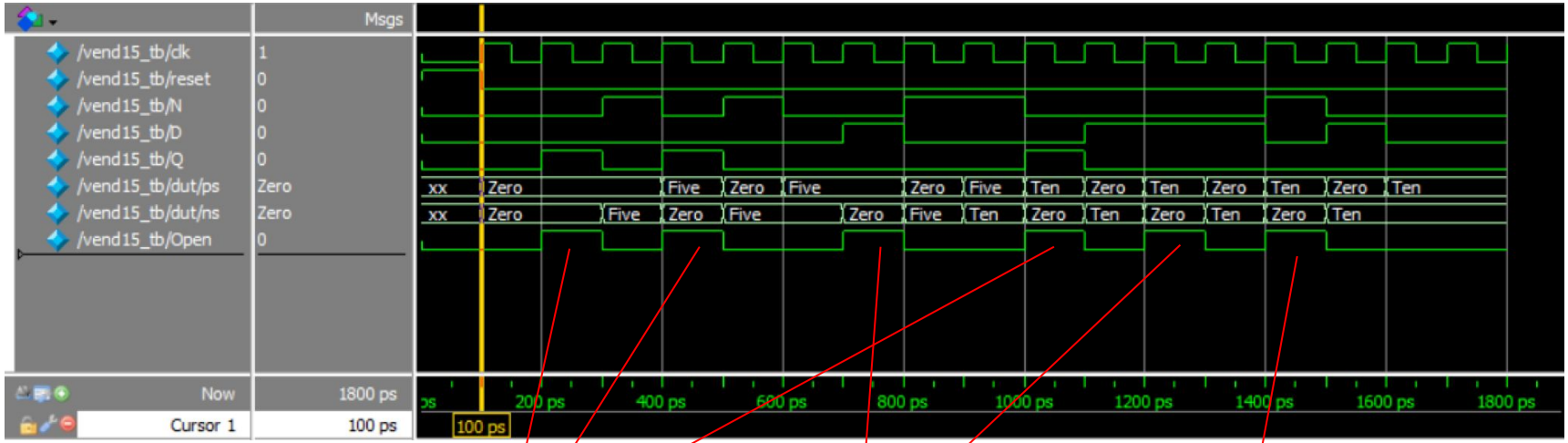- Step 3 - Verifying our output matches what we expect.




```
assign Open = Q | ((ps != Zero) & D) | ((ps == Ten) & N);
```