Levels in Processor Design

Circuit design

- build gates (AND,OR, NAND, NOR, etc.), flip-flops, etc. from transistors

Logical design

- put gates together to form registers, adders, etc. (CSE370)

Register transfer level

- describes the execution of instructions by showing how information is transferred and manipulated between adders, registers, etc.
  - combinational: the output is a function of the input, e.g., an adder
  - sequential: state is remembered, e.g., registers

Architectural description

- ISA, software conventions

System description

- memory hierarchy, I/O, number of processors, etc.

Execution Cycle

What happens when an instruction executes

(1) **fetch**
- sent the PC to memory
- transfer an instruction from memory to the CPU
- increment the PC

(2) **decode** & read the ALU source
- registers
- immediate from the instruction

(3) **execute**
- an ALU operation
- **effective address** calculation
  - address to memory
  - memory access
  - data to memory (if a store)
  - data from memory (if a load)
- branch target calculation
  - condition check
  - change the PC
  - save the return address on a **`jal`**

(4) **store** the result
- from the ALU
- from memory

Processor Datapath & Control Unit

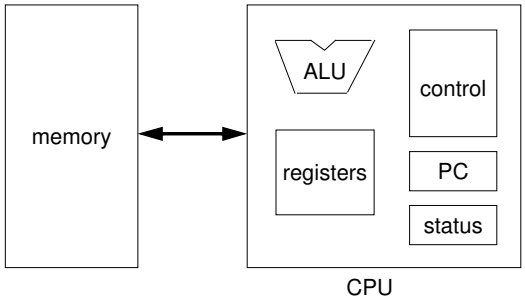

Datapath:

- **combinational** & **sequential** logic
- hardware that implements the operations: ALU, incrementer
- storage for the program (**processor state**): GPRs, PC, status
- wires & buses: data flow between the components

Control

- sends signals to the datapath elements
- specifies what operations to perform, what data to move, when to move it, where to move it

Datapath Building Blocks: Sequential

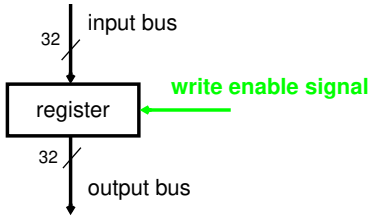

Register

- holds 32 bits
- can be read or written

Datapath Building Blocks: Sequential

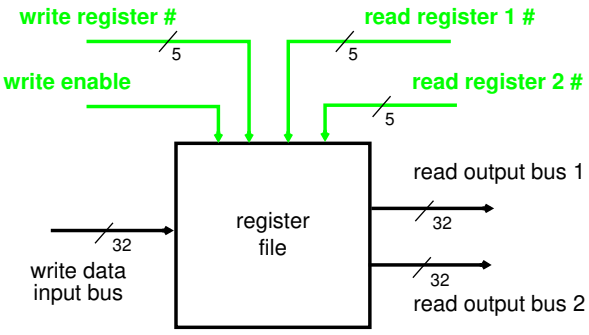

Register File

- always reads
- writes controlled by enable
- can both read and write in the same cycle
  - write first, read second
- can read two register values in the same cycle

Datapath Building Block: Sequential

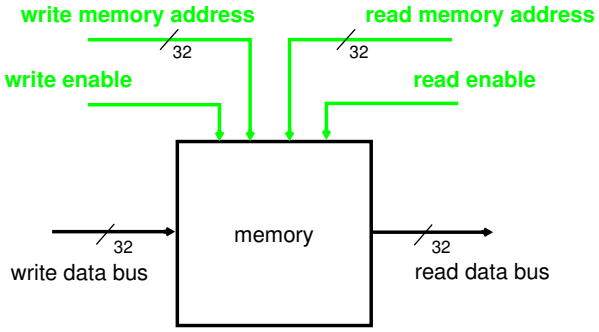

Memory

- can only read or write one location in a cycle

Datapath Building Block: Combinational

Multiplexor (MUX):

- selects one of its inputs for output
- input selected depends on **select** signal

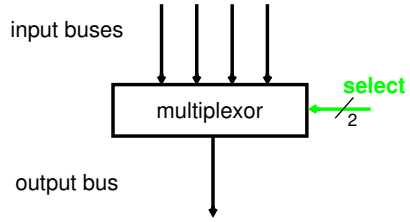

Demultiplexor (selector)

- routes the input to one of the outputs
- the output chosen depends **select**

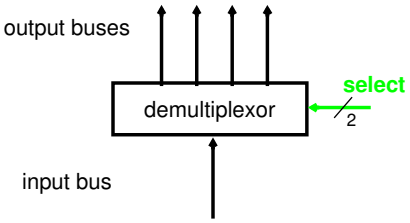

Datapath Building Block: Combinational

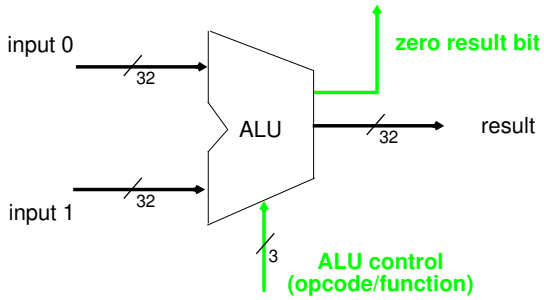

ALU

- Computes arithmetic & logical functions

Single-cycle Datapath

No hardware can be reused by the same instruction

(memory units not really on the CPU)