

Lecture 9

Single-Cycle Performance



- Last time we saw a MIPS single-cycle datapath and control unit.
- Today, we'll explore factors that contribute to a processor's **execution time**, and specifically at the performance of the single-cycle machine.
- Next time, we'll explore how to improve on the single cycle machine's performance using pipelining.

Three Components of CPU Performance

$$\text{CPU time}_{x,p} = \text{Instructions executed}_p * \text{CPI}_{x,p} * \text{Clock cycle time}_x$$


Cycles Per Instruction



Instructions Executed

- Instructions executed:
 - We are not interested in the **static instruction count**, or how many lines of code are in a program.
 - Instead we care about the **dynamic instruction count**, or how many instructions are actually executed when the program runs.
- There are three lines of code below, but the number of instructions executed would be 2001.

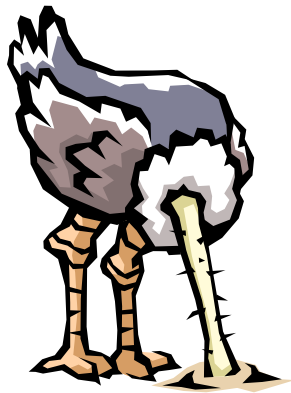
```
li    $a0, 1000
ostrich: sub $a0, $a0, 1
      bne $a0, $0, ostrich
```



CPI

- The average number of clock cycles per instruction, or **CPI**, is a function of the machine and program.
 - The CPI depends on the actual instructions appearing in the program— a floating-point intensive application might have a higher CPI than an integer-based program.
 - It also depends on the CPU implementation. For example, a Pentium can execute the same instructions as an older 80486, but faster.
- So far we assumed each instruction took one cycle, so we had $CPI = 1$.
 - The CPI can be >1 due to memory stalls and slow instructions.
 - The CPI can be <1 on machines that execute more than 1 instruction per cycle (superscalar).

Clock cycle time

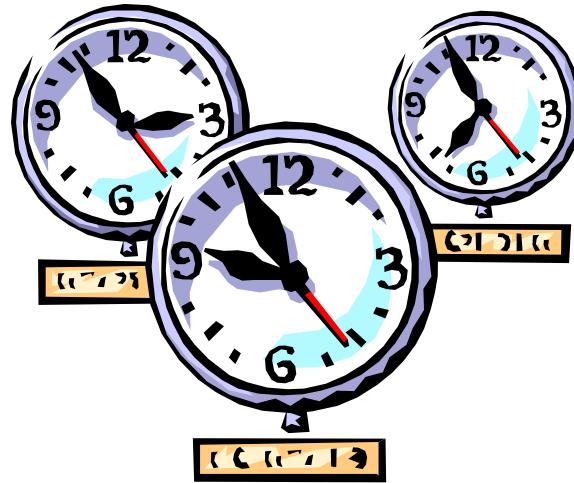

- One “cycle” is the minimum time it takes the CPU to do any work.
 - The **clock cycle time** or clock period is just the length of a cycle.
 - The **clock rate**, or frequency, is the reciprocal of the cycle time.
- Generally, a higher frequency is better.
- Some examples illustrate some typical frequencies.
 - A 500MHz processor has a cycle time of 2ns.
 - A 2GHz (2000MHz) CPU has a cycle time of just 0.5ns (500ps).

Execution time, again

$$\text{CPU time}_{x,p} = \text{Instructions executed}_p * \text{CPI}_{x,p} * \text{Clock cycle time}_x$$

- The easiest way to remember this is match up the units:

$$\frac{\text{Seconds}}{\text{Program}} = \frac{\text{Instructions}}{\text{Program}} * \frac{\text{Clock cycles}}{\text{Instructions}} * \frac{\text{Seconds}}{\text{Clock cycle}}$$

- Make things faster by making any component smaller!!

	Program	Compiler	ISA	Organization	Technology
Instruction Executed					
CPI					
Clock Cycle Time					

- Often easy to reduce one component by increasing another


Example 1: ISA-compatible processors

- Let's compare the performances two x86-based processors.
 - An 800MHz AMD Duron, with a CPI of 1.2 for an MP3 compressor.
 - A 1GHz Pentium III with a CPI of 1.5 for the same program.
- Compatible processors implement identical instruction sets and will use the same executable files, with the same number of instructions.
- But they implement the ISA differently, which leads to different CPIs.

$$\begin{aligned}\text{CPU time}_{\text{AMD,P}} &= \text{Instructions}_p * \text{CPI}_{\text{AMD,P}} * \text{Cycle time}_{\text{AMD}} \\ &= \\ &= \end{aligned}$$

$$\begin{aligned}\text{CPU time}_{\text{P3,P}} &= \text{Instructions}_p * \text{CPI}_{\text{P3,P}} * \text{Cycle time}_{\text{P3}} \\ &= \\ &= \end{aligned}$$

How the add goes through the datapath


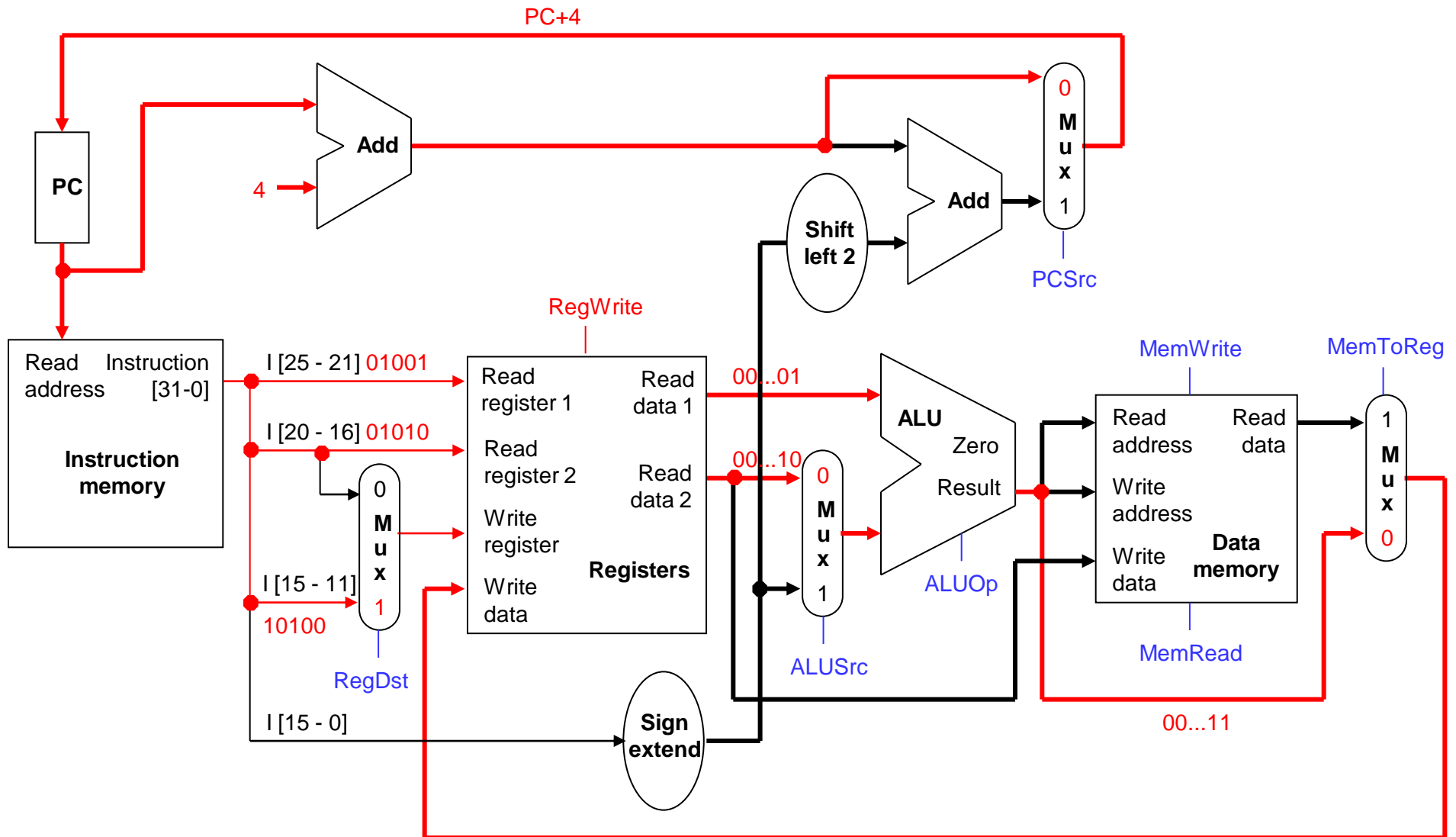


Performance of Single-cycle Design


$$\text{CPU time}_{x,p} = \text{Instructions executed}_p * \text{CPI}_{x,p} * \text{Clock cycle time}_x$$

Edge-triggered state elements

- In an instruction like `add $t1, $t1, $t2`, how do we know \$t1 is not updated until *after* its original value is read?
- We'll assume that our state elements are **positive edge triggered**, and are updated only on the positive edge of a clock signal.
 - The register file and data memory have explicit write control signals, **RegWrite** and **MemWrite**. These units can be written to only if the control signal is asserted *and* there is a positive clock edge.
 - In a single-cycle machine the PC is updated on each clock cycle, so we don't bother to give it an explicit write control signal.

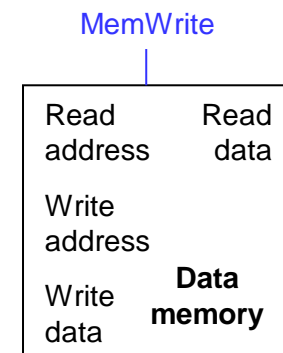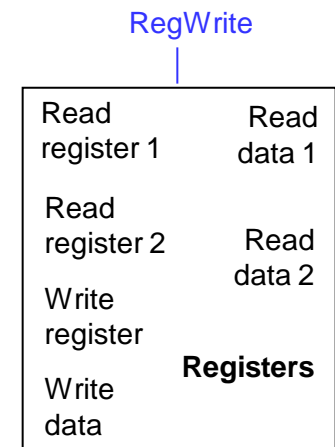

MemRead

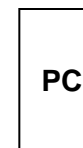


The datapath and the clock

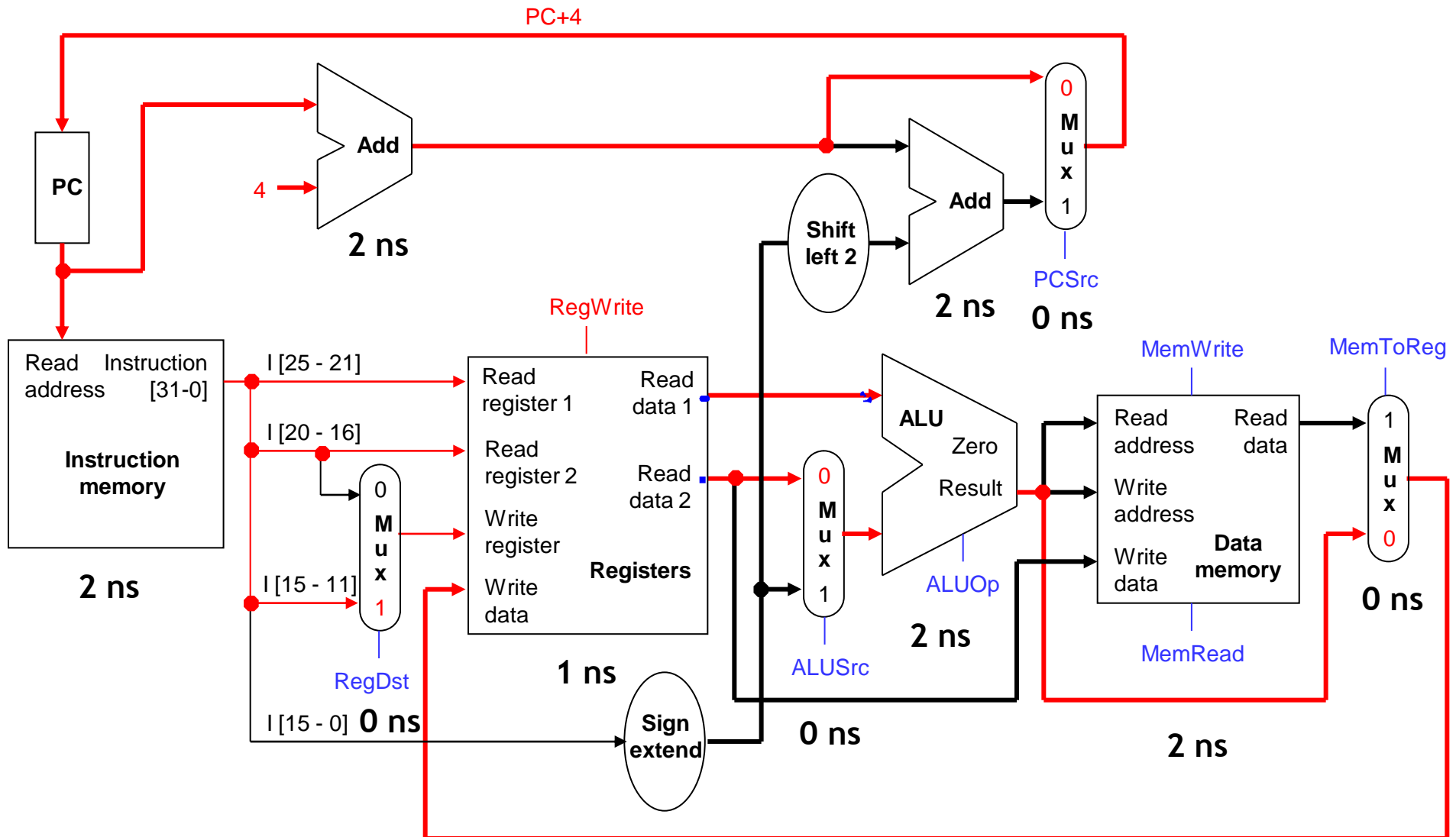1. On a positive clock edge, the PC is updated with a new address.
 2. A new instruction can then be loaded from memory. The control unit sets the datapath signals appropriately so that
 - registers are read,
 - ALU output is generated,
 - data memory is read or written, and
 - branch target addresses are computed.
 3. Several things happen on the *next* positive clock edge.
 - The register file is updated for arithmetic or lw instructions.
 - Data memory is written for a sw instruction.
 - The PC is updated to point to the next instruction.
- In a **single-cycle datapath** everything in Step 2 must complete within one clock cycle, before the next positive clock edge.




How long is that clock cycle?

Compute the longest path in the add instruction



The slowest instruction...

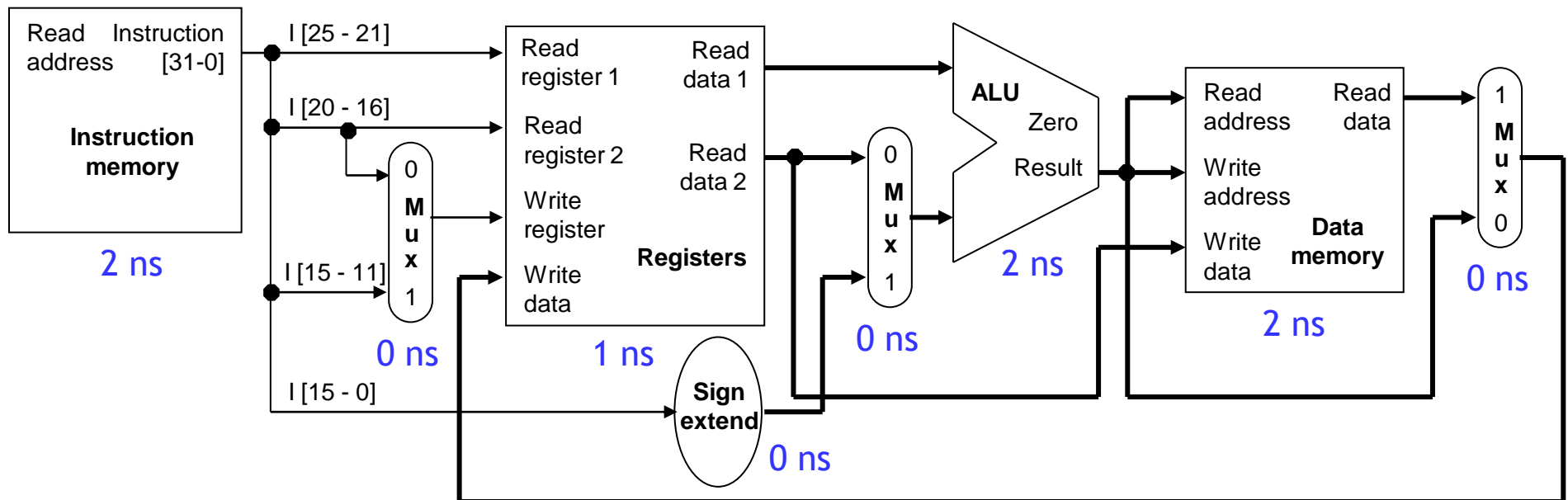
- If all instructions must complete within one clock cycle, then the cycle time has to be large enough to accommodate the *slowest* instruction.
- For example, `lw $t0, -4($sp)` is the slowest instruction needing __ns.
 - Assuming the circuit latencies below.



The slowest instruction...

- If all instructions must complete within one clock cycle, then the cycle time has to be large enough to accommodate the *slowest* instruction.
- For example, `lw $t0, -4($sp)` needs 8ns, assuming the delays shown here.

reading the instruction memory	2ns	} 8ns
reading the base register \$sp	1ns	
computing memory address \$sp-4	2ns	
reading the data memory	2ns	
storing data back to \$t0	1ns	

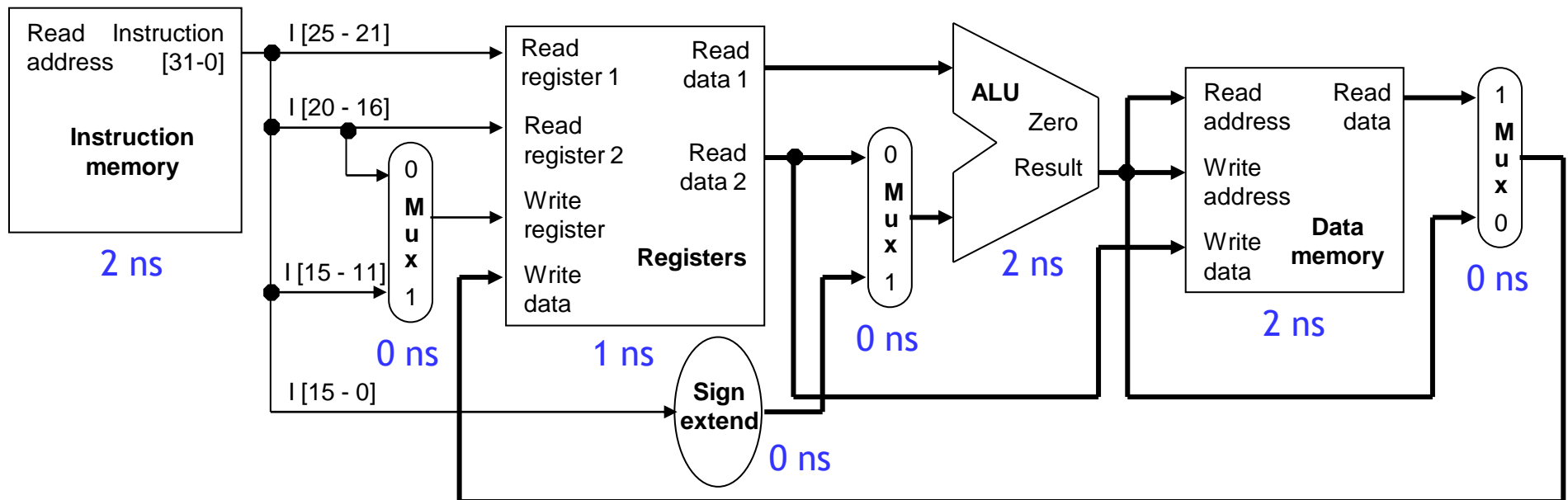


...determines the clock cycle time

- If we make the cycle time 8ns then *every* instruction will take 8ns, even if they don't need that much time.
- For example, the instruction `add $s4, $t1, $t2` really needs just 6ns.

reading the instruction memory 2 ns
reading registers \$t1 and \$t2 1 ns
computing \$t1 + \$t2 2 ns
storing the result into \$s0 1 ns

} 6 ns

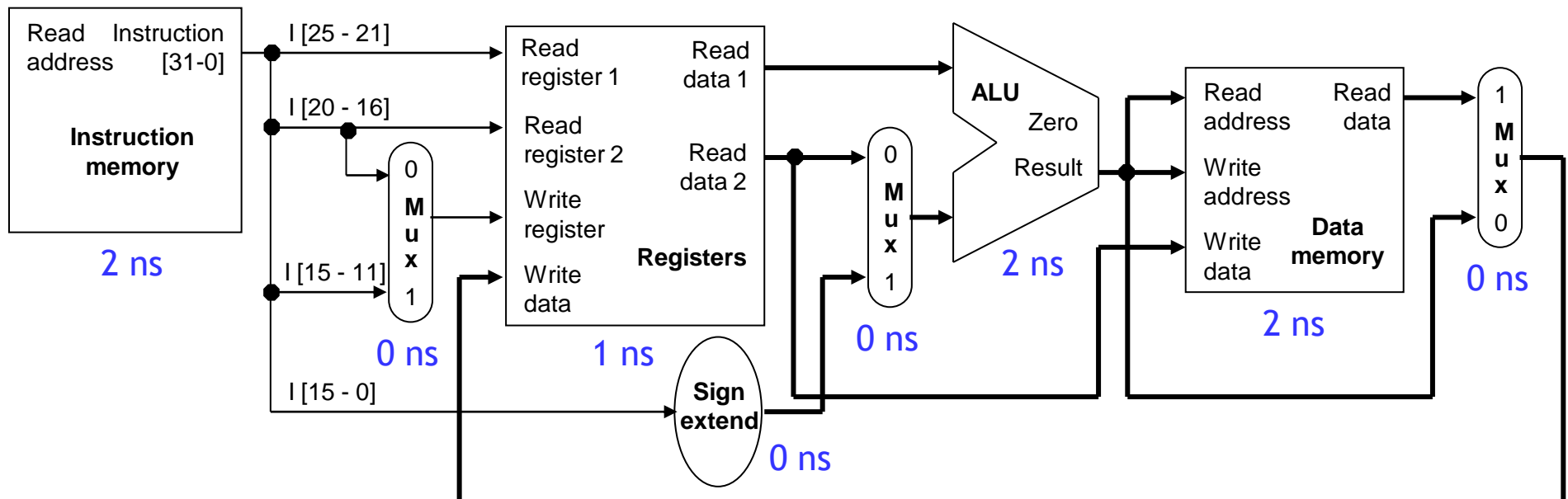

How bad is this?

- With these same component delays, a `sw` instruction would need 7ns, and `beq` would need just 5ns.
- Let's consider the `gcc` instruction mix from p. 189 of the textbook.

Instruction	Frequency
Arithmetic	48%
Loads	22%
Stores	11%
Branches	19%



- With a single-cycle datapath, each instruction would require 8ns.
- But if we could execute instructions as fast as possible, the average time per instruction for `gcc` would be:

$$(48\% \times 6\text{ns}) + (22\% \times 8\text{ns}) + (11\% \times 7\text{ns}) + (19\% \times 5\text{ns}) = 6.36\text{ns}$$

- The single-cycle datapath is about 1.26 times slower!

It gets worse...

- We've made very optimistic assumptions about memory latency:
 - Main memory accesses on modern machines is $>50\text{ns}$.
 - For comparison, an ALU on an AMD Opteron takes $\sim 0.3\text{ns}$.
- Our worst case cycle (loads/stores) includes 2 memory accesses
 - A modern single cycle implementation would be stuck at $<10\text{Mhz}$.
 - Caches will improve common case access time, not worst case.
- Tying frequency to worst case path violates first law of performance!!
 - “Make the common case fast” (we'll revisit this often)



Summary

- **Performance** is one of the most important criteria in judging systems.
 - Here we'll focus on **Execution time**.
- Our main performance equation explains how performance depends on several factors related to both hardware and software.

$$\text{CPU time}_{x,p} = \text{Instructions executed}_p * \text{CPI}_{x,p} * \text{Clock cycle time}_x$$

- It can be hard to measure these factors in real life, but this is a useful guide for comparing systems and designs.
- A single-cycle CPU has two main disadvantages.
 - The cycle time is limited by the worst case latency.
 - It isn't efficiently using its hardware.
- Next time, we'll see how this can be rectified with pipelining.

