# CSE370 Quiz 2 (4 February)      **Name** _____

Implement the function $Z(A, B, C, D) = \sum m(3, 4, 5, 9, 13, 15)$ using the PLA provided below.
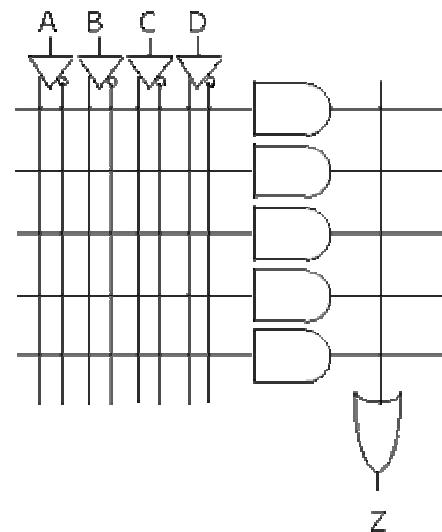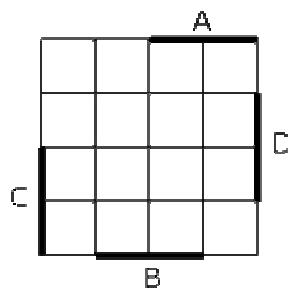
Implement the function again using the 8:1 multiplexer provided below.